PRACTICAL
ELECTRONICS
AUGUST 1973

Australia 50c
New Zealand 45c
South Africa 45c
Rhodesia 45c
Nigeria K. 40
Sweden Kr. 3.50
Malaysia $1.80

20p

BATTLE CHESS

AUDIO COMPRESSOR

550 v MEGOHMMETER

P.E. Sound Synthesiser...

REVERBERATION AMPLIFIER

Antex X25

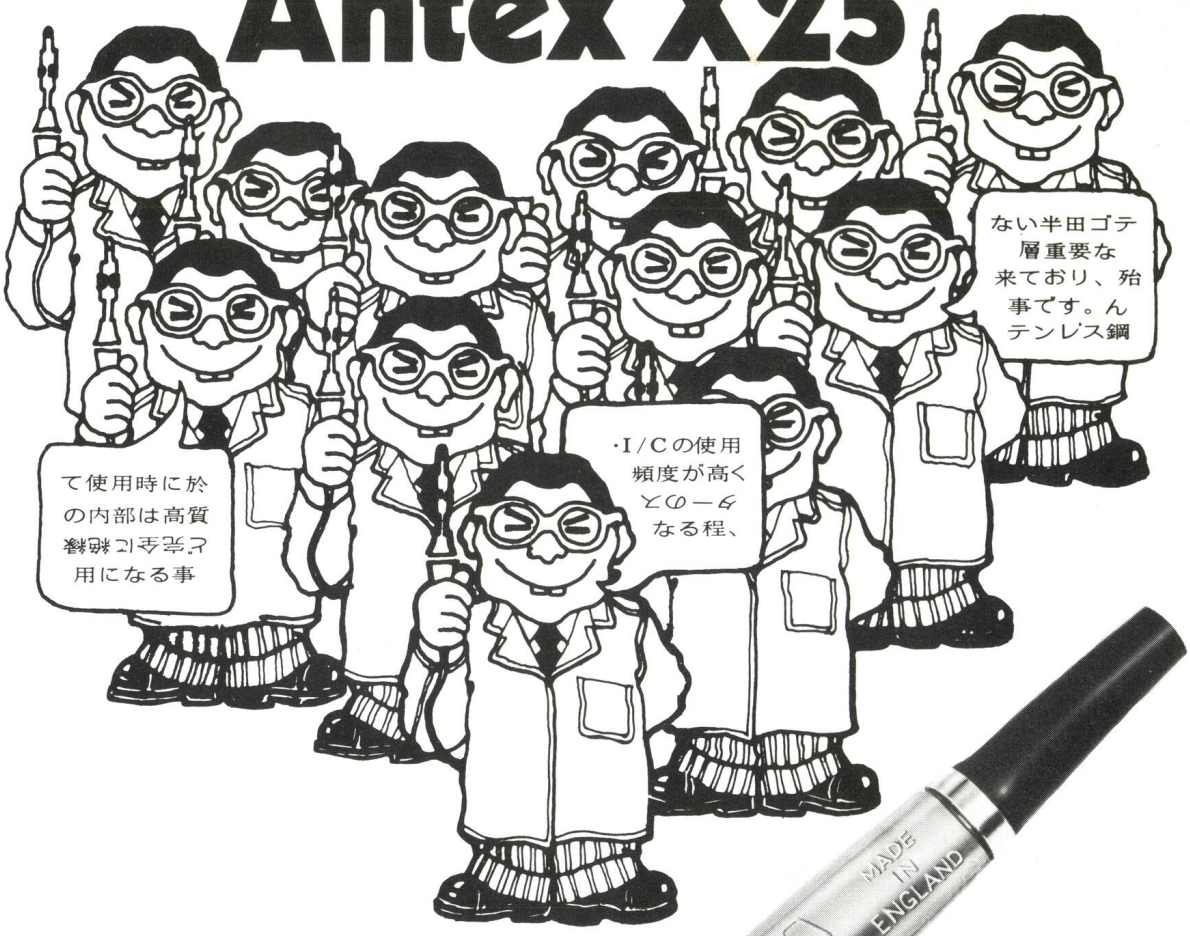

The Japanese have a Yen for it.

in case you are not familiar with Japanese:

Our distributors in Japan are telling their their customers about the importance (when soldering I.C.'s and transistors) of the low leakage of our Model X.25 soldering irons.

Model X.25 –25 watt sells at £1·75 + P & P 8p VAT18p

Model G –18 watt £1·95 + P & P 5p V.A.T. 20p

Model CCN –15 watt miniature iron £1·95 + P & P 5pVAT 20p

Ask your usual wholesaler or retailer for Antex irons or if you have any difficulty, send the coupon to us direct.

ANTEX

From radio or electrical dealers, car accessory shops or in case of difficulty direct from:
ANTEX LTD. FREEPOST
PLYMOUTH PL1 1BR
(no stamp required) Tel 0752 67377.

Please send the following: ..... ☐ Please send the ANTEX colour catalogue.

I enclose cheque/P.O./Cash (Giro No. 258 1000) .....

NAME .....

ADDRESS P.E.8

Reg. No. 393594

PRACTICAL
ELECTRONICS
VOLUME 9 No. 8 AUGUST 1973

CONSTRUCTIONAL PROJECTS

BATTLE CHESS *by D. Coles* 664
Bring the battlefield to the game of chess

AUDIO COMPRESSOR *by R. A. Penfold* 669
Provides an almost constant output from widely varying inputs

P.E. SOUND SYNTHESISER—7 *by G. D. Shaw* 678
Reverberation amplifier for springline, ring modulator and peak level meter

550V MEGOHMMETER *by B. V. Lamb* 696
A high voltage generator for checking mains insulation

SIMPLE FLASHER *by J. B. Dance* 702
Using the 555 timer chip to control the operation of flashing lights

GENERAL FEATURES

INGENUITY UNLIMITED 672
Light-Operated Power Controller—Reed Relay Current Trip—Reversing Light Warning

25 YEARS OF SEMICONDUCTORS—2 *by M. J. Rose* 692
Power devices, photo devices and integrated circuits

LOGIC TUTOR EXPERIMENTS—4 *by M. J. Hughes* 704
De Morgan's Theorem

NEW DEVICES . . . APPLICATIONS 705
The latest in circuit ideas for the experimenter

NEWS AND COMMENT

EDITORIAL—Two-Way Link 663

SPACEWATCH *by Frank W. Hyde* 674
Sun jolts the earth—Chinook winds—Asteroids

STRICTLY INSTRUMENTAL *by K. Lenton-Smith* 677
Comments on contemporary sounds

COMPONENT SHOW '73 689
Report from the recent London RECMF Show held at Olympia

INDUSTRY NOTEBOOK *by Nexus* 698
What's happening inside industry

ELECTRONORAMA 700
Looking at the latest developments in electronic watches

READOUT 710
Author of the Synthesiser answers back

IMPORTANT ANNOUNCEMENT 691
Quadraphonics comes to P.E.

Our September issue will be published on Friday, August 10, 1973

© IPC Magazines Limited 1973. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, £2·65.

"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn – and help qualify yourself for a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing *actual projects you enjoy* – making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No mathematics, no soldering – yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits – assemble components – build things – experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course AT NO EXTRA CHARGE! And this is a course anyone can afford. You can even pay for it in easy payments – in fact you could make extra cash from spare-time work when you've turned yourself into a qualified man through B.I.E.T. training.

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who *makes* things, not just another of the millions who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own powerful radio. And after the course you can go on to acquire high-powered technical qualifications, because B.I.E.T.'s famous courses go right up to City & Guilds levels.

Send now for FREE 76 page book – see how easy it is – read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

POST TODAY FOR FREE BOOK

To: BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, Aldermaston Court, Reading RG7 4PF — QH | BPE18

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

NAME .....

ADDRESS .....

.....

.....

BIET

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

P.E. SOUND SYNTHESISER

Access — Buy it with Access

SIMPLY SEND EXACT DETAILS OF NAME AND NUMBER COPIED FROM THE FACE OF YOUR ACCESS CARD AND LEAVE THE REST TO US.

'DESIGNER APPROVED KITS'

The 'RING MODULATOR' I.C.
SG 3402N
£1·74 each

ELECTRONIC ATTENUATOR
MFC 6040
£1·00 each

ZIJ NOISE DIODE
43·5p each

mini D.I.L.
741's 32p each
while stocks last

4p stamp brings latest lists

We stock a full range of professional quality components as specified for this exciting project and many prices are **down.** 2% M.O. resistors now **3·2p** ea. 5% low noise carbon film **1·8p** ea. Cermet presets now **37·5p** ea. Full range of capacitors–Ceramic, Electrolytic, Polyester, 'Styrene, 'Carbonate, Silver Mica, etc. Modular hardware kits; Dual-Rail Regulated Power Supplies; Individual component/module kits from date of publication. P.C.B. for the exciting 'Hutchinson' Tone Control Module.

Attractive discounts on quantity purchases.

EATON AUDIO P.O. Box No. 3, ST. NEOTS HUNTINGDON PE19 3JB

TERMS: MAIL ORDER ONLY. C.W.O. Cheques or crossed P.O. payable to Eaton Audio. Minimum order £2. Where P. & P. charges are not shown please add 10p in the £1 to orders under £5. Orders over £5 will be sent free of P. & P. All prices subject to V.A.T.

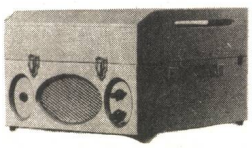

CASED AMPLIFIERS

Polished wooden cabinet 14 × 13 × 9in with hinged lid containing a sensitive (20μV) 4-valve amplifier with tone and volume controls, giving about 3 watts output to the 7 × 4in 3Ω speaker. Also a non-standard single motor tape deck. Easily converted to record player, guitar practice amp., baby alarm, etc. Supplied in good working condition with circuit diagram. Mains operated. Only **£3** (£1 up to 200 miles, £1·20 over). Special cassettes **£1** (25p). Spare heads **40p.** Damaged machines from **£1·50** to callers only. Amplifier chassis, 2 × ECC83, EL84, EZ80 **£1·65** (35p).

COMPUTER PANELS

Type A: 4 OC35, 4 GET103, etc., **50p**; Type C: 2 OC35, 2 OC76, 6 OC42, etc., **30p**; Type D: 4 OC36, 8 GET103, etc., **60p** (5p each). Type E: 4 OC29, 4 trimpots, 4 ACY19, 8 other transistors, 35 diodes, etc. **£1** (10p).

Parcel of 12 top quality boards **£2** (25p). 7lb of lower quality including some broken **£2** (40p), 56lb **£12** (c.p.). Boards from **5p** to callers. Pack of boards containing at least 500 components, including 50 transistors **60p** (15p).

7lb BARGAIN PARCELS

Hundreds of new components—capacitors, resistors, switches, crystals, pots, PC boards, etc. Outstanding value **£1·65** (35p). 500 assorted resistors, good selection **£1** (15p); 40 asstd. pots **£1** (25p); 300 asstd. capacitors, all types **£1** (25p). Heavy duty heat sinks 6 × 5 × 3in, weight 3lb with 2 power transistors, OC36 or 2N1146A **£1** (25p). Large selection of panel meters for callers. Audio oscillator 50Hz–20kHz, BFO No. 8 **£10**; RF Signal generator, Marconi TF144G, 85kHz–25MHz from **£12.** 741C TO99 or 8 pin DIL **28p**; BC107/9 14 for **£1**; 2N3055 **35p.** Veroboard in stock. Post in brackets, small parts 3p. VAT NOT INCLUDED. S.A.E. list, details.

GREENWELD ELECTRONICS (PE3)

24 Goodhart Way, West Wickham, Kent. SHOP at 21 Deptford Broadway, SE8 (next to old cinema). Callers most welcome. Tel. 01-692 2009.

SAXON ENTERTAINMENTS LTD.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT. NEW & SECONDHAND MUSICAL INSTRUMENTS. DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES

Announcing our improved range of constructor modules

FOR DOMESTIC & COMMERCIAL USE

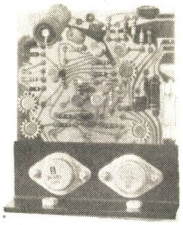

New Versions using 3A "Plastic Power" Driver Transistors now available.

To meet demand, we have included a more powerful module in our well-established and proven range. All these power amplifiers are carefully assembled, tested and guaranteed. They offer superb value for reliability and versatility.

SA35 35W RMS uses 7 transistors and 7 diodes. Carr. paid. **£4·45**

A NEW ADDITION IS THE SA50 at £5·65

Carr. paid. A rugged, well built unit, capable of 50W RMS out, with all the advantages of Saxon Amplifier design and quality. Ready now.

SA100 makes an ideal unit in disco assemblies

A real glutton for work. Reliable, tough and compact. 11 transistors, 6 diodes. Carr. paid. **£10·90**

BRIEF SPEC. FOR ALL THREE MODULES

Freq. response	15–40,000Hz ± 1dB	All modules incorporate OPEN AND SHORT CIRCUIT PROTECTION, plus proof against over-dissipation and faulty inductive loads in its SA100
Distortion	0·2% at 1kHz	
Loads	4 to 16 ohms	
Quiescent current	15mA	
Noise	Better than −75dB	
Supply voltage	SA35–45V SA50 45/65V SA100 40–70V	
Size	4½in × 4in × 1in (SA100) 4in × 3in × 1in (SA35/SA50)	

Circuits, connecting instruction and application data are supplied free with all modules.

POWER SUPPLIES FOR THE SA25/35 & SA100 AUDIO MODULES

PU45	Unstabilised supply for 2 SA25/35's	£4·90
PU70	Unstabilised supply for one or two SA100	£7·75 carr. 40p
PS45	Stabilised module for 2 SA25's or two SA35's	£3·50 carr. free
MT45	Transformer for above, heavy duty	£2·85 carr. 20p
MT30	Transformer for unstabilised supply complete with rectifier diodes mounted	£3·50 carr. 20p
PS70	Stabilised supply module for one or two SA100's	£4·90 carr. free
MT70	Transformer for PS70	£4·90 carr. 40p

ALL MODULES ARE BUILT ON GLASS FIBRE P.C. BOARD AND SUPPLIED FULLY TESTED

TWO NEW PA/MIXER CONTROL UNITS

Built for hard work!

In extra slimline easy-fit case.

Using grouped pairs of inputs (high Z and low Z inputs) with individual bass, treble and volume controls on each pair, plus master controls. These low-noise units will feed all makes of amplifiers, making them ideal for clubs, discos, etc. Standard jack sockets, compact design. In strong metal cases. All Units guaranteed for 3 years.

- **HIGH AND LOW IMPEDANCE INPUTS**
- **BASS/TREBLE/VOLUME ON EACH PAIR**
- **MASTER CONTROL ON OUTPUT**

M4H
4 high Z, 4 low Z inputs, 4 sets of controls. Case 10" × 8" and only 2½in deep. Carr. paid.
£18·50 + V.A.T.

M6HL
12 inputs (6 high Z, 6 low Z). Carr. paid 18" × 8" × 2½".
£27·50 + V.A.T.

Channel section modules, for building your own: gain—16 × (24dB) Tone controls—18dB swing. Carr. paid.
£3·50 + V.A.T.

CONTROL UNITS

Mono (as shown). Carr. 20p. **£6·50**

Stereo. Carr. 30p. **£15·80**

Two decks, and full headphone monitoring. The unit is mains operated and measures 17½in × 3in × 4in deep and is finished with a smart white on black facia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume, Microphone volume, bass treble, mains on/off.
COMPARABLE TO UNITS AT OVER TWICE THE PRICE. (N.B.—Stereo only has mic. Input.)

PLEASE ADD 10% FOR V.A.T. TO TOTAL VALUE OF YOUR ORDER

S.A.E. brings Saxon equipment and bargains list

- **160 watts version with power supply (Carr. 50p) £27·90**

120 WATT HEAVY DUTY MODULE

Rugged class A driver stage. This module will run from all our mixers, etc., and most other makes. Delivers 120W into an eight ohm load and employs 4 TO3 can (115W) output transistors.

SPECIFICATION

Power output, 120W into 8 ohms
Freq. response, 20–20,000Hz ± 2dB
Input sensitivity, 200mV into 10K
Construction, Fibreglass board
Size, 8in × 4in × 4in (5in with supply)
Low distortion parallel push-pull output stage.

Module only (Carr. 20p) **£13·90**

Module and power supply (Carr. 40p) **£18·95**

SOUND AND LIGHT UNITS

Our popular 3 channel model handles up to 3kW (3,000W) of lighting and incorporates versatile sound control arrangement to enable professional standards to be achieved. Both units are excellent examples of Saxon quality and value.

3 CHANNEL UNIT

Includes bass, middle and treble as well as master controls, 2 amplifier sockets eliminate need for split leads. Up to 3kW lighting load. Smartly finished steel case. Carr. 30p. **£19·75**

SINGLE CHANNEL UNIT

Operates from 5–100W amplifiers. Supplied for bass note operation, is easily adapted for treble or mid-range at a cost of about 5p. Carr. pd. **£8·90**

COMPLETE AMPLIFIERS

CSE 100 £34·90 carr. free

This versatile unit is now available in a black vynide case and so represents even better value than ever delivering speech and music powers of up to 100W RMS and continuous signal outputs of 70W. Two individually controlled inputs with wide range bass and treble controls.

SAXON 100 £48·50 carr. free

With an RMS output of 120W speech and music, 100W continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

LOUDSPEAKERS British made bargains!! 12in 25W 8/15 ohms **£5·95** carr. 30p. 15in 50W 8/15 ohm **£14·50** carr. 50p. 12in 40W 15,000 gauss magnet system 8/15 ohm **£11·50** carr. 40p.

600 Watt 3 colour Light Boxes Smart Rexine finish **£15** carr. free.

A.K.G. MICROPHONES
D11 DHL IDEAL DISCO MIKE ONLY **£9·45** (rrp £11·00). S.A.E. for special price list.

Order and personal shoppers to:

SAXON ENTERTAINMENTS LTD., 329 Whitehorse Road, W. Croydon, Surrey CR0 2HS

Telephone 01-684 6385
From 9.30 a.m.-5.30 p.m.

Prices quoted do not include V.A.T. 10% must be added on to total value of order for V.A.T

TRADE AND EXPORT ENQUIRIES INVITED

TERMS OF BUSINESS
Cash with order (C.W.O.). For C.O.D. please add 35p extra, cash by regd. letter please.

You'll hardly be able to believe your ears!

Can you really get sound quality like this for less than £18?

Yes you can! with the new STEREO 21

Until now, richly satisfying sound has always cost a richly satisfying p
But not any more! For an almost unbelievable £17·95, you can
Stereo 21—audio for the connoisseur.
Whatever your taste in music, you can hear it on STE
21 the way its composers heard it in their dre
Beethoven or Mahler . . . Ellington or Jell
Morton . . . Das Nibelung or Jesus C
Superstar . . . Carols from King's Co
Chapel or the return of a Beatle . . . e
thing from a prettily fluting baroque o
to the newest pop group at full throt
STEREO 21 does them all justice!
And have you ever seen a handsomer a
installation? Compact enough to go
university student's bedroom-study, ele
enough for the suavest penthouse pad in T
STEREO 21 offers you all the pride of posses
as well as a thrilling musical experience!
Top-quality amplifier, BSR turntable, matc
speakers. Deck and speaker cabinets you sir
wrap round and glue to build. Screw in the an
fier and connect up (all push fit, no solde
whatsoever), so simple literally anyone
do it. Except for glue and panel pins
parts supplied including
instructions—all for £17·95 (
the cost of post and packir
you buy by mail), and
round it all off—a mo
back Guarantee if y
pleasure in STEREO 21 is
complete!

**Just think—in only a few d
you could be giving your e
the treat of a lifetime—AND in
ducing your envious friends
STEREO 21!**

Personal shoppers and mail order price

£17·95

Plus £1·50 P&P.

Diamond styli, if required, £1·37 extra

R T V C

RADIO AND TV COMPONENTS (ACTON) LTD.
21d High Street, Acton, London W3 6NG
323 Edgware Road, London W2

*Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envel
Goods not despatched outside U.K.*

VISCOUNT III—
a boost in the output

OUNT III now gives you an imposing 20 watts per channel—and the price quoted is actually USIVE OF VAT!
money's important, of course, but not nearly so important as *value for money!* And that's thing you get in abundance with VISCOUNT III. We design it . . . we make it . . . we sell it t to you—passing on all the economies that come from cutting out middle-men! That's nly way you can get so much quality for so little money!
unique VISCOUNT III amplifier, plus the Garrard SP25 Mk III deck, plus the magnificent Type III matched speakers (or Duo Type II for a small room) give you an audio installation will prove unbeatable for listening pleasure! On the brushed aluminium front panel of the fier you'll find all the facilities you need—volume, bass, treble and balance controls, plus hes for mono/stereo, on/off function and bass and treble filters. Plus headphone socket on ack. And the teak finish will harmonise and enhance virtually any style of interior decor!
heart-stopping timbre of Tom Jones at his most virile . . . the last lingering harmonics of o performance by Heifetz or Menuhin . . . the pathos and the panache of Liza Minelli . . . the stic sonorities of the brass band and the elfin subtleties of the virtuoso clavichordist—every nuance with a fidelity that you have *never* experienced before!
e and hear VISCOUNT III! If it's inconvenient to travel, buy by post in the confidence that won't be disappointed (and with a 24-carat Money-Back Guarantee to give you extra urance). Don't settle for second-best!

KERS: Duo Type II Size approx. 17in × 10¾in × 6¾in. Drive unit 13in × 8in with parasitic tweeter. Max. power ts 8 ohms. Simulated Teak cabinet. **£14·00** a pair, £2·20 p. & p. Duo Type III Size approx. 23¾in × 11¾in × 9¾in. unit 13¾in × 8¾in with HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. a pair + £3·30 p. & p.

ES: SYSTEM 1

unt III R 102 amplifier	£24·20 + £1 p & p
Type II speakers	£14·00 + £2·20 p & p
rd SP25 Mk. III with cartridge plinth & cover	£18·00 + £1·75 p & p
total	£56·20

lable complete for only £49·00 + £3·50 p. & p.

ES: SYSTEM 2

unt R 102 amplifier	£24·20 + £1 p & p
Type III speakers	£32·00 + £3·30 p & p
rd SP25 Mk III with cartridge plinth & cover	£18·00 + £1·75 p & p
total	£74·20

lable complete for £65·00 + £4 p. & p.

STILL ONLY £49 COMPLETE

TOURIST PUSH-BUTTON RADIO KIT £6·60

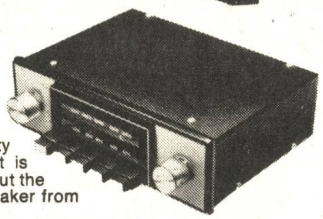

Tourist PB is suitable for 12 volt ing on both negative and positive vehicles it covers the full medium long wave bands. It is permeability and sturdily constructed. Output is 2·5 watts into an 8 ohms speaker. But the ist PB will operate into any loudspeaker from 15 ohms.
t from the output stage, which is an integrated circuit, the only other ronic components that need soldering are some capacitors, resistors, etc. kit includes a pre-built RF tuner unit, and fully modulised IF stages which ore-aligned before despatch. As well as electronic components this kit contains 2 diamond-spun aluminium knobs, elegant matching front panel, washers, screws and wire.
Tourist PB can be mounted in any standard size dash panel and it has an inated tuning scale. Chassis size is: 7in wide, 2in high and 4¼in deep.
rcuit diagram and comprehensive instructions 55p free with parts.
lly retractable and lockable car aerial £1·37 post paid.

RADIO KIT £6·60 p. & p. 55p
aker with baffle and fixing strips **£1·65.** 23p p. & p., post free if bought with kit. Send stamped addressed envelope for leaflet.

u can solder on printed circuit board, you can build this push-button car o kit. It's simple—just follow the step-by-step instructions.

RELIANT Mk IV £13·50

*5 Electrically Mixed Inputs. *3 Individual Mixing controls. *Separate bass and treble controls common to all 5 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State Circuitry. *Attractive Styling.
INPUTS 1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram. Tuner, Monitor, Organ, etc.). All 250mV sensitivity. Output 20 watts into 8 ohms (suitable for 15 ohms). Size approx. 12½ × 6 × 3½ ins.
£13·50 p. & p. 60p.

UNISOUND MODULES

ONLY £7·64 + 55p p. & p.

For the man who wants to design his own stereo—here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.

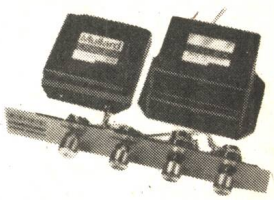

UND 50 45 WATT MONO AMPLIFIER. Ideal for Disco. Output Power: watts R.M.S. (Sine Wave) Frequency Response 3dB points 30Hz and 18KHz. al Distortion: less than 2% at rated output. Signal to noise ratio: better h 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control 2 inputs at 200mV into 470K. Size: 19½ × 10½ × 8ins. Amplifier £31·35 plus £1·65 p. and p. Output for 3, 8 and 15 ohm speakers.

£31·35 + £1·65 p. & p.

ALL PRICES INC. VAT

IN-CAR ENTERTAINMENT AT HOME

With this elegant stereo 8 track add on unit, audio enthusiasts now have the opportunity to extend their systems to include the playing of 8 track cartridges. Simply select your channel, by push button, four digital lamps indicate channel selected. Mains operated.

£9·90 p. & p. 80p

The Viscount III, the fabulous Stereo 21 and the Unisound Modules will all accept this unit, simply connect up.

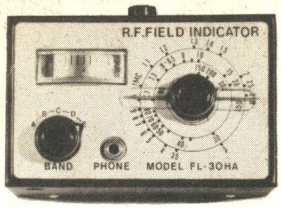

R.F. FIELD INDICATOR
Model FL-30HA. Frequency Range: 5 ranges 1Mc/s to 250Mc/s, **£3.**

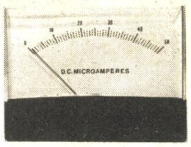

4½in × 3½in METER. 30μA, 50μA or 100μA, **£2·50.**

TAPE RECORDER LEVEL METER
500μA, **50p**

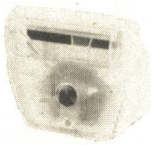

MULTI-METER
Model 200H
20,000 ohm/volt, **£4·80.**

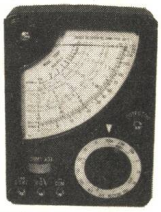

CARDIOID DYNAMIC MICROPHONE
Model UD-130. Frequency response 50–15,000c/s. Impedance Dual 50K and 600 ohms, **£4·50.**

MULTI-METER Model
C-7081GN Range Doubler 50,000 ohm/volt, 15μA High Sensitivity Meter, **£11·25.**

All items advertised in previous numbers of this magazine still available. There is 10% V.A.T. charge on all items. Please add 10p for P. & P. on orders under £5. LARGE S.A.E. for List No. 5. Special prices for quantity quoted on request.

M. DZIUBAS
158 Bradshawgate • Bolton • Lancs. BL2 1BA

SINCLAIR IC12 **£2·00**

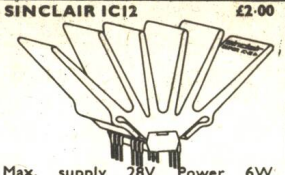

Max. supply 28V. Power 6W RMS. Complete with free printed circuit board and 44-page instruction booklet.

SWANLEY IC TOMORROW— £2·50
The World's most powerful IC amplifier. Similar to the above but operates at 35V max. supply and gives 12W RMS output. Manufactured for us by a leading semiconductor company. Supplied with our instructions and a 6-month guarantee, but no printed circuit.

SINCLAIR EQUIPMENT

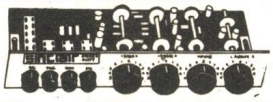

Z30	£3·50	Stereo 60	£7·80
PZ5	£3·97	Z50	£4·25
PZ8	£6·60	PZ6	£6·40
AFU	£4·50		

Transformer for PZ8 **£2·95.**
Project 60 tuner **£16·80.**
Project 605 **£19·90.**

EXECUTIVE CALCULATOR £50

PROJECT 60 KIT **£2·50**
Our extremely popular kit contains the extra capacitors, din plugs and sockets, cables and fuseholder needed to complete Project 60.

KITS FOR IC12 AND IC TOMORROW
Except for the power kits and speakers all items suit both integrated circuits.

DELUXE KIT
Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version **£1·45.** Stereo version with balance control **£3·30.**

POWER KIT FOR IC12
A set of components to construct a 28V 0·5A power supply **£2·27.** Also suitable Sinclair PZ5 **£3·97.**

POWER KIT FOR IC TOMORROW
A set of components to construct a 35V 1A power supply **£2·97.**

LOUDSPEAKERS FOR IC12
8 ohm types. 5″ **£1·00.** 5″ × 8″ **£1·45.**

PREAMPLIFIER KITS.
Type 1 for magnetic pickups, mics. and tuners with 3 position equalisation switch. Mono model **£1·20.** Stereo model **£2·20.** Type 2 for ceramic or crystal pickups. Mono **60p.** Stereo **£1·20.**
SEND S.A.E. FOR FREE LEAFLET ON KITS AND TBA651.

S-DECS AND T-DECS

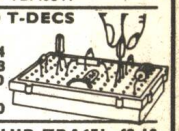

S-Decs	£1·44
T-Decs	£2·88
μ-Decs A	£3·00
16 dil IC carriers	£1·20

IC RADIO CHIP TBA651 £2·10
The world's most advanced IC radio chip. Contains RF Amp, oscillator, mixer, IF Amps, wide range AGC circuitry and voltage stabiliser. With data **£2·10.** Send S.A.E. for free leaflet. Kit of resistors, capacitors and IF filters **£1·75** extra.

SWANLEY ELECTRONICS
32 Goldsel Road • Swanley • Kent BR8 8EZ
Postage 10p per item. Please add 10% extra to total cost of order for VAT. Official credit orders from schools, etc., welcome. Full lists 10p post free. Send S.A.E. for free 8-page book on IC TOMORROW, IC12 kits and TBA651.

Give us six months, and we'll turn your hobby into a career.

You have a hobby for a very good reason. It gives you a lot of pleasure.

So if you can find a job that involves your hobby, chances are you'll enjoy your work more, and you'll do better work.

Now CDI can help you find such a job. A job where you'll be responsible for the maintenance of a computer installation. A job that pays well too. If you're interested in mechanics or electronics (without necessarily being a mathematical genius), have a clear, logical mind and a will to work, then we can train you to be a Computer Engineer inside six months.

So give us a call. CDI. We're the Training Division of one of the world's largest computer manufacturers. And we have the experience to know if you can make it. A ten minute talk with us, and you could be on the way to spending the rest of your life with your hobby.

Ring
01-637 2171
between 9 a.m. and 9 p.m. and ask for Mr PLATT

It's quicker and easier to phone, but if you prefer, send this coupon to: Control Data Institute, Wells House, 77 Wells Street, London, W.1.
Please give me further information.

Name

Address

Age Phone PE8

CONTROL DATA INSTITUTE CONTROL DATA LIMITED

The Training Division of one of the world's largest Computer manufacturers.

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD

COMPLETE TELEPHONES

EX G.P.O. NORMAL HOUSEHOLD TYPE

ONLY £1·05

POST & PACKING 45p EACH

TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

ONLY 27½p

POST & PACKING 16½p

TESTED AND GUARANTEED PAKS

B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV 1 amp. plastic	55p
B81	10	Reed Switches, 1" long ¼" dia. Highspeed P.O. type	55p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	55p
H4	250	Mixed Resistors. Approx. quantity counted by weight	55p
H7	40	Wirewound Resistors. Mixed types and values	55p
H9	2	OCP71 Light Sensitive Photo Transistor	55p
H28	20	OC200/1/2/3 PNP Silicon uncoded TO-5 can	55p
H30	20	1 Watt Zener Diodes, Mixed Voltages 6·8–43V	55p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked	55p
H38	30	Short lead Transistors, NPN Silicon Planar types	55p
H39	10	Integrated circuits 6 gates BMC 962, 4 flip flops BMC 945	55p
H40	20	BFY 50/2, 2N696, 2N1613, NPN Silicon uncoded TO-5	55p
H41	2	BD131/BD132 Complementary Plastic Transistors	55p

UNMARKED UNTESTED PAKS

B1	50	Germanium Transistors PNP, AF and RF	55p
B66	150	Germanium Diodes Min. glass type	55p
B83	200	Trans. manufacturers' rejects all types NPN; PNP, Sil. and Germ.	55p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	55p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	55p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BSY95A, etc.	55p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	55p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	55p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	55p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	55p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts	55p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can	55p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1·10 each

OVER

1,000,000

TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very keen prices. Please send for free catalogue.

600,000 Silicon planar plastic transistors. Unmarked, untested, factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70, etc.

Audio NPN, similar to ZTX300, 2N3708/9 BC107/8/9, BC168/9, etc.

Please state Audio NPN or Audio PNP when ordering.

ALL AT 500 for **£3·30**, 1,000 for **£5·50**, 10,000 for **£44.**

P & P 11p per 1,000

OUR VERY POPULAR 4p TRANSISTORS

TYPE "A" PNP Silicon Alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.
TYPE "G" NPN Silicon, similar ZTX300 range.
TYPE "H" PNP Silicon, similar ZTX500 range.

8 RELAYS FOR VARIOUS TYPES P & P 27½p **£1·10**

Our famous P1 Pak is still leading in value for money

Full of Short Lead Semiconductors and Electronic Components, approx. **170.** We guarantee at least **30** really high quality factory marked Transistors PNP and NPN, and a host of Diodes and Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak **P.1.** Only **55p.** **11p P & P on this Pak.**

A CROSS HATCH GENERATOR FOR £3·85 ! ! !

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Television.

This complete kit of parts costs £3·85, post paid.

A MUST for Colour T.V. Alignment.

STEREO DECODER £4·95

A ready built unit, ready for connection to the I.F. stages of your existing FM Radio or Tuner Unit. A tell tale light can be connected to show the presence of a Stereo transmission and correct operation of the Unit.
The Unit is in the form of a small printed circuit, and no further alignment is necessary, as all preset adjustments have already been carried out at the factory.
It is recommended that a L.E.D. is used as the indicating light and a suitable device is available from us at 36½p.
Supplied with necessary instructions and written guarantee.

FREE CATALOGUE FOR

TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS

100,000 Plastic Power Transistors

in stock, more on way!

NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1	VCE Min. 15	HFE Min. 15	
	1–12	13–25	26–50
40 watt	22p	20p	18p
90 watt	26½p	24½p	22p
Range 2	**VCE Min. 40**	**HFE Min. 40**	
	1–12	13–25	26–50
40 watt	33p	31p	29p
90 watt	38½p	36½p	33p

Complementary pairs matched for gain at 3 amps. **11p** extra per pair. Please state NPN or PNP on order.

INTEGRATED CIRCUITS. We stock a large range of I.C.s at very competitive prices (from **11p** each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available. This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights, etc. Pocket Size, **15p**, Wall Chart, **18p.**

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at **16½p** each } Now new low
16 pin type at **18p** each } profile type.

BOOKS

We have a large selection of Reference and Technical Books in stock.
These are just two of our popular lines:
B.P.I. Transistor Equivalents and Substitutes: **40p**
This includes many thousands of British, U.S.A., European and C.V. equivalents.
The Iliffe Radio Valve & Transistor Data Book 9th Edition: P & P 23½p. **75p**
Characteristics of 3,000 valves and tubes. 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.
Send for lists of publications.

N.B.—Books are void of V.A.T.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME.....

ADDRESS .....

.....

ALL PRICES INCLUDE 10% V.A.T.

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 11p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE.

BI-PRE-PAK LTD

Co. Reg. No. 820919

DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

A DEXTER DIMMASWITCH

ALLOWS COMPLETE LIGHTING CONTROL

The DEXTER DIMMASWITCH is an attractive Dimma unit which simply replaces the normal light switch. It is available as a complete "ready to install" unit or "simple to assemble" kit. Two models are available controlling up to 300W or 600W of all lights, except fluorescents, at mains 200-250V, 50Hz. All DEXTER DIMMASWITCH models have built-in radio interference suppression.

600 watt **£3.52** Kit form **£2.97**
300 watt **£2.97** Kit form **£2.42**

All plus 12p post and packing
Prices include VAT. Please send c.w.o. to:

DEXTER & COMPANY
1 ULVER HOUSE
19 KING STREET
CHESTER CH1 2AH
Tel: 0244-25883

AS SUPPLIED TO H.M. GOVERNMENT DEPARTMENTS, HOSPITALS, LOCAL AUTHORITIES, ETC.

EX COMPUTER PC PANELS
2 × 4in packed with semiconductors and top quality resistors, capacitors, diodes, etc. Guaranteed min. 35 transistors plus data. 10 boards **50p** (9p).

SPECIAL BARGAIN PACK
25 boards **£1** (25p). Panels with 4 power transistors sim OC28 **50p** (9p).

ELECTROLYTICS
68,000μ 16V, 4½ × 2in dia. 25,000μ 25V, 20,000μ 30V, 5,000μ 90V, 35,000μ 15V, 8,000μ 55V, 4½ × 3in dia. **50p** (15p). 15,000μ 15V, 10,000μ 35V, 4½ × 2in dia. **30p** (10p). 12,000μ 25V wire ends **15p** (5p), 12 for **£1·50** (15p).

20A DIODES	4 for **£1** (7p)
3A DIODES	4 for **50p** (5p)
8 BLACK TOGGLES dpst	**50p** (8p).
250 MIXED CAPACITORS	**60p** (8p)
250 MIXED RESISTORS	**60p** (8p)
150 HI-STAB RESISTORS	**60p** (8p)
200 SI PLANAR DIODES UNTESTED	**50p** (5p)
SUB-MIN. CO-AX. PLUGS & SKTS.	4 pairs **50p** (5p)
REED RELAYS, MIXED	10 for **50p** (5p)
MICRO SWITCHES	8 for **50p** (8p)
ASSORTED RELAYS	8 for **£1** (12p)
MIN. GLASS NEONS	12 for **50p** (5p)
10 WAY TERMINAL BLOCKS	10 for **55p** (5p)
QH BULBS 12V 55W	**50p** (5p)
PAPST EXTRACTOR/BLOWER FANS 100 cfm 4½ × 4½ × 2in.	**£3·50** (28p)

Postage and package shown in brackets.
Please add 10% VAT to prices.

KEYTRONICS
(Mail Order only)
44 EARLS COURT ROAD
LONDON W8
01-478 8499

I-N-T-E-R-L-O-C-K-I-N-G PLASTIC STORAGE DRAWERS

NEAT! HANDY! TIDY!

DISCOUNT PRICES

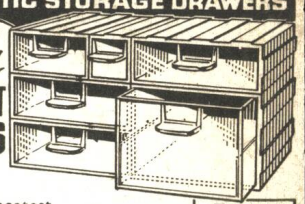

5 SIZES ALL INTERLOCK

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/removable space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT TRADE PRICES!

SINGLE UNITS (1D) (5ins × 2¼ins × 2¼ins). **£1·25** DOZEN.

DOUBLE UNITS (2D) (5ins × 4¼ins × 2¼ins). **£2·10** DOZEN.

TREBLE (3D) £2·20 for 8.

DOUBLE TREBLE 2 drawers, in one outer case **(6D2), £3·25** for 8, **EXTRA LARGE SIZE (6D1) £3·10** for 8.

PLUS QUANTITY DISCOUNTS!
Orders £6 and over DEDUCT 5% in the £
Orders £10 and over DEDUCT 7½% in the £
Orders £20 and over DEDUCT 10% in the £

PACKING/POSTAGE/CARRIAGE: Add 35p to all orders under £10. Orders £10 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES

Please add 10% V.A.T. to total remittance

IVORYET LIMITED
(Dept. PE8) 124 Cricklewood Broadway, London, N.W.2
Tel. 01-450 4844

Collect Wireless World Circards. And build a valuable dossier on circuit design.

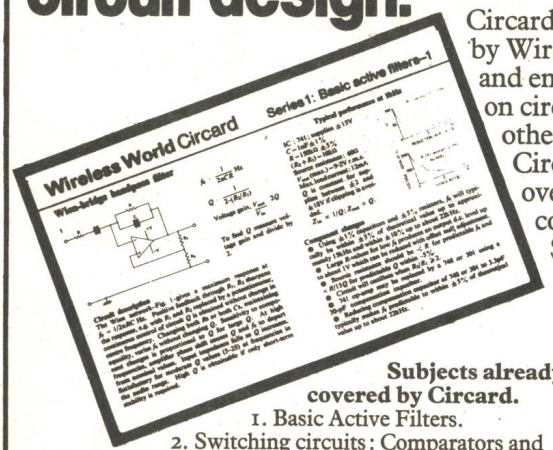

Circards is a new and comprehensive system, launched by Wireless World, to provide professional engineers and enthusiasts with valuable up-to-the-minute data on circuit design. Data not available from any other single source.

Circard sets come in wallets and cost £1 (£1.15 overseas) per set. A subscription to Nos. 6-15 costs £9 (£10.50 overseas) – sets published monthly.

Start your personal dossier on circuit design by completing and returning the coupon below.

Subjects already covered by Circard.
1. Basic Active Filters.
2. Switching circuits: Comparators and Schmitts. 3. Waveform Generators.
4. AV Measurements. 5. Audio Circuits: preamplifiers, mixers, filters and tone controls.

Subjects to be published during the year.
6. Power Amplifiers. 7. Constant Current circuits.
8. Opto-electronics. 9. Basic Logic Gate circuits.
10. Astables. 11. Micropower circuits.
12. Wideband Amplifiers. 13. Alarm circuits.
14. Pulse Modulators. 15. Digital counters.

To: J. Rider, Wireless World, IPC Business Press Limited. Sundry Sales Dept, 33 Bowling Green Lane, London, EC1R 0NE.

Please send me set no(s) ..... @ £1 (£1.15 o/s) each □*

I wish to subscribe to set Nos. 6-15 @ £9 (£10.50 o/s)
I enclose cheque/money order for £..... □*
*Tick as required

Name.....

Address.....

.....

Company registered in England. Registered office: Dorset House, Stamford Street, London SE1 9LU. Registered No: 677128

AMTRON kits are so absorbing

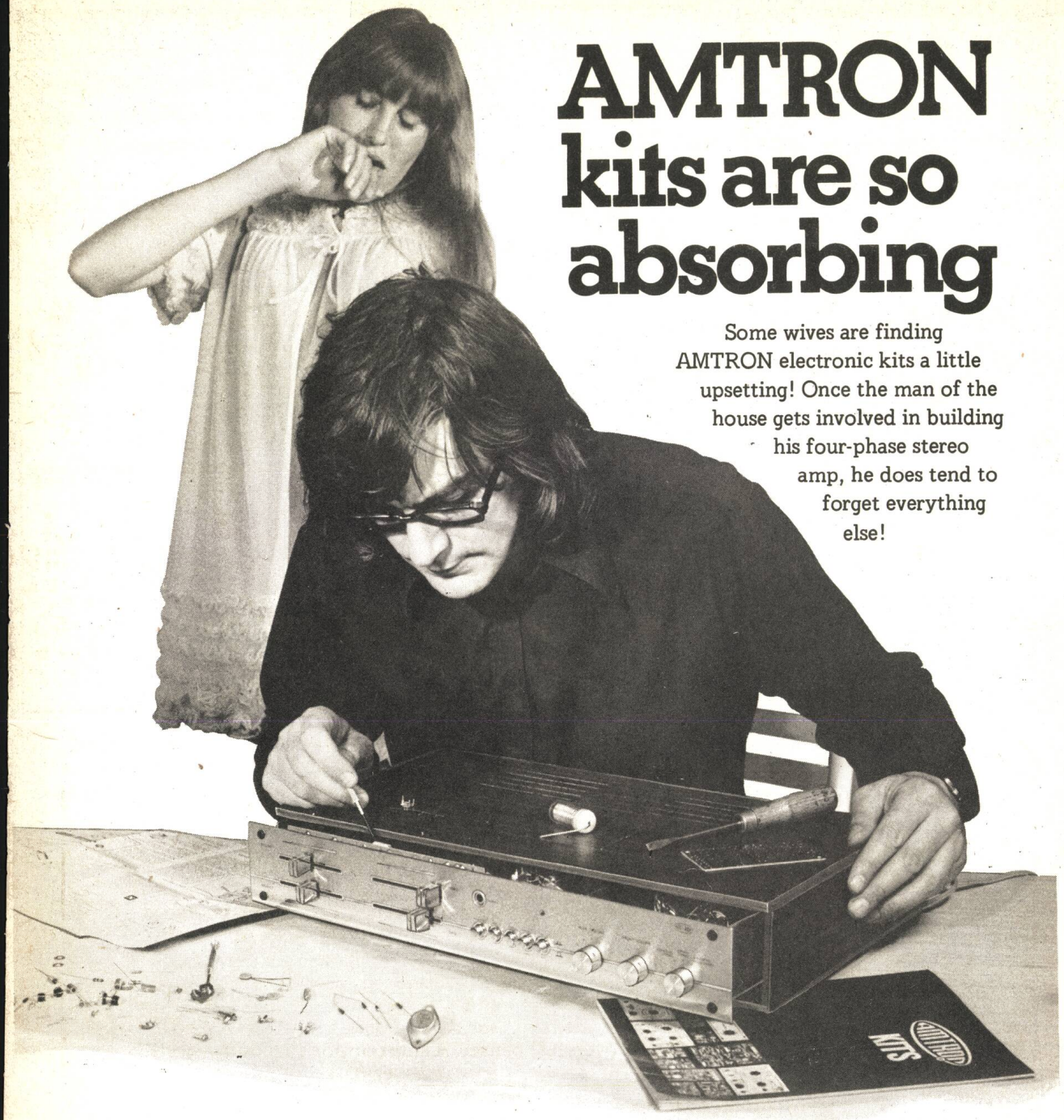

Some wives are finding AMTRON electronic kits a little upsetting! Once the man of the house gets involved in building his four-phase stereo amp, he does tend to forget everything else!

AMTRON produce a varied range of 200 electronic kits which include Power supplies; L.F. instruments; tuners; receivers and I.C. digital equipment.

Kits are sold in attractive blister packs which contain solder and full instructions.

Prices range from £1.10 to £80.

Next time the "little lady" starts to complain, try buying her a kit, and before you know it she'll be an AMTRON enthusiast too.

Contact your local stockist

AMTRON® UK

Trade & Education enquiries welcome

AMTRON U.K. LTD. 4 & 7 CASTLE STREET, HASTINGS, SUSSEX. TEL: HASTINGS 2875

TO SPARK YOUR IMAGINATION!

Kit comprises EVERYTHING: Case, cables, coil connectors, Silicon grease, 8-page instruction leaflet.

the

SPARKRITE

Electronic Ignition Kit only £9·35

Fascinating to build. Fantastic improvement to your car's performance. Complete Capacitive Discharge ignition system, fully proven, components fully guaranteed. Printed circuit design. All metalwork drilled ready. Fitted to car in 15 minutes when built.

• Sustained peak performance. • Up to 20% fuel saving. • Instant all-weather starting. Faster acceleration, higher top speed. • Suitable for all engines up to 8 cyls. • Longer spark plug life. • Longer battery life. • Contact breaker burn eliminated. • Purer exhaust gas emission.

A new development from the manufacturers of Gunton ignition. Price: **£9.35** inc. V.A.T. and postage. (12 volt only. State Pos. or Neg. earth). Ready built unit also available **£11.55** inc. V.A.T. and postage. GUARANTEED 5 YEARS.

ORDER NOW To: ELECTRONICS DESIGN ASSOCIATES,
82 Bath Street, Walsall WS1 3DE. Phone: 33652

Please send me one SPARKRITE Kit complete. I enclose P.O./Cheque for £9·35. Or for ready built unit £11·55.

NAME .....

ADDRESS .....

.....

.....

(Live near Walsall? Call in for an actual workshop demo. It really is convincing).

PE8

SPA RADIO

335–337 HIGH STREET, CHELTENHAM
GLOUCESTER. Tel 54303

Please Note: Add 10% V.A.T. to order total including post, packing and insurance. All goods new and manufacturer guaranteed. Post, packing and insurance in brackets.

Spatronic PB8C Mains 8 Track Cartridge Playback Unit. B.S.R. chassis, encased and wired to feed existing stereo system, **£11** (45p).
B.S.R. T145 Unit. As above but chassis only (wired), **£8·55** (40p).
B.S.R. C114 Mini-changer fitted X5H Comp. Cartridge. Unit fitted with 18½V overwind on motor for mono amplifier, **£3·90** (50p).
B.S.R. Model MP60 Single Play Turntable Unit (chassis), **£8·50** (70p).
B.S.R. Model MP60. As above but fitted G800 Mag. Cartridge, **£11·50** (75p).
Many bargain B.S.R. Auto Units for callers only at **£5 to £6** plus V.A.T.
Garrard SP25 Mk. 3 Single Play Turntable Unit (chassis). **£10·25** (75p).
Garrard SP25 Mk. 3 fitted plinth and cover, wired ready to play. **£18·75** (95p).
Garrard 2025 T/C fitted KS40A Cer. Stereo Cartridge (chassis), **£7.65** (75p).
Spatronic P1 Plinth/Base, Solid Afrormosia for above decks, **£2·10** (30p).
Spatronic C1 Cover to fit above plinth (most are tinted), **£1** (30p).
Garrard AP76 Single Play Trans. Turntable (chassis), **£19·50** (95p).
Garrard Zero 100S Single Play Trans. Turntable (chassis), **£34·50** (£1·20).
Spatronic P2 Plinth/Base, Solid Afrormosia for above decks, **£3** (35p).
Spatronic C2 Cover to fit above plinth (most are clear), **£1·60** (35p).
Spatronic E2 Equipment Cabinet designed for the B.S.R. C114 Mini-player. To house either a Mono Player or the Mullard Unilex. Ask for leaflet. Systems on permanent demonstration here.
Mullard Unilex Stereo Modules and Control Panel (complete), **£11·30** (75p).
Acos GP93.1 Stereo Crystal Cartridge. Exc. many amplifiers, **£1·30** (5p).
B.S.R. SC5 high quality Ceramic Cart. Perfect for Unilex, Dulci and many other ceramic input amplifiers, **£1·75** (6p).
Goldring G800 Magnetic Cartridge (very special offer), **£3·90** (20p).
Jap NN55 5in Cer. Magnet Speaker. Perfect for cassette ext. 8 ohm, **£1·10** (10p).
Electro-Acoustic 8RM 8in Cer. Magnet Speaker. State 8 or 15 ohm. Also Single or Dual Cone. Single, **£1·90**; Dual, **£2·15** (25p).
Electro-Acoustic 10RM Cer. Magnet Speaker. State 8 or 15 ohm. Also Single or Dual Cone. Single, **£2·25**; Dual, **£2·55** (28p).
Celestion PS12T/C 12in Dual Cone 20W Unit for hi-fi or good quality P.A. or Discotheque. Many cabinets for callers, **£8** (65p).
Goodmans 12P Disco/P.A. Speaker. 8 and 15 ohm heavy duty, **£10·50** (65p).
Dulci Model 207 7 + 7W R.M.S. Stereo Amplifier, **£15·90** (60p).
Kyoto Model S2000 10 + 10W R.M.S. Stereo Amplifier, **£23·90** (75p).
Keletron KSA700 7 + 7W R.M.S. Stereo Amplifier, **£22** (70p).
Keletron KSA1500 15 + 15W R.M.S. Stereo Amplifier, **£29** (80p).
Keletron KS4 Two Speaker System, 4W R.M.S., 8W music. Size: H. 11in; W. 6in, D. 6in. Freq. response 70–15,000Hz. Each **£7·30** (75p).
Keletron KS6 Three Speaker System, 6W R.M.S., 12W music. Size: H. 15in, W. 8in, D. 7in. Freq. Response 60–19,000Hz, **£9** (85p).
Keletron KS8 Three-Speaker System, 8W R.M.S., 16W music. Size: H. 19in, W. 10in, D. 9in. Freq. response 40–19,000Hz, **£11·75** (95p).

WINDSCREEN WIPER DELAY KIT

Complete kit of parts including drilled and tinned fibreglass printed circuit board.

The unit provides intermittent wiper operation with a delay up to approximately 60 seconds which can be varied to optimise visibility in conditions of light rain, spray, etc. The original wiper switch overrides when normal operation is required.

Suitable for most British cars

£2·86 inc. V.A.T. and P.&P.

ESSEX X-RAY CO. LTD.
Cash with order
57 THEYDON PARK RD.
THEYDON BOIS, EPPING, ESSEX CM16 7LR

LIQUID WHEEL AND CASSETTE PROJECTORS

Specially designed for discotheque lighting this machine uses a 300 watt power cooled bulb that has a two-position intensity switch combined with a long lamp life protection circuit. An image up to 20ft across can be projected in a darkened room at a distance of 35ft. Cassette machine (illustrated) will take a range of cassettes including moire patterns. The liquid wheel machine will only accept liquid or crystal wheels but gives a more vivid effect.

Price (cash with order) liquid wheel projector **£33·95**; cassette projector **£36·95.**
Supplied complete with one effect post free.

M.V. AMPLIFICATIONS
ORCHARD MEADOW, UFFINGTON ROAD, STAMFORD, LINCS.

THIS IS THE FIRST PAGE OF THE GREAT BI-PAK SECTION

BRAND NEW FULLY GUARANTEED DEVICES

AC107	0·22	AD162	0·37	BC148	0·11	BD137	0·50	BF188	0·44	OC19	0·39	2G371	0·18	2N2219	0·22	2N3054	0·51	2N4059	0·11
AC113	0·22	AD161 &		BC149	0·13	BD138	0·55	BF194	0·13	OC20	0·70	2G371B	0·13	2N2220	0·24	2N3055	0·55	2N4060	0·13
AC115	0·26	AD162(MP)		BC150	0·20	BD139	0·61	BF195	0·13	OC22	0·42	2G373	0·19	2N2221	0·22	2N3391	0·16	2N4061	0·13
AC117K	0·22		0·61	BC151	0·22	BD140	0·66	BF196	0·16	OC23	0·46	2G374	0·19	2N2222	0·22	2N3391A	0·18	2N4062	0·13
AC122	0·13	ADT140	0·55	BC152	0·19	BD155	0·88	BF197	0·16	OC24	0·62	2G377	0·33	2N2368	0·19	2N3392	0·16	2N4284	0·19
AC125	0·19	AF114	0·27	BC153	0·31	BD175	0·66	BF200	0·50	OC25	0·42	2G378	0·18	2N2369	0·16	2N3393	0·16	2N4285	0·19
AC126	0·19	AF115	0·27	BC154	0·33	BD176	0·66	BF222	1·05	OC26	0·28	2G381	0·18	2N2369A	0·16	2N3394	0·16	2N4286	0·19
AC127	0·19	AF116	0·27	BC157	0·20	BD177	0·72	BF257	0·50	OC28	0·55	2G382	0·18	2N2411	0·27	2N3395	0·19	2N4287	0·19
AC128	0·19	AF117	0·27	BC158	0·13	BD178	0·72	BF258	0·66	OC29	0·55	2G401	0·33	2N2412	0·27	2N3402	0·23	2N4288	0·19
AC132	0·16	AF118	0·39	BC159	0·13	BD179	0·77	BF259	0·94	OC35	0·46	2G414	0·33	2N2646	0·52	2N3403	0·23	2N4289	0·19
AC134	0·16	AF124	0·33	BC160	0·50	BD180	0·77	BF262	0·61	OC36	0·55	2G417	0·28	2N2711	0·23	2N3404	0·31	2N4290	0·19
AC137	0·16	AF125	0·28	BC161	0·55	BD185	0·72	BF263	0·61	OC41	0·22	2N388	0·39	2N2712	0·23	2N3405	0·46	2N4291	0·19
AC141	0·16	AF126	0·31	BC167	0·13	BD186	0·72	BF270	0·39	OC42	0·27	2N388A	0·61	2N2714	0·23	2N3414	0·17	2N4292	0·19
AC141K	0·19	AF127	0·31	BC168	0·13	BD187	0·77	BF271	0·33	OC44	0·17	2N404	0·22	2N2904	0·19	2N3415	0·17	2N4293	0·19
AC142	0·16	AF139	0·33	BC169	0·13	BD188	0·77	BF272	0·88	OC45	0·14	2N404A	0·31	2N2904A	0·23	2N3416	0·31	2N5172	0·13
AC142K	0·19	AF178	0·33	BC170	0·13	BD189	0·83	BF273	0·39	OC70	0·11	2N524	0·46	2N2905	0·23	2N3417	0·31	2N5457	0·35
AC151	0·17	AF179	0·55	BC171	0·16	BD190	0·83	BF274	0·39	OC71	0·11	2N527	0·54	2N2905A	0·23	2N3525	0·83	2N5458	0·35
AC154	0·22	AF180	0·55	BC172	0·16	BD195	0·94	BFW10	0·66	OC72	0·16	2N598	0·46	2N2906	0·17	2N3646	0·10	2N5459	0·44
AC155	0·22	AF181	0·50	BC173	0·16	BD196	0·94	BFX29	0·30	OC74	0·16	2N599	0·50	2N2906A	0·20	2N3702	0·11	2S301	0·55
AC156	0·22	AF186	0·50	BC174	0·16	BD197	0·99	BFX84	0·24	OC75	0·17	2N696	0·14	2N2907	0·22	2N3703	0·11	2S302A	0·46
AC157	0·27	AF239	0·41	BC175	0·24	BD198	0·99	BFX85	0·33	OC76	0·17	2N697	0·15	2N2907A	0·24	2N3704	0·12	2S302	0·46
AC165	0·22	AL102	0·72	BC177	0·21	BD199	1·05	BFX86	0·24	OC77	0·28	2N698	0·27	2N2923	0·16	2N3705	0·11	2S303	0·61
AC166	0·22	AL103	0·72	BC178	0·21	BD200	1·05	BFX87	0·27	OC81	0·17	2N699	0·39	2N2924	0·16	2N3706	0·10	2S034	0·77
AC167	0·22	ASY26	0·28	BC179	0·21	BD205	0·88	BFX88	0·24	OC81D	0·17	2N706	0·09	2N2925	0·16	2N3707	0·12	2S305	0·93
AC168	0·27	ASY27	0·33	BC180	0·27	BD206	0·88	BFY50	0·22	OC82	0·17	2N706A	0·10	2N2926 (G)		2N3708	0·08	2S306	0·93
AC169	0·16	ASY28	0·28	BC181	0·27	BD207	1·05	BFY51	0·22	OC82D	0·17	2N708	0·13		0·14	2N3709	0·10	2S307	0·93
AC176	0·22	ASY29	0·28	BC182	0·11	BD208	1·05	BFY52	0·22	OC83	0·22	2N711	0·33	2N2926 (Y)		2N3710	0·10	2S321	0·62
AC177	0·27	ASY50	0·28	BC182L	0·11	BDY20	1·10	BFY53	0·19	OC84	0·22	2N717	0·39		0·12	2N3711	0·10	2S322	0·46
AC178	0·31	ASY51	0·28	BC183	0·11	BF115	0·27	BFX25	0·94	OC139	0·22	2N718	0·27	2N2926 (O)		2N3819	0·31	2S322A	0·46
AC179	0·31	ASY52	0·28	BC183L	0·11	BF117	0·50	BSX19	0·17	OC140	0·22	2N718A	0·55		0·11	2N3820	0·55	2S323	0·62
AC180	0·19	ASY54	0·28	BC184	0·13	BF118	0·77	BSX20	0·17	OC169	0·28	2N726	0·31	2N2926 (R)		2N3821	0·39	2S324	0·77
AC180K	0·22	ASY55	0·28	BC184L	0·13	BF119	0·77	BSY25	0·17	OC170	0·28	2N727	0·31		0·11	2N3823	0·31	2S325	0·77
AC181	0·19	ASY56	0·28	BC186	0·31	BF121	0·50	BSY26	0·17	OC171	0·28	2N743	0·22	2N2926 (B)		2N3903	0·31	2S326	0·77
AC181K	0·22	ASY57	0·28	BC187	0·31	BF123	0·55	BSY27	0·17	OC200	0·28	2N744	0·22		0·11	2N3904	0·33	2S327	0·77
AC187	0·24	ASY58	0·28	BC207	0·12	BF125	0·50	BSY28	0·17	OC201	0·31	2N914	0·16	2N3010	0·77	2N3905	0·31	2S701	0·46
AC187K	0·22	ASZ21	0·44	BC208	0·12	BF127	0·55	BSY29	0·17	OC202	0·31	2N918	0·33	2N3011	0·16	2N3906	0·30	40361	0·44
AC188	0·24	BC107	0·10	BC209	0·13	BF152	0·61	BSY38	0·20	OC203	0·28	2N929	0·23	2N3053	0·19	2N4058	0·13	40362	0·50
AC188K	0·22	BC108	0·10	BC212L	0·12	BF153	0·50	BSY39	0·20	OC204	0·28	2N930	0·23						
ACY17	0·28	BC109	0·11	BC213L	0·12	BF154	0·50	BSY40	0·31	OC205	0·39	2N1131	0·22						
ACY18	0·22	BC113	0·11	BC214L	0·16	BF155	0·77	BSY41	0·31	OC309	0·44	2N1132	0·24						
ACY19	0·22	BC114	0·17	BC225	0·28	BF156	0·53	BSY95	0·14	OCP71	0·48	2N1302	0·16						
ACY20	0·22	BC115	0·17	BC226	0·39	BF157	0·61	BSY95A	0·14	ORP12	0·48	2N1303	0·16						
ACY21	0·22	BC116	0·17	BCY30	0·27	BF158	0·61	Bu105	2·20	ORP60	0·44	2N1304	0·19						
ACY22	0·18	BC117	0·17	BCY31	0·29	BF159	0·66	C111E	0·55	ORP61	0·44	2N1305	0·19						
ACY27	0·20	BC118	0·11	BCY32	0·33	BF160	0·44	C400	0·33	P346A	0·22	2N1306	0·23						
ACY28	0·21	BC119	0·33	BCY33	0·24	BF162	0·44	C407	0·28	P397	0·46	2N1307	0·23						
ACY29	0·39	BC120	0·88	BCY34	0·28	BF163	0·44	C424	0·22	ST140	0·14	2N1308	0·26						
ACY30	0·31	BC125	0·13	BCY70	0·16	BF164	0·44	C425	0·55	ST141	0·19	2N1309	0·26						
ACY31	0·31	BC126	0·20	BCY71	0·20	BF165	0·44	C426	0·39	TI843	0·33	2N1613	0·22						
ACY34	0·23	BC132	0·13	BCY72	0·16	BF167	0·24	C428	0·22	UT46	0·30	2N1711	0·22						
ACY35	0·23	BC134	0·20	BCZ10	0·22	BF173	0·24	C441	0·33	2G301	0·21	2N1889	0·35						
ACY36	0·31	BC135	0·13	BCZ11	0·28	BF176	0·39	C442	0·33	2G302	0·21	2N1890	0·50						
ACY40	0·19	BC136	0·17	BCZ12	0·28	BF177	0·39	C444	0·39	2G303	0·21	2N1893	0·41						
ACY41	0·20	BC137	0·17	BD121	0·66	BF178	0·33	C450	0·24	2G304	0·27	2N2147	0·79						
ACY44	0·39	BC139	0·44	BD123	0·72	BF179	0·33	MAT100	0·21	2G306	0·44	2N2148	0·63						
AD130	0·42	BC140	0·33	BD124	0·66	BF180	0·33	MAT101	0·22	2G308	0·39	2N2160	0·66						
AD140	0·53	BC141	0·33	BD131	0·55	BF181	0·33	MAT120	0·21	2G309	0·39	2N2192	0·39						
AD142	0·53	BC142	0·33	BD132	0·66	BF182	0·44	MAT121	0·22	2G339	0·22	2N2193	0·39						
AD143	0·42	BC143	0·33	BD133	0·72	BF183	0·44	MPF102	0·46	2G339A	0·18	2N2194	0·39						
AD149	0·55	BC145	0·50	BD135	0·44	BF184	0·28	MPF104	0·41	2G344	0·20	2N2217	0·24						
AD161	0·37	BC147	0·11	BD136	0·44	BF185	0·33	MPF105	0·41	2G345	0·18	2N2218	0·22						

DIODES AND RECTIFIERS

AA119	0·09	BY133	0·23	OA10	0·39
AA120	0·09	BY164	0·55	OA47	0·08
AA129	0·09	BYX38/30		OA70	0·08
AAY30	0·10		0·46	OA79	0·08
AAZ13	0·11	BYZ10	0·39	OA81	0·08
BA100	0·11	BYZ11	0·33	OA85	0·10
BA116	0·23	BYZ12	0·33	OA90	0·07
BA126	0·24	BYZ13	0·28	OA91	0·07
BA148	0·16	BYZ16	0·44	OA95	0·08
BA154	0·13	BYZ17	0·39	OA200	0·07
BA155	0·16	BYZ18	0·39	OA202	0·08
BA156	0·15	BYZ19	0·31	SD10	0·06
BY100	0·17	CG62		SD19	0·06
BY101	0·13	(OA91 Eq.)		1N34	0·08
BY105	0·19		0·06	1N34A	0·08
BY114	0·13	CG651—		1N914	0·07
BY126	0·16	(OA70–OA79)		1N916	0·07
BY127	0·17		0·07	1N414B	0·07
BY128	0·17	OA5	0·39	1S021	0·11
BY130	0·18	OA58L	0·23	1S951	0·07

Cut these 3 pages out and keep for reference

NEW COMPONENT PAK BARGAINS

Pak No.	Qty.	Description	Price
C 1	250	Resistors mixed values approx. (count by weight)	0·55
C 2	200	Capacitors mixed values approx. (count by weight)	0·55
C 3	50	Precision Resistors 1% mixed values	0·55
C 4	75	¼th W Resistors mixed preferred values	0·55
C 5	5	Pieces assorted Ferrite Rods	0·55
C 6	2	Tuning Gangs, MW/LW VHF	0·55
C 7	1	Pack Wire 50 meters assorted colours	0·55
C 8	10	Reed Switches	0·55
C 9	3	Micro Switches	0·55
C10	15	Assorted Pots & Pre-Sets	0·55
C11	5	Jack Sockets 3 × 3·5m 2 × Standard Switch Types	0·55
C12	40	Paper Condensers preferred types mixed values	0·55
C13	20	Electrolytics Trans. types	0·55
C14	1	Pack assorted Hardware—Nuts/Bolts, Gromets, etc.	0·55
C15	4	Mains Slide Switches, full POINT	0·55
C16	20	Assorted Tag Strips & Panels	0·55
C17	10	Assorted Control Knobs	0·55
C18	4	Rotary Wave Change Switches	0·55
C19	3	Relays 6—24V Operating	0·55
C20	4	Sheets Copper Laminate approx. 10in × 7in	0·55

Please add 10p post and packing on all component packs, plus a further 10p on pack Nos. C1, C2, C19 and C20.

Component Lists for mail order available on request.

Plus much more—send now for the BI-PAK "component catalogue"

5p to cover postage, etc.

JUMBO COMPONENT PAKS

Mixed Electronic Components

Resistors, capacitors, pots, electrolytics and coils plus many other useful items. Approximately 3lb in weight. Price including P. & P. £1·65.

EXCEPTIONALLY GOOD VALUE

BRAND NEW POST OFFICE TYPE TELEPHONE DIALS ONLY 83p each

THE NEW S.G.S. EA 1000 AUDIO AMP MODULE *Guarantee

3 Watts R.M.S. ONLY £2·89 each

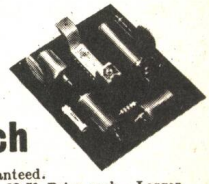

Module Tested and Guaranteed.
Qty. 1—9 £2·89; 10—25 £2·51 Price each. Larger quantities quoted on request. Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.

SYSTEM 12 STEREO

Each Kit contains two Amplifier Modules, 3 watts RMS, two loudspeakers, 15 ohms, the pre-amplifier, transformer, power supply module, front panel and other accessories, as well as an illustrated stage-by-stage instruction booklet designed for the beginner.
Further details available on request.

ONLY £18·64 FREE P. & P.

NOW—TURN OVER FOR MORE FANTASTIC OFFERS

The largest selection

NEW LOW PRICED TESTED S.C.R.'S

	PIV 50	100	200	400	600	800
	£p	£p	£p	£p	£p	£p
1A TO5	0·26	0·28	0·34	0·48	0·59	0·70
3A TO66	0·28	0·37	0·41	0·52	0·63	0·77
5A TO66	0·34	0·52	0·54	0·62	0·75	0·88
5A TO64	0·34	0·52	0·54	0·62	0·75	0·88
7A TO48	0·52	0·55	0·63	0·74	0·85	0·99
10A TO48	0·56	0·64	0·67	0·83	1·07	1·32
16A TO48	0·59	0·70	0·83	1·03	1·38	1·65
30A TO48	1·27	1·54	1·76	1·93	—	4·40

SIL. RECTS. TESTED

PIV	300mA DO7	750mA SO16	1A Plastic	1·5A SO16	3A SO10	10A SO10	30A SO32A
50	0·04	0·06	0·06	0·08	0·16	0·23	0·66
100	0·04	0·07	0·06	0·15	0·18	0·26	0·83
200	0·06	0·10	0·07	0·16	0·22	0·27	1·10
400	0·07	0·15	0·08	0·22	0·30	0·41	1·38
600	0·08	0·18	0·11	0·26	0·38	0·50	2·05
800	0·11	0·19	0·12	0·28	0·41	0·61	2·20
1000	0·12	0·30	0·16	0·33	0·51	0·70	2·75
1200	—	0·37	—	0·42	0·63	0·83	—

TRIACS

VBOM	2A TO-66	6A TO-66	10A TO-48
	£p	£p	£p
100V	33	55	83
200V	55	66	99
400V	77	83	1·21

DIACS

FOR USE WITH TRIACS
BR100 (D32) **41p** each

FREE

One 50p Pak of your own choice free with orders valued £4 or over.

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed

Pak No.		EQVT
T1	8	2G3713 OC71
T2	8	D1374 OC75
T3	8	D1216 OC81D
T4	8	2G381T OC81
T5	8	2G382T OC82
T6	8	2G344B OC44
T7	8	2G345B OC45
T8	8	2G378 OC78
T9	8	2G399A 2N1302
T10	8	2G417 AF117

All **55p** each pak

2N2060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS. Our price **28p** each.

120 VCB NIXIE DRIVER TRANSISTOR. Sim. BSX21 & C407, 2N1893 FULLY TESTED AND CODED ND 120. 1-24 **19p** each. TO-5 N.P.N. 25 up **17p** each.

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqvt. ZTX300 **6p** each. Any Quantity.

ZENER DIODES

400mW (DO-7 Case), range 2–33V, **15p** each. 1·5W (Top-Hat), range 2–33V, **20p** each. 10W (SO-10 Stud), range 2–33V, **33p** each.

10 amp POTTED BRIDGE RECTIFIER on heat sink. 100PIV. 99p each

NEW LINE Plastic Encapsulated 2 Amp. BRIDGE RECTS.

50V RMS	**35p** each
100V RMS	**41p** each
400V RMS	**51p** each

Size 15mm × 6mm.

UNIJUNCTION TRANSISTORS

Direct replacement for TIS43 and BEN3000 also electrically equivalent to 2N2646 Qty.: 1–24 **30p** each, 25–99 **28p** each, 100+ **22p** each.

CADMIUM CELLS

ORP12 **48p**
ORP60, ORP61 **44p** each

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706/8. BSY-27/28/95A. All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

		£p
20	For	0·55
50	For	1·10
100	For	1·92
500	For	8·25
1000	For	14·30

SIL. G.P. DIODES £p

300mW	30	0·55
40PIV(Min.)	100	1·65
Sub-Min.	500	5·50
Full Tested	1,000	9·90

Ideal for Organ Builders.

POWER TRANS BONANZA!

GENERAL PURPOSE GERM. PNP
Coded GP100. BRAND NEW TO-3 CASE. PO88. REPLACE:—OC25–28–29–30–35–36. NKT 401–403–404–405–406–430–451–452–453. T13027–3028, 2N260A, 2N456A–457A–458A, 2N511 A & B. 2G220–222, ETC. VCBO 80V VCEO 50V IC 10A PT. 30 WATTS Hfe 30–170.

PRICE	1–24	25–99	100 up
	47p each	44p each	40p each

SILICON High Voltage 250V NPN TO-3 case. G.P. Switching & Amplifier Applications. Brand new Coded R 2400 VCBO 250/VCEO 100/IC 6A/30 Watts. HFE type 20/fT 5MHZ.
OUR PRICE EACH:

1–24	25–99	100 up
55p	50p	44p

2N3055
115 WATT SIL POWER NPN
55p EACH

AD161/162 *PNP*
M/P COMP GERM TRANS. OUR LOWEST PRICE OF 60p *PER PAIR*

KING OF THE PAKS — Unequalled Value and Quality

SUPER PAKS — NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.		Description	Price
U 1	120	Glass Sub-Min. General Purpose Germanium Diodes	0·55
U 2	60	Mixed Germanium Transistors AF/RF	0·55
U 3	75	Germanium Gold Bonded Sub-Min. like OA5, OA47	0·55
U 4	40	Germanium Transistors like OC81, AC128	0·55
U 5	60	200mA Sub-Min. Silicon Diodes	0·55
U 6	30	Sil. Planar Trans. NPN like BSY95A. 2N706	0·55
U 7	16	Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000	0·55
U 8	50	Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0·55
U 9	20	Mixed Voltages, 1 Watt Zener Diodes	0·55
U10	20	BAY50 charge storage Diodes DO-7 Glass	0·55
U11	25	PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0·55
U12	12	Silicon Rectifiers Epoxy 500mA up to 800 PIV	0·55
U13	30	PNP-NPN Sil. Transistors OC200 & 2S 104	0·55
U14	150	Mixed Silicon and Germanium Diodes	0·55
U15	25	NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	0·55
U16	10	3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0·55
U17	30	Germanium PNP AF Transistors TO-5 like ACY 17-22	0·55
U18	8	6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0·55
U19	25	Silicon NPN Transistors like BC108	0·55
U20	12	1·5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0·55
U21	30	AF. Germanium Alloy Transistors 2G300 Series & OC71	0·55
U23	30	MADT's like MHz Series PNP Transistors	0·55
U24	20	Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0·55
U25	25	300MHz NPN Silicon Transistors 2N708, BSY27	0·55
U26	30	Fast Switching Silicon Diodes like IN914 Micro-Min.	0·55
U27	12	NPN Germanium AF Transistors TO-1 like AC127	0·50
U29	10	1 Amp SCR's TO-5 can, up to 600 PIV CRS1/25-600	1·15
U30	15	Plastic Silicon Planar Trans. NPN 2N2926	0·55
U31	20	Silicon Planar Plastic NPN Trans. Low Noise Amp 2N3707	0·55
U32	25	Zener Diodes 400mW DO-7 case 3–18 volts mixed	0·55
U33	15	Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0·55
U34	30	Silicon PNP Alloy Trans. TO-5 BCY26 2S302/4	0·55
U35	25	Silicon Planar Transistors PNP TO-18 2N2906	0·55
U36	25	Silicon Planar NPN Transistors TO-5 BFY50/51/52	0·55
U37	30	Silicon Alloy Transistors SO-2 PNP OC200, 2S322	0·55
U38	20	Fast Switching Silicon Trans. NPN 400MHz 2N3011	0·55
U39	30	RF. Germ. PNP Transistors 2N1303/5 TO-5	0·55
U40	10	Dual Transistors 6 lead TO-5 2N2060	0·55
U41	25	RF Germanium Transistors TO-5, OC45, NKT72	0·55
U42	10	VHF Germanium PNP Transistors TO-1 NKT667, AF117	0·55
U43	25	Sil. Trans. Plastic TO-18 A.F. BC113/114	0·55
U44	20	Sil. Trans. Plastic TO-5 BC115/NPN	0·55
U45	7	3A SCR. TO66 up to 600PIV	1·10

Code Nos. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

SILICON PHOTO TRANSISTOR. TO-18 Lens end NPN Sim. to BP × 25 and P21. BRAND NEW. Full data available. Fully guaranteed. Qty. 1·24 25·99 100 up
Price each **69p 44p 38p**

F.E.T.'S

2N3819	31p	2N5458	35p
2N3820	55p	2N5459	44p
2N3821	34p	BFW10	66p
2N3823	31p	MPF105	41p

NEW 6TH EDITION

TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK **99p** each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX STOCK. SEND FOR FREE LIST.

SILICON 50 WATTS MATCHED NPN/PNP
BIP 19 NPN TO-3 Plastic. BIP 20 PNP. Brand new. VCBO 100/VCEO 50/IC 10A. HFE type 100/ft 3mHZ.
OUR PRICE PER PAIR:

1–24 prs: 66p	25–99 prs. 61p	100 prs. 55p

QUALITY TESTED SEMICONDUCTORS

Pak No.			P
Q 1	20	Red spot transistors *pnp*	0
Q 2	16	White spot R.F. transistors *pnp*	0
Q 3	4	OC77 type transistors	0
Q 4	6	Matched transistors OC44/45/81/81D	0
Q 5	4	OC75 transistors	0
Q 6	5	OC72 transistors	0
Q 7	4	AC128 transistors *pnp* high gain	0
Q 8	4	AC126 transistors *pnp*	0
Q 9	7	OC81 type transistors	0
Q10	7	OC71 type transistors	0
Q11	2	AC127/128 Complementary pairs *pnp/npn*	0
Q12	3	AF116 type transistors	0
Q13	3	AF117 type transistors	0
Q14	3	OC171 H.F. type transistors	0
Q15	7	2N2926 Sil. Epoxy transistors mixed colours	0
Q16	2	GET880 low noise Germanium transistors	0
Q17	5	*npn* 2 × ST.141 & 3 × ST.140	0
Q18	4	MADT'S 2 × MAT 100 & 2 × MAT 120	0
Q19	3	MADT'S 2 × MAT 101 & 1 × MAT 121	0
Q20	4	OC44 Germanium transistors A.F.	0
Q21	4	AC127 *npn* Germanium transistors	0
Q22	20	NKT transistors A.F. R.F. coded	0
Q23	10	OA202 Silicon diodes sub-min.	0
Q24	8	OA81 diodes	0
Q25	15	IN914 Silicon diodes 75PIV 75mA	0
Q26	8	OA95 Germanium diodes sub-min IN69	0
Q27	2	10A 600 PIV Silicon rectifiers IS425R	0
Q28	2	Silicon power rectifiers BYZ13	0
Q29	4	Silicon transistors 2 × 2N696, 1 × 2N697, 1 × 2N698	0
Q30	7	Silicon switch transistors 2N706 *npn*	0
Q31	6	Silicon switch transistors 2N708, *npn*	0
Q32	3	*pnp* Silicon transistors 2 × 2N1131, 1 × 2N1132	0
Q33	3	Silicon *npn* transistors 2N1711	0
Q34	7	Silicon *npn* transistors 2N2369, 500MHz (code P397)	0
Q35	3	Silicon *pnp* TO-5. 2 × 2N2904 & 1 × 2N2905	0
Q36	7	2N3646 TO-18 plastic 300MHz *npn*	0
Q37	3	2N3053 *npn* Silicon transistors	0
Q38	7	*pnp* transistors 4 × 2N3703, 3 × 2N3702	0

ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify Electronic calculations features the following scales: Conversion of Frequency and Wavelength. Calculation of L, C and fo of Tuned Circuit. Reactance and Self Inductance. Area of Circle. Volume of Cylinders. Resistance of Conductor. Weight of Conductors. Decibel Calculation. Angle Functions. Natural Logs and "e" Function. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and H. A must for every electronic engineer and enthusiast. Size: 2cm × 4cm. Complete with case and instructions. Price each: £3·6

INTEGRATED CIRCUIT PAKS

Manufacturers' "Fall Outs" which include Functional and Part-Functional Units. These are classed as 'out-of-spec' from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price
UIC00	12 × 7400	0·55
UIC01	12 × 7401	0·55
UIC02	12 × 7402	0·55
UIC03	12 × 7403	0·55
UIC04	12 × 7404	0·55
UIC05	12 × 7405	0·55
UIC06	8 × 7406	0·55
UIC07	8 × 7407	0·55
UIC10	12 × 7410	0·55
UIC13	8 × 7413	0·55
UIC20	12 × 7420	0·55
UIC30	12 × 7430	0·55
UIC40	12 × 7440	0·55
UIC41	5 × 7441	0·55
UIC42	5 × 7442	0·55
UIC43	5 × 7443	0·55
UIC44	5 × 7444	0·55
UIC45	5 × 7445	0·55
UIC46	5 × 7446	0·55
UIC47	5 × 7447	0·55
UIC48	5 × 7448	0·55
UIC50	12 × 7450	0·55
UIC51	12 × 7451	0·55
UIC53	12 × 7453	0·55
UIC54	12 × 7454	0·55
UIC60	12 × 7460	0·55
UIC70	8 × 7470	0·55
UIC72	8 × 7472	0·55
UIC73	8 × 7473	0·55
UIC74	8 × 7474	0·55
UIC75	8 × 7475	0·55
UIC76	8 × 7476	0·55
UIC80	5 × 7480	0·55
UIC81	5 × 7481	0·55
UIC82	5 × 7482	0·55
UIC83	5 × 7483	0·55
UIC86	5 × 7486	0·55
UIC90	5 × 7490	0·55
UIC91	5 × 7491	0·55
UIC92	5 × 7492	0·55
UIC93	5 × 7493	0·55
UIC94	5 × 7494	0·55
UIC95	5 × 7495	0·55
UIC96	5 × 7496	0·55
UIC100	5 × 74100	0·55
UIC121	5 × 74121	0·55
UIC141	5 × 74141	0·55
UIC151	5 × 74151	0·55
UIC154	5 × 74154	0·55
UIC193	5 × 74193	0·55
UIC199	5 × 74199	0·55
UICXI	25 Assorted 74's	1·65

Paks cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

BI-PAKS NEW COMPONENT SHOP NOW OPEN WITH A WIDE RANGE OF ELECTRONIC COMPONENTS AND ACCESSORIES AT COMPETITIVE PRICES—

18 BALDOCK STREET (A10), WARE, HERTS.
TEL. (STD 0920) 61593
open MON.-SAT. 9.15 a.m. to 6 p.m., FRIDAY until 8 p.m.

All mail orders please add 10p post and packing.
Send all orders to BI-PAK, P.O. BOX 6, WARE, HERTS.

-the lowest prices!

74 Series T.T.L. I.C's

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS

	1	25	100+		1	25	100+
SN7400	0·17	0·16	0·13	SN7486	0·35	0·34	0·33
SN7401	0·17	0·16	0·13	SN7489	6·05	5·78	5·50
SN7402	0·17	0·16	0·13	SN7490	0·74	0·71	0·64
SN7403	0·17	0·16	0·13	SN7491	1·10	1·05	0·99
SN7404	0·17	0·16	0·13	SN7492	0·74	0·71	0·64
SN7405	0·17	0·16	0·13	SN7493	0·74	0·71	0·64
SN7406	0·39	0·34	0·31	SN7494	0·85	0·82	0·75
SN7407	0·39	0·34	0·31	SN7495	0·35	0·82	0·75
SN7408	0·20	0·14	0·18	SN7496	0·86	0·93	0·86
SN7409	0·20	0·19	0·18	SN74100	1·82	1·76	1·71
SN7410	0·17	0·16	0·13	SN74104	1·07	1·04	0·97
SN7411	0·28	0·24	0·26	SN74105	1·07	1·04	0·97
SN7412	0·39	0·34	0·31	SN74107	0·44	0·42	0·40
SN7413	0·32	0·29	0·27	SN74110	0·51	0·59	0·55
SN7416	0·48	0·44	0·42	SN74111	1·38	1·27	1·21
SN7417	0·48	0·44	0·42	SN74118	1·10	1·05	0·99
SN7420	0·17	0·16	0·13	SN74119	1·40	1·38	1·21
SN7422	0·55	0·53	0·50	SN74121	0·44	0·41	0·38
SN7423	0·55	0·53	0·50	SN74122	1·54	1·43	1·21
SN7425	0·55	0·53	0·50	SN74123	3·08	2·97	2·86
SN7426	0·50	0·46	0·44	SN74141	0·74	0·71	0·64
SN7427	0·50	0·46	0·44	SN74145	1·65	1·54	1·43
SN7428	0·77	0·72	0·66	SN74150	3·30	2·97	2·75
SN7430	0·17	0·16	0·13	SN74151	1·10	1·05	0·99
SN7432	0·50	0·46	0·44	SN74153	1·32	1·21	1·05
SN7433	0·88	0·83	0·77	SN74154	1·98	1·87	1·76
SN7437	0·71	0·68	0·66	SN74155	1·54	1·43	1·32
SN7438	0·71	0·68	0·66	SN74156	1·54	1·43	1·32
SN7440	0·17	0·16	0·13	SN74157	2·09	1·98	1·87
SN7441	0·74	0·71	0·64	SN74160	1·98	1·87	1·76
SN7442	0·74	0·71	0·64	SN74161	1·98	1·87	1·76
SN7443	1·43	1·88	1·32	SN74162	4·40	4·13	3·85
SN7444	1·43	1·38	1·32	SN74163	4·40	4·13	3·85
SN7445	1·98	1·95	1·93	SN74164	2·42	2·37	2·31
SN7446	1·07	1·04	0·97	SN74165	2·48	2·42	2·37
SN7447	1·10	1·07	1·05	SN74166	3·85	3·58	3·30
SN7448	1·10	1·07	1·05	SN74174	2·53	2·42	2·31
SN7450	0·17	0·16	0·13	SN74175	1·76	1·65	1·54
SN7451	0·17	0·16	0·13	SN74176	2·75	2·64	2·53
SN7453	0·17	0·16	0·13	SN74177	2·75	2·64	2·53
SN7454	0·17	0·16	0·13	SN74180	2·20	1·76	1·54
SN7460	0·17	0·16	0·13	SN74181	6·05	5·50	5·23
SN7470	0·32	0·29	0·27	SN74182	2·20	1·98	1·76
SN7472	0·32	0·29	0·27	SN74184	3·85	3·58	3·30
SN7473	0·41	0·39	0·35	SN74190	2·15	2·09	2·04
SN7474	0·41	0·39	0·35	SN74191	2·09	2·04	1·98
SN7475	0·50	0·48	0·46	SN74192	2·15	2·09	2·04
SN7476	0·44	0·43	0·43	SN74193	2·20	1·98	1·93
SN7480	0·74	0·71	0·64	SN74194	2·97	2·86	2·75
SN7481	1·32	1·27	1·21	SN74195	2·20	2·09	1·98
SN7482	0·96	0·95	0·94	SN74196	1·98	1·87	1·76
SN7483	1·21	1·16	1·05	SN74197	1·98	1·87	1·76
SN7484	1·10	1·05	0·99	SN74198	6·05	5·50	4·95
SN7485	3·96	3·85	3·74	SN74199	6·05	5·50	4·95

LINEAR I.C.'s—FULL SPEC.

Type No.	Price 1–24	25–99	100+
BP201C—SL201C	0·70	0·59	0·50
BP710C—SL701C	0·70	0·55	0·50
BP702C—SL702C	0·70	0·55	0·50
BP702—72702	0·59	0·50	0·44
BP709—72709	0·40	0·39	0·33
BP709P—μA709C	0·40	0·38	0·33
BP710—72710	0·40	0·46	0·44
BP711—μA711	0·40	0·48	0·44
BP741—72741	0·55	0·50	0·45
μA703C	0·31	0·29	0·27
TAA263	0·77	0·66	0·61
TAA293	0·99	0·83	0·77
TAA350	1·87	1·74	1·65
EA1000	2·90		

ROCK BOTTOM PRICES LOGIC DTL 930 Series I.C's

Type No.	Price 1–24	25–99	100 up
BP930	0·13	0·12	0·11
BP932	0·14	0·13	0·12
BP933	0·14	0·13	0·12
BP935	0·14	0·13	0·12
BP936	0·14	0·13	0·12
BP944	0·14	0·13	0·12
BP945	0·28	0·27	0·24
BP946	0·13	0·12	0·11
BP948	0·28	0·27	0·24
BP951	0·72	0·66	0·61
BP962	0·13	0·12	0·11
BP9093	0·44	0·42	0·39
BP9094	0·44	0·42	0·39
BP9097	0·44	0·42	0·39
BP9099	0·44	0·42	0·39

NUMERICAL INDICATOR TUBES

MODEL	CD66	GR116	3015F Minitron
Anode Voltage (Vdc)	170min	175min	5
Cathode Current (mA)	2·3	14	8
Numerical Height (mm)	16	13	9
Tube Height (mm)	47	32	22
Tube Diameter (mm)	19	13	12 wide
I.C. Driver Rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	£1·87	£1·70	£1·50

All indicators 0·9 + Decimal point. All side viewing. Full data for all types available on request.

RTL MICROLOGIC CIRCUITS

	Price each 1–24	25–99	100 up
Epoxy TO-5 case			
μL900 Buffer	38p	36p	29p
μL914 Dual 2i/p gate	38p	36p	29p
μL923 J-K flip-flop	55p	51p	49p

Date and Circuits Booklet for IC's Price 8p.

DUAL IN LINE SOCKETS

(14 & 16 Lead)	1–24	25–99	100+
TSO14	0·33	0·30	0·28
TSO16 16 pin type	0·34	0·35	0·33
BPS14 14 pin type (low cost)	0·17	0·15	0·12
BPS16 16 pin type (low cost)	0·18½	0·16	0·13

BI-PAK DO IT AGAIN!

50W pk 25w (RMS)

0·1% DISTORTION!
HI-FI AUDIO AMPLIFIER

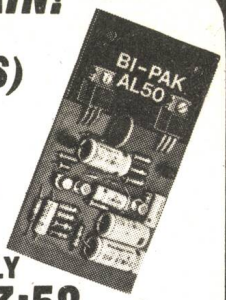

THE AL50

- ✱ Frequency Response 15Hz to 100,000—1dB.
- ✱ Load—3, 4, 8 or 16 ohms.
- ✱ Distortion—better than ·1% at 1KHz.
- ✱ Signal to noise ratio 80dB.
- ✱ Supply voltage 10–35 Volts.
- ✱ Overall size 63mm × 105mm × 13mm.

ONLY £3·58 each

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and ALSO was conceived to fill the need for all your A.F. amplification needs.
FULLY BUILT—TESTED—GUARANTEED.

STABILISED POWER MODULE SPM80

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1·5 amps at 35 volts. Size: 68mm × 105mm × 30mm.
These units enable you to build Audio Systems of the highest quality at a bitherto unobtainable price. Also ideal for many other applications including:—Disco Systems, Public Address, Intercom Units, etc. Handbook available, 10p **PRICE £3·25**

TRANSFORMER BMT80 £2·15 p. & p. 28p

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.
Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

SPECIFICATION

Frequency Response	20Hz — 20kHz ± 1dB
Harmonic Distortion	better than 0·1%
Inputs: 1. Tape Head	1·25mV into 50K Ω
2. Radio, Tuner	35mV into 50K Ω
3. Magnetic P.U.	1·5mV into 50K Ω
All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within	± 1dB from 20Hz to 20kHz.
Bass Control	± 15dB at 20Hz
Treble Control	± 15dB at 20kHz
Filters: Rumble (High Pass)	100Hz
Scratch (Low Pass)	8kHz
Signal/Noise Ratio	better than —65dB
Input overload	+26dB
Supply	+35 volts at 20mA
Dimensions	292mm × 82mm × 35m

ONLY £13·15

SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £25·30 FREE p.&p.

All prices quoted in new pence *Giro No. 388-7006*
Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 10p. Overseas add extra for airmail. Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER DEPT. No. 11 MAYES RD. LONDON N22 6TL

COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY (WE CLOSE ALL DAY THURSDAY)

13 SOUTH MALL, EDMONTON, N.9 803 1685

"CRESCENT" BUBBLE LIGHT SHOW

A new and exciting feature for the professional disc jockey or to give the private party an electric atmosphere, a projected kaleidoscope of colour makes the music you produce more interesting and will appeal to the visual as well as the audio senses.

This budget system compares very favourably with the more sophisticated and much higher priced models.

Specification—Projector: 150W, convection cooled, at 30ft the projected image = 16ft; Motor: 1 rev per 2 min. Liquid Wheel: 6in diameter multicolour.

The Motor is fitted to the Projector and can only be purchased as a single unit. The Liquid Wheel, however, is our very popular standard model & may be purchased separately. A bargain—Projector with Motor ready for instant use, **£15**; 6in Liquid Wheel, **£5**=**£20** + 75p carr.

TRI-VOLT BATTERY ELIMINATOR

Enables you to work your Transistor Radio, Amplifier or Cassette, etc., from the a.c. mains through this compact Eliminator. Just by moving a plug you can select the voltage you require, 6, 7½ or 9 volt. This means all your transistor power pack applications can be handled by this one unit. Approx. size 2¾in × 2¼in × 3¼in. Our Price **£2·75** plus 10p P. & P. Same model suitably wired for the Philips Cassette **£3** plus 10p P. & P.

DIGITAL CLOCK KIT

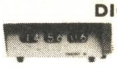

24-hr. Nixie dig. clock kit. We supply: a complete set of components; a complete set of easy to follow instructions; printed circuits made to make construction as simple as possible; a cabinet and front panel to give a professional finish. All for the price of the components. **£22·50** + 50p P. & P. Please send S.A.E. if you require more information.

AL20 5 WATT AUDIO AMPLIFIER

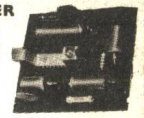

A low cost high quality 5 watt audio amplifier designed for use in stereo systems, record players and other audio equipment.

Supply Voltage = 9 to 30 volts.
Frequency = 50 to 25 kHz.
Overall Size = 3in × 2½in × 1in approx.

Full technical data and diagrams with each module.

All guaranteed and a bargain at **£2·63** plus 5p P. & P.

V.A.T.

From 1st April, 1973, will you please include on your Total (Goods plus Postage and Packing) Value Added Tax at the Standard Stated Rate.

200/250V MAINS RELAY

Heavy duty contacts. 2,500Ω coil. All new and unused D.P.D.T. mains relays **50p** + V.A.T. Carr. Free. Special quantity price: **£40** per 100 relays.

MAINS TRANSFORMER

Fused Primary 240V. Secondary 220V @ 50mA. 6·3V @ 1A. This transformer is made to a very high standard and is a small size: 2in × 2¼in × 2¼in. **63p** plus 15p P. & P.

TRI-VOLT CAR SUPPLY

Enables you to work your Transistor Radio, Amplifier or Cassette, etc. from the 12 volt car supply. Positive or negative earth. Approx. size = 2in. × 3¼in. × 1¼in. This converter supplies 6, 7½ or 9 volts and is transistor regulated. A real money saving device for **£2·50** plus 10p P. & P.

MINI LOUDSPEAKERS

2¼in 80 ohm, **50p**; 2¼in 40 ohm, **50p**. Please include 5p P. & P. on each L.S.

ADD LUXURY TO YOUR CAR

WITH A MOTOR DRIVEN CAR AERIAL

Spec.: 5 Section
Extended Length 100cm.
Length under Fender 40cm
Cable Length 120cm

Supplied complete with Fixing Bracket and Control Switch. **£6·75** plus 25p P. & P.

EMI LOUDSPEAKER 450

10W 13in × 8in ± two 2·2½in tweeters and cross-over. All wired and ready for use. This ever-popular 450 in 3–8–15 ohm imp.

£3·75 plus 38p P. & P. each.

CRESCENT CASSETTES

Top quality cassettes at unbeatable prices (complete with standard storage case): C60 **28p**, C90 **38p**, C120 **48p** plus 5p P. & P.

"CRESCENT BEAT BRITE"

SINGLE CHANNEL SOUND TO LIGHT UNIT This fantastic little box approx. 4" × 3" × 2½" when connected to the output of a sound source from 1 to 100 watts produces a psychedelic light display of up to 1000 watts. Complete with a sensitive level control the unit is fused and cannot harm your amplifier. A Bargain at **£7·50** plus 10p.

LOW VOLTAGE AMPLIFIER

5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output.

With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier.

£1·75 plus 13p P. & P.

7in × 4in LOUDSPEAKER

A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well-known hi-fi set maker. Size: 7in × 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12kHz. Power handling: 5W. Unbeatable. Price: **£1·60**. Free postage on this item.

PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel: Bass—Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 500W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) **£18·50** plus 38p P. & P.

If you require more information please send S.A.E.

Lasky's Audio-Tronics Catalogue 1973

The new 1973 VAT edition of Lasky's famous Audio-Tronics Catalogue will be available in early April—FREE on request. The 48 tabloid size pages—many in full colour—have been reprinted with VAT price changes for your convenience, together with many new items. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals), Tape Recording and Audio Accessories. Send for your copy now and see for yourself that VAT can mean a saving on many of the 1000's of items we offer.

FREE Send this coupon with 15p for post and inclusion on our regular mailing list.

NAME .....

ADDRESS .....

.....

PE14

.....

LASKY'S RADIO LIMITED, 3-15 CAVELL STREET, LONDON E.1.

D.I.Y. TECHNICAL BOOKS

PAL RECEIVER SERVICING (280pp)	£3·50
MAKING AND REPAIRING TRANSISTOR RADIOS ...	£1·00
HOW TO REPAIR SMALL APPLIANCES	£1·20
TRANSISTOR RADIO SERVICING MADE EASY... ...	£1·70
CAR RADIO SERVICING MADE EASY	£1·30
HI-FI PROJECTS FOR THE HOBBYIST	£1·00
TAPE RECORDING FOR THE HOBBYIST	£1·30
RADIO HANDBOOK (896 pp)	£6·00
ELECTRONIC EXPERIMENTS AND PROJECTS ...	£1·25
TRANSISTOR-TV SERVICING GUIDE	£2·25
99 WAYS TO IMPROVE YOUR HI-FI	£1·50
99 WAYS TO IMPROVE YOUR ELECT-PROJ.	£1·50
101 EASY HAM RADIO PROJECTS	£1·50
ELECTRONIC GAMES, TOYS YOU CAN BUILD ...	£1·40
HOW TO BUILD SPEAKER ENCLOSURES	£1·50
1-2-3-4 SERVICING STEREO AMPS.	£2·50
99 ELECTRONIC PROJECTS	£1·50
HANDBOOK OF BASIC ELECTRONIC EQUIPMENT ...	£1·75

Add 10% **FOR POSTAGE AND PACKING**

WHEEL (PE), **41A ADELAIDE GROVE, LONDON W12**

GET BETTER ALL-ROUND PERFORMANCE WITH DEXTER CAPACITOR DISCHARGE IGNITION

The Dexter Capacitor Discharge Ignition Unit can improve performance in many ways:—

★ EASIER STARTING ★ REDUCED FUEL CONSUMPTION ★ BETTER ACCELERATION ★ HIGHER TOP SPEED ★ EXTENDED LIFE FOR BATTERY AND SPARK PLUGS ★ NO MORE CONTACT-BREAKER POINT BURN ★ IMPROVED COMBUSTION ★

The Dexter Capacitor Discharge Ignition Unit is fully suppressed to prevent radio interference. It can be fitted easily and simply to your car, and costs only £9.80 plus 25p post and packing.

12 Volt neg. earth only. Fully guaranteed for 12 months

DEXTER & CO. 1 Ulver House, 19 King Street, Chester CH1 2AH. Tel: 0244-25883

I.L.P. (Electronics) Ltd

100 WATTS!

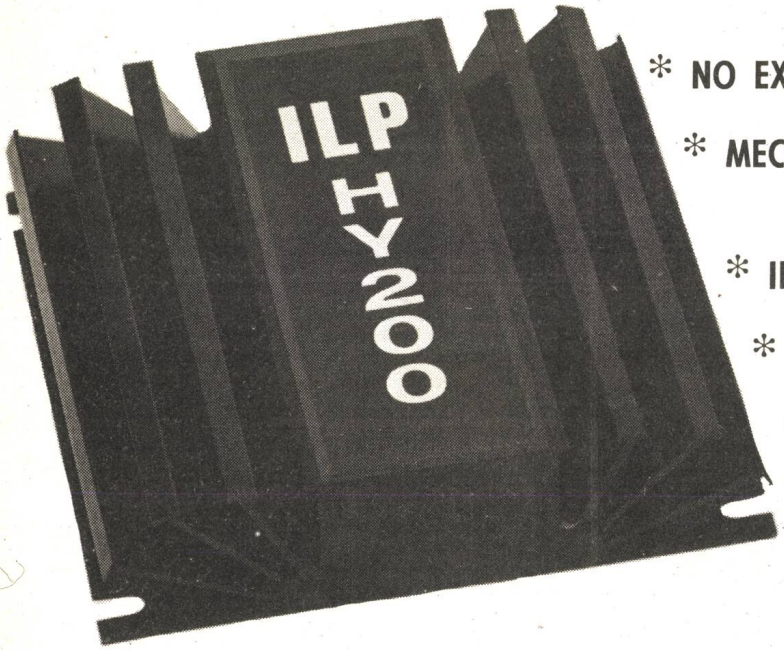

* NO EXTERNAL COMPONENTS
* MECHANICALLY & ELECTRICALLY ROBUST
* INTEGRAL HEATSINK
* HERMETICALLY SEALED UNIT
* ATTRACTIVE APPEARANCE
* LOW COST
* BRITISH BUILT

With the development of the HY200, ILP bring you the first **COMPLETE** Hybrid Power Amplifier.

COMPLETE: because the HY200 uses no external components!

COMPLETE: because the HY200 is its own heatsink!

By the use of integrated circuit technique, using 27 transistors, the HY200 achieves total component integration. The use of specially developed high thermally conductive alloy and encapsulant is responsible for its compact size and robust nature.

The module is protected by the generous design of the output circuit, incorporating 25amp transistors. A fuse in the speaker line completes protection.

Only 5 connections are provided, input, output, power lines and earth.

OUTPUT POWER: 100 watts RMS; 200 watts peak music power. **INPUT IMPEDANCE:** 10kΩ. **INPUT SENSITIVITY:** 0Dbm (0·775volt RMS). **LOAD IMPEDANCE:** 4–16Ω. **TOTAL HARMONIC DISTORTION:** less than 0·1% at 100 watts, typically 0·05%. **SIGNAL : NOISE:** better than 75Db relative to 100 watts. **FREQUENCY RESPONSE:** 10Hz–50KHz ±1Db. **SUPPLY VOLTAGE:** ±45volts. **APPLICATIONS:** P.A., Disco, Groups, Hi-Fi, Industrial. **PRICE: £14·90** inc. VAT & P&P. Trade applications welcomed.

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.

G. F. MILWARD 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

TRANSISTORS

Output Transistors
BD 112 ... 25p
OC 36 ... 50p
BD 145 ... 25p

Small Signal N.P.N.
BC 108 ... 10p
BC 109 ... 10p
BF 194 ... 10p

Transmitting Types
BFR 64 ... £1
BKY 89A ... £5
BLY 93A ... £9

Microwave Varactor Diodes
BXY 27/28/32/35/36/37/38/39/40/41 ... £1

Microwave Detector
CAY 10 ... £5

Microwave Mixer
CL 7331 ... £20

Microwave Gunn Effect Oscillator
CL 8370 ... £10
CL 8380 ... £10
CL 8390 ... £10
CL 8470 ... £40

Microwave Tunnel Diodes
AEY 13 ... £5
AEY 16 ... £10

R.F. Transistors
BF 180 ... 20p
BF 194 ... 10p
AF 124 ... 20p

Field Effect Transistors
BFW 12/13/14 ... 25p

Micro-miniature N.P.N.
BFS 18R ... 10p
LDA 400/403/450/452 ... 10p

Infra-red Transmitters
CQY 11A ... £4
CQY 12A ... £10

Light-sensitive Trans
OCP 70 ... 20p

Complementary Drivers, 2 watts (per matched pair)

INTEGRATED CIRCUITS
TBA 500 Luminance I.C. ... £1
TBA 510 Chrominance I.C. ... £1
FEQ 101 64bit Memory ... £1
7400 ... 12p
7401 ... 12p
7410 ... 12p
7420 ... 12p
7440 ... 12p
7453 ... 12p
7470 ... 24p
7472 ... 24p
7473 ... 32p
7474 ... 32p
7482 ... 88p
7483 ... 95p
7490 ... 58p
7491 ... 78p
7492 ... 58p
7493 ... 58p
7495 ... 68p
5400 ... 10p
6404 ... 10p

NEW! NEW! NEW! NEW!
An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.
Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner.
Light sensitive aerosol spray ... £1·00 plus
Developer and Etchant ... 50p postage

NEWER THAN NEW! !

Fibre Glass Board pre-treated with light-sensitive lacquer enabling you to produce prototype printed circuits within five minutes.
75mm × 100mm ... 33p
150mm × 100mm ... 66p
150mm × 200mm ... £1·32

Epoxy-Resin
75mm × 100mm ... 22p
100mm × 150mm ... 44p
150mm × 200mm ... 88p

Copper-clad Fibre Board
12in × 6in ... 45p

Copper-clad Epoxy Resin Board
12in × 6in ... 25p

MULLARD POLYESTER CAPACITORS
500,000 in STOCK!!!
0·001µF 0·0018µF 0·0056µF 0·015µF
0·0012µF 0·0022µF 0·01µF 0·033µF
0·0015µF 0·0027µF 0·012µF 0·082µF
20p dozen; **75p**—100; **£5**–1,000; **£40**–10,000
0·15µF 0·18µF 0·22µF 0·39µF 0·68µF
20p dozen; **£1**–100; **£6·50**–1,000; **£50**–10,000

VEROBOARD
2½in × 1in × 0·15in ... 6p
3¾in × 2½in × 0·15in ... 16p
3¾in × 3¾in × 0·15in ... 20p
5in × 2½in × 0·15in ... 20p
5in × 3¾in × 0·15in ... 28p
17in × 2½in × 0·15in ... 55p
17in × 3¾in × 0·15in ... 74p
3¾in × 2½in × 0·1in ... 21p
3¾in × 3¾in × 0·1in ... 24p
5in × 2½in × 0·1in ... 23p
5in × 3¾in × 0·1in ... 28p
Spot Face Cutter **38p.** Pin Insert Tool **48p.** Terminal Pins (0·1 or 0·15) 36 for **18p.**
Special Offer Pack consisting of 5 2½in × 1in boards and a Spot Face Cutter—**50p.**
"ODDS & ENDS"—**1p** sq in.

ERIE MONOLITHIC CERAMIC CAPACITORS
3p each; **20p** dozen; **£1·75** per 100
10pF 68pF 560pF
15pF 100pF 620pF
22pF 150pF 680pF
33pF 220pF 1,000pF
39pF 330pF
47pF 470pF

£1 100 ¼ WATT RESISTORS, 100 CERAMIC CAPACITORS, 100 DIODES
POSTAGE 15p — PACK No. 1

£1 1 VEROBOARD CUTTER, 5 2½in x 0·15 BOARDS, 50 SQ.IN "ODD PIECES" VERO
POSTAGE 15p — PACK No. 3

£1 20 ASSORTED UNUSED MARKED, TESTED TRANSISTORS BC108, ETC.
POSTAGE 15p — PACK No. 5

£1 6 COMPUTER PANELS CONTAINING MASSES OF DIODES, TRANSISTORS, INDUCTORS, RESISTORS AND CAPACITORS
POSTAGE 25P — PACK No. 7

£1 100 RESISTORS, 100 CERAMIC CAPACITORS, 100 POLYSTYRENE CAPACITORS
POSTAGE 15p — PACK No. 2

£1 100 RESISTORS, 100 CERAMIC CAPACITORS, 50 MULLARD POLYESTER CAPACITORS
POSTAGE 15p — PACK No. 4

£1 1 TRANSISTORISED SIGNAL TRACER KIT, 1 TRANSISTORISED SIGNAL INJECTOR KIT
POSTAGE 15p — PACK No. 6

£1 100 RESISTORS, 100 CAPACITORS (ASSORTED TYPES)
POSTAGE 15P — PACK No. 8

POSTAGE (MINIMUM) 15P PER ORDER — **ALL GOODS PLUS 10% V.A.T.**

BI-PRE-PAK

5W AMP for only £1.98
(inclusive of P.& P. and VAT)

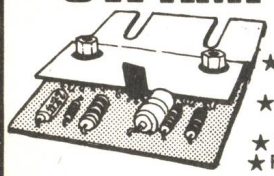

★ Nominal 12-14V (650mA into 3 ohms)
★ Power output into 3 ohms = 5W 8 ohms = 2W 15 ohms = 1W
★ Distortion typically 0·5%
★ Frequency response at 3dB points 10Hz to 30kHz
★ Sensitivity (with/without tone control) 130mV
★ Size only 2¼" × 1¾"

This matchbox sized amplifier will run satisfactorily from a 12V car battery. Can also be used for portable voice reinforcement such as public functions where mains supply is not accessible. A small mains unit is available. Two amplifiers are ideal for Stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit..
Discounts are available for quantity orders.

Cheapest in the U.K. Built and tested.

I enclose £ ..... for ..... amplifiers
Name .....
Address .....

BI-PRE-PAK LTD Co. Reg. No. 820919
Dept. A, 222/224 West Road Westcliff-on-Sea, Essex SS8 9DF
Tel.: Southend (0702) 46344

Multicore Solder Cream for high quality joints in the Electronics Industry

New Multicore Solder Cream was designed for jobs where second best will just not do. Like manufacturing diodes for instance. Or making a tuner chassis, or soldering thick-film circuits. Multicore Solder Cream, a finely graded solder alloy powder in a thixotropic organic vehicle, is easier, quicker, more economic and more reliable than conventional techniques.

Multicore Solder Cream is different. It doesn't spit or need stirring. It can be applied by syringe, automatic dispensers or screen printing—giving instant soldering with good spread, strong joints with low contact angles. Suitable as a temporary adhesive during assembly, the clear colour flux residue—without solder globules—makes inspection easier. There are three types of Multicore Solder Cream—one of them may be just what you're looking for.

For full information on this or any other Multicore products, please write on your company's letterhead direct to:

Multicore Solders Ltd., Maylands Avenue, Hemel Hempstead, Herts. HP2 7EP. Tel: Hemel Hempstead 3636. Telex: 82363.

Build yourself a TRANSISTOR RADIO

WITH AFTER SALES SERVICE

ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS ALSO AIRCRAFT BAND.

Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Fine tone moving coil speaker. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in × 7in × 4in.

Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

TOTAL BUILDING COSTS **£9·35** P.P. & INS. 52p (OVERSEAS P. & P. £1·05)

ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in × 7in × 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£7·68** P. P. & INS. 47p (OVERSEAS P. & P. £1·05)

ROAMER SEVEN Mk. IV

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Extra medium waveband provides easier tuning of Radio Luxembourg, etc. Built-in ferrite rod aerial for MW and LW. Retractable 4 section 24in chrome plated telescopic aerial for SW. Socket for car aerial. Powerful push-pull output. 7 transistors and 2 diodes, including micro-alloy R.F. transistors. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9in × 7in × 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£6·58** P. P. & INS. 47p (OVERSEAS P. & P. £1·05)

ROAMER SIX

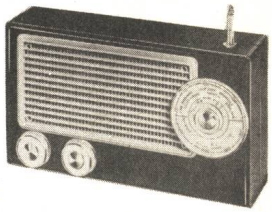

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages—6 transistors and 2 diodes including micro-alloy R.F. transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in × 5¼in × 2¾in approx. Easy build plans and parts price list 25p (FREE with parts).

TOTAL BUILDING COSTS **£4·38** P. P. & INS. 31p (OVERSEAS P. & P. £1·05)

POCKET FIVE

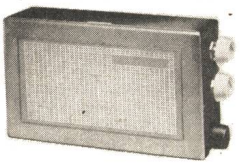

3 TUNABLE WAVEBANDS: MW, LW, TRAWLER BAND WITH EXTENDED MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5¼in × 1¾in × 3¾in. Easy build plans and parts price list 10p (FREE with parts).

TOTAL BUILDING COSTS **£2·50** P. P. & INS. 24p (OVERSEAS P. & P. 65p)

TRANSONA FIVE

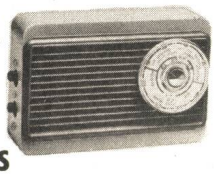

5 TRANSISTORS AND 2 DIODES

3 TUNABLE WAVE BANDS: MW, LW AND TRAWLER BAND. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6¼in × 4¼in × 1¼in. Easy build plans and parts price list 10p (FREE with parts).

TOTAL BUILDING COSTS **£2·75** P. P. & INS. 25p (OVERSEAS P. & P. 65p)

TRANS EIGHT

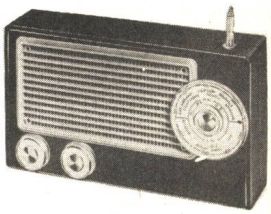

8 TRANSISTORS AND 3 DIODES

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in × 5¼in × 2¾in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£4·95** P. P. & INS. 33p (OVERSEAS P. & P. £1·05)

"EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT. Components include: Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine tone moving coil Speaker: Terminal Strip: Ferrite Rod Aerial: 2 Plugs and Sockets: Battery Clips: 4 Tag Boards Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three ¼in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and easy build plans 25p (FREE with parts).

ALL PARTS INCLUDING CASE AND PLANS **£6·05** P. P. & INS. 33p (OVERSEAS P.&P. £1·05)

FULL AFTER SALES SERVICE

★ Callers side entrance "Lavell" Shop
★ Open 10-1, 2.30-4.30 Monday-Friday, 9-12 Saturday
★ PLEASE NOTE: ALL PRICES INCLUDE V.A.T.

RADIO EXCHANGE LTD

61a HIGH ST., BEDFORD MK40 1SA. Tel. 0234 52367

Reg. no. 788372

I enclose £..... please send items marked

ROAMER TEN	☐	ROAMER SEVEN	☐
ROAMER EIGHT	☐	TRANS EIGHT	☐
TRANSONA FIVE	☐	ROAMER SIX	☐
POCKET FIVE	☐	EDU-KIT	☐

Parts price list and plans for.....

Name .....

Address .....

.....

P.E. 55

Sinclair Project 60

Now—the Z.50 Mk.2

with built-in automatic transient overload protection

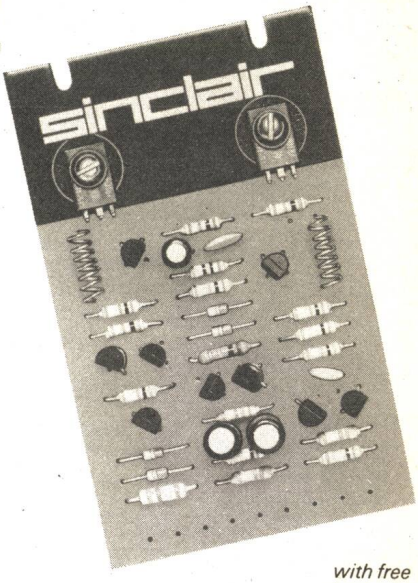

When originally introduced, the Sinclair Z.50 proved how it was possible to design and produce a popularly priced modular power amplifier having characteristics to challenge the world's costliest amplifiers. Many thousands of Z.50's are now giving excellent service day in, day out. But we have also learned that constructors do not always use their Z.50's ideally. That is why we have introduced modifications whereby risk of damage through mis-use is greatly reduced and performance further enhanced. The Z.50 Mk.2 has improved thermal stability, more accurately regulated D.C. limiting to ensure more symetrical output voltage swing and clipping and still less distortion at lower power. Z.50 Mk.2 is compatible with all other Project 60 modules, and may be incorporated to advantage in existing systems. Eleven silicon epitaxial planar transistors are now used, two more than in the original Z.50; circuitry has been re-designed, making this versatile high performance amplifier better than ever.

with free manual
£5.48

Z.30 the power amplifier for quality and economy

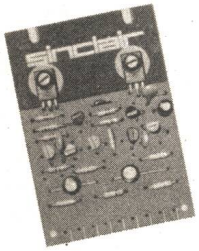

with free manual
£4.48

The Z.30 provides excellent facilities for the constructor requiring a high fidelity audio system of less power than that available from Z.50's. Using a power supply of 35 volts, Z.30 will deliver 15 watts RMS into 8 ohms, or 20 watts RMS into 3 ohms using 30 volts. Total harmonic distortion is a fantastically low 0.02% at 15 watts into 8 ohms with signal to noise ratio better than 70 dB unweighted. Input sensitivity 250mV into 100K ohms. Size 80 x 57 x 13 mm ($3\frac{1}{8}$ x $2\frac{1}{4}$ x $\frac{1}{2}$) Z.30, Z.50 and Z.50 MK.2 modules are compatible and interchangeable.

Brilliant new technical specifications

Input impedance 100 KΩ
Input (for 30w into 8Ω) 400mV
Signal to noise ratio, referred to full o/p at 30v HT 80dB or better
Distortion 0.02% up to 20W at 8Ω. See curve
Frequency response 10Hz to more than 200 KHz ±1dB
Max. supply voltage 45v (4Ω to 8Ω speakers) (50v 15Ω speakers only)
Min. supply voltage 9v
Load impedance – minimum : 4Ω at 45v HT
Load impedance – maximum : safe on open circuit

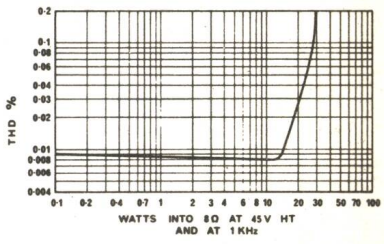

Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	**Z.30**	Crystal P.U., 12V battery volume control, etc.	**£4.48**
Mains powered record player	**Z.30, PZ.5**	Crystal or ceramic P.U. volume control, etc.	**£9.45**
12W. RMS continuous sine wave stereo amp. for average needs	**2 x Z.30s, Stereo 60; PZ.5**	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	**£23.90**
25W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	**2 x Z.30s, Stereo 60; PZ.6**	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	**£26.90**
80W. (3 ohms) RMS continuous sine wave de luxe stereo amplifier. (60W. RMS into 8 ohms)	**2 x Z.50s, Stereo 60; PZ.8, mains transformer**	As above	**£34.88**
Indoor P.A.	**Z.50, PZ.8, mains transformer**	Mic., guitar, speakers, etc., controls	**£19.43**

F.M. Stereo Tuner **(£25)** & A.F.U. **(£5.98)** may be added as required.

Guarantee

If, within 3 months of purchasing any product direct from Sinclair Radionics Ltd., you are dissatisfied with it, your money will be refunded at once. Many Sinclair appointed Stockists also offer this same guarantee in co-operation with Sinclair Radionics Ltd.

Each Project 60 module is tested before leaving our factory and is guaranteed to work perfectly. Should any defect arise in normal use, we will service it at once and without any charge to you, if it is returned within two years from the date of purchase. Outside this period of guarantee a small charge (typically £1.00) will be made. No charge is made for postage by surface mail. Air Mail is charged at cost.

sinclair

Sinclair Radionics Ltd., R.O. London Rd., St. Ives, Huntingdonshire PE17 4HJ (Phone: St. Ives 64311). Regd. Bus. No. England 699483.

the world's most advanced high fidelity modules

Stereo 60 Pre-amp/control unit

Designed specifically for use on Project 60 systems, the Stereo 60 is equally suitable for use with any high quality power amplifier. Since silicon epitaxial planar transistors are used throughout, a really high signal-to-noise ratio and excellent tracking between channels is achieved. Input selection is by means of press buttons, with accurate equalisation on all input channels. The Stereo 60 is particularly easy to mount.

SPECIFICATIONS—Input sensitivities: Radio – up to 3mV. Mag. p.u. 3mV: correct to R.I.A.A. curve ±1dB :20 to 25,000 Hz. Ceramic p.u. – up to 3mV : Aux – up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE +12 to —12dB at 10KHz: BASS +12 to —12dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

Built, tested and guaranteed. **£9.98**

Project 60 Stereo F.M. Tuner

The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other advanced features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stero decoder and switchable squelch circuit for silent tuning between stations. In terms of high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with most other high fidelity systems.

SPECIFICATIONS—Number of transistors: 16 plus 20 in I.C. **Tuning range:** 87.5 to 108MHz. **Sensitivity:** 7μV for lock-in over full deviation. **Squelch level:** Typically 20μV. **Signal to noise ratio:** >65dB. **Audio frequency response:** 10Hz – 15KHz (±1dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2μV. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. maximum **Operating voltage:** 25–30VDC. **Indicators:** Stereo on ; tuning. **Size:** 93 x 40 x 207mm.

Built and tested. Post free. **£25**

Super IC.12 Integrated circuit high fidelity amplifier

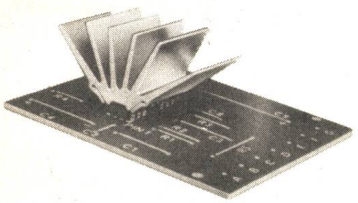

Having introduced Integrated Circuits to hi-fi constructors with the IC.10, the first time an IC had ever been made available for such purposes, we have followed it with an even more efficient version, the Super IC.12, a most exciting advance over our original unit. This needs very few external resistors and capacitors to make an astonishingly good high fidelity amplifier for use with pick-up, F.M. radio or small P.A. set up, etc. The free 40 page manual supplied, details many other applications which this remarkable IC. make possible. It is the equivalent of a 22 transistor circuit contained within a 16 lead DIL package, and the finned heat sink is sufficient for all requirements. The Super IC.12 is compatible with Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board.

SPECIFICATIONS

Output power: 6 watts RMS continuous (12 watts peak). 6–8Ω. **Frequency Response:** 5Hz to 100KHz ±1dB. **Total Harmonic Distortion:** Less than 1%. (Typical 0·1%) at all output powers and frequencies in the audio band (28V). **Load Impedance:** 3 to 15 ohms. **Input Impedance:** 250 Kohms nominal. **Power Gain:** 90dB (1,000,000,000 times) after feedback. **Supply Voltage:** 6 to 28V. **Quiescent current:** 8mA at 28V. **Size:** 22×45×28mm including pins and heat sink..

Manual available separately 15p post free,

With FREE printed circuit board and 40 page manual.
£2.98 Post free

Power Supply Units
The new PZ.8 Mk.3

The most reliable power supply unit ever made available to constructors. Brilliant circuitry makes failure from over load and even direct shorting of the output impossible. This is due to an ingenious re-entrant current limiting principle which, as far as we know has never before been available in any comparable unit outside the most expensive laboratory equipment. Ripple and residual noise have been reduced to the point of almost total elimination. This is, of course, the perfect unit for Project 60 assemblies, particularly where the new Z.50 MK.2 amplifiers are used. Nominal working voltage – 45.

PZ.8 Mk.3—£7.98
(Mains transformer, if required) £5.98
PZ.5 30v. unstabilised
(not suitable for Project 60 tuner) **£4.98**
PZ.6 35v. stabilised
(not suitable for IC. 12) **£7.98**

Project 605

the easy way to buy and build Project 60 without soldering

Project 605 in one pack contains : one PZ.5, two Z.30's, one Stereo 60 and one Masterlink, which has input sockets and output components grouped on a single module and all necessary leads cut to length and fitted with clips to plug straight on to the modules thus eliminating all soldering.

Complete with comprehensive manual, post free **£29.95**
All you need for a superb 30 watt high fidelity stereo amplifier

Order form

Please send
I enclose cash/cheque/money order.

Name

Address

PE/7/73

SINCLAIR RADIONICS LTD., LONDON ROAD
ST. IVES, HUNTINGDONSHIRE PE17 4HJ

sinclair

Add 10% V.A.T. to all prices quoted on page opposite and above

parts for PRACTICAL ELECTRONICS projects

After many requests, Electro Spares are now supplying lists of components for **all** the projects featured in "Practical Electronics", commencing with May 1973 issue. Just forward an S.A.E. (preferably 9" × 4" minimum), and state which project is of interest to you—we will forward an individually priced list of the components required.

No need to buy a full kit—you need only purchase the parts you require at any one time.

All Electro Spares supplied components are new, branded products of reputable manufacturers, and carry full makers' guarantee.

We regret we cannot supply lists for projects published **before** May 1973 issue.

"ONE SOURCE" BUYING MAKES SENSE—
IT CAN SAVE YOU TIME, MONEY AND POSTAGE

"p.e." f.m. varicap stereo tuner

Electro Spares offer a kit of high quality parts to the published specification for this remarkable tuner, featured in "Practical Electronics", May 1973.

Features include pushbutton "Spot On" tuning, with up to 5 pre-set stations (no difficult tuning dial and drive cord). Easy, "no problem" construction, requiring only a few simple setting up adjustments with a D.C. Voltmeter. Uses **NEW** pre-set modules for R.F. and I.F. circuits—no circuit alignment. High efficiency integrated circuit Phase Lock Loop Decoder for perfect stereo reception, with stereo lamp indicator.

Fibre Glass P.C. Board, neat slim line cabinet, with brushed aluminium front panel, push buttons, etc., etc.

IDEAL FOR USE WITH THE "TEXAN", "P.E. GEMINI" AND ANY GOOD QUALITY STEREO AMPLIFIER.

Please send S.A.E. for full details.

"p.e. gemini" stereo amplifier

QUALITY HI-FI FOR THE HOME CONSTRUCTOR

30 Watts (R.M.S.) per Channel into 8 ohms!

Total Harmonic Distortion 0.02%!

Frequency Response (—3 dB) 20Hz — 100kHz!

We are still continuing to supply components for this fabulous amplifier, which is now recognised as practically the ultimate in High Fidelity. We know of no better unit for the home constructor, and can supply a booklet, containing full specification, complete constructional information, wiring diagrams, fault finding guide, etc., etc., price 55p plus 4p postage.

Our **new, low** comprehensive price list is supplied with each booklet, or supplied separately on receipt of large S.A.E.

FOR PEOPLE WHO REQUIRE THE **BEST**—
IT HAS TO BE THE **"p.e. gemini"**

NOTE OUR NEW ADDRESS—WITH NEW MAIL ORDER DEPARTMENT FOR QUICK EFFICIENT SERVICE.

PLEASE PAY US A CALL—VISITORS WELCOME—EASY PARKING.

Electro-Spares

288 Ecclesall Road
Sheffield S11 8PE
Tel.: Sheffield 668888

"THE COMPONENT CENTRE OF THE NORTH"

COMPARE OUR PRICES

Speaker Bargains	£p
E.M.I. 13in × 8in 3, 8 & 15 ohms plain	2·00
with tweeter	2·25
twin tweeter	3·50
Type 350 -20 watt with tweeter 8 ohms. P.P. 37p.	7·25
8in × 5in 3, 8 & 15 ohms	1·10
6½" (93850) 8 ohm	2·20
8" (14A/1000) 8 ohm 10 watt	4·00
EMI 3½" Tweeter C/Magnet 8 ohm	1·00
FANE 7in × 4in 3 & 8 ohms	90
8in 8 ohm, dual cone	2·10
CELESTION 8in 15 ohm	1·40
BAKER GROUP 25 12in 25W 8 or 15 ohm	6·00
Postage 25p per speaker	
5" 8 ohm c/magnet P.P. 10p	80
2½in 8 or 64 ohm P.P. 10p	45

Kit-torm cabinets, teak	
(17in × 10in × 6in)	2·95
with a 13in × 8in or 8in cut out 18in × 11in × 9in with 13in × 8in cut out for EMI 350	£3·95
(12in × 12in × 6in) with a 8in × 5in or 8in cut out. (please specify cut out)	2·25
Add 35p per Cabinet for post & packing	

Microphone Bargains	£p
CM 20 Crystal Hand	45
DX143 Dynamic, cassette-type stick	1·00
CM70 PLANET stick metal, switch crystal	1·45
DM160 Dynamic uni-dir, ball metal	3·75
UD130 50K/600 ohm uni-dir, ball metal	4·50
TW209 Lesson dual imp ball metal uni-dir	5·75
Condenser Mike uni-dir 600 ohm	7·95
Guitar mike	45
Lapel type, crystal	40
Postage 17p each	

Cartridges—with standard fittings & stylii	£p
ACOS GP91/2SC or GP91/3SC stereo compatible	90
ACOS GP94 stereo ceramic	1·50
ACOS GP95 stereo crystal	1·15
ACOS GP96 stereo ceramic	1·50
9THAC Sonotone stereo ceramic (diamond)	1·70
9THAC/G Sonotone stereo ceramic (diamond) slimline	1·70
ACOS GP67/2C mono crystal	65
ACOS GP101 compatible crystal	65
19-TI Sonotone stereo crystal	80
Postage 5p per cartridge	

Battery Eliminators	
240v input 6 or 9v d.c. output at 150 mA	1·99
12v d.c. input (for cars, fits in lighter socket) 6, 7½ or 9v d.c. output at 300 mA	2·50
P. & P. 10p	

Tapes—"MYLAR" base finest quality British made.

5in	600ft	36p	5½in	1800ft	85p
5in	900ft	45p	7in	1200ft	55p
5in	1200ft	60p	7in	1800ft	80p
5½in	900ft	49p	7in	2400ft	95p
5½in	1200ft	55p			

Postage 9p each

Plastic Library Cases for
5in Reels **16p** 7in Reels **21p**
5½in Reels **19p** P. & P. 5p each

THIS MONTH'S SPECIAL OFFER

EMI Loudspeaker Enclosure Kit (LEK 450/8). Comprising 2 EMI 450 Speakers (8 ohm 10 watt, T/Tweeter plus cross-over) and 2 EMI Cabinet Kits 18"×10"×11", Plus acoustic wadding, glue, screws, instructions, etc. Recom. Retail price £29·20, Bargain at **£18·00** inc. VAT, plus 50p P. & P.

Add 10% V.A.T. on prices incl. P. & P.

RIVERSDALE ELECTRONICS

Mail Order Dept. E8/73, P.O. Box 470, Manchester M60 4BU
SEND 25p FOR COMPLETE CATALOGUE

ALL OUR MERCHANDISE IS FULLY GUARANTEED

A.M.C. ELECTRONICS LTD.

SCORPIO ELECTRONIC IGNITION UNIT

COMPLETE KIT WITH ALL PARTS AND COMPREHENSIVE CONSTRUCTION AND FAULT FINDING DATA

COMPLETE KIT	£10·95 including V.A.T. and postage.
DATA	10p including V.A.T. and postage.
TRANSFORMER	£2·53 including V.A.T. and postage.
P.C.B. GLASS FIBRE	70p including V.A.T. and postage.

LATEST NEWS — P.E. TRIFFID. **P.C.B. 70p including post and V.A.T**
Please add 15p to orders under £1·50. Send S.A.E. for other itemised prices.

AMCEL, MAIL ORDER 160 DRAKE STREET, ROCHDALE LANCASHIRE OL16 1PY

PARKERS SHEET METAL FOLDING MACHINES HEAVY VICE MODELS

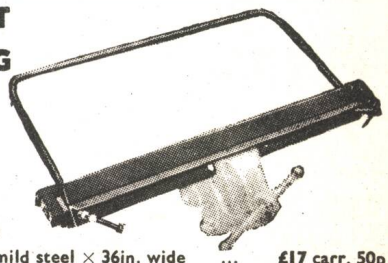

With Bevelled Former Bars

No. 1. Capacity 18 gauge mild steel × 36in. wide ... **£17** carr. 50p
No. 2. Capacity 18 gauge mild steel × 24in. wide ... **£12** carr. 38p
No. 3. Capacity 16 gauge mild steel × 18in. wide ... **£12** carr. 38p

Also new bench models. Capacities 36in. x 18 gauge **£35.** 24in. x 16 gauge **£32.** Carriage 75p. Add 10% VAT to total price of machine and carriage.

End folding attachments for radio chassis. Tray and Box making for 36in. model, 27½p per ft. Other models 17½p. The two smaller models will form flanges. As supplied to Government Departments, Universities, Hospitals.

One year's guarantee. Money refunded if not satisfied. Send for details.

A. B. PARKER, Folding Machine Works, Upper George St., Heckmondwike, Yorks. Heckmondwike 3997

Henry's

YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards – call and see for yourself.

INTEGRATED CIRCUITS

Why buy alternatives when you can buy the genuine article from us at competitive prices from stock. BRANDED FROM TEXAS I.T.T FAIRCHILD

Type	1/11 p	12/24 p	25/99 p
SN7400	0·20	0·18	0·16
SN7401	0·20	0·18	0·16
SN7402	0·20	0·18	0·16
SN7403	0·20	0·18	0·16
SN7404	0·20	0·18	0·16
SN7405	0·20	0·18	0·16
SN7406	0·30	0·27	0·25
SN7407	0·30	0·27	0·25
SN7408	0·20	0·19	0·18
SN7409	0·45	0·42	0·35
SN7410	0·20	0·18	0·16
SN7411	0·23	0·22	0·20
SN7412	0·42	0·40	0·35
SN7413	0·30	0·27	0·25
SN7416	0·30	0·27	0·25
SN7417	0·30	0·27	0·25
SN7420	0·20	0·18	0·16
SN7422	0·48	0·44	0·40
SN7423	0·48	0·44	0·40
SN7425	0·48	0·40	0·35
SN7427	0·42	0·39	0·35
SN7428	0·50	0·45	0·42
SN7430	0·20	0·18	0·16
SN7432	0·42	0·39	0·35
SN7433	0·70	0·61	0·44
SN7437	0·65	0·60	0·50
SN7438	0·65	0·60	0·50
SN7440	0·20	0·18	0·16
SN7441AN	0·75	0·72	0·70
SN7442	0·75	0·72	0·70
SN7443	1·00	0·95	0·90
SN7445	2·00	1·75	1·60
SN7446	2·00	1·75	1·60
SN7447	1·75	1·60	1·45
SN7448	1·75	1·60	1·45
SN7450	0·20	0·18	0·16
SN7451	0·20	0·18	0·16
SN7453	0·20	0·18	0·16
SN7454	0·20	0·18	0·16
SN7460	0·20	0·18	0·16
SN7470	0·30	0·27	0·25
SN7472	0·30	0·27	0·25
SN7473	0·40	0·37	0·35
SN7474	0·40	0·37	0·35
SN7475	0·55	0·52	0·50
SN7476	0·45	0·42	0·39
SN7480	0·80	0·75	0·67
SN7481	1·25	1·15	1·10
SN7482	0·87	0·80	0·70
SN7483	1·00	0·90	0·85
SN7484	0·90	0·85	0·80
SN7486	0·45	0·41	0·38
SN7490	0·75	0·70	0·65
SN7491AN	1·00	0·95	0·90
SN7492	0·75	0·70	0·65
SN7493	0·75	0·70	0·65
SN7494	0·80	0·75	0·70
SN7495	0·80	0·75	0·70
SN7496	1·00	0·97	0·95
SN7497	6·25	5·50	5·00
SN74100	2·50	2·30	2·00
SN74104	1·45	1·35	1·20
SN74105	1·45	1·35	1·20
SN74107	0·50	0·45	0·40
SN74110	0·80	0·70	0·60
SN74118	1·00	0·95	0·90
SN74119	1·90	1·78	1·65
SN74121	0·60	0·55	0·50
SN74122	1·35	1·25	1·10
SN74123	2·70	2·55	2·47
SN74141	1·00	0·95	0·90
SN74145	1·50	1·40	1·30
SN74150	3·35	2·95	2·15
SN74151	1·10	0·95	0·90
SN74153	1·35	1·27	1·20
SN74154	2·00	1·75	1·55
SN74155	1·55	1·47	1·35
SN74156	1·55	1·47	1·35
SN74157	1·80	1·70	1·50
SN74160	2·60	2·40	2·25
SN74161	2·60	2·40	2·25
SN74162	3·40	3·25	2·70
SN74163	3·40	3·25	2·70
SN74164	2·75	2·30	2·10
SN74165	4·00	3·50	3·00
SN74166	4·00	3·50	3·00
SN74167	6·25	5·60	5·10
SN74170	4·10	3·55	3·05
SN74174	2·00	1·75	1·30
SN74175	1·35	1·27	1·15
SN74176	1·60	1·35	1·20
SN74177	1·60	1·35	1·20
SN74180	1·55	1·30	1·20
SN74181	7·00	6·00	5·50
SN74182	2·00	1·80	1·60
SN74184	2·40	2·00	1·80
SN74185A	2·40	2·00	1·80
SN74190	1·95	1·85	1·75
SN74191	1·95	1·85	1·75
SN74192	2·00	1·90	1·80
SN74193	2·00	1·90	1·80
SN74194	2·50	2·25	1·90
SN74195	1·85	1·70	1·60
SN74196	1·50	1·40	1·30
SN74197	1·50	1·40	1·30
SN74198	4·60	3·70	3·35
SN74199	4·60	3·70	3·35

PRICES OF 7400 SERIES ARE CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX
LARGER QUANTITY PRICES PHONE (01) 402 4891
HIGH POWER SN 74 H00 } Now in stock—send
LOW POWER SM 74 L00 } for list No. 36

A SELECTION OF SEMI-CONDUCTORS FROM STOCK

AAY30	10p	BC147	12p	BU105	2·25	OC44	15p
AAY42	15p	BC169C	12p	BY100	15p	OC45	15p
AAZ13	10p	BC182	10p	BY126	15p	OC57	50p
AC107	35p	BC214	15p	BY127	15p	OC71	15p
AC126	25p	BCY32	75p	BYZ13	35p	OC72	25p
AC127	25p	BCY34	35p	C106D	65p	OC77	45p
AC128	25p	BCY39	1·00	GET111	55p	OC81	25p
AC176	25p	BCY42	30p	GET115	55p	OC83	25p
AC187	25p	BCY43	25p	GET880	45p	OC140	55p
AC188	25p	BCY55	2·50	LM309K (T03)	1·87	OC170	25p
ACY17	30p	BCY70	15p	MAT121	25p	OC171	30p
ACY20	20p	BCY71	20p	MJE340	50p	OC200	45p
ACY21	20p	BCY72	15p	MJE370	70p	OC201	75p
ACY39	55p	BCY87	2·99	MJE520	75p	OC202	80p
AD140	50p	BCZ11	50p	MJE2955	1·10	OC203	50p
AD149	50p	BD124	80p	MJE3055	75p	OCP71	1·25
AD161	35p	BD131	75p	MPF105	40p	ORP12	50p
AD162	35p	BD132	80p	NKT214	20p	ORP60	40p
AF117	20p	BF115	25p	NKT216	40p	P346A	20p
AF118	50p	BF167	25p	NKT217	40p	RAS310AF	45p
AF124	25p	BF173	25p	NKT403	70p	RAS508AF	55p
AF139	30p	BF179	30p	NKT404	50p	TAA263	75p
AF186	40p	BF180	30p	OA5	50p	TIL209	39p
AF239	40p	BF194	15p	OA10	35p	TIP29A	50p
ASY27	30p	BF195	15p	OA81	10p	TIP30A	60p
ASY28	25p	BFS61	25p	OA91	7p	TIP31A	60p
BA102	30p	BFS98	25p	OA200	7p	TIP32A	70p
BA115	7p	BFX13	25p	OA202	10p	TIP33A	1·00
BA145	15p	BFX34	75p	OC16	75p	TIP34A	1·50
BAX13	5p	BFX37	30p	OC20	95p	TIP35A	2·50
BAX16	7p	BFX88	20p	OC23	85p	TIP36A	3·00
BC107	10p	BFY50	20p	OC25	40p	TIP41A	75p
BC108	10p	BFY51	20p	OC28	65p	TIP42A	85p
BC109	10p	BFY52	20p	OC35	50p	2N2369A	25p
BC109C	12p	BFY64	50p	OC36	65p	2N2906	20p
BC113	15p	BFY90	59p	OC42	40p	2N2926 (all cols)	10p
BC117	20p	BLY36	8·00			2N3053	20p
BC143	35p	BSX20	15p			2N3054	50p
		BSY27	15p				

2N3055	55p	2N3440	75p
2N3442	1·25	2N3525	75p
2N3614	59p	2N3615	75p
2N3702	10p	2N3704	10p
2N3705	10p	2N3714	1·80
2N3771	1·75	2N3773	2·00
2N3790	2·25	2N3819	35p
2N3820	50p	2N3866	85p
2N3903	15p	2N3906	12p
2N4061	12p	2N4062	12p
2N4126	15p	2N4871	35p
2N5457	30p	2N5777	55p
28001	1·00	28012	10·00
28018	6·25	28026	8·90
28301	50p	28303	65p
28324	95p	40250	50p
40360	40p	40361	40p
40362	50p	40408	50p
40486	75p	40636	1·10
40430	1·00		

VAT

Prices DO NOT include Value Added Tax. From 1st April 10% must be added and shown separately to your total order (inclusive post/packing). Help us help you receive your order without delay.

QUANTITY DISCOUNTS

10% 12+ ; 15% 25+ ANY ONE TYPE
20% 100+ ; 25% 250+

From above sections except Integrated Circuits and Special Offers where discounts are included.
Minimum order value £1 please.
Postage 7p on all orders.

SPECIAL OFFERS! SEMI-CONDUCTORS

BFY90 59p
1000 MC/S
25 + 50p
100 + 45p
500 + 40p

AF117 Mullard 25p
25 + 17p
100 + 15p
500 + 12p

OC170 Mullard 25p
25 + 20p
100 + 18p
500 + 15p
1000 + 13p

BY127 Mullard 15p
25 + 12p
100 + 10p
500 + 9p
1000 + 8p

OA202 10p
25 + 8p
100 + 7p
500 + 6p
1000 + 5p

OC35 Mullard 50p
25 + 45p
100 + 40p
500 + 35p
1000 + 30p

2N2926 10p
All Colours
25 + 9p
100 + 8p
500 + 6p
1000 + 5p

2N3819 Texas 35p
25 + 30p
100 + 25p
500 + 20p
1000 + 15p

BC107, BC108, BC109 10p each
All Makes
25 + 8p
100 + 7p
500 + 6p
1000 + 5p

AD161, AD162 35p each
25 + 32p
100 + 28p
500 + 25p
1000 + 22p

2N3053 20p
25 + 18p
100 + 15p
500 + 12p
1000 + 10p

2N3055 55p
25 + 50p
100 + 45p
500 + 38p
1000 + 33p

ZENER DIODES

400 M/W 5% Miniature
BZY 88 Range

All voltages 3·3 – 33 Volt
10p each.

25+	9p
100+	8p
500+	6·5p
1000+	5p

Any one type.

1½ Watt 5% Wire Ends Metal Case
All voltages 6·8 – 100 Volts
20p each

25+	18p
100+	16p
500+	12p
1000+	10p

Any one type.

3 Watt Plastic Wire Ends 5%
3EZ Range

All voltages 6·8 – 100 Volts
30p each.

SILICON RECTIFIERS WIRE ENDED PLASTIC

Type	P.I.V.	1-11
1 amp miniature		
IN4001	50	6
IN4002	100	7
IN4003	200	8
IN4004	400	8
IN4005	600	10
IN4006	800	12
IN4007	1000	15
1·5 amp miniature		
PL4001	50	8
PL4002	100	9
PL4003	200	10
PL4004	400	10
PL4005	600	12
PL4006	800	15
PL4007	1000	16

LINEAR (O/P AMPS)

702C	TO5	75p
709C	TO99	35p
709C	D.I.L.	35p
723C	TO99	£1·00
723C	D.I.L.	95p
725C	TO99	£4·50
741C	TO99	55p
741C	D.I.L.	55p
747C	TO99	£1·10
747C	D.I.L.	£1·10
72741P	D.I.L.	60p
72748P	D.I.L.	60p

SINCLAIR IC12 £1·80

TOSHIBA
TH9013P
20 WATT AMP
£4·47 POST PAID
TH9014P Pre Amp £1·50

DATA AND CIRCUITS REF. 42 10p

FREE WITH PURCHASES

TRANSISTORS, IC's, TRIACS, BRIDGES, SCR's, LDR's

NEW FREE BOOKLET
(No. 36) OVER 1500 TYPES—
Send for yours today!

PLESSEY INTEGRATED CIRCUIT
3 Watt Amplifier SL403 D
Complete with 8-page booklet, circuits and data
£1.50 each

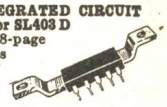

TRIACS

STUD WITH ACCESSORIES

Type	Volts P.I.V.	Price 1-11
3 AMP RANGE		
SC35A	100	75p
SC35B	200	79p
SC35D	400	85p
6 AMP RANGE (TO48)		
SC40A	100	85p
SC40B	200	90p
SC40D	400	£1·00
SC40E	500	£1·20
10 AMP RANGE (TO48)		
SC45A	100	95p
SC45B	200	£1·00
SC45D	400	£1·25
SC45E	500	£1·45
15 AMP RANGE (TO48)		
SC50A	100	£1·25
SC50B	200	£1·35
SC50D	400	£1·65
SC50E	500	£1·85
DIAC D32		25p
TRIACS— Additional Types		
40430	(TO66)	85p
40669	(Plastic)	£1·00
40486	(TO5)	80p

NEW BRIDGE RECTIFIERS

SMALL SIZE AND LOW COST

Type	Volts P.I.V.	Price 1-11
HALF AMP		
BO5/05	50	20p
BO5/10	100	25p
ONE AMP ¼ × ⅜ H TUBULAR		
B1/05	50	25p
B1/10	100	25p
B1/20	200	30p
B1/60	600	35p
ONE AMP (G.I.) TUBULAR		
W005	50	30p
W01	100	35p
W02	200	40p
W06	600	45p
TWO AMPS ½ H × ½ L × ¼		
B2/05	50	35p
B2/100	100	40p
B2/200	200	45p
B2/600	600	50p
B2/1000	1000	60p
FOUR AMPS ½H × ½L × ¼		
B4/100	100	60p
B4/200	200	65p
B4/400	400	70p
B4/600	600	75p
B4/800	800	£1·00
SIX AMPS ½H × ½L × ¼		
B6/100	100	70p
B6/200	200	75p
B6/400	400	90p
B6/600	600	£1·00

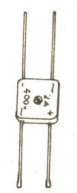

Type	Volts P.I.V.	Price 1-11
SILICON CONTROLLED RECTIFIERS		
ONE AMP		
CRS 1/05	50	25p
CRS 1/10	100	30p
CRS 1/20	200	30p
CRS 1/40	400	35p
CRS 1/60	600	45p
THREE AMP (TO48)		
CRS 3/05	50	30p
CRS 3/10	100	30p
CRS 3/20	200	35p
CRS 3/40	400	45p
CRS 3/60	600	55p
FIVE AMP (TO66)		
CRS 5/400	400	60p
SEVEN AMP (TO48)		
CRS 7/100	100	60p
CRS 7/200	200	65p
CRS 7/400	400	70p
CRS 7/600	600	95p
SIXTEEN AMP		
SCR 16/100	100	65p
SCR 16/200	200	70p
SCR 16/400	400	80p
SCR 16/600	600	£1·00

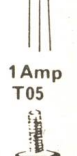

Henry's RADIO LIMITED
EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Open:- 9 am-6 pm 6 days a week (309 closed Thursday) All stores open all day Saturday

JOSTY KIT

NEW FROM DENMARK

Already Established As One Of The Best Selling Kits in Europe

JOSTY KIT today

is counted among the leading manufacturers of electronic kits in Europe. Constantly the experienced engineers at the **JOSTY** laboratories work on improvement of existing kits and on new developments. Only the best materials and components have been used. The circuit-boards are manufactured according to the newest developments in this field and are supplied with all holes drilled and printed showing the exact placing of the components. Our long standing experience enables us to guarantee every **JOSTY KIT** for **ONE YEAR** for all parts as well as the correct function of the assembled kit. **JOSTY KIT'S** are a quality produce of DENMARK.

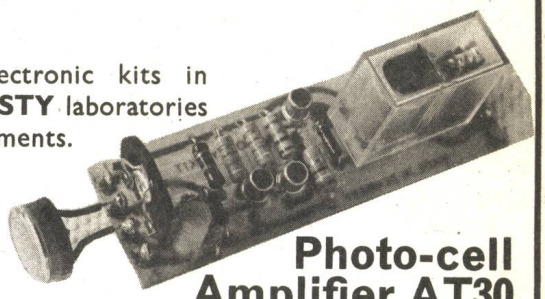

Photo-cell Amplifier AT30

NO more searching for Components, it's all in the bag the Josty way.

ELECTRONIC CONSTRUCTION KITS

We are sorry, you may have a little difficulty obtaining these kits at present. We at Josty are doing everything we can to produce more kits but in the meantime they are only available from

APPOINTED JOSTY KIT STOCKISTS

T. Pattison,
5 Maritime Terrace,
Blandford Street,
Sunderland,
Co. Durham.

Red Radio Shop,
31 Crowtree Rd.,
Sunderland,
Co. Durham.

J. R. Gough,
27 East Smithy St.,
South Shields,
Co. Durham.

Payne & Hornsby Ltd.,
3 Andrews House,
Gallowgate,
Newcastle-on-Tyne.

Richley & Freeman Ltd.,
100 Percy St.,
Newcastle-on-Tyne.

Aitken Bros. Ltd.,
35 High Bridge,
Newcastle-on-Tyne.

Hamilton Music Store,
Corporation Rd.,
Middlesbrough,
Teesside.

B. Williams,
16 Borough Rd.,
Middlesbrough,
Teesside.

McKenna & Brown Ltd.,
135 High St.,
Redcar,
Teesside.

Jaytron Ltd.,
178–9 Phibsborough Rd.,
Dublin 7,
Ireland.

Bond & Mason,
94 Church Rd.,
Stockton,
Teesside.

T. Jaques,
Waterdale Rd.,
Doncaster,
Yorks.

Modern Electronics,
5 Sunny Bar,
Doncaster,
York.

Misons,
Citadel Row,
Carlisle,
Cumberland.

Teleview Rentals,
414 Catcote Rd.,
Hartlepool,
Co. Durham.

JOSTY KIT RETAIL PRICE LIST (APRIL, 1973)

Model No.	Description	RRP Excluding V.A.T.	V.A.T.	Total RRP incl'd. V.A.T.
AF20	Mono Transistor Amplifier	4·80	0·48	5·28
AF30	Mono Transistor Pre-Amplifier	2·61	0·26	2·87
AF310	Mono Amplifier (for Stereo use two)	5·91	0·59	6·50
AT5	Automatic Light Control	2·58	0·26	2·84
AT30	Photo Cell Switching Unit	5·70	0·57	6·27
AT50	400W Triac Light Dimmer Speed Control	4·80	0·48	5·28
AT55	1,300W Triac Light Dimmer Speed Control	5·70	0·57	6·27
AT56	2,200W Triac Light Dimmer Speed Control	6·90	0·69	7·59
AT60	Psychedelic Light Control, Single Channel	7·80	0·78	8·58
AT65	Psychedelic Light Control, 3 Channel	14·55	1·45	16·00
HF61	Medium Wave Transistor Radio	3·33	0·33	3·66
HF65	F.M. Transistor Transmitter	2·70	0·27	2·97
HF75	F.M. Transistor Receiver	2·88	0·28	3·16
HF310	F.M. Tuner Unit	15·81	1·58	17·39
HF325	De-Luxe F.M. Tuner Unit	24·12	2·41	26·53
HF330	Stereo Decoder for use with HF310 or HF325	9·96	0·99	10·95
HF395	Aerial Amplifier for AM/FM Bands I, II and III	1·77	0·17	1·94
GP310	Stereo Pre-Amp to use with 2, AF310	21·27	2·12	23·39
GU330	Tremelo Unit for guitars, etc.	7·50	0·75	8·25
NT10	Power Supply 100m/a 9V Stabilised, 12V Unstabilised	6·15	0·61	6·76
NT300	Professional Stabilised Power Supply 2 × 30V, 2·2A	12·51	1·25	13·76
NT305	Transistor Converter 12/15V, a.c./d.c. to 6V, 7·5V, or 9V d.c.	4·50	0·45	4·95
NT310	Power Supply 240V a.c. to 2 × 18V d.c. at 2A	4·80	0·48	5·28
NT315	Power Supply 240V a.c. to 4·5—15V d.c. 500m/a	9·57	0·95	10·52

Sole UK Distributors

RADIO SUPPLIES

(Components) Ltd.

P.O. BOX 27 • 39 WHITBY STREET • HARTLEPOOL TS24 7BR

TELEPHONE 0429-5750 or 68002

PE

TWO-WAY LINK

COMMUNICATION is a fundamental function of electronics. It is particularly appropriate therefore to discuss certain aspects of communication relating to this magazine and its readers. First, one unquestionable fact: the link forged between a magazine and its readers is of inestimable value and significance. To this it can be confidently added that a magazine devoted to a creative hobby is especially favoured in that feedback from its readers is often likely to be in the form of examples of readers' own personal efforts and experiences. Such direct positive evidence of a live and actively committed readership is perhaps the best and most encouraging reward the editorial staff of such a publication could wish for.

PRACTICAL ELECTRONICS is proud of the two-way link established between individual readers and the magazine. We believe this is mutually stimulating. The existence of this link has long been evident, and has been demonstrated most effectively in our pages through the medium of *Ingenuity Unlimited*. Reference to the popularity and importance of this feature is not out of place. It has often been commented upon that the circuit ideas published constitute a most valuable source of reference to designers and constructors alike. We agree, and feel sure that many a reader must have saved time and effort through studying the ideas in *Ingenuity Unlimited*.

The varied nature of these miscellaneous circuits is, in itself, quite instructive. It indicates a wide catholic range of interests and shows that the inventive spirit is as much alive as ever; a refreshing and reassuring antidote to the drab uniformity of thought and action which characterises many aspects of modern life.

The circuits published in *I.U.* are generally of modest proportions, but that is no true measure of their actual or potential worth. They represent the new outlook and approach to electronics which has emerged in the course of the last few years. The dramatic scaling down in physical size of components over the last decade has given electronics greater—almost total—freedom in the environmental sense, and in many instances it is released entirely from the shackles of the mains umbilical cord. One result of all this has been the creation of an enormous variety of small circuits, many owing their origination to the enterprising efforts of private individuals to solve some problem or meet some particular need through the agency of electronics, the very thought of which would have been preposterous a few years ago. Many of these are worth recording for the benefit of others.

We are glad to be able to present some of the fruits of this kind of private enterprise in *Ingenuity Unlimited*. And never let it be forgotten that such relatively simple circuits as these may sometimes prove to be the seeds from which bigger and grander concepts grow.—F.E.B.

Editor
F. E. BENNETT

Editorial
R. D. RAILTON *Assistant Editor*
D. BARRINGTON *Production Editor*
G. GODBOLD
S. R. LEWIS B.Sc.

Art Dept.
J. D. POUNTNEY *Art Editor*
J. A. HADLEY
R. J. GOODMAN

Advertisement Manager
D. W. B. TILLEARD
Phone: 01-634 4202

P. J. MEW
Phone: 01-634 4210

C. R. BROWN, *Classified*
Phone: 01-634 4301

Editorial & Advertising Offices:
Fleetway House, Farringdon St.,
London EC4A 4AD
Phone: *Editorial* 01-634 4452
Advertisements 01-634 4202

BATTLE CHESS

By D. COLES

THE GAME of chess is more Machiavellian than military in its tactics and strategy and the circuit described here provides a version which is much more like the action of a military battle than court intrigue. Thus: Battle Chess.

No claim to originality is made by the author since Edgar Rice Burroughs—of Tarzan fame—once wrote a book called the "Chessmen of Mars" in which the idea was developed fully. The trouble with the Martian game was the requirement for real people, expected to fight to the death. The finding of 32 people willing to play chess in this way would undoubtedly prove difficult but the Battle Chess circuit is designed to simulate the duels which occur.

THE GAME

In basic concept Battle Chess uses the moves of its namesake but introduces a variety of programmable factors which come into play each time there is a confrontation. Thus one piece does not merely "take" its opponent—they have to fight the situation out in an electronic simulation.

PROGRAMMING

A number of factors have been programmed into the simulation circuit which parallel those found in real life military situations:

1. The strength of the various chessmen.
2. The addition of arms which increase the fighting strength of a chessman.
3. The reduction in fighting power due to supply problems (i.e. ditsance between duelling chessmen and their respective King's squares).
4. The proximity of supporting chessmen.
5. The effects of morale.

Combinations of resistors are used to determine factors 1 to 4. Resistance values interact with each other to affect the frequency of multivibrators (see Fig. 1).

Morale, on the other hand, is time dependent, being at its highest immediately after a successfully completed duel. The charge remaining in a capacitor simulates the effects of morale; the charge leaks away to nothing and the probability of winning the next duel drops from exceptionally high for the previously winning player to the normal value over a period of about ten minutes.

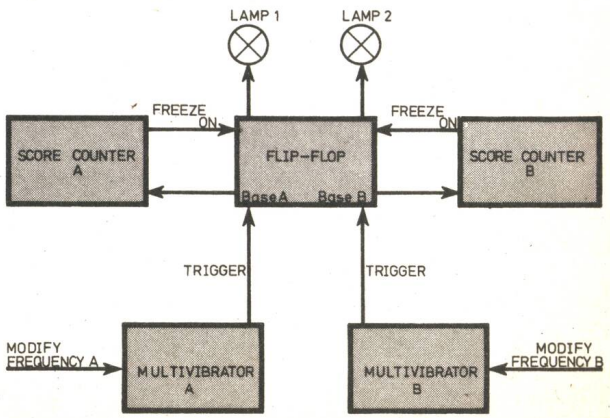

Fig. 1. Block schematic of the Battle circuit showing how the basic units are interconnected

The factors which combine in the game of Battle Chess make it virtually impossible to predict the outcome of a simulated duel. Thus the tactics and strategy which have to be developed by the player are more dynamic, more subject to caprice, than those used in conventional chess and are designed to approximate the real life strategy of a series of military engagements.

THE SIMULATION CIRCUIT

The circuit is shown in block form in Fig. 1 and in detail in Fig. 2.

Two conventional multivibrators A and B have their frequencies determined by external resistances connected between points 1 and 2 and the negative rail. The pulses of each multivibrator simulate the thrusts and parries of a duel and the resistances which combine to set the frequency of oscillation

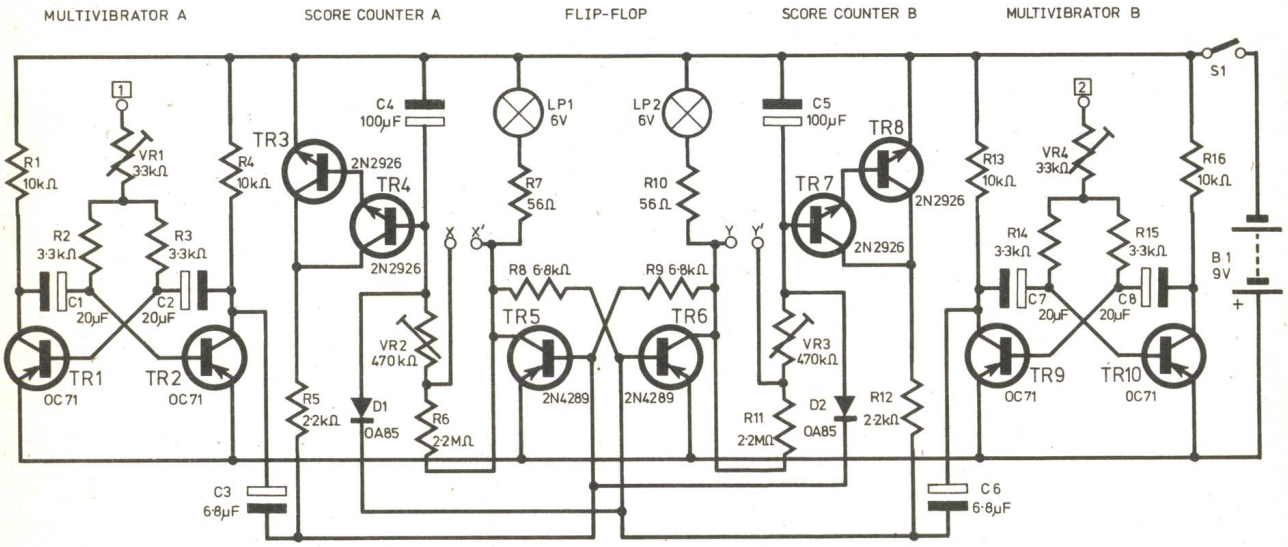

Fig. 2. Detailed circuit diagram of the equipment. When setting the timing of the various sections it may be necessary to select the electrolytic capacitors C1 to C8 if the variable resistors VR1 to VR4 are unable to provide sufficient adjustment to "pull" the periods into agreement

represent the value of the chessman, its distance from its King's square—representing G.H.Q.—and the number of friendly chessmen and their relative positions.

Pulses from each multivibrator are fed to a central flip-flop *via* capacitors C3 and C6. These pulses switch the flip-flop so that lamps LP1 and LP2 are switched on alternately with a continuously varying mark/space ratio. The lamps, as well as providing a visual analogue of the duel, eventually indicate which side has won.

Depending on which flip-flop transistor is ON, a current flows in R7 or R10 providing a potential difference which charges capacitors C4 and C5 through resistors R6 and R11. Additional resistors may be inserted at points XX′ and YY′ to reduce the overall resistance and allow C4 or C5 to charge faster.

These additional resistances simulate weapons used by the battling chessmen. When either C4 or C5 reaches a voltage of about 0·7 volts, the associated score counter, a Darlington pair, switches on, causing two things to happen. The Darlington pair output biases the flip-flop *via* R5 or R12, causing it to freeze with the winning side indicated by the light which remains lit.

The opposing capacitor's charge is neutralised through diodes D1 or D2 so that the other Darlington remains unswitched. The charge in the winning capacitor remains at the switching voltage as long as the lamp remains lit and leaks away once the circuit is switched off. This slowly leaking charge represents the player-army's morale and if a fight is started before the charge has gone, it takes less time to build up to its switching value.

CONSTRUCTION

The simulation circuit layout is not critical and the Veroboard method of construction is ideal.

The multivibrators may be constructed first and checked by temporarily connecting 3·3kΩ resistors between points 1 and 2 and the negative rail. Connect the 9 volt battery and check oscillation with a voltmeter across R4 and R13.

The flip-flop should be built on next, together with its trigger pulse feeds, C3 and C6. Connecting the battery should now cause the lamps to flash alternately in response to the multivibrators and clearly show the variation in mark/space ratio.

When constructing the score counters remember that diodes D1 and D2 must be good ones. A reverse leak on one or both of these, even if only four to five micro-amps, will upset the impartiality of the circuit. Pliers used as a heat shunt when connecting them will reduce the risk of damaging their characteristics.

To test the score counters, connect the battery once more and briefly touch a 10kΩ resistor, connected to the positive rail, to the positive lead of C3. The lights should cease to flash, LP1 should stay lit and LP2 extinguish.

Leave the circuit in this state to check that it is a stable condition; if the situation changes it will almost certainly be one of the diodes at fault. Repeat the test with C5.

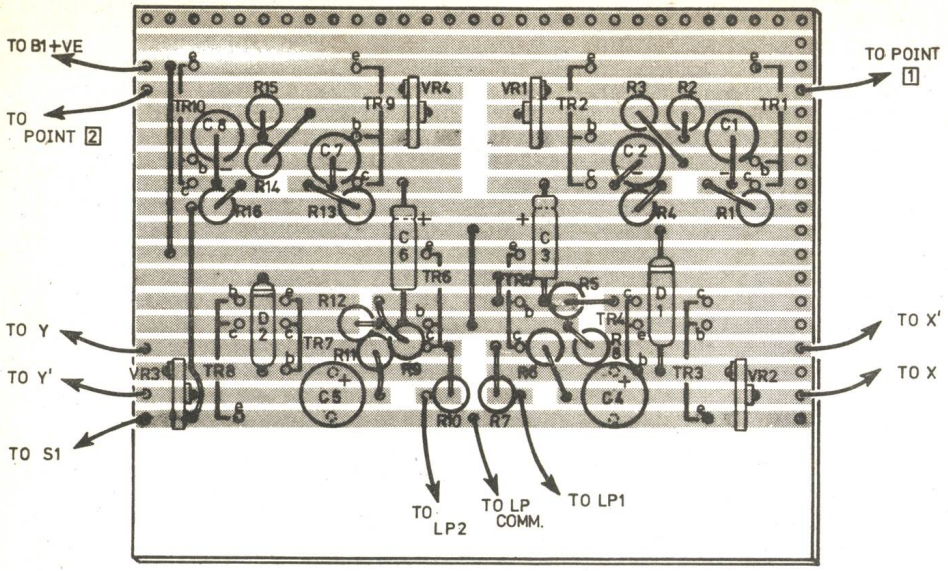

Fig. 3. Veroboard layout of the components on 0·1 inch pitch board. In the present case this was cut from a sheet edge to give a blank area which can be drilled for fixing as required

Finally, test that the flip-flop is charging the score capacitors properly. Temporarily connect a 1MΩ resistor across the points XX′. Discharge the score capacitors by shorting their positive leads to the negative rail before switching on. The lamps should flash for 10 to 15 seconds and then LP1 will remain on and LP2 off. Repeat with the 1MΩ resistor across the points YY′ and the opposite situation should occur. Failure at this stage could be due to poor solder joints, leaky diodes or slight tracking between the Veroboard copper strips.

THE PLAYING BOARD

The playing board consists of a matrix of 64 4-way sockets. Each side utilises two of the pin sockets and the connections to each side are similar and may be considered separately.

One of the pin sockets acts as a power feed and is connected to the negative line through a series resistor and a switch contact as in Fig. 4. Current is transferred to the other pin socket through the resistance of the chessman as shown in Fig. 5 and to the multivibrator through a second series resistor and switch contact. The two switches (1-pole, 8-way) act as Rank and File co-ordinates and locate the

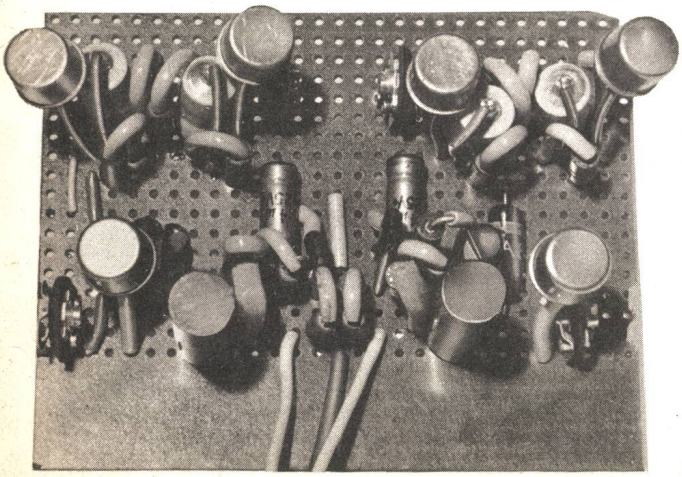

Completed circuit board for Battle Chess

COMPONENTS . . .

BATTLE CIRCUIT

Resistors

R1, R4, R13, R16	10k Ω	R6, R11	2·2M Ω
R2, R3, R14, R15	3·3k Ω	R7, R10	56 Ω
R5, R12	2·2k Ω	R8, R9	6·8k Ω

Capacitors

C1, C2, C7, C8	20μF	
C3, C6	6·8μF	All 12V working
C4, C5	100μF	

Potentiometers

VR1, VR4	3·3k Ω	
VR2, VR3	470k Ω	All Skeleton Preset

Transistors and Diodes

TR1, TR2, TR9, TR10	OC71, OC72 or similar
TR3, TR4, TR7, TR8	2N2926 or similar
TR5, TR6	2N4289 or similar
D1, D2	OA85

Miscellaneous

LP1, LP2 6V, 60mA
S1 Single pole ON/OFF (pushbutton type)
B1 PP7, PP9 or similar
Veroboard

PLAYING BOARD

Resistors

R101, R115	4·4k Ω
R102, R116	3·3k Ω
R103, R117	2·7k Ω
R104, R108, R118, R128	2·2k Ω
R105, R109, R114	1·7k Ω
R119, R122, R127	
R106, R110, R113, R120,	1·2k Ω
R123, R126	
R107, R111, R112, R121,	1·0k Ω
R124, R125	
RX (28 off)	10k Ω

Miscellaneous

Four Phono sockets
64 four-way sockets
4 single-pole 8-way wafer switches
Wire, hardboard, 2in × ½in section wood, glue, screws, panel pins.

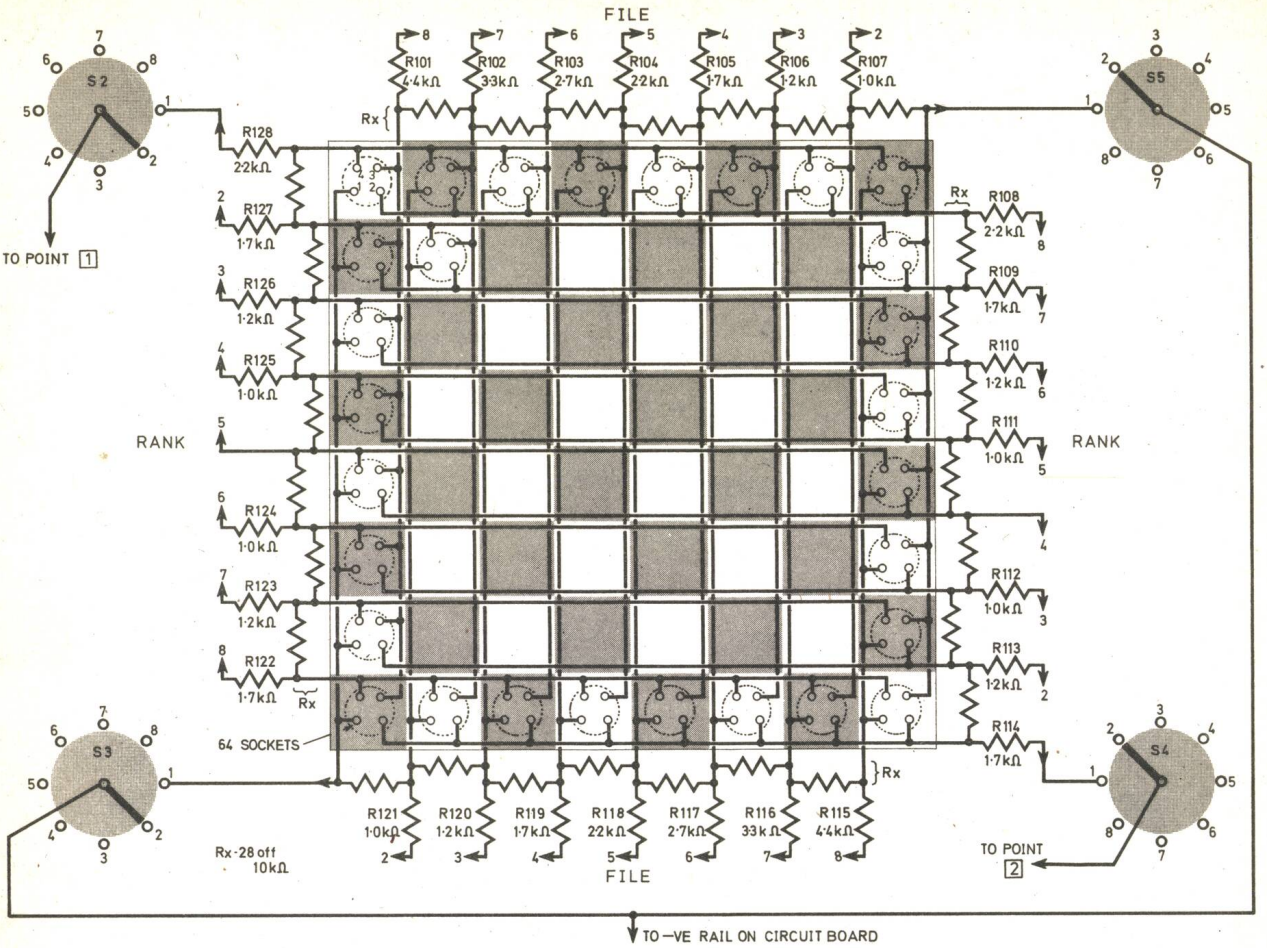

Fig. 4. Wiring of the playing board and Rank & File selection switches. Only the sockets at the periphery have been shown but, of course, there is a socket in each square, wired in a similar manner to all the others

chessmen which are to take part in the duel. The combined resistance of the two series resistors reduces the base biasing current in proportion to the chessman's distance from its King's square.

In addition to the series resistance and the chessman, each Rank and File is connected to its neighbouring Rank or File by a 10kΩ resistor so that a parallel path exists through every other friendly chessman. Thus the number and closeness of the other chessmen modify the final value of the biasing resistance; in effect, they lend their support.

BALANCING

Variations in the chessmen, the weapons, and the playing board resistors are quite in order and may be interpreted as the usual random variations to be found in any army. However, the battle simulator must be balanced so that should an identical situation occur, neither side has a better chance of winning. The four variable resistors VR1 to VR4 are used to balance the circuit.

Starting with the multivibrators temporarily solder a 4·7kΩ resistor to each biasing network at 1 and 2 in turn, using 1 per cent or 5 per cent resistor if possible. Using a voltmeter across R4 or R13, count the number of oscillations in a ten second interval. Using the variable resistors, VR1 or VR4 alter the frequencies until they are, as nearly as possible, equal.

To balance the score counters, temporarily solder two 2·2MΩ resistors across points XX′ and YY′. Switch on the simulator and note which lamp goes out permanently first. Alter VR2 and VR3 until only a small change in each preset changes the lamp which goes out. In between each try, it will be necessary to switch off and discharge C4 and C5.

THE PLAYING BOARD

The playing board circuit is shown in Fig. 4 together with details of switch connections. The 64 sockets are arranged in an 8 × 8 array on a hardboard mounting which forms the top of the circuit cabinet and the playing board. The four single-pole, eight-way switches are mounted two at each end, the press on, press off mains switch, the lamps and phono sockets can be mounted in any convenient position. The line and interconnecting resistors are suspended in the wiring. The wiring can be tied into looms and attached to the inside of the wooden sides with wiring clips. The sockets can be attached with Araldite.

The sides and ends of the cabinet are fastened to the hardboard top with glue and panel pins. The bottom, another piece of hardboard, is secured to the sides with a few screws so that it can be removed for servicing. Dimensions have not been given since size and proportions will vary with the constructor.

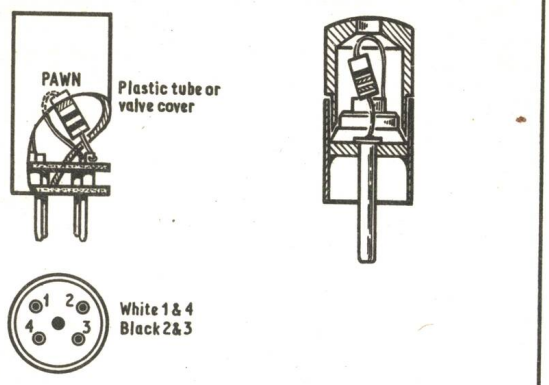

Fig. 5. A suggested form of chessman and weapon

CHESSMEN

Resistors	
King	0 Ω (link)
Queen	330 Ω
Knight	1·2k Ω
Bishop	2·7k Ω
Rook (Castle)	5·6k Ω
Pawn	8·2k Ω
Miscellaneous	
Holders	32 four-way plug bases

WEAPONS

Resistors	
Sword	2·2M Ω
Dagger	5M Ω
Mace	22M Ω
Miscellaneous	
Plugs	Phono plugs in quantity to suit

CHESSMEN AND WEAPONS

In the present example the chessmen are constructed on the four-way plug bases by soldering the correct resistors between the requisite pins as in Fig. 5 and Aralditing a length of plastic tube onto the base. The tube length may be varied to indicate the power of the piece; say three inches for a King reducing to one inch for a pawn. The name of the chessmen should be marked on the outside of the tube. The weapons are constructed similarly, using the phono plugs. Remember the Queening rule for pawns which successfully reach the opposite side of the board and make two Queens for each side.

The more ambitious might wish to mount genuine chessmen on the bases or perhaps even make pieces of their own devising. There are plenty of techniques available today to do this.

FINAL TESTING

When all the wiring is complete and the circuit board secured inside with small brackets, the complete unit may be tested. Switch both sets of co-ordinate switches to Rank 1, File 8 and place a pawn from each side at this position. Switch on the simulator and observe the rate at which the lights flash. Switch off and move the pawns to square: Rank 8, File 1 and switch on; the lights should now flash more slowly. Try the same tests with Kings; the same thing should happen except that the rate of flashing will be higher in both cases. Sometime during these tests a win will be indicated; when this happens, switch off and wait for the score capacitors to discharge, or alternatively discharge by shorting while switched off.

Try adding other pieces to the board in different positions and note the different flashing frequencies of each combination. In some cases the difference will be hard to distinguish since the alteration will be small.

RULES OF PLAY

The chessmen move as for conventional chess and for the same distances.

When one player wishes to take an opposing piece and gain the occupied square, the attacking player must verbally challenge the other. Attacking and defending chessmen should be indicated and the defender cannot retreat from the challenge.

Rank and File co-ordinates are set on the switches to indicate the squares holding each piece. Weapons may be selected at any time and plugged into the phono sockets. The battle simulator is now switched on and the two lamps will flash alternately for, typically, 20 or 30 seconds. The light which remains on after the flashing has ceased indicates the winner who can now occupy the disputed square. The loser is removed from the game and the winner confiscates the loser's weapons for his own arsenal.

TACTICS

The interaction of Player/Chessman/Position/Weapons/Morale alters the probability of any particular piece winning and if two roughly equal chessmen are opposed it is virtually impossible to predict a duel's outcome. The tactics used in Battle Chess can be effective in placing a player in a stronger position.

For example, wherever possible arrange to do battle as near as possible to your own King's square or try to arrange that your own combatant is close to a number of friendly pieces—the more powerful, the better.

Force battles to take place within 5 or 10 minutes of a previously successful battle or fight a delaying action for a similar time if a battle has just been lost. This avoids or uses the morale charge on the capacitor.

Of course there are the obvious comments like "don't throw pieces away in needless battles, they may be useful for support if not for combat" and finally always remember, you may win a battle but lose the war.

NOTES

Although the rules of play suggested follow the rules of conventional chess, the equipment can be used to simulate modern battle conditions quite successfully. The playing board may be marked out with a map, and infantry, tanks, missiles can be substituted for pawns, knights, rooks, etc. In this case, the constructor is left to formulate his own rules. ★

audio compressor

By R. A. Penfold

AN AUDIO compressor is an audio amplifier which is designed to provide a constant output level, from a wide variety of input levels. Thus it is sometimes referred to as a constant volume amplifier. It merely consists of an audio amplifier which is fitted with some form of automatic gain control.

AUDIO COMPRESSION

Reasons for using audio compression vary, as it can be used in several applications. It is often used in tape recording when something such as a debate is to be recorded, and only one microphone is to be used.

The use of compression obviates the need to re-adjust the recording level each time a different person speaks, as, once the level is set for one speaker, the correct modulation depth will be obtained for all the others. This is of course providing that all the speakers are close enough to the microphone, to provide a sufficient output to operate the compressor. This technique also removes the possibility of overmodulation at unexpectedly high volume levels.

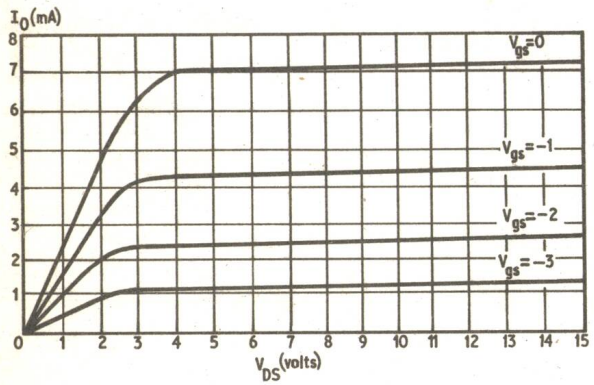

Fig. 1. Drain current plotted against drain to source voltage for a typical *n*-channel f.e.t.

Speech compression is used in some amateur transmitters in order to maintain a high average modulation level, without running the risk of over-modulating an a.m. transmitter, or exceeding the maximum power rating of the power amplifier of an S.S.B. transmitter.

Simple peak clipping circuits are sometimes used instead, but these introduce a comparatively high degreee of distortion, and are not as effective.

USING AN F.E.T.

When subject to a low voltage between the drain, and source terminals, an f.e.t. exhibits the characteristic of an ordinary resistor. This is illustrated in Fig. 1, which shows typical transfer characteristics of an *n*-channel f.e.t., at various gate voltages.

It will be seen that the value of the resistor formed by the f.e.t. can be varied by altering the gate bias voltage. It can be varied from a few hundred ohms to many megohms.

THE CIRCUIT

A circuit diagram of an audio compressor utilising an f.e.t. in a voltage controlled attenuator is shown in Fig. 2. The input impedance to the unit is high (typically 2·5 megohm), and is suitable for use with a crystal microphone. The output is at a low impedance, and will drive virtually any amplifier. For low level inputs (i.e. below the level at which compression begins) a voltage gain of about 275 is available with the gain control at maximum.

In order to obtain the required high input impedance, the input transistor, TR1, is operated in the emitter follower mode. This is direct coupled to TR2, which is a common emitter amplifier.

For TR1 to produce a very high input impedance it must have a fairly high impedance in its emitter circuit. R4 is therefore used to raise the input impedance to TR2, in order to achieve this.

The bootstrapping technique has been employed in order to virtually eliminate the shunting effect the biasing resistors, R1, R2, and R3 would otherwise have on the input impedance. C3 is the bootstrapping capacitor.

Transistors TR1 and TR2 are used mainly as a buffer amplifier, and provide only a small voltage gain.

VOLTAGE CONTROLLED ATTENUATOR

The output from TR2 is fed via C4 to the voltage controlled attenuator. R7 and R8 form a tap on the main supply rail, and produce a suitably low supply voltage for the f.e.t. TR3. The drain to source impedance of TR3, and R9 form an attenuator.

With no negative bias at TR3 gate, the drain to source impedance is very low, and the attenuation factor of the circuit is very low. By giving a negative bias at TR3 gate, the drain to source impedance can be greatly increased, and the attenuation factor of the circuit thus also greatly increased. A voltage controlled attenuator is thus formed.

The output from the attenuator is fed via C5 to the input of a very high gain common emitter amplifier, TR4, which is followed by an emitter follower stage, TR5. From the emitter of TR5, some of the signal is fed via C8 to the volume control, VR1, and then to the output socket. The remainder of the signal is used to produce the biasing voltage for the attenuator.

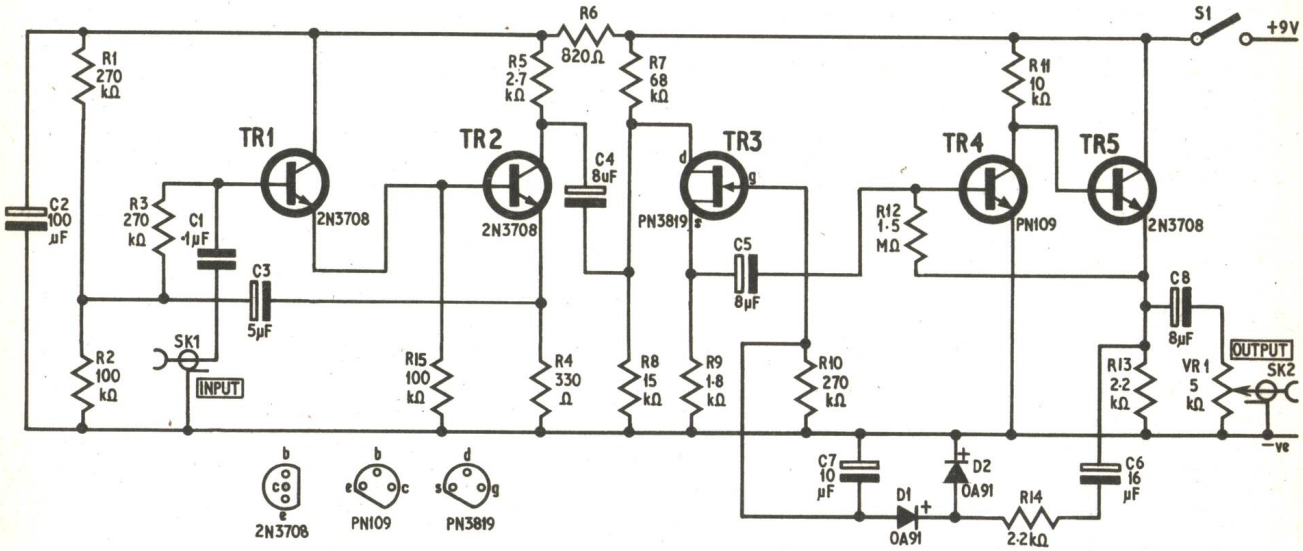

Fig. 2. Circuit diagram of the complete Audio Compressor

RECTIFYING CIRCUIT

It is fed via C6, and R14 to a rectifying circuit, consisting of D1 and D2. This arrangement is used as it provides a fast attack speed, but with a long decay. C7 smoothes the a.f. half cycles to a d.c. negative bias, which is then fed to the gate terminal of the f.e.t.

There is not a linear relationship between the gate bias voltage, and the drain to source resistance of the f.e.t. With a low level input, only a small bias voltage will be produced, and this will only alter the value of the resistor formed by TR3 by a few tens of ohms. This will have a negligible effect upon the attenuation factor of the circuit.

Raising the input level slightly will increase the bias voltage, and due to the logarithmic relationship between bias voltage, and drain to source resistance, this will cause a much larger increase in this resistance, say a few hundred ohms. This will result in a noticeable, although still only small increase in the attenuation factor of TR3 and R9.

INPUT LEVEL

It is at this point that raising the input level will begin to have a very noticeable effect on the voltage controlled attenuator, as only a very small change in bias is required to cause an increase of several kilohms in the drain to source resistance of TR3. Thus an increase in the input level causes the gain of the amplifier to drop considerably, and so reduce the output level. The output level will therefore tend to remain almost constant, even though the input level may vary considerably, providing the input is above the level at which compression commences.

Even with quite high input levels (up to about 0·25V r.m.s.) there will be only a small degree of distortion in the circuit. The use of modern silicon transistors in the input stage ensures a low noise level.

TIME CONSTANT

The attack of the a.g.c. circuit is very fast, being virtually instantaneous, but the time constant capacitor, C7, produces a fairly long decay time (about two seconds). For most applications this is very desirable, as it prevents the gain from rising during brief pauses in the signal, and the noise which would subsequently accompany this.

However, the decay time can be altered to suit individual requirements by altering the value of C7, the larger its value, the longer the decay time.

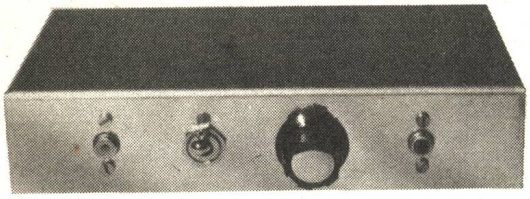

audio compressor

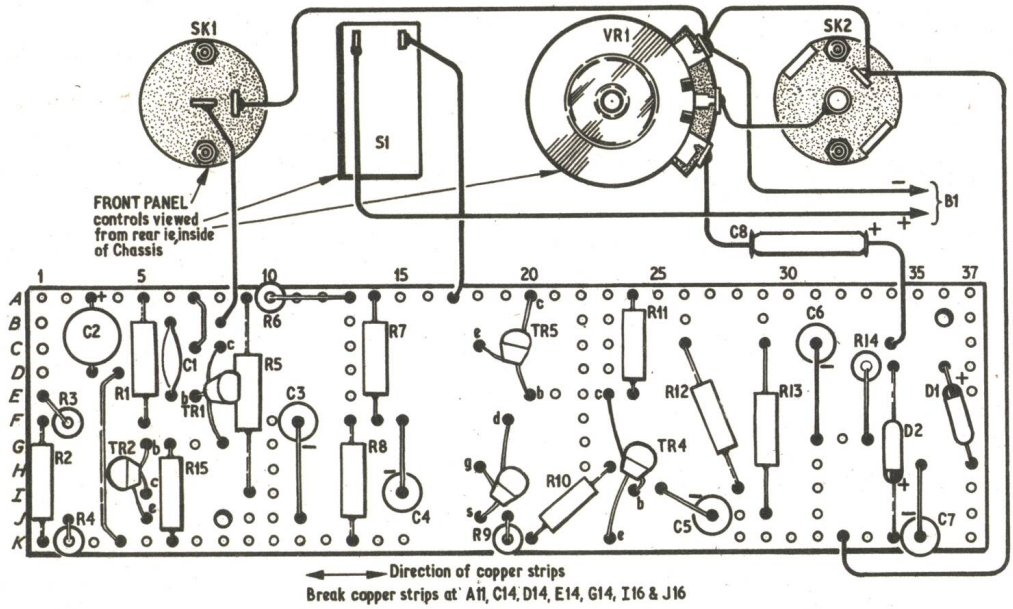

Fig. 3. Layout of the components on the Veroboard panel and interconnections to the other components. Note breaks in copper strips

COMPONENTS . . .

Resistors

R1	270k Ω	R8	15k Ω
R2	100k Ω	R9	1·8k Ω
R3	270k Ω	R10	270k Ω
R4	330 Ω	R11	10k Ω
R5	2·7k Ω	R12	1·5M Ω
R6	820 Ω	R13	2·2k Ω
R7	68k Ω	R14	2·2k Ω
		R15	100k Ω

Miniature ¼W, ±10%

Potentiometer

VR1 5k Ω logarithmic

Semiconductors

TR1, TR2, TR5 2N3708 (3 off)
TR3 PN3819
TR4 PN109 } (Arrow Electronics Ltd.)
D1, D2 OA91 or similar (2 off)

Capacitors

C1 0·1μF disc ceramic
C2 100μF
C3 5μF
C4 8μF
C5 8μF
C6 16μF
C7 10μF
C8 8μF
All 10V electrolytic except C1

Miscellaneous

S1 S.P.S.T. toggle switch.
Vero board panel, 0·1in matric
7in × 4in × 1½in
Aluminium chassis with base plate (H. L. Smith and Co.)
SK1, SK2 phono sockets (2 off)
Control knob, 9V PP6 battery and clips to suit, hardware

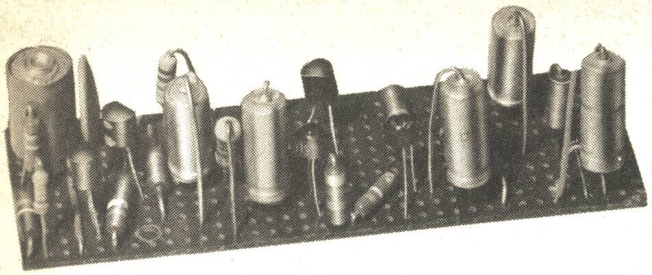

CONSTRUCTION

Constructional requirements will vary widely, as some constructors may wish to build the unit as an integral part of some piece of equipment, while others may wish to build it as a self-contained unit, as was the prototype. In either case the Veroboard layout shown in Fig. 3 can be used. 0·1in matrix board is used, and the copper strips run lengthwise. These are cut at a number of points as detailed in the diagram.

A 7in × 4in × 1·5in aluminium chassis fitted with a base plate is used as a case for the prototype. The Veroboard panel is mounted on stand-off insulators in order to hold it a little way clear of the metal case. A PP6 battery is used to power the unit, this particular type being a good fit in the case, and has virtually its shelf life with normal use.

Phono sockets were use for SK1, and SK2 on the prototype, but almost any type of two way socket is of course suitable. Due to the high input impedance of the unit it is essential that the input lead is screened, in order to avoid unwanted noise pick up.

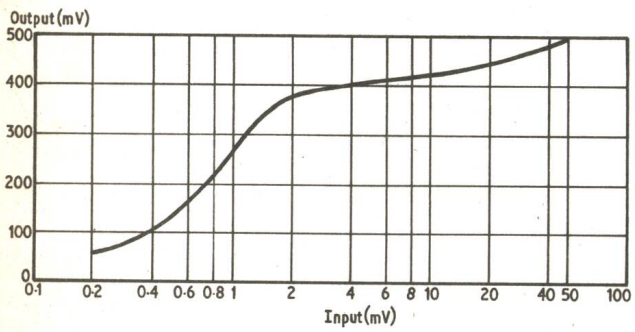

Fig. 4. Graph showing the relationship between the input and output voltages of the Audio Compressor. It can be seen that while the input changes from 2 to 50 millivolts the output only changes by 25 per cent

RESULTS

A graph of the results obtained on the prototype compressor is shown in Fig. 4. This shows input voltage versus output voltage. With an input of 1mV or less the gain is fairly constant at about 275, or a little less. Above this the gain decreases slightly as the input voltage is raised, until it reaches about 2·6mV, and increasing the input voltage above this level has very little effect upon the output. ★

INGENUITY UNLIMITED

A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.
This is YOUR page and any idea published will be awarded payment according to its merits.

LIGHT-OPERATED POWER CONTROLLER

THE circuit shown in Fig. 1 will control the a.c. power delivered to a mains load according to the level of light incident on a light-dependent resistor PCC1. An advantage of this circuit is its extreme simplicity and consequent ease of construction.

As the mains voltage rises the capacitor C1 is charged via the potentiometer formed by R1 and PCC1. When the voltage across C1 rises sufficiently, the bi-directional trigger diode D1 breaks down and C1 is discharged into the gate of the triac CSR1, switching it into its low resistance state. The combination of a 0·1μF capacitor and the breakover voltage of the diac of around ±30V gives a sufficient pulse to ensure the triggering of most commonly available triacs. The diac also ensures that the maximum voltage rating of the LDR is not exceeded. Since the triac and the diac are bi-directional this situation occurs on both positive and negative-going half-cycles of the mains supply, the triac returning to its high resistance state at each zero point in the cycle.

The point in each half-cycle at which the triac is fired is determined by the incident light on PCC1, full power being delivered to the load when this point occurs very early in the cycle—i.e. with the LDR in

REED RELAY CURRENT TRIP

A SIMPLE over current protection device for a series regulated power suppply can be made using a thyristor and a reed relay. The circuit diagram is shown in Fig. 1.

When a fault current appears across VR1 and R1, R2, diode D1 conducts a positive going signal to the gate of the thyristor CSR1 which triggers it on. The reed relay then closes applying a negative voltage to the base of TR1 cutting it off and reducing the output voltage to zero.

The action of this cutout is much faster than a fuse thus protecting the sensitive semiconductors in the circuit being supplied. The lamp LP1 will show a fault condition until the SCR is shorted by S1. If the fault is still present the thyristor will fire cutting off the supply again.

The trip current is set by VR1. The reed relay is a miniature type about an inch long with 250 turns of 32 s.w.g. enamelled copper wire wound onto the reed relay body.

G. Daddy,
Hull.

darkness. The power that can be controlled by the circuit depends only on the ratings of the triac and on the adequacy of its heat sink.

Components L1, L2, C2, R2 provide suppression of the radio interference generated by the switching of the triac and also protect the triac against mains-borne transients to which these devices are highly susceptible. Note that R2 is necessary to limit the discharge current of C2 which might otherwise exceed the peak surge current of the triac when it fires, and destroy it.

Owing to the triac's low tolerance to over-voltage transients, this circuit can not be recommended for use with motor loads without the incorporation of additional protection. If circuit values are altered, to change the light threshold or the operating range of the unit for example, care should be taken not to exceed the current/power ratings of the LDR, the diac and the triac gate.

Circuit values are such that incident daylight will result in no power being applied to the load, while the level of light around dusk will give full power.

I. Page,
London, S.W.13.

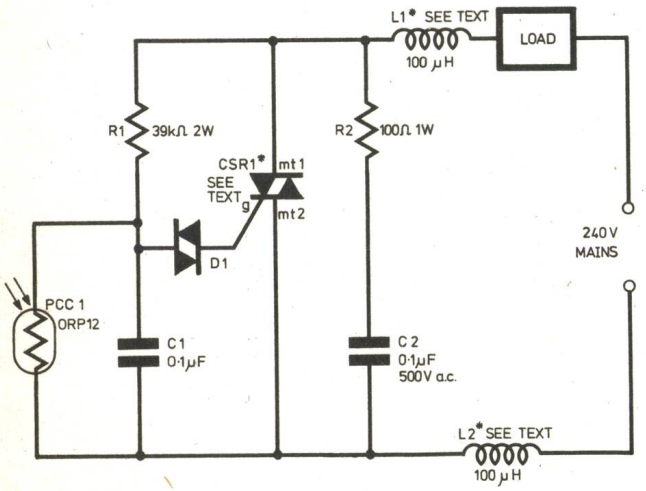

REVERSING LIGHT WARNING

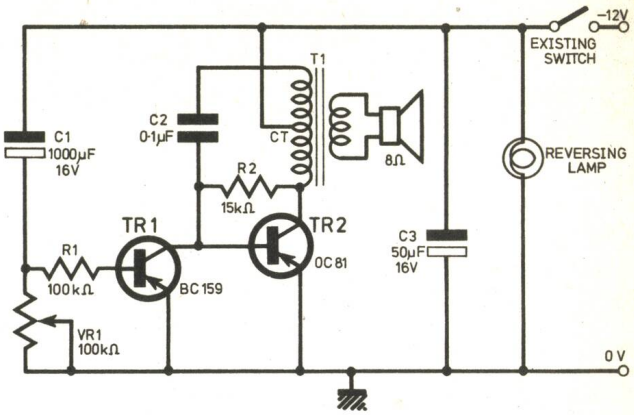

MANY cars have reversing lights fitted which are operated by a switch on the dash; this must by law be illuminated, but I have found it quite easy to leave the switch on accidentally for periods during the daytime.

I therefore devised the circuit shown in Fig. 1. This is wired in parallel with the reversing light(s), and sounds a warning if left on for more than about a minute. When power is applied, C1 slowly charges up through VR1 and TR1, the latter remaining switched on until C1 is almost fully charged. TR2 is a conventional oscillator, but cannot operate until TR1 turns off, when it produces a fairly loud tone in the speaker.

Components are not critical. TR1 can be any silicon *pnp* transistor, and any of the OC72/75/81/82 range will work as TR2. Transformer T1 is a small audio output transformer out of an old transistor radio.

The circuit was made up on a small piece of tagboard, and mounted behind the dashboard.

D. L. Atkin,
Sheffield.

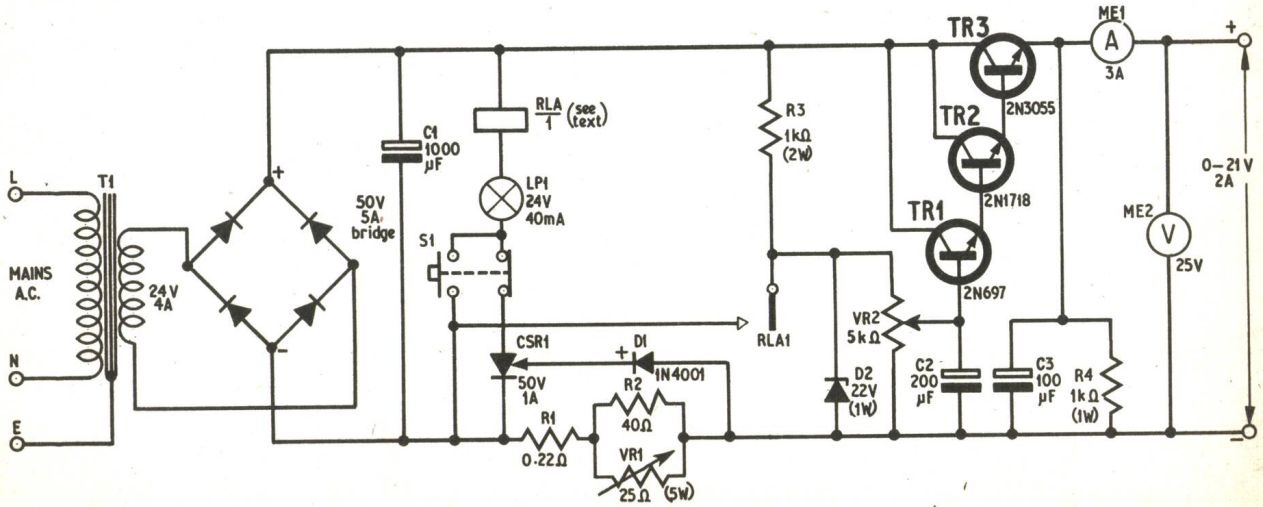

SPACEWATCH

BY FRANK W. HYDE

SUN JOLTS THE EARTH

Solar storms release an enormous amount of energy which can affect the spin of the earth on its axis. Some ten years ago the French astronomer, A. Danjon, announced that the very large solar flare of 1959, significantly affected the length of the day. At that time he was not very well supported by colleagues.

However, the very energetic solar storm which occurred in August 1972 showed an even greater effect on the earth. A change of more than 10 milliseconds was recorded. This particular solar storm is the greatest that has been recorded during the 370 years that observations have been made.

The storm, which began on August 2, started with very pronounced sun spot activity and continued for a week. At that time there were probes orbiting the earth and sun and the *Pioneer 10* spacecraft was on its way towards Jupiter. It was thus a time when an enormous amount of data was to hand to record the solar activity.

The recorded cosmic rays and the ejected plasma measurements have enabled an estimate to be made of the manner in which the magnetosphere is affected. The storm also gave a clue to the mechanism involved. There is always a short interval between the time of storm and the jolt that the earth receives. The theory is that the particles and the plasma disturb the atmospheric circulation, thereby affecting the earth's spin.

CHANDLER WOBBLE

That the length of day is increasing has been known for a long time since it can be determined by observation. The main effect is from the tidal action between the sun-earth-moon system. Another condition that affects the length of day is the Chandler wobble.

Named after its discoverer, the poles of the earth wobble against the star background in a regular way over a period of fourteen months. The effect is by no means well understood but it is thought to be due to the fluidic centre core of the earth. The wobble effect on the slowing down of the earth's rotation is superimposed on the main tidal variation.

In addition to the Chandler wobble there is still another effect and that is the seasonal variation of the large scale atmospheric movements. Here again the actual mechanism is not fully understood though it is noted that this effect is on the same scale as that of the solar activity.

CHINOOK WINDS

The strong winds which blow on the eastern slopes of the Rocky Mountains are known as the Chinook winds and in some areas do much damage as there has been no way in which to predict when these winds will come. It is thought that the winds are related to the temperature inversion layer of the atmosphere on the windward side of the Continental Divide.

It is now thought that the Chinook wind of the Northern Plains is produced because the weight of the air causes a compression which in turn raises the temperature. While this is helpfully welcomed in some places it is not in others.

EARLY WARNING

To provide some means of prediction, audio methods are being tried out and powerful audio pulses are being directed at the atmosphere. These pulses transmitted vertically upwards every twenty seconds, at a frequency of 1,000Hz, are reflected by the inversion layers. High power is required because some of the temperature inversion layers are as high as 7,000ft.

By using a doppler sounder it is hoped to measure the profiles of the winds. The very obvious advantage of this, in addition to warning, is the possible effects of pollution carried by air. Siting factories and other process plants could be predetermined and a possible reduction of pollution effects controlled.

ASTEROIDS

The earth seems to have a wider influence in the solar system than was first thought. There are from time to time reports that certain asteroids come close to the earth and but for the grace of cosmic law the home planet would be exposed to a catastrophe. It has now been established that certain of the asteroids are specifically involved.

The asteroids which have been the subject of special study are the Apollo group consisting of Toro and Geographos, which cross the earth's orbit, and three of the Amor group, Eros, Amor and Ivar, which cross Mars' orbit. These asteroids all have orbits round the sun but are perturbed in these orbits by the influence of the planets.

Of the five asteroids named Geographos is perturbed only at random. The others have regular periodical perturbations in respect of the earth's orbital period. The way in which this occurs is rather complex for there is libration in the sense that the whole pattern of the orbit rocks about the earth-sun line. Libration or rocking implies a periodic variation in the orbital period but the period can oscillate without libration.

ORBITAL PERIODS

The periods that emerge are in the ratio five earth periods to eight Toro which would result in a period of 150 years were it not complicated by a relation with Venus. This ratio of 5 Venus periods to 13 Toro gives a 180 year period. The Toro orbit is therefore an unstable one and it is expected that this may change after 2200 A.D.

The complicated nature of these variations of one body relative to another is further indicated by the fact that the earth perturbs Eros once every seven years and also the asteroid Amor is involved. In the case of Ivar two perturbations take place in each 28 years. This has a libration of 300 years and is the most stable of the orbits.

TAILPIECE

It seems that there is to be a further revival of the Velikovsky theories. Claims are being made as to confirmation of such events as the Jupiter radiations and the magnetic remanence in the older moon rocks with a suggestion that the main craters and valleys are no more than 300 years old.

At any rate no one can say that the astronomical world and that of space is dull.

LARGE STOCKS, ATTRACTIVE DISCOUNTS DEPENDABLE SERVICE

Everything brand new and to makers' specifications.

ELECTROVALUE

Electronic Component Specialists

TRANSISTORS BY SIEMENS AND NEWMARKET

2N3055 *npn* silicon power	**60p**
AC153K *pnp* germanium low power	**32p**
AC176K *npn* germanium low power	**32p**
AD161 *npn* germanium medium power	**42p**
AD162 *pnp* germanium medium power	**40p**
AF139 *pnp* germanium UHF	**49p**

NPN: BC107 **13p**, BC108 **12p**, BC109 **13p**, BC167 **11p**, BC168 **10p**, BC169 **11p**.

PNP: BC177 **21p**, BC178 **19p**, BC179 **21p**, BC257 **12p**, BC258 **11p**, BC259 **13p**.

Standard groupings available.

BD135 *npn* medium power	**37p**
BD136 *pnp* medium power	**38p**

DIODES

OA90, OA91, OA95, **6p** each; OA200, **9p**; OA202, **10p**.

Other semiconductors: AC128, **17p**; AF117, **32p**; BFY51, **19p**. Full lists and technical data will be found in Catalogue No. 6. See also amendments list.

SIEMENS' THYRISTORS
0·8A 400V **56p**, 600V **70p**.
3A 400V **60p**, 600V **88p**.

ZENER DIODES full range E24 values: 400mW: 2·7V to 36V, **14p** each; 1W: 6·8V to 82V, **21p** each: 1·5W: 4·7V to 75V, **48p** each. Clip to increase 1·5W rating to 3 watts (type 266F) **4p**.

DIN PLUGS AND SOCKETS

by Hirshmann, 4A rating

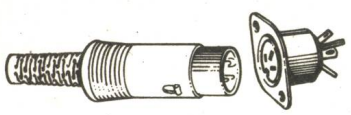

2 way LS —socket **10p**, plug **12p**
3 way scr.—socket **10p**, plug **12p**
5 way scr.—socket **11p**, plug **15p**

TRANSISTOR ACCESSORIES
TO3 cover, **7p**; Heat sinks 1°C/W, type 6W1. undrilled, **60p**.

SWITCHES

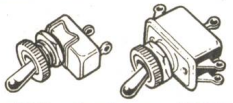

1011 SPST toggle, **20p**; 409 DPDT toggle, **29p** (these are chrome plated, 2·5A rating); 7201 sub-miniature DPDT 250V a.c./2A, **48p**.

ROTARY SWITCHES

Radiospares Miniature Maka-switch (in assembly kit form). Shaft, **48p**. Wafers, MBB-2P5W, 1P11W: BBM1P12W, 2P6W, 3P4W, 4P3W, 6P2W, **32p** each.

WAVECHANGE SWITCHES

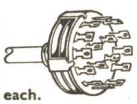

1P12W, 2P6W, 3P4W, 4I3W, **24p** each.

ELECTROLYTIC CAPACITORS AXIAL LEAD

Rated voltage: / Capacity μF	3V	6·3V	10V	16V	25V	40V	63V	100V
0·47	—	—	—	—	—	—	10p	7p
1·0	—	—	—	—	—	10p	—	7p
2·2	—	—	—	—	10p	—	7p	8p
4·7	—	—	—	10p	—	7p	8p	7p
10	—	—	—	—	7p	8p	7p	8p
22	—	—	7p	7p	—	7p	7p	9p
47	7p	—	8p	8p	8p	7p	9p	12p
100	8p	7p	7p	7p	7p	9p	11p	19p
220	7p	8p	8p	8p	9p	10p	17p	27p
470	8p	9p	9p	10p	12p	17p	24p	43p
1,000	10p	12p	12p	17p	20p	24p	40p	—
2,200	14p	17p	22p	25p	36p	40p	—	—
4,700	25p	28p	37p	41p	54p	—	—	—
10,000	40p	43p	—	—	—	—	—	—

Prices subject to amendment by the manufacturer.

POLYCARBONATE—5% TOLERANCE
250V up to 0·1μF: 100V, 0·1μF and above.
0·01; 0·012; 0·015; 0·018; 0·022; 0·027; 0·033; 0·047; 0·056; **4p** each. 0·068; 0·082; 0·1; 0·12; 0·15; **4p** each. 0·18; 0·22; **5p** each. 0·27; 0·33; **6p**. 0·39 **7p**. 0·47 **8p**. 0·56 **10p**. 0·68 **11p**. 1μF **13p**. *Prices subject to amendment by the manufacturer.*

Minitron Digital Counter
Type 3015F. Seven Filament segment indicators to make 0-9 + decimal point. Compatible with standard logic modules, nett **£2**. Decoder driver type FLL 121T nett **£1·36**. DIL socket, nett **£2**.

RESISTORS – 10%, 5%, 2%

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99 (see note below)	100 up
C	1/20W	5%	82Ω–220KΩ	E12	9	8	**7·5**
C	1/8W	5%	4·7Ω–470KΩ	E24	1	0·9	**0.75 nett**
C	1/4W	5%	4·7Ω–10MΩ	E12	1	0·9	**0·75 nett**
C	1/2W	5%	4·7Ω–10MΩ	E24	1·2	1	**0·95 nett**
C	1W	5%	4·7Ω–10MΩ	E12	2·5	2	**1·6 nett**
MO	1/2W	2%	10Ω–1MΩ	E24	4	3	**2 nett**
WW	1W	10% ± 1/20Ω	0·22Ω–3·9Ω	E12	7	7	**6**
WW	3W	5%	1Ω–10KΩ	E12	7	7	**6**
WW	7W	5%	1Ω–10KΩ	E12	9	9	**8**

Codes: C = carbon film, high stability, low noise.
MO = metal oxide, Electrosil TR5, ultra low noise.
WW = wire wound, Plessey.
Values:
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51 62, 75, 91 and their decades.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.)

Send S.A.E. for latest supplement of additional lines and price amendments to our No. 6 Catalogue

KNOBS

All grub screw fitting for ¼in shafts. Black. For other types —see Catalogue No. 6, p. 54.

F.14 (20mm) pack of 2, **32p**; F.13 (26mm) pack of 2, **38p**; F.12 (33mm) pack of 2, **40p**; F.19 (20mm) pack of 2, **32p**; F.18 (26mm) pack of 2, **38p**; F.17 (33mm) pack of 2, **40p**; KB.4 (20mm) pack of 4, **40p**; K30/3 (17mm) aluminium, **24p** each.

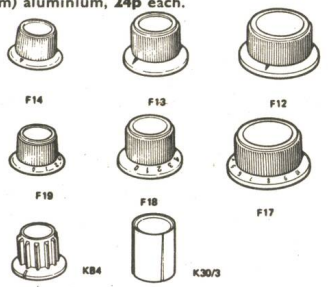

TRANSFORMERS—MAINS

MT3 30V/2A plus 4 taps	**£2·85**
MT103 50V/1A plus 4 taps	**£2·55**
MT104 50V/2A plus 4 taps	**£3·50**
MT127 60V/2A plus 4 taps	**£3·80**
13TO5 13V/½A, CT	**£1·25**
28TO5 12+12V, 2–0–2V.	**£1·65**

IT'S ALL IN THE LATEST ELECTROVALUE CATALOGUE

No. 6 (4th printing) contains details of 100's of semiconductors; ICs with circuit diagrams, R's and C's of practically every kind, accessories, components, tools, materials, etc., information and equivalent tables, etc. Well illustrated (96 pages, 5¼in × 8¼in) **25p** post free with refund voucher for 25p allowable on orders over £5 or more.

with 25p refund voucher

POTENTIOMETERS

Rotary, carbon track, double wipe
SINGLE P20 lin. 100Ω to 2·2MΩ, **12p**; P20 log. 4·7KΩ to 2·2 Meg. **12p**; JP20 log. 4·7KΩ, to 2·2MΩ, **12p**; **Dual gang** lin. 4·7KΩ to 2·2MΩ, **42p**; Dual log. 4·7KΩ to 2·2MΩ, **42p**; Log/antilog, 10K, 22K, 47K, 1MΩ only, **42p**; Dual antilog. 10K only, **42p**. Any type with 2A D.P. mains switch, **12p** extra.
Only decades of 10, 22 and 47 available in ranges quoted.

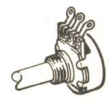
TYPE P20

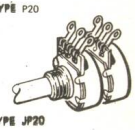
TYPE JP20

DUAL CONCENTRIC DP20 in any combination of P20 values, **60p**; with switch, **72p**.
SLIDER
Lin. or log. 10K to 1 meg. in all popular values, each **26p**.
Control knobs blk./white/red yel./gr./blue/dk. grey/lt. grey, **5p** each.

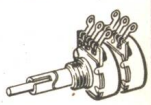
TYPE DP20

CARBON SKELETON PRESETS
Small high quality, PR lin. 100Ω, 220Ω, 470Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10MΩ. Vertical or horizontal mounting, **5p** each.

SLIDER

DISCOUNTS

All items offered for sale in accordance with our stated terms of business, copy of which available on request.
Not allowed on nett price items. 10% on orders for £5 or more. 15% on orders of £15 or more.
Prices subject to alteration without prior notice. Prices quoted DO NOT include V.A.T.
Orders received from U.K. customers must be accompanied by an additional 10% of the nett value for V.A.T.
Overseas orders are exempt.

POSTAGE AND PACKING FREE
SURCHARGE 10p on small mail orders under £2. Overseas orders carriage and insurance charged at cost.

ELECTROVALUE

(Dept. PE8), 28 ST. JUDE'S ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Hours: 9—5.30. Sat. 1 p.m. Tel.: Egham 3603 Telex 264475
Eng. Reg. No. 1047769 Registered Office: 28 St. Jude's Rd., Englefield Green, Egham, Surrey TW20 0HB

PHOTOELECTRIC KIT

CONTENTS. P.C. Chassis Board, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, Diode, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation with a few additional components.

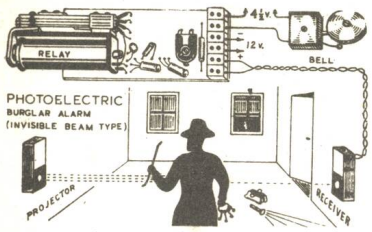

PHOTOELECTRIC KIT
£2·85

Postage and Pack. 15p (U.K.)
Commonwealth
SURFACE MAIL 25p
AIR MAIL £1·40
Australia, New Zealand, S. Africa, Canada and U.S.A.
Also Essential Data Circuits and Plans for Building 10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT
Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.
CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks. Infra-red filter, projector lamp holder, screws, nails, brackets, building plans, etc. Price **£1·45**. Postage and Pack. 10p (U.K.). Commonwealth: Surface Mail 20p, Air Mail 50p.

LONG RANGE INVISIBLE BEAM OPTICAL KIT
CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price **£2·10**. Postage 15p (U.K.). Commonwealth: Surface 20p, Air Mail £1·15.

BIOFEEDBACK AMPLIFIER KIT
Tunable, General-Purpose, Interference-Rejecting Differential Amplifier for experimental investigation of signals produced by the brain, heart and muscles. When used with an oscilloscope, or aural indicator, it enables you to monitor your brain-waves, learn to relax, meditate, etc.
CONTENTS: All Capacitors, Resistors, Pots, Semiconductors, I.C., Electrodes, Leads, Chassis, Case, Batteries, Plans and Instructions. Price **£4·75** postage and pack. 25p (U.K.). Commonwealth: Surface 30p. Air Mail £1.

ALPHA-BETHA-THETA BRAINWAVE MONITOR KIT
Aural Brainwave Indicator for use with a Biofeedback Amplifier. Converts subsonic brain frequencies into audible signals for easy recognition.
CONTENTS: Resistors, Pots, Capacitors, Transistors, Diodes, Leads, Chassis, Case, Earphone, Battery, Plans and Instructions. Price **£3·25**, postage and pack. 15p (U.K.). Commonwealth: Surface 25p. Air Mail 75p.

YORK ELECTRICS Mail Order Dept.
335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send S.A.E. for full details, a brief description of all Kits and Projects

FERRANTI
ZN414 Radio i.c.
only £1.32 WITH DATA

WE ARE SPECIALISTS IN FERRANTI SEMICONDUCTORS

BFS59	15p	ZTX310	9p	ZTX504	43p	ZS170	10p
BFS60	20p	ZTX311	10p	ZTX510	17p	ZS171	13p
BFS61	20p	ZTX312	10p	ZTX530	21p	ZS172	16p
BFS96	15p	ZTX313	11p	ZTX531	22p	ZS174	17p
BFS97	23p	ZTX314	13p	ZTX550	17p	ZS176	23p
BFS98	20p	ZTX320	31p	ZTX551	17p	ZS178	38p
ZTX107	9p	ZTX330	15p	2N3055	72p	ZS270	11p
ZTX108	8p	ZTX331	16p	* DIODES *		ZS271	16p
ZTX109	11p	ZTX382	13p			ZS272	18p
ZTX212	14p	ZTX383	15p	ZS120	8p	ZS274	19p
ZTX213	14p	ZTX384	18p	ZS121	10p	ZS276	26p
ZTX214	15p	ZTX450	17p	ZS122	13p	ZS278	37p
ZTX300	12p	ZTX451	17p	ZS123	16p	* ZENERS *	
ZTX301	13p	ZTX500	12p	ZS124	18p	KS030A to	
ZTX302	17p	ZTX501	13p	ZS140	25p	KS180A—	
ZTX303	14p	ZTX502	17p	ZS141	43p	all types	19p
ZTX304	21p	ZTX503	14p	ZS142	33p		

ALL DEVICES TOP GRADE, BRAND NEW, AND FULLY GUARANTEED
WE CAN SUPPLY ANY FERRANTI DEVICE. Send S.A.E. for quotation
PRICES SLASHED! RCA CA3090Q **£3·25**; CA3075 **99p.** Limited quantity only.
P. E. Triffid. ZT1711 **24p**; 2N1132 **25p.**
POSTAGE AND PACKING 10p—Free over £2. Send S.A.E. for our full price list and data sheet.
ALL PRICES INCLUDE V.A.T.

DAVIAN ELECTRONICS
PO BOX 38, OLDHAM, LANCS. OL2 6XJ

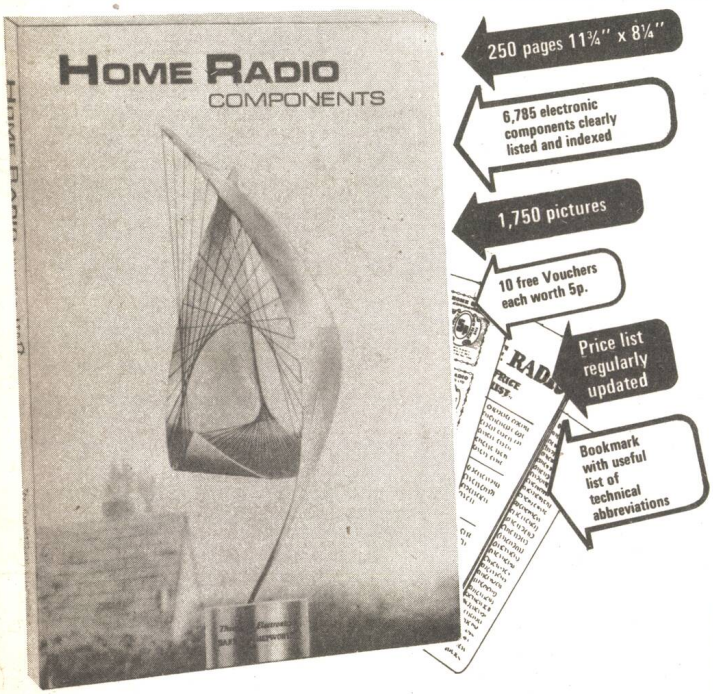
HOME RADIO
COMPONENTS
250 pages 11¾" x 8¼"
6,785 electronic components clearly listed and indexed
1,750 pictures
10 free Vouchers each worth 5p.
Price list regularly updated
Bookmark with useful list of technical abbreviations

The Catalogue you MUST have!

Details of our popular Credit Account Service and our Easy Ordering System are included in the catalogue.

Only 55p.
plus 22p POST AND PACKING

POST THIS COUPON
with cheque or P.O. for 77p.

Name _____
Address _____
_____

HOME RADIO (Components) LTD. Regd. No. 912966 London
Dept. PE, 234-240 London Road, Mitcham CR4 3HD

The price of 77p. applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

Strictly Instrumental

by K. Lenton-Smith

THE piano, without which no home was complete several decades ago, is now becoming a rarity because of lack of living room space and other home entertainment attractions. This could be one of the reasons that the guitar is often the choice of younger members of the household.

For those wishing to take up a keyboard instrument, the Electric Piano is ideal as it occupies very little room.

ELECTRIC PIANO

The majority of these instruments suffer from only one disadvantage musically in that the keyboard is usually a standard five octave (organ) manual, against the seven octaves of a conventional piano. Nevertheless, five octaves are probably sufficient for performing many piano pieces. The cost of a compact electric piano may be well under £200 and, with pre-amplified output, it is small enough to be easily carried in one hand.

The percussive attack of a conventional piano will readily penetrate a semi-detached house's party wall: the volume of its electronic counterpart may be closely controlled. Earphones may be used for practising late in the evening. The electric piano allows changes of timbre, such as harpsicord, honky-tonk, etc.

Like the majority of commercial electronic organs, the generated waveform is square. The usual arrangement is a Hartley (sine wave) oscillator, followed by a series of Eccles-Jordan frequency dividers (square wave) for each of the 12 chromatic notes of the scale. The dividers are invariably integrated circuits as these are cheaper and smaller than discrete components and there is a saving in labour costs.

Piano tuners introduce small frequency variations to give an ordinary piano added brilliance: from middle "*C*', notes above are progressively sharpened slightly, those below flattened. A system of electronic frequency division—where tuning must be mathematically accurate—would thus not appear to be ideal. In practice, however, this discrepancy is not noticeable and, given a good amplification system (which could well be the domestic hi-fi), a most realistic piano results.

KEYING METHODS

Diode-keying is normally used in electric pianos as this keying method can produce the attack/decay characteristics of a piano fairly closely. Keying transients are practically eliminated by diode-keying and precious metal keyswitches are not vital.

Some instruments employ a changeover keyswitch where a capacitor is kept charged while the key is at rest, depression of the key connecting the charged capacitor to the gating circuit. Filtering is required to round up the square waveform somewhat, usually in the form of a passive low pass filter for "piano" tone.

The keyboard may be split by a special control so that a "walking bass" may be played without drowning the melody line. The Italian-made "Instapiano" is an attractive example, retailing at about £160 before VAT. It measures approximately 48in × 10in × 4in.

PLAYING TECHNIQUE

The electric piano has a number of advantages, not least that there is plenty of published piano music available. Though it may take a little getting used to, pianists have no difficulty in accustoming themselves to the electric piano.

Where two manuals and a pedal clavier are concerned, printed music is not so readily available—unless the player particularly likes Bach and Handel.

The pianist who turns to the organ has some formidable problems: as long as a note is held it will sound, unlike the automatic decay of the piano/electric piano. Thus, attempting to play piano scores on an organ results in disaster—and what does one do with the pedals except "double" the left hand part?

Any constructional project is a challenge to get the beast working! Those who build musical instruments have a further challenge: they have to master the keyboard, and organists who like lighter music will find three-stave scores few and far between.

CHORD SYMBOL BASIS

A number of readers will have built the P.E. Organ, or have access to an organ, and may have experienced difficulty buying music. The usual light music score includes the piano part, guitar symbols, vocal line and chord symbols; the last two are the important items for the organist. With practice, it is possible to play both manuals and pedals using this information only, on sight.

Memorising what each chord symbol involves might, at first, appear to be a mammoth task. Relatively few key signatures are used in popular music as the publishers have to bear in mind the transposing instruments (normally *B* flat and *E* flat) which may be involved. The same chords appear frequently and can be memorised as easily as the resistor colour code! But it must be admitted that the "bridge" often moves into a strange key and demands quick thinking.

The right hand part (melody) should be registered in a way that makes the tune fairly incisive; single notes are often sufficient and, where chords are used, the melody should still stand out.

The left hand part is the problem and should be considered along with the pedals; accompaniment registration should be quieter and less clear cut than the upper manual. The root of the chord symbol can be used for the pedal on the downbeats, at least for a start, alternating with the fifth (i.e., *C* — *G*) except where a diminished chord is indicated. The left hand plays the notes indicated by the chord symbol, according to the time signature and rhythm, using an "anchor note" if possible.

THE GOOD COMPANIONS

Two magazines designed to complement each other in every way—together satisfying the needs of everyone involved in electronics.

PE

Everyday Electronics **caters especially for the newcomer to this field, and shows, in full detail, how to build many simple and useful items; it also offers advice and facts on constructional methods and component purchase, and explains circuit operation in straightforward terms.**

This month *EE* features the construction of a Waa-Waa Pedal, a Slave Flash for photographers, and an Electronic Doorbell.

It's all quite simple with *Everyday Electronics*. August issue on sale Friday, July 20. 15p.

PE Sound Synthesiser 7
REVERBERATION AMPLIFIER
RING MODULATOR
PEAK LEVEL METER

By G.D.SHAW

THIS month the Ring Modulator, Peak Level Meter circuit and Reverberation Amplifier will be described.

THE RING MODULATOR

With the ring modulator the combination of tones follows a complex inter-relationship in which each frequency is continuously compared with and modified by the other, The resultant output provides a tone which consists of the sum and difference of the two constituent frequencies appearing at the same time and irrespective of the phase angle relationship. A typical output waveform is illustrated in Fig. 7.1.

A simplified version of a transistorised ring modulator manufactured in integrated circuit form by Silicon General, the SG3402N, is shown in Fig. 7.2 and it will be seen that the device consists essentially of a pair of cross-coupled differential pairs jointly controlled by a third. Two inputs—carrier and modulator—are required and it is important to differentiate between them since the input characteristics are dissimilar. Application of equal amplitude signals to both inputs will provide an output showing about 3dB voltage gain over either input. Removal of the modulator with the carrier still applied will result in attenuation of the output signal by about 50dB but if the input situation is reversed the output attenuation is only about 35dB.

Although designed primarily for communications work the SG3402N is capable of working satisfactorily at quite low audio frequencies by the simple expedient of increasing the value of the input and decoupling capacitors.

The frequency response of the prototype Ring Modulator is shown in Fig. 7.3 and will be seen to be effectively flat over most of the audio frequency spectrum. The theoretical circuit is shown in Fig. 7.4.

The maximum input signal to the SG3402N should not normally exceed 50mV and thus resistive attenuators are employed to raise the signal level, at the input sockets, to one more compatible with the signal level normally routed around the Synthesiser. With the value of resistors employed in the attenuators the maximum input signal at the sockets is thus 500mV.

IC2 serves to amplify the output to about 1·5V at the rated input levels and measured at an input frequency to both channels of 1kHz. The ring modulator shares a circuit board with the peak level meter and the board layout is shown in Fig. 7.5.

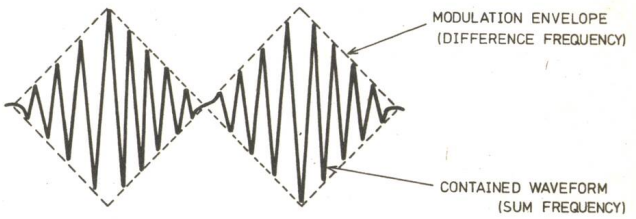

Fig. 7.1. Typical output waveform of the Ring Modulator

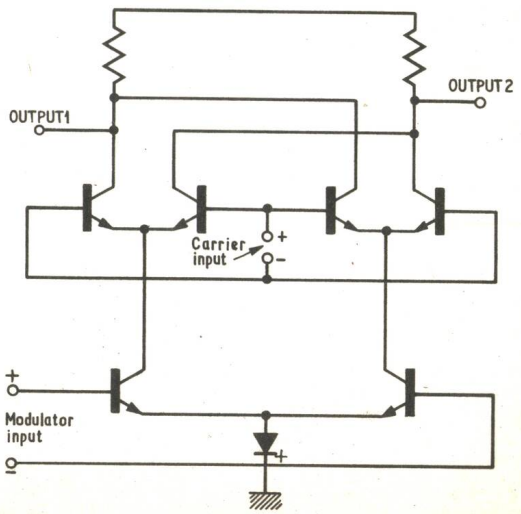

Fig. 7.2. Schematic of a transistorised Ring Modulator

RANGE OF SOUNDS PRODUCED

The type of modulation produced by the ring modulator is wholly unique and thus also is the range of sounds which can be achieved. If two pure tones are modulated together and one of them is reduced in frequency the resultant output would follow the pattern shown in the table below which relates the sum and difference output frequencies with the carrier and modulator input frequencies.

	Frequency (Hz)						
Carrier	700	600	500	400	300	200	100
Modulator	400	400	400	400	400	400	400
Sum	1100	1000	900	800	700	600	500
Difference	300	200	100	0	100	200	300

It can be seen that, whereas the resultant sum reduces in frequency at the same rate as the carrier, the frequency reduces until it reaches zero (carrier and modulator frequencies equal) and then, as the carrier continues to fall to a frequency lower than that of the modulator, the difference frequency begins to increase at a proportional rate.

When the inputs to the Ring Modulator carry harmonics in addition to the pure tones then further series of frequency relationships are established for each of the component harmonics relative to one another and to the respective fundamentals.

When the inputs to the Ring Modulator are of symmetrical triangular waveform, such as those generated by the v.c.o., an extremely complex set of frequency relationships is established due to the fact that, in common with the square wave, the triangular waveform consists of a long series of odd harmonics.

SOUNDS PRODUCED

The Ring Modulator may be used in many fascinating ways from the creation of truly "out of this world" sounds, the transposition of tones, bell-like sounds, Dalek voices and so on.

In the transposition of tones the only stipulation is that the modulating frequency should be higher than the carrier (this latter input consisting of the signal for treatment). For any range of carrier frequencies the modulator frequency has to be calculated or determined empirically, to provide the best overall effect.

An interesting experiment can be carried out by cascading two Ring Modulators. The first uses the v.c.o. output to drive carrier and modulator inputs so that the output is the octave, or second harmonic, of the v.c.o. frequency. The output of the first Ring Modulator is used to drive the modulator input of the second whilst the carrier input is derived direct from the v.c.o. Thus the difference frequency of the second Ring Modulator will follow, exactly, the performance of the v.c.o. while the sum frequency will approximate to a quarter-tone accompaniment about $1\frac{1}{2}$ octaves higher. There are very wide possibilities for further experiment in this kind of mode.

A true bell tone is very complex and is difficult to imitate with exactitude. A fairly close approximation may be achieved by adjusting two v.c.o.s to a mid-range frequency, say 4kHz, such that there is a slow beat between them. One v.c.o. then drives the carrier and the other v.c.o. the modulator input of the Ring Modulator. A very important characteristic of the bell-like sound lies in its envelope presentation and this will be dealt with in detail in next month's article.

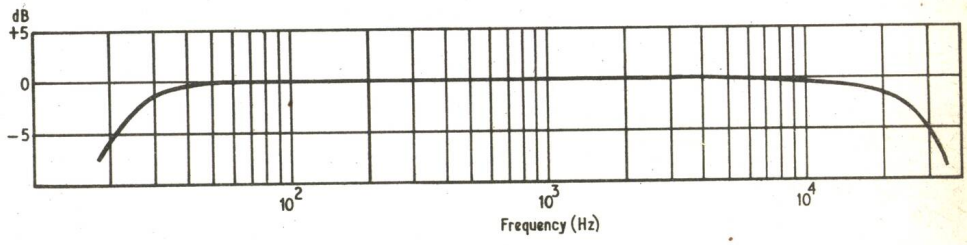

Fig. 7.3. Frequency response of prototype Ring Modulator

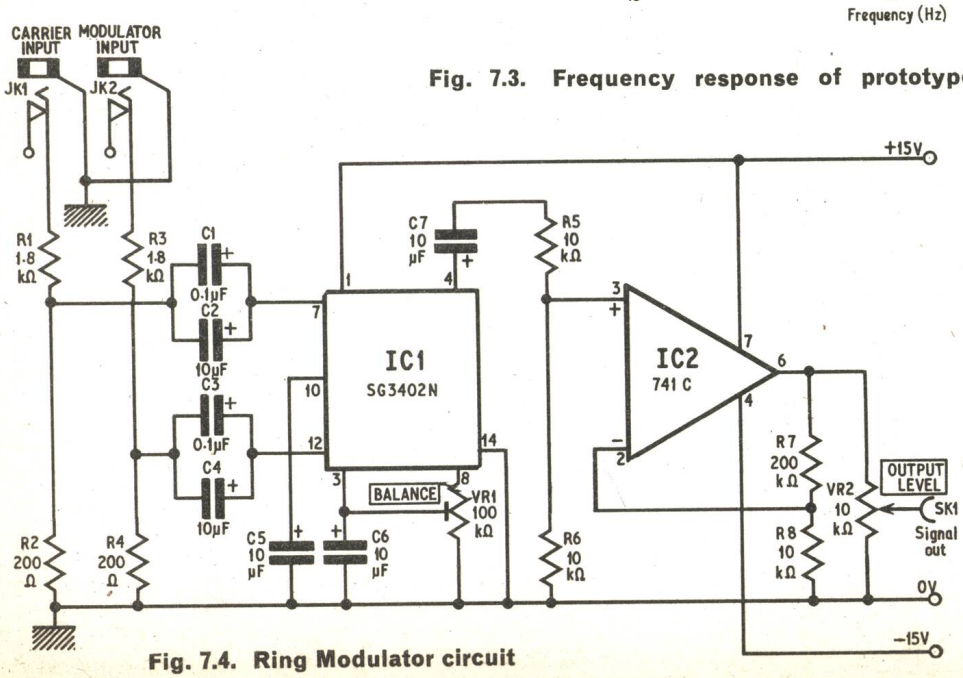

Fig. 7.4. Ring Modulator circuit

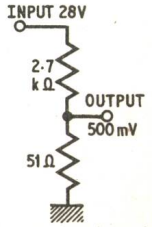

Fig. 7.5. Simple resistive attenuator for use with the Ring Modulator

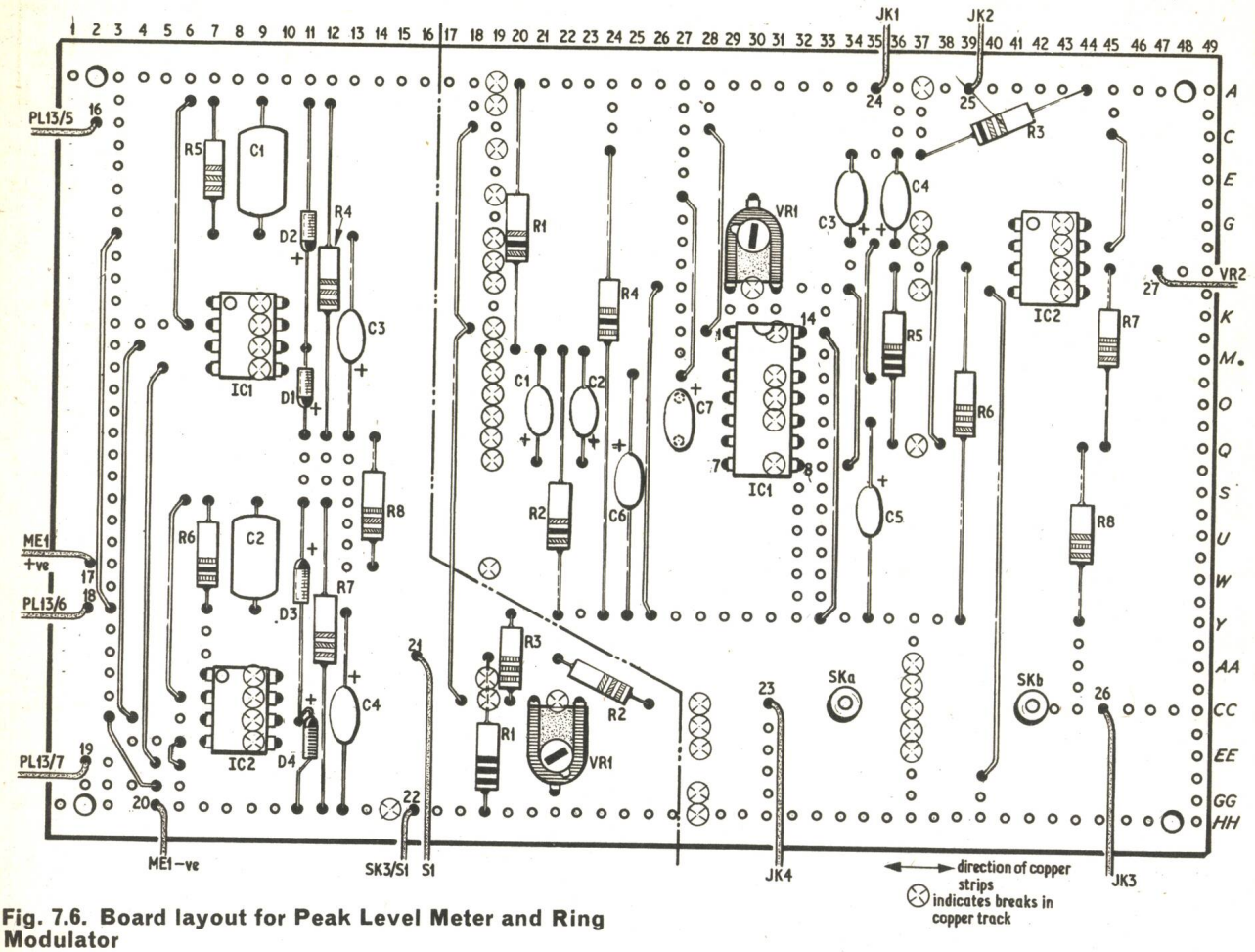

Fig. 7.6. Board layout for Peak Level Meter and Ring Modulator

COMPONENTS . . .

PEAK LEVEL METER CIRCUIT

Resistors

R1	91k Ω
R2–R3	20k Ω (2 off)
R4	91k Ω
R5–R6	3·3k Ω (2 off)
R7	91k Ω
R8	110k Ω

All 5% ½ watt carbon

Capacitors

C1–C2	1,500pF (2 off)
C3–C4	22μF 16V tantalum

Potentiometers

VR1 50k Ω carbon preset

Diodes

D1–D4 IN914 (4 off)

Integrated Circuits

IC1-IC2 741C (2 off)

Miscellaneous

ME1 MR38P SEW panel meter (G. W. Smith Ltd.)
SK3 2mm miniature socket

RING MODULATOR

Resistors

R1	1·8k Ω	R5	10k Ω
R2	200 Ω	R6	10k Ω
R3	1·8k Ω	R7	200k Ω
R4	200 Ω	R8	10k Ω

All 5% ½ watt carbon

Capacitors

C1	0·1μF 35V	C3	0·1μF 35V
C2	10μF 16V	C4–C7	10μF 16V (4 off)

All tantalum

Potentiometers

VR1 100k Ω carbon preset
VR2 10k Ω miniature moulded carbon

Integrated Circuits

IC1 SG3402N
IC2 741C

Miscellaneous

JK1, JK2 3·5mm miniature jack sockets (2 off), SK1 2mm miniature socket, Veroboard as required

ZN414 £1.25 POST FREE

The I.C. Radio in a TO18 can. Supplied complete with data sheet No. 10 which contains specification, circuit and details and prices of components such as ferrite rods, compression trimmers etc.

I.C. Sockets

Dual-in-line or Zig-Zag (Quil), 14 and 16 pin
Our Price 1p per pin

Slider Pots

Single	Dual	log
10K	10 + 10K	or
25K	25 + 25K	lin
50K	50 + 50K	
100K	100 + 100K	Knobs
30p	**50p**	10p.

NEW LISTS

LOUDSPEAKERS	No. 4
COILS AND INDUCTORS	No. 5
TRANSFORMERS	No. 6

(postage 5p)

Diodes & Rectifiers

AA119	9p	BA156	15p	BY176	£1·50
AA120	9p	BA243	56p	BY182	£1·50
AA129	9p	OA47	10p	BY250	23p
BA102	25p	OA79	9p	IN4001	6p
BA115	17p	OA90	7p	IN4002	7p
BA130	10p	OA91	7p	IN4003	8p
BA145	20p	OA200	10p	IN4004	8p
BA148	20p	BY100	15p	IN4005	10p
BA154	13p	BY126	15p	IN4006	12p
BA155	14p	BY127	15p	IN4007	15p

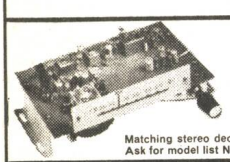

FM TUNER chassis fully transistorised 9 volt operation. OUR PRICE **£6·25**
Matching stereo decoder **£4·97**
Ask for model list No. 11.

VDR's & Thermistors

A15B	75p	GL23	£1·00	VA1005	15p
CZ1	15p	R53	£1·32	VA1026	13p
CZ4	13p	R54	£1·46	VA1033	13p
CZ13A	13p			VA1040	10p
E298 ED/A258	10p			VA1053	10p
E298 ZZ/06	10p			VA1055S	10p
GL16	£1			VA1034	10p

Resistors

¼ watt 5% Carbon Film – low noise Hi-Stabs
All E24 values **1p** each plus p. & p. 7p for up to 50 Resistors and a further 2p for each additional 50. Deduct **33⅓%** for 100 of one type or **25%** for mixed orders over £1 in value.

1 W	10% Carbon Composition	3p each
2 W	10% Carbon Composition	6p each
2½ W	5% Wire wound	9p each
5 W	Wire wound	9p each
10 W	Wire wound	10p each

plus p. & p. 7p for up to 25 resistors plus 1p for each additional 25.

3 Watt Audio Amplifier
Our Price inc. handbook **£2·49**

10+ less 15%
25+ less 25%
100+ less 33⅓%

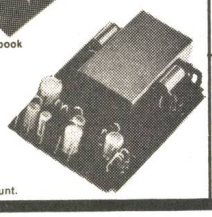

5 Watt Audio Amplifier
Our Price **£3·99**
Less quantity discount.

Potentiometers

5KΩ	50KΩ	500KΩ
10KΩ	100KΩ	1MΩ
25KΩ	250KΩ	2MΩ

log or lin less switch (& 1KΩ lin)	12p
log or lin with switch	24p
dual less switch	40p
dual with switch 10K, 100K & 1M log only	52p
10K log · 10K antilog less switch	40p

Eliminators

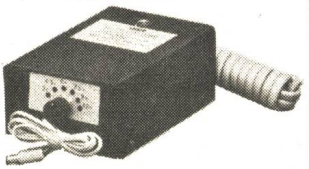

6 volt @ 50mA	£1.50
9 volt @ 50mA	£1.50
6 + 6 volt, 50mA	£2.50
9 + 9 volt, 50mA	£2.50
7½ volt for cassette recorders	£2.00
6, 7½ or 9 volt	£3.00
3, 4½, 6, 7½, 9, 12 @ 500mA (illus.)	£3.99

Car Battery Converter **fully stabilised** to provide 6, 7½ or 9 volts **£4.99**
(p. & p. **15p** on all types)

Presets

Vertical or Horizontal

0·1 watt 5p		0·25 watt 7p		
100	1K Ω	10K Ω	100K Ω	1M Ω
250	2·5K Ω	25K Ω	250K Ω	2·5M Ω
500	5K Ω	50K Ω	500K Ω	5M Ω

Capacitors

dise ceramic		low voltage	
·01μF 18v	5p	0·1μF 30v	5p
·022μF 18v	5p	0·22μF 6v	5p
·047μF 12v	5p	0·47μF 3v	5p
ceramic plate		**30V**	
1000pf	10p	4700pf	10p
2200pf	10p	10,000pf	10p

Ceramic – plate		63V (C333)	
1·8pf	8·2pf	33pf	120pf
2·2pf	10pf	39pf	150pf
3·3pf	12pf	47pf	180pf
3·9pf	15pf	56pf	220pf
4·7pf	18pf	68pf	270pf
5·6pf	22pf	82pf	330pf
6·8pf	27pf	100pf	

all 5p. each

mylar film			100V		
1000pf	2p	·01μF	3p	·068μF	4p
2000pf	2p	·02μF	3p	·1μF	4p
5000pf	2p	·04μF	3p	·2μF	5p
		·05μF	3p		

polystyrene **160V**
10pf to 10,000pf in multiples of 10, 15, 22, 33, 47 & 68. **3p each**

metallised polyester		250V (C280)			
·01μF	3p	·068μF	3½p	·47μF	8p
·015μF	3p	·1μF	4p	·68μF	11p
·022μF	3p	·15μF	4p	1μF	13p
·033μF	3p	·22μF	5p	1·5μF	20p
·047μF	3p	·33μF	6½p	2·2μF	24p

metallised polyester		400V (C281)			
·01μF	4½p	·047μF	6p	·22μF	10p
·015μF	4½p	·068μF	6p	·33μF	14p
·022μF	4½p	·1μF	7p	·47μF	15p
·033μF	5½p	·15μF	8p		

silvered mica 1% (>50pf) 500V

2·2pf–820pf	7p	4·7nF–5600pf	19p
1nF–2·2nf	9p	6800pf–·01μF	29p
2·7nF–3·6nF	16p		

mixed dielectric		600V			
·01μF	7p	·047μF	7p	·22μF	16p
·022μF	7p	·068μF	8p	·47μF	24p
·033μF	7p	·1μF	8p	1μF	33p

mixed dielectric		1000V			
1000pf	6p	6800pf	9p	·1μF	12p
2200pf	6p	·01μF	9p	·22μF	22p
3300pf	6p	·022μF	9p	·47μF	30p
4700pf	6p	·047μF	12p		

Ceramic 12KV.d.c.		8KV.d.c.		HI-K 750V.	
10pf	9p	200pf	9p	1000pf	5p
15pf	9p	220pf	9p	1500pf	5p
22pf	9p	250pf	9p	2000pf	5p
68pf	9p	270pf	9p	3000pf	5p
82pf	9p	300pf	9p	5000pf	5p
100pf	9p	750V DISC		10,000pf	5p
120pf	9p	470pf	5p	feed-through	
140pf	9p	1000pf	5p		
150pf	9p	5000pf	5p		
180pf	9p	10,000pf	5p	1000pf	5p

CHROMASONIC electronics

Please add 10% V.A.T. to your total order

MAIL ORDERS: Where no p. & p. charge is shown, a minimum of 7p applies, p. & p. on overseas orders is charged at cost.
ADDRESS TO: **M. O. Dept.**
56, Fortis Green Road, London, N10 3HN.
Telephone 01-883 3705

Heat Sinks

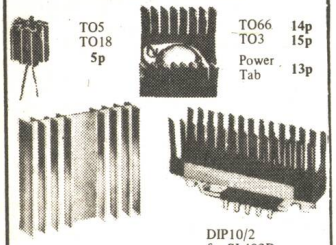

TO5 TO18 **5p**
TO66 TO3 **14p 15p**
Power Tab **13p**
10D **50p**
DIP10/2 for SL403D **15p**

Veroboard

	Copperclad 0.1"	Copperclad 0.15"	Plain 0.15"
2½" x 1"	6p	6p	–
2½" x 3¾"	20p	16p (9)	10p
2½" x 5"	24p	21p (7)	12p
3¾" x 3¾"	24p	21p (8)	–
3¾" x 5"	27p	27p (10)	17p
17" x 2½"	67p	50p	37p
17" x 3¾"	90p	70p	52p
17" x 5"	–	–	75p

Spot-face Cutter	36p
Pin Insertion Tool	47p
Terminal Pins	18p per pack of 36

NEW LISTS

BOXES, CHASSIS, etc.	No. 7
TRANSISTORS, I.C.'s, etc.	(soon)

(postage 5p)

Aluminium Boxes

Including baseplate and screws

No.	L.	W.	D.	Price	p. & p.
(7)	2¾"	x 5¼"	x 1½"	35p	8p
(8)	4"	x 4"	x 1½"	35p	8p
(9)	4"	x 2¾"	x 1½"	35p	8p
(10)	4"	x 5¼"	x 1½"	40p	8p
11	4"	x 2½"	x 2"	35p	8p
12	3"	x 2"	x 1"	32p	9p
13	6"	x 4"	x 2"	50p	10p
14	7"	x 5"	x 2½"	58p	12p
15	8"	x 6"	x 3"	75p	18p
16	10"	x 7"	x 3"	85p	20p

Transistors & Integrated Circuits

AC107	25p	BC147	10p	BF196	15p	OC81	19p	2N1304	22p	2N5172	15p
AC126	17p	BC148	10p	BF197	15p	OC140	20p	2N1711	25p	BZY88 ZENERS SERIES	10p ea.
AC127	15p	BC149	10p	BF272	53p	OC170	23p	2N1893	30p		
AC128	15p	BC157	12p	BFY50	24p	OC171	30p	2N2926 all	10p	LO05TI	£1.50
AC176	15p	BC158	10p	BFY51	21p	ZTX107	15p	2N3053	23p	LO36TI	£1.50
AC187	25p	BC159	12p	BRY39	36p	ZTX108	12p	2N3054	50p	LO37TI	£1.50
AC187K	25p	BC169	15p	BSX21	26p	ZTX109	15p	2N3055	49p	MC1303L	£1.75
AC188	25p	BC268	15p	BSY95A	14p	ZTX300	12p	2N3702	12p	MC1330	80p
AC188K	25p	BD115	67p	BU105/02	£1.75	ZTX301	15p	2N3703	12p	MC1350	75p
ACY20	20p	BD131	70p	MJE340	67p	ZTX302	20p	2N3704	10p	MC1351	£1.00
AD140	40p	BD132	70p	MPF192	40p	ZTX303	20p	2N3705	10p	MC1352	£1.00
AD149	40p	BD131/2M.P.	149p	MPF103	37p	ZTX304	25p	2N3706	10p	MFC4000B	49p
AD161 AD162	60p	BF160	21p	MPF104	37p	ZTX341	20p	2N3707	15p	MFC4010A	55p
AF114	18p	BF167	20p	MPF105	40p	ZTX500	15p	2N3708	12p	LM380	£1.45
AF115	18p	BF173	20p	MPF106	45p	ZTX501	15p	2N3709	12p	SL403D	£1.50
AF116	18p	BF180	25p	OC28	40p	ZTX502	20p	2N3710	12p	TAD100	£1.50
AF117	18p	BF181	30p	OC35	40p	ZTX503	17p	2N3711	12p	FILTER LP1175	£1.50
AF139	28p	BF184	25p	OC44	15p	ZTX504	50p	2N3819	35p		
BC107	10p	BF185	25p	OC45	15p	ZTX531	25p	2N3903	15p	µA709C	34p
BC108	10p	BF194	15p	OC71	11p	2N697	18p	2N3904	17p	µA710	45p
BC109	10p	BF195	15p	OC72	17p	2N706	12p	2N3905	21p	µA723C	95p
				OC76	15p	2N708	15p	2N3906	12p	µA741C	47p

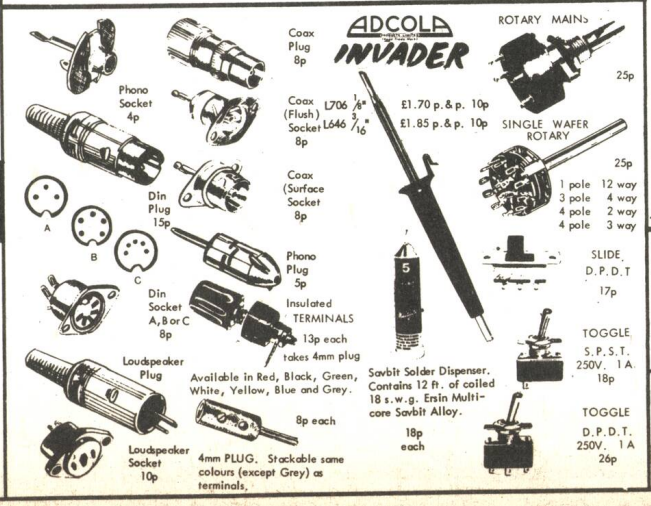

Mullard & Siemens Electrolytics

CAP µF	VOLTAGE 4	6.3	10	16	25	40	63
1	—	—	—	—	—	—	6p
1·5	—	—	—	—	—	—	6p
2·2	—	—	—	—	—	—	6p
3·3	—	—	—	—	—	—	6p
4·7	—	—	—	—	—	—	6p
6·8	—	—	—	—	—	6p	6p
10	—	—	—	—	6p	—	6p
15	—	—	—	6p	—	6p	6p
22	—	—	6p	—	6p	—	6p
33	—	6p	—	6p	—	6p	—
47	6p	—	6p	—	6p	6p	6p
68	—	6p	—	6p	—	6p	10p
100	6p	—	6p	—	6p	6p	12p
150	—	6p	—	6p	6p	10p	12p
220	6p	—	6p	6p	10p	12p	18p
330	6p	—	6p	10p	—	—	21p
470	—	6p	10p	—	12p	18p	40p
680	—	10p	—	12p	18p	21p	—
1000	10p	—	12p	18p	21p	40p	60p
1500	—	12p	18p	21p	—	—	—
2200	—	18p	21p	40p	45p	55p	93p
3300	—	21p	—	—	—	—	—
4700	21p	—	—	60p	75p	93p	—

CAP µF	VOLTAGE 16	25	40	64
500			33p	40p
1250			50p	—
1600			—	75p
2000		40p	50p	—
2500		—	—	93p
3200		50p	—	—
4000			75p	93p
6400		75p	93p	—

Quantity Prices on application.

Hi-Volt Electrolytics

1; 2; 4; 8µF 450V	14p	32µF 450V	20p
16µF 450V	15p	50µF 350V	20p
8+8µF; 450 V.W	18p	32+32µF; 350 V.W	25p
8+16µF; 450 V.W	20p	32+32µF; 450 V.W	43p
16+16µF; 450 V.W	25p	50+50µF; 350 V.W	35p

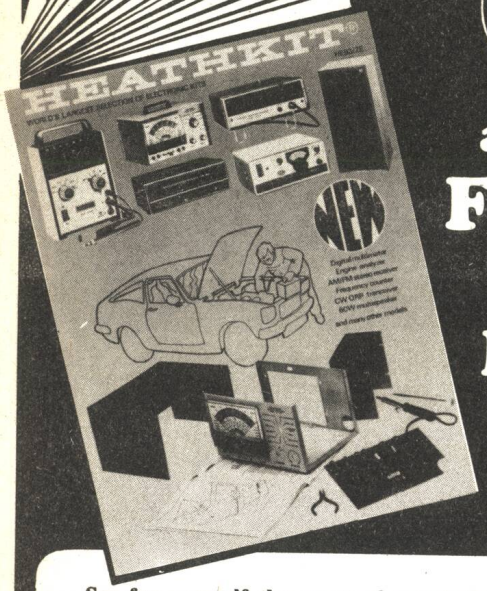

NEW and it's FREE ~The Book of kits

See for yourself the range of wonderful new kits that Heath have presented in the latest catalogue. We now offer something for everyone, including stereo hi-fi equipment, radios, intercoms, calculators, automotive testers, shortwave and amateur radio, testers and instruments for technicians and hobbyists . . . all at money-saving prices. And payment is so easy—choose cash or our low deposit terms (starting at £2 per month for up to £40 credit).

You can build a Heathkit model using only a soldering iron and a few simple hand tools. Foolproof assembly is guaranteed using the step-by-step construction manual included with every kit.

Add to this a technical consultant service both before and after purchase and you will see why kit building the Heathkit way is so popular all over the world.

Send now for your free copy of the Heathkit electronic kit catalogue—and if your friend is likely to borrow it, fill his name and address in below and we'll send him a copy too !

☐ **Please send a FREE Heathkit Catalogue to my friend**

NAME _____

ADDRESS _____

_____

HEATH Schlumberger

HEATH (GLOUCESTER) LTD., DEPT. PE/08/73
BRISTOL ROAD, GLOUCESTER GL2 6EE

☐ **Please send me a FREE Heathkit Catalogue**

☐ **I want to know more about your Cash and Low Deposit Terms, without obligation.**

NAME _____

ADDRESS _____

_____

HEATH Schlumberger

HEATH (GLOUCESTER) LTD., DEPT. PE/08/73
BRISTOL ROAD, GLOUCESTER GL2 6EE

FIRST TIME EVER at **£42·50.** Solartron CD711S2 Double Beam Oscilloscope d.c.—9MHz; 3mV/cm; trigger delay; crystal calibrator; 4in flat faced tube. In good working condition. Carriage £1·50.

SOLARTRON CT 316 (D300 range). DC to 6 mcs. 3" tube. TB up to 0·75 micro secs per centimetre. Built in calibrator. Size 8½"×11"×20". Price **£22·50.** Carr. £1·25.

MARCONI VALVE VOLTMETER type TF 958(CT208) DC to 100 mcs. 5" mirror backed meter complete with probe, leads etc. **£12·50.** Carr. £1·25.

GRATICULES. 12cm × 14cm in High Quality plastic. **30p** each. P. & P. 5p.

MODERN TELEPHONES type 706. Two tone grey, **£3·75** each. The same but black, **£2·75** each. P. & P. 25p each.
Also **TOPAZ YELLOW £4·50** each. P. & P. 25p.

STANDARD GPO DIAL TELEPHONE (black) with internal bell, **87p** each. P. & P. 50p. Two for **£1·50.** P. & P. 75p. All telephones complete with bell and dial.

20Hz to 200kHz WB SINE AND **SQUARE GENERATOR.** Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use. 9V supply required. **£6·85** each. P. & P. 25p. (Not cased, not calibrated.)

WOBBULATOR. Sweeps 8 to 45MHz ready to use. 6·3V a.c. required. **£9** each. P. & P. 25p. (Not cased, not calibrated.)

CAPACITOR PACK. 50 Brand new components only **50p.** P. & P. 17p.

5 MOVING COIL METERS various. **£2.** P. & P. 37p.

POTS—10 different values. Brand new—**50p.** P. & P. 17p.

COMPONENT PACK consisting of 2·2 pole 2 amp push on/off switches; 4 pots, various, brand new; 250 resistors ¼ and ½ watt, many high stabs, etc. Fine value at **50p** per pack. P. & P. 17p.

P.C.B. PACKS S & D. Quantity 2sqft —no tiny pieces. **50p** plus P. & P. 20p.

FIBRE GLASS as above **£1** plus P. & P. 20p.

5 CRYSTALS 70 to 90kHz. Our choice, **50p.** P. & P. 15p.
Matched pairs, **50p** per pair. P. & P. 15p.

TRIMMER PACK. 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min. strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW, **25p** the lot. P. & P. 10p.

ELECTRONIC TIMER UNITS —wall or bench mounting—2 Hybrid timer boards may be removed leaving excellent 12V battery charger; d.c. Power supply, etc. Price only **£2·50** incl. carriage.

LIGHT EMITTING DIODES (Red) from Hewlett-Packard. Brand New **38p** each. Holder **1p** each. Information 5p.

PHOTOCELL equ. OCP71, **13p** each.

PHOTO-RESIST type Clare 703. Two for **50p.**

AMERICAN OSCILLOSCOPE type USM24. A 10 meg scope—all min. valves complete with circuit diagram. Mains input 115 volt 50 cycles therefore **£20.** With step-down transformer **£22·50.** Carr. £1·50.

MOTOR MIN. SYNCHRONOUS. Size 1⅞" × 2" × ⅜", 240V operation, 3·6 RPM, **25p** each. P & P 5p.

DELIVERED TO YOUR DOOR 1 cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY **£3·50.**

PLEASE ADD 10% V.A.T.

OPEN 9 a.m. to 7.30 p.m. ANY DAY

CHILTMEAD LTD

7/9 ARTHUR ROAD, READING, BERKS.
(rear Tech. College) **Tel.: Reading 582605/65916**

PRACTICAL ELECTRONICS "SCORPIO" ELECTRONIC IGNITION SYSTEM

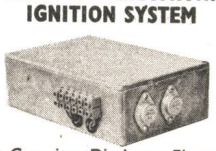

This Capacitor-Discharge Electronic Ignition system was described in the November and December issues of Practical Electronics. It is suitable for incorporating in any 12V ignition system in cars, boats, go-karts, etc., of either pos. or neg. earth and up to six cylinders. The original coil, plugs, points and contact-breaker capacitor fitted in the vehicle are used. No extra or special components are required.
Helps to promote easier starting (even under sub-zero conditions), improved acceleration, better high-speed performance, quicker engine warm-up and improved fuel economy. Eliminates excessive contact-breaker point burning and the need to adjust point and spark-plug gaps with precision.
Construction of the unit can easily be completed in an evening and installation should take no longer than half an hour. A complete complement of components is supplied with each kit together with ready-drilled roller-tinned professional quality fibre-glass printed-circuit board, custom-wound transformer and fully-machined die-cast case. All components are available separately. Case size 7¼in × 4¼in × 2in. approx.
Complete assembly and wiring manual **25p,** refundable on purchase of kit. Price: **£10·50** plus 50p P. & P.

PSYCHODELIC LIGHTING UNIT Mk. 3

This unit represents a natural progression from our phenomenally successful Mk. 1 and 2 Units. As before the drive voltage is derived directly from the amplifier output or across the speakers. The unit converts the audio frequency signals into a three-coloured light display; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source.
The unit is constructed on professional fibre-glass printed-circuit board material and uses latest full-wave triac circuitry. There is a master-level control, together with independent sensitivity controls for each channel. The original minimum ambient light level controls have been redesigned permitting their use as faders; allowing dimming from max. to zero at the turn of a knob. R.F.I. suppression is now incorporated as standard as well as provision for D.J. "Pulse-Flash" controls. The choice of two inputs enables operation from both high and low power amplifiers. Max. power 1·5kW per channel at 240V a.c.
Complete assembly built and tested. Size 9in × 7in × 3in. Price **£25** carr. paid.

PLEASE NOTE ALL THE ABOVE PRICES ARE SUBJECT TO V.A.T. ADJUSTMENT

DABAR ELECTRONIC PRODUCTS

98a Lichfield Street, Walsall, Staffs. WS1 1UZ

TELEPHONE: WALSALL 34365 **TELEGRAMS: DABELEC Walsall Staffs.**

Dalek voices are produced by modulating a modified speech waveform at about 15-20Hz. Speech, and certain types of music waveforms, can present a very peaky characteristic. The peaks are multiplied and added to in the Ring Modulator and thus, if the signal is remodulated several times, or if the initial frequency is high enough, the final output contains a large proportion of sound which bears a remarkable resemblance to white noise. The cure for this problem is to limit the dynamic range of the signal.

Although exact details for such a procedure lie outside the scope of this series a passable method is to feed the offending signal to one of the input amplifiers and, observing the output on the oscilloscope, adjust the gain of the amplifier so that a large proportion of the peaks are suitably clipped. If insufficient gain is available to allow an adequate degree of clipping the input amplifiers may be cascaded. The achievement of clipping means, of course, that the amplifier output signals are swinging between the positive and negative saturation levels and it will be necessary to attenuate the signal quite considerably. Fig. 7.5 shows a simple resistive attenuator which will give a signal of about 500mV from a 28V source.

CONSTRUCTION

Construction of the Ring Modulator is quite straightforward and the only critical requirement lies with the observation of polarity of the tantalum capacitors. Reversal of any of the capacitors will result in noisy operation and, in the case of the output capacitor, no operation at all. Tantalum capacitors have been specified in order to conserve space and there is no reason why 10V electrolytics should not be used with an alternative layout.

SETTING UP

Setting up the Ring Modulator consists only of providing a modulation balance. Set VR1 to its mid position and apply a common sine wave signal to both inputs. The output of the ring modulator will be a sine wave which is twice the frequency of the applied signal. If the modulation is out of balance alternate peaks of the output signal will be at different amplitudes. VR1 should be adjusted to bring the peaks into line at which point the modulation is balanced.

It is a wise precaution to repeat this measurement from time to time to adjust for settling down changes in the circuit.

THE PEAK LEVEL METER

In the prototype Synthesiser the meter circuit was based on a precision rectifier built around a pair of operational amplifiers arranged in such a way as to eliminate the effect of the diode forward voltage drop. Although the circuit proved to be very responsive it was found, in practice, to present a number of disadvantages. In the case of a.c. signals the meter would read only the r.m.s. value and although it was possible to determine the actual peak-to-peak value by application of a form factor for known wave shapes the determination of peak-to-peak values for complex waveforms proved to be a very hit and miss affair.

In a similar manner, when endeavouring to set up reasonably accurate programming voltage levels, the rapid response of the meter frequently made it difficult to establish the peak value with any certainty.

Fig. 7.7. Circuit diagram of Peak Level Meter

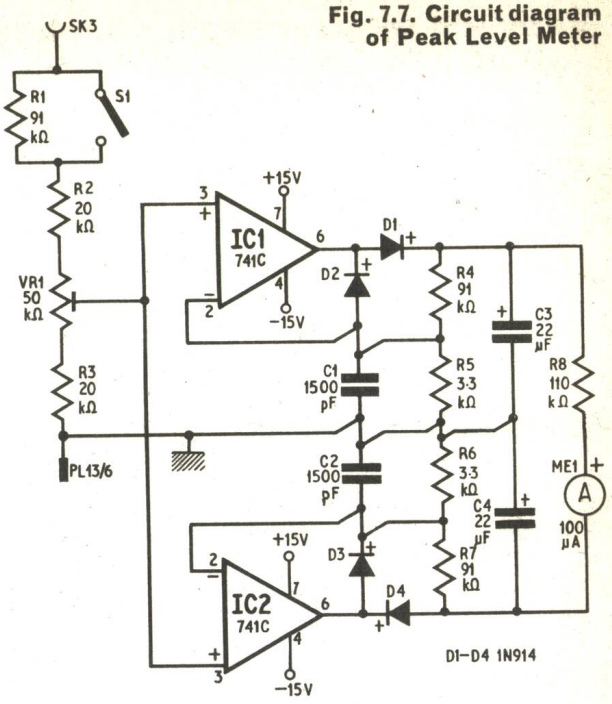

In consequence it was decided to redesign the meter circuit to provide a peak reading facility which would be independent of waveform configuration and which would have a reasonably long decay time to ease the establishment of transient level readings. The final circuit is shown in Fig. 7.7. IC1 and its associated circuitry is used to read the positive going peaks while IC2 deals with the negative side of the signal. The operation of the circuit is as follows.

CIRCUIT OPERATION

The input sensitivity of the circuit at the i.c. is about 200mV for full scale deflection of the meter. A positive going peak of this value appearing at the input of IC1 will swing the output positive to a level determined by the values of R4 and R5, about 6·2V with the values shown, and capacitor C3 will charge at a rate determined essentially by the effective current output of the i.c. The charging time for C3 is thus rather less than 2mS.

If, after the capacitor is charged, the 200mV peak is replaced by a lower amplitude peak the tendency would be for the i.c. to swing hard negative due to the effect of the positive voltage from the capacitor appearing at the inverting input via R4. This tendency is prevented by D2 which limits the negative excursion of the output to about 700mV.

Capacitor C3 discharges through R4 + R5 in parallel with R8 + R (meter) and with the values shown takes about 1 second. C1 serves to decouple a.c. from the feedback loop and thus effectively extends the accurate range of the meter to about 15kHz.

The negative reading side of the circuit around IC2 operates in the same way. The circuit is adjusted to give full scale deflection with inputs of 1·0V and 0·5V by means of the attenuator R1, 2, 3 and VR1.

In using the meter it should be borne in mind that the peak values recorded represent only half the total peak to peak value of the signal being measured

and this applies whether the signal is symmetrical or assymmetrical about zero. When measuring low frequency programming signals of greater than 1Hz the minimum reading of the meter between peaks does not represent the lowest level of programming signal.

This particular meter circuit can be used to measure the peak level of single transients of not less than 2mS duration.

ADVANTAGES

In tape recording the peak level meter scores heavily over the more conventionally employed v.u. meter. This latter meter will record what is essentially the mean value of signal presented to the recording amplifier and if, as is generally the practice, the mean level is kept to about −3dB transient peaks are likely to be clipped or otherwise distorted. The use of a peak level meter, on the other hand, enables the peaks to be kept within the limits imposed by the recording amplifier and thus enhances the overall quality of the recording.

THE REVERBERATION AMPLIFIER

Reverberation, or re-echo, in varying degrees is a characteristic observed in the majority of large halls, public buildings, cathedrals and so on. In a properly designed and proportioned hall the inherent reverberation characteristic can provide a high degree of enhancement to the sounds occurring therein.

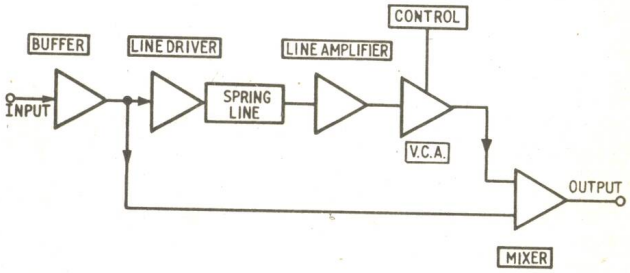

Fig. 7.8. Block diagram of Reverberation Amplifier

COMPONENTS . . .

REVERBERATION AMPLIFIER

Resistors

R1	10k Ω	R15	3·9kΩ
R2	270k Ω	R16	110k Ω
R3	39k Ω	R17	13k Ω
R4–R5	10k Ω	R18	13k Ω
R6	47k Ω	R19	0·5 Ω } 3W wire-wound
R7	10k Ω	R20	0·5 Ω }
R8	6·8k Ω	R21	56 Ω }
R9	390 Ω	R22	10k Ω
R10	10k Ω	R23	10k Ω
R11	20k Ω	R24	120k Ω
R12	10k Ω	R25	10k Ω
R13	10k Ω	R26	See text
R14	10k Ω		

All 5% ½ watt carbon unless otherwise stated

Capacitors

C1, C2	0·1μF ceramic
C3	620pF silver mica
C4	4μF 15V elect.
C5	0·1μF ceramic
C6	0·1μF ceramic
C7, C8	10μF 16V tantalum
C9	0·003μF ceramic
C10	See text
C11, C12	100μF elect. 22V

Transistors and Diodes

TR1	2N2905	TR3	BC209C
TR2	2N2219	D1, D2	IN914

Potentiometers

VR1	5k Ω lin.
VR2a/b	10k Ω lin. (two ganged)
VR3	10k Ω lin.

Integrated Circuits

IC1, IC2	741C
IC3	MFC6040
IC4, IC5, IC6	741C

Miscellaneous

Spring line type HR42 (Henry's Radio), JK3, JK4 3·5mm jack sockets (2 off), SK2 2mm miniature socket

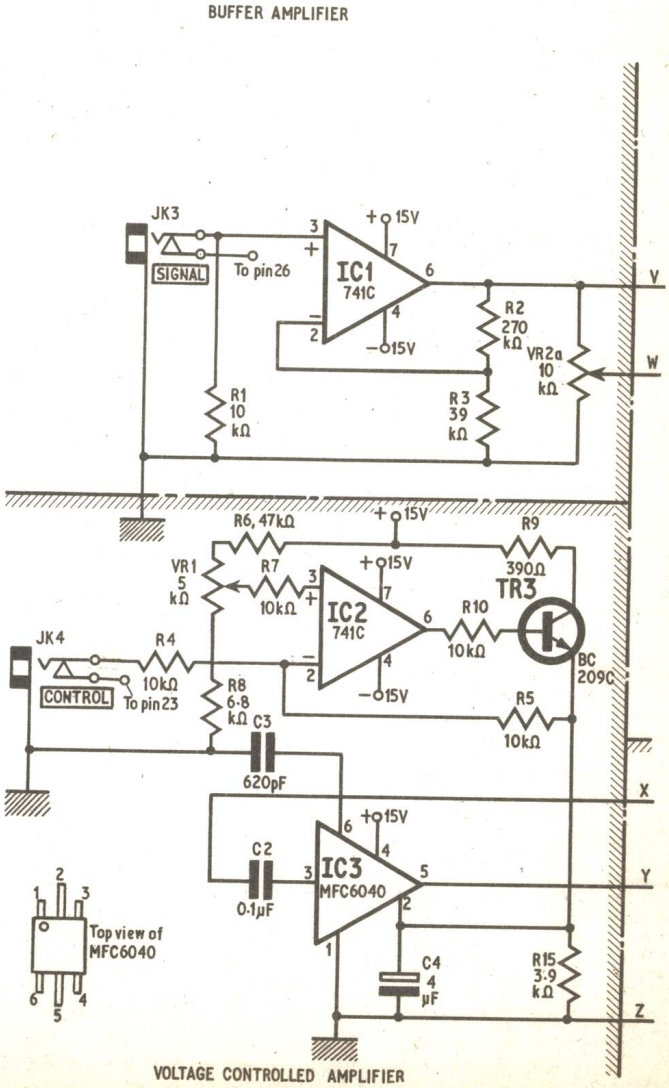

There are a number of ways in which a reverberation characteristic may be simulated and for the Synthesiser the spring line has been adopted. The spring line consists essentially of a coiled wire, usually steel, which is supported at each end in a compliant mounting. At the supported ends of the wire are fitted electro-magnetic transducers. The line driving transducer is excited by an electrical signal and the varying field produced causes mechanical wave motion to be set up in the spring line. When the wave motion reaches the far end of the line it sets up an electrical disturbance in the line output transducer which is, in turn, amplified and added to the original signal.

Part of the original mechanical wave motion is reflected back down the spring line where it serves to modify further on-coming waves.

Because a mechanical wave motion travels much more slowly than its electrical counterpart the signals received by the line output transducer are delayed in relation to their source, such delay being a function of the length of wire used in the spring line. Thus the mixing of the mechanically routed signal with the source signal constitutes the addition of an echo. However, since the wave motion, once initiated, travels back and forth along the line until its amplitude becomes negligible, multiple echoes are received and added to the original signal.

The spring provides a further useful feature having its origin in the fundamental resonance of the system. When the driving signal passes through the frequency at which the system resonates the output is characterised by a sudden increase in amplitude which can be as much as three times the value of the normal mean signal. Similarly when the input signal passes through any of the harmonics of the resonant frequency there is an increase in output signal amplitude, and this despite the fact that the useful range of the HR42 spring line, specified for this project, is limited at its upper end to about 4kHz. In the prototype unit quite high resonant peaks were occurring at up to 25kHz.

The combination of multiple echoes and varying amplitude imparts a very useful "singing" quality to an otherwise uninteresting sound.

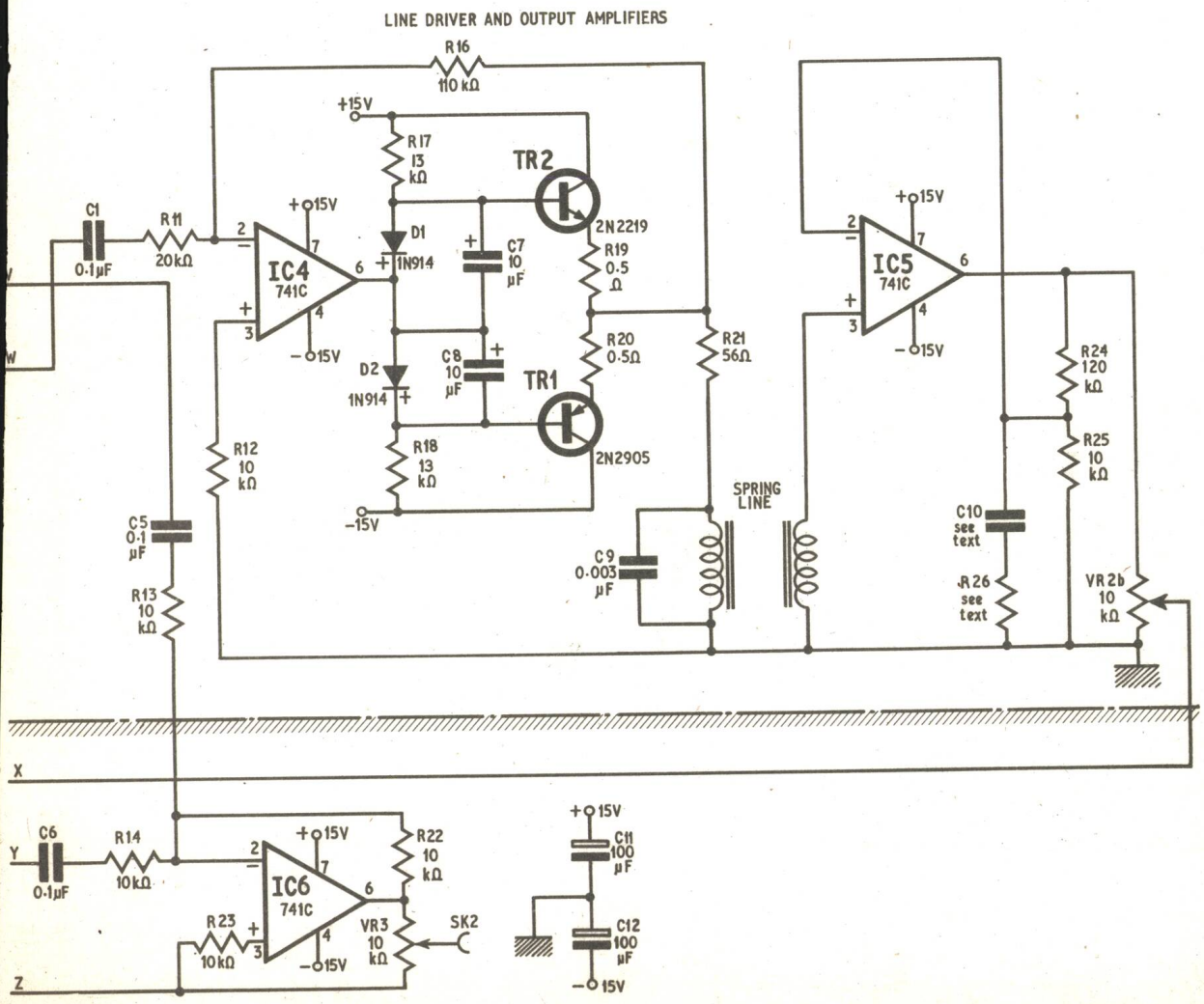

Fig. 7.9. Circuit diagram of Reverberation Amplifier

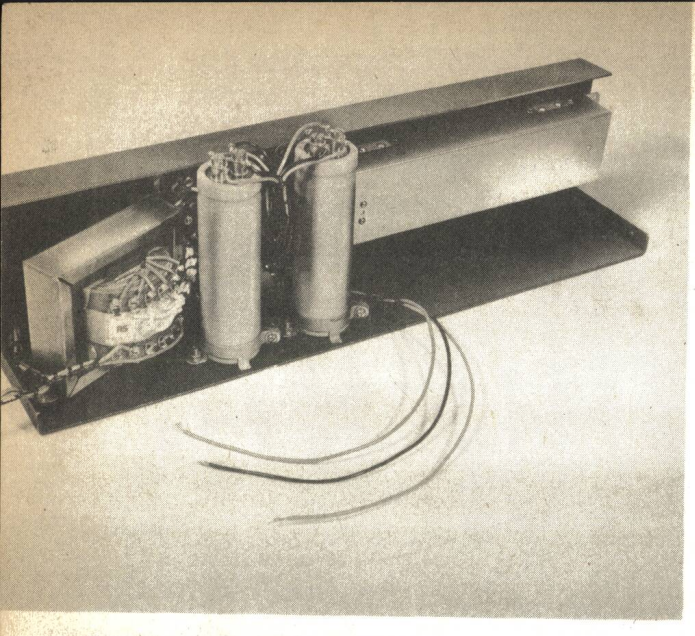

The spring line unit is attached to the p.s.u. sub-frame

DESIGN CONSIDERATIONS

In the prototype the line driving amplifier employed a single transistor operating in what was effectively Class A. The current consumption was thus quite high even in the quiescent state and small variations in the power supply rails gave rise to noise in the system which was apparent when the line was not being driven hard. For the modular version of the Synthesiser therefore the Reverberation Amplifier was redesigned to reduce current consumption, reduce hum and noise to negligible proportions and to enable a complete divorcing of the voltage controlled part of the system so that the amplifier may be built as a separate unit outside the Synthesiser project altogether.

A fortuitous advantage of the re-design provides sufficient power capability to drive two HR42 or one HR42 and one HR162 spring lines in series. It is also theoretically possible to drive up to four of the above spring lines in any combination although this latter method has not been tested.

The advantage in using more than one spring line in the system lies in the fact that it is rare for two units to have identical resonances and delays and thus two or more units can only improve the overall reverberation characteristic.

CIRCUIT ACTION

The Reverberation Amplifier is shown in block form in Fig. 7.8 and the circuit diagram in Fig. 7.9. The input signal is led to a buffer stage, which has a gain of about six, and the output is divided to drive the line amplifier and output mixer. The line driving amplifier consists of a pre-amplifier built around a 741 and having a gain of about five which, in turn, provides drive to a complementary pair of output transistors having a current gain of about a hundred and arranged in what may be described as a modified form of Class B. The output from this latter stage provides drive direct to the spring line through a current limiting resistor.

The output from the spring line is amplified by another 741 having a gain of about nine and then led to the input of the voltage controlled amplifier based on the Motorola MFC6040. This latter device has a maximum gain of 13dB and a maximum attenuation of about 77dB relative to the input signal which should not normally exceed 500mV r.m.s. The overall gain of the spring line route is thus arranged so that when the line is being driven hard at a non-resonant frequency, and with the v.c.a. at maximum gain, the output of the v.c.a. is equal to the output of the buffer stage and thus the mixer is receiving equal components of reverberated and non-reverberated signal.

The choice of component values for C10 and R26 may be arrived at by experiment on the basis of the measured response of individual spring lines. To limit the gain to 6dB a value of 2·5 kilohms for R26 will suffice.

The value of C10 is calculated on the basis of the frequency at which the 6dB gain is required. For a frequency of 15kHz the value of C10 is 1nF.

The v.c.a. is controlled by a separate 741 arranged in the differential mode. The non-inverting

Photograph of the assembled module

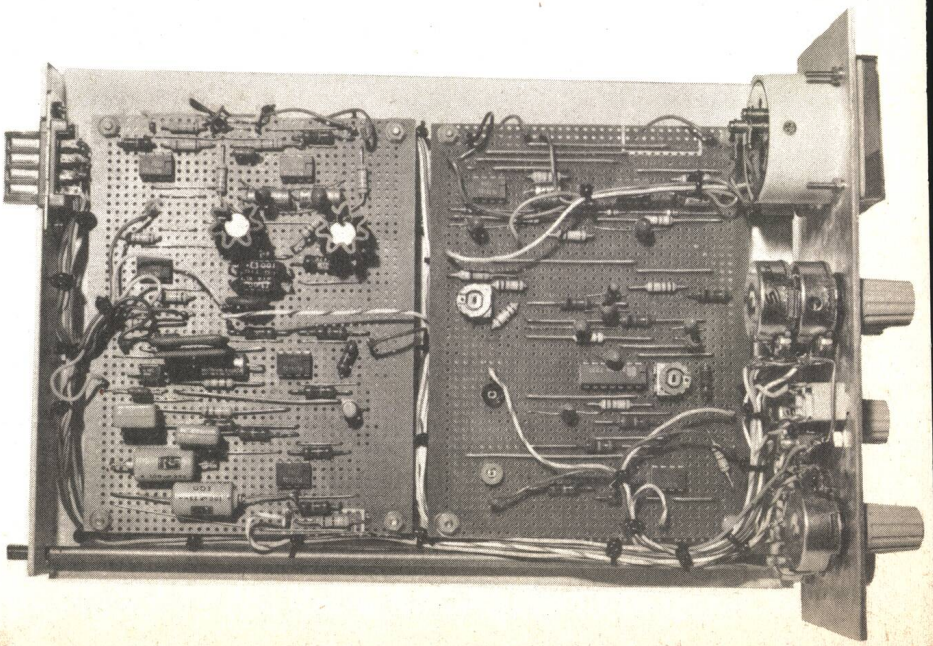

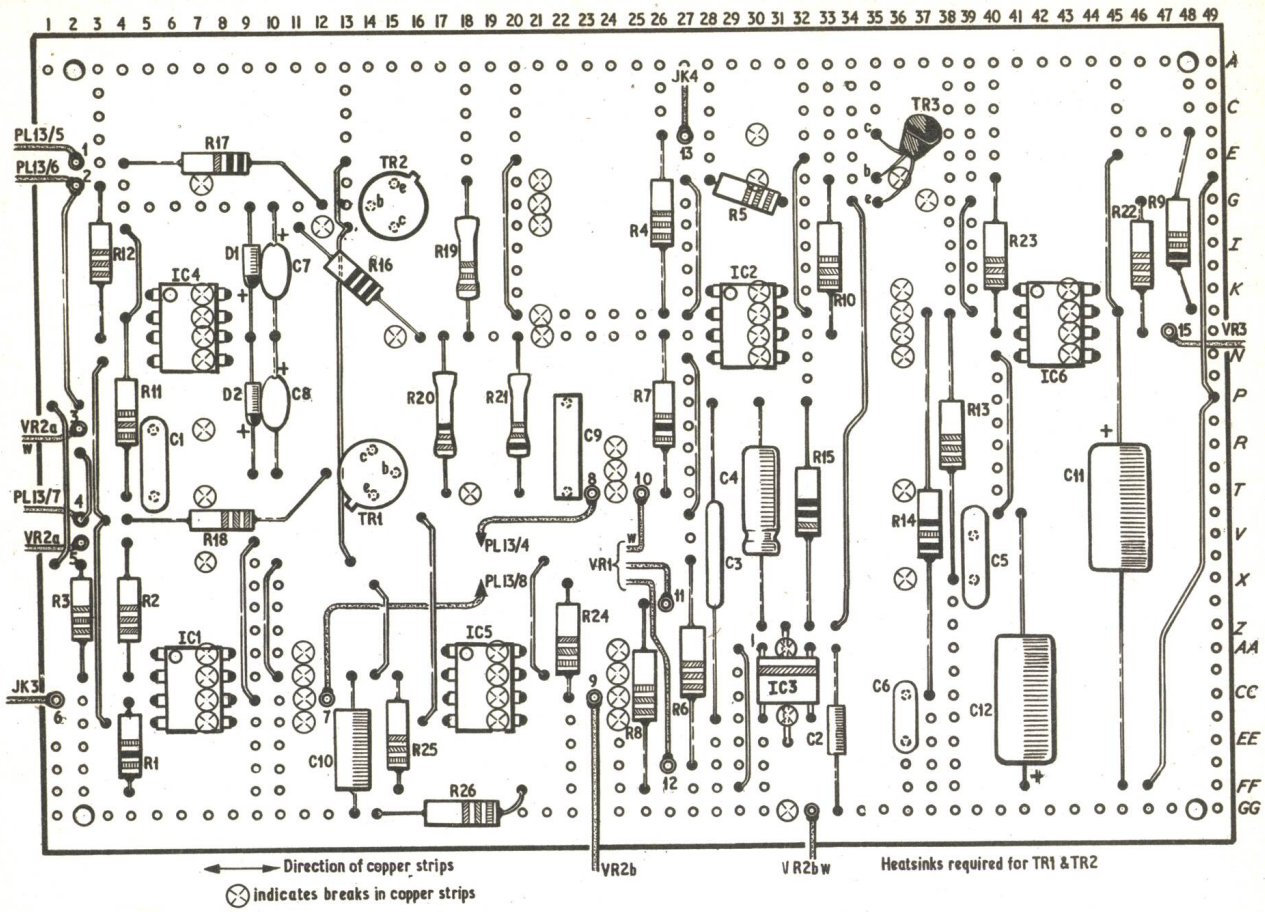

Fig. 7.10. Board assembly of Reverberation Amplifier

input is driven by a positive voltage derived from the divider R6, R8, and VR1. The high and low ends of VR1 are thus at 3·0V and 1·75V respectively. The inverting input of the 741 is driven by a control voltage which should have a swing of 2·5V maximum.

With VR1 at its minimum setting a control voltage swinging from zero to −2·5V will have the effect of attenuating the output of the MFC6040. With VR1 at its maximum setting a control voltage swinging from zero to +2·5V will have the effect of amplifying the output of the MFC6040 from −77dB to +13dB relative to its input signal. The inverting input of the 741 acting as control amplifier is prewired to a ramp generator which will, of course, provide the first mode of v.c.a. operation described due to its negative going output.

If external automatic control of reverberation is not required it is essential that a grounded jack plug be inserted into the control socket otherwise the output of the control amplifier will be insufficient to swing the MFC6040 through its full range.

The current sink at the control input of the MFC6040 is specified as being 2mA but on several

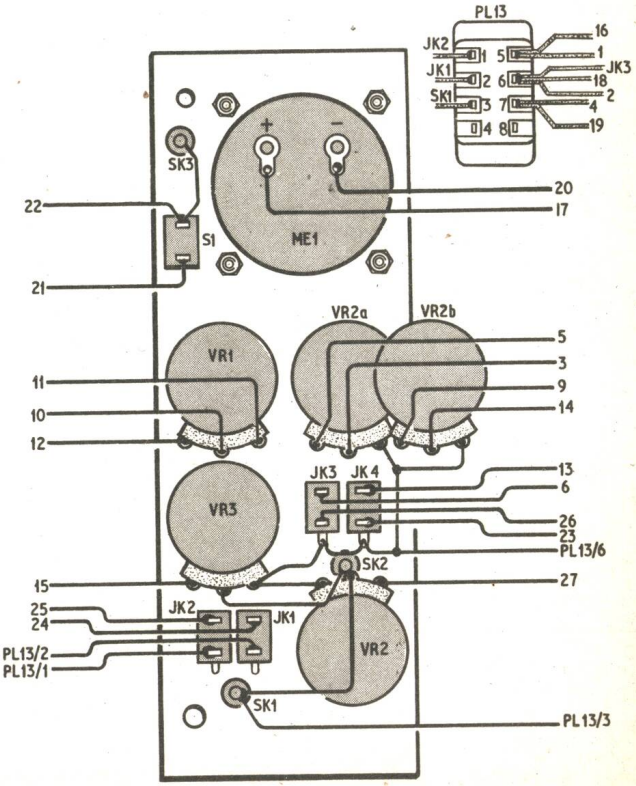

Fig. 7.11. Front Panel Wiring

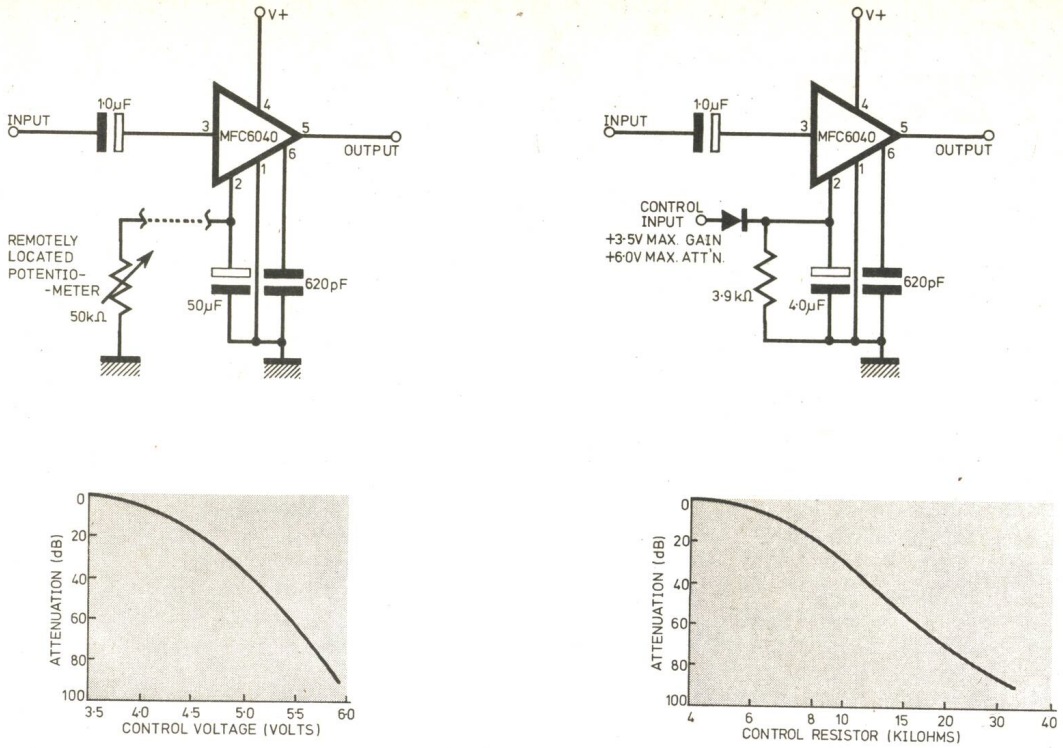

Fig.7.12. Two methods of providing external control using a potentiometer and voltage control input. The relevant response curves are located below each circuit. Here the 0dB reference equals a 13dB gain

tested in this mode of operation quite a wide variation in current sink was noted, the highest being 25mA. Consequently it is prudent to provide a series transistor on the output of the control amplifier, with overall feedback, in order that the 741 is not overloaded. The effect of overload will not necessarily damage the 741 but it could result in a reduction of the output voltage swing which would, in turn, affect the operation of the 6040.

OMITTING THE V.C.A.

For some possible applications the use of voltage control will not be required and, in these instances, the MFC6040 and associated control amplifier may be omitted from the circuit entirely. In these circumstances the gain of the line output amplifier, IC5, will have to be increased by a factor of 0·33 if equal reverberated and non-reverberated components are required at the mixer. The output of IC5 is, of course, led direct to C6 on the mixer in these latter circumstances.

CONSTRUCTION

Fig. 7.10 illustrates the recommended circuit board layout. Construction is quite straightforward and the only setting up required lies in checking the signal levels at the outputs of the buffer, line driver and line output amplifiers to ensure that equal signal components from both sources are presented at the mixer when the line is being driven hard at a suitable non-resonant frequency.

Adjustment of the gain of the line output amplifier may be necessary and is dependent upon the mechanical attenuation of the line which may differ unit to unit.

Overall construction of the module should generally follow the pattern previously described and the wiring of the components on the front panel and McMurdo plug are shown in Fig. 7.11.

In this module the McMurdo plug has insufficient ways to carry all the necessary signals and two extra leads are required to carry the control and audio signals to the reverberation amplifier. Reference to the block diagram in the first part of the series will show that the control signal is derived from RG2 while the audio signal is derived from the right channel of the output amplifiers yet to be described. Suitable leads should be run from the respective McMurdo sockets on these latter modules to a point immediately adjacent the left hand Vero endplate and secured to the connector mounting rail by a tie of lacing cord. From this point they should run along the end plate and be trimmed so that they protrude about three inches beyond the front face of the mainframe. Terminated in 1mm miniature plugs, they can be mated with their respective sockets on the Ring Modulator circuit board when the finished module is being inserted into the mainframe.

A fully comprehensive revision of all module interconnections will appear in part nine of the current series.

For the benefit of constructors who may wish to explore the possibilities of the MFC6040, Fig. 7.12 shows two possible methods of providing external control with the resistance attenuation curve and the control voltage attenuation curve of this very versatile device.

In Part 3, VRZ is 100Ω.

Next month: The Envelope Shaper will be described.

RECMF Components Show '73

DESPITE the recent adoption of the title International London Electronic Components Show, the RECMF of old seems still to be so called both on the official catalogue and by many of the exhibitors and visitors. However, this year it bears little resemblance to the Radio Show of old. Perhaps the word "subdued" would describe the feeling best.

In size the 1973 event was not much more than half its previous size, a factor with very mixed blessings. Obviously less to see but, to the footsore visitor, the possibility of seeing most of what was there without total self destruction. And, with less stands, the opportunity to see around, particularly from the gallery which of recent years has tended to become rather crowded.

The last three years have left their mark on the industry very clearly, as the drop in the number of exhibitors showed and it is a shame that some of the more famous semiconductor manufacturers chose not to attend. In fact the usual bustle, not just of visitors, but of new products looking for markets seemed to be muted almost out of existence.

Generally the atmosphere was one of trading rather than of displaying goods, many of the stands were totally bereft of components or equipment and, in this sense were a sad disappointment to the engineer looking for new "toys". However, the current world shortage situation in many component areas probably goes a long way to explaining this.

RADIO RECEIVER I.C.s

Perhaps one thing which stands out from the show is the advances being made in integrated circuits. It is almost possible to build anything using i.c. techniques these days and several of the manufacturers are trying to prove just that.

Fairchild displayed a set of interesting chips which can make up an a.m. or f.m. radio with stereo facilities. These included their 720 single chip a.m. receiver, the 753 f.m. gain block, the 758 phase-lock loop stereo decoder, the 3075 f.m. i.f. amplifier and limiter, detector and audio pre-amplifier, and the 706 audio power amplifier with a 5W capacity.

Both mono and stereo were demonstrated using either one or two of the power amplifier chips and considering the nature of the halls at Olympia, reception was very impressive.

To an extent of course, this type of display is really more of an application demonstration than a display of new concepts since the basics of such systems have been around for some time. However, it does illustrate the way in which we can expect developments to go as more and more roles are taken over by the chip.

FILTERS USING I.C.s

Take the case of Siliconix of Swansea, well known in the semiconductor market. They are investigating the ability of multi-amplifier chips to provide variable filters, of great value in audio control and generation applications.

They have already developed some prototype circuits using their L114 triple operational amplifier and have established that it is possible to obtain a tuning range from 0 to 10kHz, that high Qs up to 400 can be obtained, that high and low bandpass is simultaneously possible and that both gain and Q are easily programmable.

Indeed, they have even developed a digitally programmed filter using one of their own DG 507 chips to do the logic control.

With all this compression of componentry on to chips one almost wonders where the discrete component went. But one only has to look at any circuit board to see the still tremendous need for power rail droppers, couplers and so on.

MULTI-PURPOSE INSTRUMENT

On the more constructional side there were a number of interesting items. For the portable instrument constructor there was the Pakit kit multi-purpose instrument. An analogue display and movement is available to fit a moulded plastic case which has ample room for circuitry and components. Available from Elcometer Instruments Ltd., the Pakit can be bought complete with a rechargeable power supply, self-designed front panel, leather carrying case and printed circuit.

The basic unit with case will probably market for something under £20.

CASES AND PACKAGING

For the inveterate casemaker there was a display of coated aluminium panel material from Bakelite Xylonite Ltd., which provides both strong covering, attractive colours and, as an added bonus fairly high electrical insulation by virtue of the plastic coating material.

For the man who is always losing components on the bench there was an interesting adaption of the plastic packaging market. Dunlavin Converters have developed their Ducon Carripallet system for packaging delicate materials to the point where it can be used for other applications.

Thus the Carripallet is a multi-cavity foam plastic pad measuring 400 × 400 × 50mm and with 25 cells. Laid on its back, which is a cardboard support layer, it can be used as a multi-compartment tray. As the material is flexible foam plastic it will not damage delicate parts and indeed components can be stuck upright in it if required.

Normally items of this type are sold in large quantity only, but we understand that single sheets are available and will probably cost about £1 each.

Weller were at the show with their latest low voltage temperature-controlled soldering pencils (no longer irons we see), the W-MCP available with a variety of tip shapes.

PANEL METERS

On the meter front several so-called panel meters were on display including the Dinline 50, the first such product to come from the Avo stable. The name is based on the rectangular styling which follows the DIN (IEC 51) specification.

A digital panel meter is something that, only a short while ago, would have been regarded as an instrument rather than a component. By miniaturisation and recent price reductions in digital i.c.s, Analogic are able to offer a versatile 3-digit digital panel meter at only £25 in quantity. Designated the 2530, this unit can measure, display and transmit voltages and currents of either polarity. The 2530 has fully floating inputs just like any analogue meter so that measurements with respect to any arbitrary level in a circuit can be made.

A filament readout is used for good readability and low cost. This meter can be incorporated in many types of instrument giving a really competitive alternative to analogue measuring instruments.

West Hyde displayed their Contil digital panel meter card with three digit display in Atron tubes and costing less than £25.

Integrated Photomatrix showed their digital panel meter kit using a MOS LSI chip and l.e.d. display which is available for £36·75. Of course the IPL unit is considerably smaller than many other displays on show.

LARGE SCALE INTEGRATION

One of the fastest-growing areas of semiconductor technology must be the MOS large scale integration (LSI) field. All the major companies appear to be competing to see who can cram the most MOSTS into a single 24-pin package.

One of the latest contenders in this competition is the Motorola MCM6571L character general i.c. It contains a read only memory of 8,192 bits which can produce 128 different characters, including upper and lower case and Greek symbols, each character being formed by a matrix of seven horizontal and nine vertical dots. As well as the stored characters themselves there are 128 bits which are used to automatically control each character position so that the "tails" of letters such as p, q, and j come below the base line as in normal typewritten material.

Another piece of news in the MOS LSI field comes from General Instrument Microelectronics who announced that slashing price reductions have been made on their C500 calculator i.c. Its new price of £13·70 (1 off) represents an £18 drop from its previous value. G.I. hope that this new low price will encourage designers to regard the calculator i.c. as just another component for use in many types of instrument where arithmetic operations are to be carried out. For instance, they could be used in a weighing scales which automatically displays the price of the goods after the price per pound is typed in.

NEW LOW-PRICE FOR L.E.D. DISPLAYS

While MOS manufacturers are aiming at miniaturisation, the display device manufacturers are aiming at bigger and brighter components. One of the innovators of l.e.d. displays, Monsanto, announced new low prices for their displays.

Single l.e.d.s can now be bought for 5p in large quantities making it possible for manufacturers to use them in such applications as diagnostic lamps on printed circuit boards, panel lamps, and battery "low" indicators.

On the numeric display side the MAN5, a green seven-segment device is down to £3·99 from £9 (1 off) and the MAN64A, a 0·4in numeric display down to £4·27 from £7·85.

NEW TIMER INTEGRATED CIRCUIT

Another example of large scale integration, but this time combining digital and analogue functions was on show at the Elremco stand. Designated the LR171E, this i.c. has an enormous range of applications because of its inherent flexibility.

It uses a digital counter so that timing ranges of seconds, hours or even weeks can easily be obtained. A digital-to-analogue converter is used to give a current output which means that a cheap meter can be used to give an indication of time elapsed.

It has eight operational modes, delayed on, delay interval etc., and has three digital outputs which give indications at $\frac{1}{8}$, $\frac{1}{4}$ and $\frac{1}{2}$ of a preset time period.

The i.c. is TTL compatible and has integral output drivers for a triac or SCR. Price is £12 for one off.

RUSSIAN COMPONENTS

Many manufacturers are finding difficulty obtaining such ubiquitous components as resistors and capacitors and so it is not really surprising to see more and more imported components creeping into instruments such as calculators.

Z & I Aero Services are importers of Russian resistors and capacitors and supply both to industry and non-professional users. The components are cheap, clearly marked with their values (not colour coded) and readily obtainable.

NOVEL BREADBOARDING AID

A novel breadboarding system which has great potential in the amateur field was shown by Critchley Bros. Ltd. Manufactured by the German firm of Christel Wainwright, the system is called "Mini-Mounts." Each Mini-Mount is a small rigid board with a copper pattern on one side and adhesive on the other. Components are soldered onto the boards which are then positioned anywhere on a convenient baseboard (which could be copper-plated to give a good ground plane), and stuck in place.

This system has many advantages over other similar systems: no holes need be drilled; the adhesive holds the Mini-Mounts firmly in place yet they can be moved if the circuit requires; components and Mini-Mounts can be re-used if care is taken.

Mini-Mounts to take DIL i.c.s, and other such components are available so the system gives great scope to the designer.

NEW SHAPE FOR LAMINATIONS

Though by no means a spectacular breakthrough, the new design for transformer laminations by Kent Insulations shows how old and tested designs can be improved with a little ingenuity. Instead of the usual "E" shape the new type has a tapered centre arm so that excellent mechanical and magnetic contact is made when the two halves are fitted together.

MULTI-MEMORY MACHINE

On the Advance Electronics stand and in fact using the same case as the Advance calculators was a new accounting aid from Phytron. Called the Analysis 14 this calculator incorporates 13 accumulating memories each of which can be debited or credited at any time simply by selecting the required store with one of thirteen keys. Only credit and debit (i.e. addition and subtraction) are available, the manufacturers suggesting that this instrument is to complement, rather than replace, the normal desk calculator which can multiply and divide.

At £210 this calculator cannot really be termed inexpensive by modern standards and one wonders whether a machine without a print-out is really useful in accounting, where mistakes cost money.

CONCLUSIONS

One wonders why a star attraction like the actual *Apollo* capsule "Charlie Brown" which circled the moon four years ago, which was on show on the Livinstone Hire stand together with a piece of moonrock, received so little publicity. This could have attracted great crowds, was this what the organisers were afraid of?

At a time when electronics is developing so fast, the show was not up to expectations and one can only hope that the companies will stop hiding their lights under bushels and give us some really interesting shows in the future. ★

STARTING NEXT MONTH!

PRACTICAL ELECTRONICS Proudly Presents the

PE RONDO..

QUADRAPHONIC SOUND SYSTEM

- ☐ *4 x 20 watt (continuous in 8 ohms) high quality power amplifier*
- ☐ *High quality preamplifier and control unit with wide dynamic range*
- ☐ *A.M./F.M. receiver of advanced design*
- ☐ *CBS SQ quadraphonic decoder*

The PE RONDO is a total system incorporating the very latest technology and it will be described in full with all constructional details in a series of articles starting next month.

The receiver incorporates a varicap f.m. tuner with integrated circuit i.f. amplifier, quadrature detector and phase-locked-loop stereo decoder; and a unique i.c. phase-locked-loop synchrodyne a.m. medium-wave mono tuner.

Optional i.c. matrix decoders: CBS SQ quadraphonic decoder or CBS SQ logic-enhanced quadraphonic decoder. Additional decoders will be presented as further systems become viable.

Modular construction techniques give flexibility, whilst the use of state-of-the-art i.c. technology allows all electronics to be housed in one compact unit. The system is completed by four shelf-mounting speakers, construction of which will also be fully described in this series of articles.

Also: PHASING UNIT · PHOTOGRAPHIC THERMOMETER & EXPOSURE METER

PRACTICAL
ELECTRONICS

SEPTEMBER ISSUE ON SALE AUGUST 10, 1973

25 YEARS OF SEMICONDUCTORS

PART 2

By M. J. Rose (MULLARD LTD.)

POWER DEVICES, PHOTO DEVICES AND INTEGRATED CIRCUITS

THE first article described the types of transistor and small-signal diode available. This article considers power devices, photo devices using, or emitting light, and the most revolutionary semiconductor device of all—the integrated circuit.

POWER DIODES

The amount of power that can be handled by a semiconductor diode is limited by the junction temperature. Provided the heat dissipated within the device can be conducted away so that the maximum permissible junction temperature is not exceeded, the diode will operate satisfactorily. Therefore a power diode should have as large a junction area as possible, and a low thermal resistance to the case. The cooling area can be increased by mounting the diode on a suitably shaped heatsink.

Germanium power diodes were developed using these techniques, and could carry currents of approximately 10A and withstand peak inverse voltages of up to 600V. The introduction of silicon, however, led to their replacement during the 1960's by silicon diodes with junctions alloyed or diffused with aluminium.

AVALANCHE DIODES

As the reverse voltage across a junction diode is increased, a voltage is reached where avalanche breakdown occurs, marked by a sudden increase of current. Provided the diode can withstand the current at breakdown, it will recover when the reverse voltage is decreased below the breakdown value. Avalanche diodes are designed to withstand such breakdown currents, and so can be used safely in applications where voltage transients are likely to be encountered.

By the end of the 1960's other protection devices such as high-speed fuses had been developed so that semiconductor-diode rectifier systems were firmly established in such applications as battery chargers, electroplating and electrolysis processes, and electric furnace supplies. These semiconductor systems occupied less space than the existing systems, had a higher rectifier efficiency, and for the first time presented power engineers with a device that had no wear-out effects.

A high-voltage rectifier stack is shown in the photograph of Fig. 8. Diodes are mounted on heatsinks around a central fixing stud. Such stacks can be cooled by natural convection, or for higher currents by forced-air cooling or immersion in an oil bath.

Fig. 8 High-voltage rectifier stack operating at 12kV and 5A with natural convection cooling (length approximately 10in)

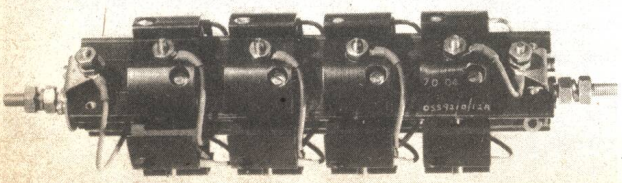

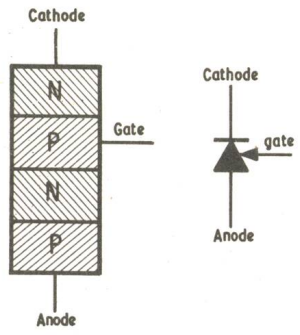

Fig. 9 Structure and circuit symbol of thyristor

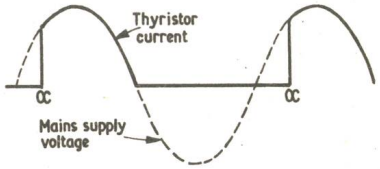

Fig. 10 Phase control using thyristor

THYRISTORS

The thyristor or controlled silicon rectifier was developed for power control in parallel with the silicon rectifier diode. The rectifier action of the thyristor allows a current to flow in one direction only, but in addition current can only flow when the thyristor has been triggered.

In form, the thyristor is a four-layer *pnpn* device, as shown in Fig. 9. The circuit symbol is also shown in this figure. If the anode is positive with respect to the cathode, and a positive voltage is applied to the gate, the thyristor conducts. Once conduction has been established, the gate voltage can be removed.

Therefore the thyristor can be triggered by a pulse provided the duration is sufficient to allow the current to be established. The thyristor is made non-conducting by reducing the current to below a holding value.

The method of power control with thyristors is shown by the waveforms in Fig. 10. By varying the trigger angle within the half-cycle (α), the amplitude of the current pulses passed by the thyristor, and hence the power delivered to the load, can be varied. This control technique is called phase control.

A second method of control is burst triggering, used for loads with a high thermal inertia such as furnaces. In this method, complete half-cycles of the mains supply are passed by the thyristor, the ratio of half-cycles passed to those blocked determining the power to the load.

TRIACS

Another device for power control similar to the thyristor is the triac or bidirectional thyristor. This device is equivalent to two thyristors connected in inverse-parallel with a common gate connection. The circuit symbol for a triac is shown in Fig. 11. A current will flow through the device when the gate is sufficiently positive or negative with respect to terminal mt1, the direction of current flow depending on the relative polarities of mt1 and mt2.

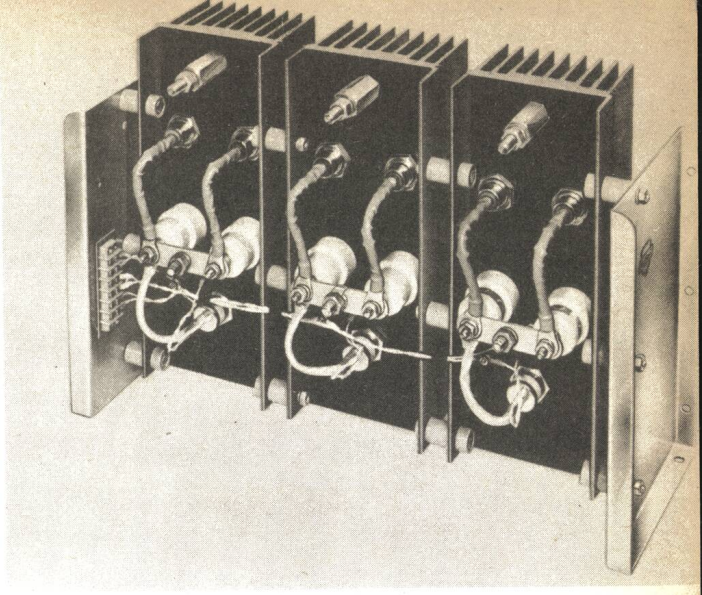

Fig. 12 Thyristor stack for operation on 440V three-phase mains to control 110A per phase

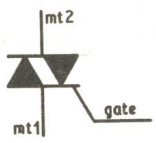

Fig. 11 Circuit symbol for triac

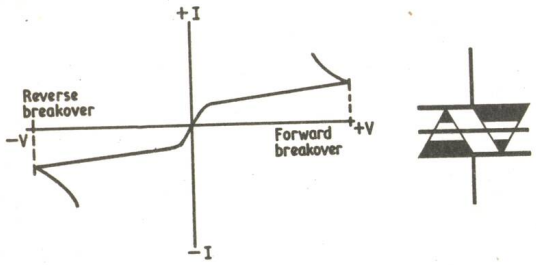

Fig. 13 Breakdown characteristic and circuit symbol for diac

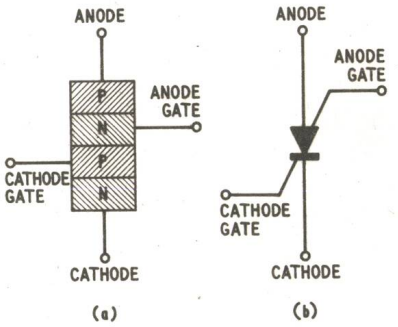

Fig. 14 Structure and circuit symbol for silicon controlled switch

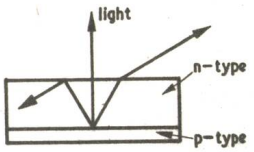

Fig. 15 Diagram showing construction of a typical light emitting diode

The currents that could be handled by thyristors, and the inverse voltages they could withstand, increased during the 1960's as the manufacturing techniques were improved. Present-day thyristors can handle currents up to 1000A and withstand inverse voltages of over 2kV. Protection devices have been developed as with rectifier diodes to ensure reliable operation under practical conditions.

A typical thyristor stack with thyristors connected in a bridge configuration for the control of power to a load is shown in Fig. 12. The thyristors are mounted on heatsinks.

THE DIAC

The diac, or bidirectional diode thyristor, is a useful trigger device for thyristors and triacs. It uses avalanche breakdown, but as the characteristic in Fig. 13 shows, the voltage decreases after breakdown so that the gate circuit is not overloaded on triggering.

SILICON CONTROLLED SWITCH

Another four-layer *pnpn* device is the silicon controlled switch or SCS. Unlike the thyristor and triac, both intermediate layers of the SCS are accessible making it a four-terminal device. The structure and circuit symbol are shown in Fig. 14.

The SCS (like the thyristor) has two stable states: conducting and non-conducting. The SCS can be used in two circuit configurations. In one, the load is connected in the anode gate circuit so that the SCS operates as a four-terminal device. In the other, the load is in the anode circuit and the anode gate is not connected. The SCS then acts as a low-power thyristor or three-terminal device.

PHOTOTRANSISTORS AND PHOTODIODES

Light falling on a junction in a semiconductor diode or transistor affects the current through the device. The energy of the light dislodges electrons and so increases the number of carriers available at the junction.

Constructive use of this effect is made in photodiodes and phototransistors where the change in current with light can be used in such applications as light meters and alarm systems.

Other semiconductor materials exhibit a change of resistance with light, and this effect is used in photoconductive cells (or light-dependent resistors). The choice of semiconductor material determines which part of the spectrum the device responds to, for example cadmium sulphide responds to visible light while lead sulphide is used for infrared detectors.

LIGHT EMITTING DIODES

Another type of photodevice is the electroluminescent or light-emitting diode (Fig. 15). This device is made from gallium arsenide or gallium arsenide phosphide, and when a sufficiently high current (a few milliamperes) is passed through, light is emitted. Such diodes can be used as indicator lights directly coupled into, for example, computing systems.

INTEGRATED CIRCUITS

Of all the semiconductor devices that followed the invention of the transistor, the most revolutionary both in reducing the size of equipment and improving reliability is the integrated circuit.

The problems of manufacturing different circuit elements on the same silicon chip were overcome so that integrated circuits that were both practicable and economic became available by the mid-1960's.

Today two types of integrated circuit (i.c.) are available, the bipolar and MOS, each with their advantages and disadvantages for particular applications.

BIPOLAR I.C.

The bipolar i.c., as the name implies, uses bipolar transistors manufactured by the planar process. Diodes are formed by a single diffusion, capacitors by using a reverse-biased diode junction, and resistors by a single diffusion like a stretched-out diode with connections at both ends. The main problem with the manufacture of bipolar i.c.s is isolation between components.

MOS INTEGRATED CIRCUITS

The transistor used in MOS i.c.s is a field-effect transistor, the MOSFET or MOST. Because MOS i.c.s are almost exclusively used in digital applications, an MOST can form the load for another MOST, the transistors are directly coupled, and the capacitances on which information is stored are formed by the gate capacitances of the MOSTs themselves. Thus only transistors and connections need to be formed on the chip.

One advantage of MOS i.c.s over the bipolar type already mentioned, is the fact that no isolating diffusion is needed on the chip. In addition, an MOST is smaller than the equivalent bipolar transistor. Both these reasons lead to a higher packing density being achieved with MOS i.c.s. On the other hand, bipolar i.c.s have a higher operating speed, and can drive higher current and capacitive loads which MOS i.c.s cannot do without interface circuits.

Thus the choice of MOS or bipolar i.c. may well depend on the requirements of the application rather than any clear-cut advantage of a particular type.

In general, it can be said that small scale integration (SSI) is rarely economical with MOS i.c.s so that gate packs and flip-flops will use bipolar i.c.s.

Large scale integration (LSI) for such devices as random-access memories (RAMs) and read-only memories (ROMs) will use MOS i.c.s. The choice for medium scale integration (MSI) will depend on the application.

COMPLEMENTARY MOS

A limitation on the use of MOS i.c.s occurs through the use of field-effect transistors. The current-carrying channel for the transistor is formed in the substrate, and so normally only *p*-channel or *n*-channel devices but not both can be formed on any one i.c.

To overcome this, a technique called complementary symmetry MOS or CMOS has been developed. Areas of *p*-material are diffused into an *n*-type substrate so that both *n*-channel and *p*-channel MOSTs can be formed.

More diffusions are required for CMOS than with normal MOS i.c.s, and a lower packing density results. On the other hand, there are considerable advantages for the user, particularly higher operating speeds and lower dissipation.

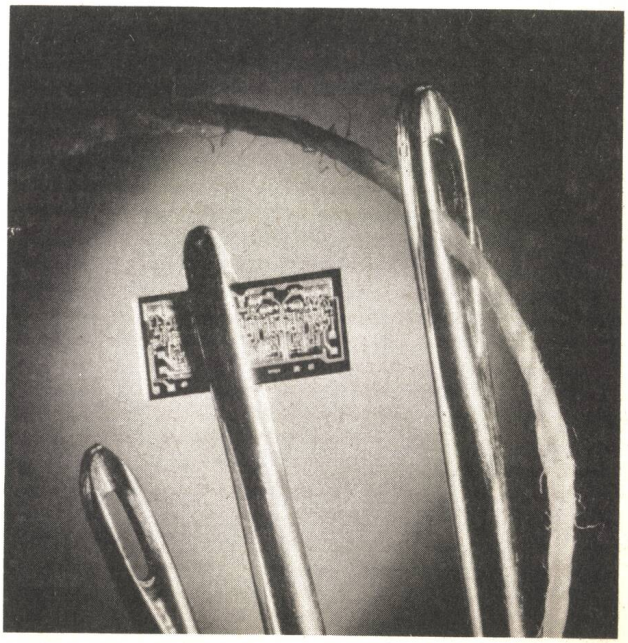

Fig. 16 Integrated circuit chip compared with ordinary sewing needle, the chip being 1·5 × 3mm

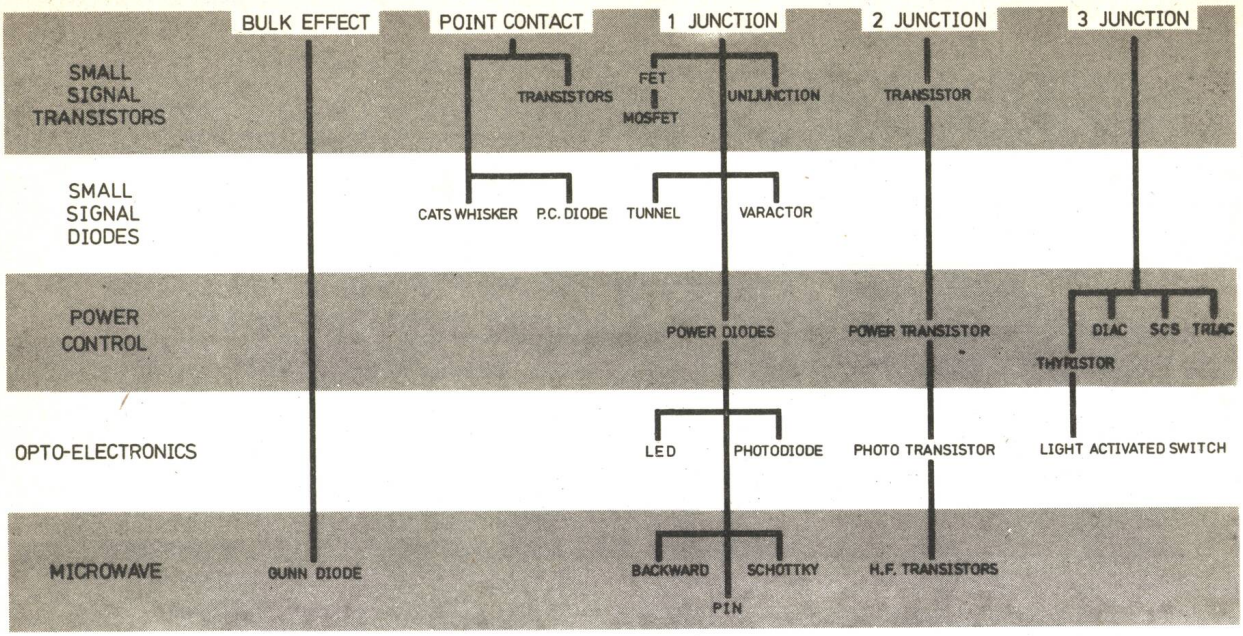

FAMILY TREE OF SEMICONDUCTOR DEVICES

LINEAR I.C.s

The i.c.s described above are digital circuits. Later in the 1960's linear i.c.s were developed. In terms of the number of devices contained, these i.c.s are more complex than the equivalent discrete stages they replace, although cheaper and with better performance. Today a wide range of linear i.c.s is available covering r.f. and i.f. amplifiers, operational amplifiers, TV signal-processing circuits and audio amplifiers with output powers up to several watts.

The reduction in size possible with an i.c. is impressive, typified by such photographs as that in Fig. 16 showing a silicon chip containing over 120 devices passing through the eye of an ordinary sewing needle.

COLLECTOR DIFFUSION ISOLATION

Another process which overcomes many of the disadvantages of conventional bipolar i.c.s has been developed by Ferranti from an American idea. Known as the collector diffusion isolation (CDI) process, it makes use of thin epitaxial layers but needs only five masking processes making it comparable to MOS technology in simplicity.

Fig. 17 shows the structure of a CDI transistor. The process uses a *p*-type substrate into which buried low resistivity *n*+ areas are diffused where each resistor, transistor or diode is to be formed. A thin epitaxial *p*-type layer is then diffused. The collector diffusion is then made producing low resistivity *n*+ channels round each component. This diffusion serves three purposes: to make contact with the buried *n*+ area which forms the collector; to provide isolation between components; and to define base and resistor areas.

A shallow *p*-type layer is diffused over the whole slice to define resistor values. A shallow emitter diffusion then follows.

The CDI process reduces transistor areas by up to a third and also enables digital and linear circuits to be combined on one slice. The main disadvantage is that there is no *pnp* transistor available, though a *p*-channel f.e.t. under development should overcome this difficulty.

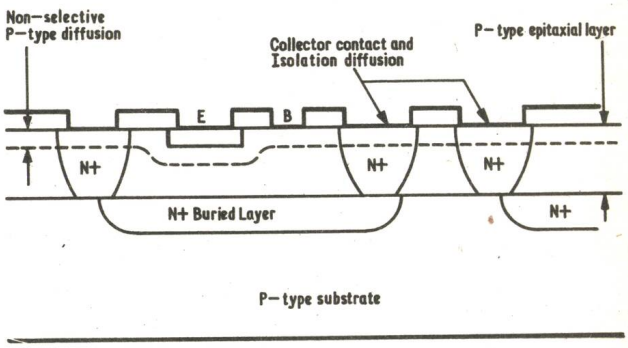

Fig. 17 Structure of a CDI transistor (*Ferranti*)

CONCLUSIONS

From the original low-power low-frequency transistor have developed transistors capable of operating high in the radio frequencies, transistors handling powers of over 100W, transistors capable of switching wave-forms with rise times of 1ns. Signal diodes operating in the microwave frequencies have been developed, and diodes and thyristors capable of operating on high-voltage supplies controlling powers measured in megawatts. Devices reacting to and producing light are available, and devices containing a complete computer processing system on a chip only 3·5mm square.

Although the transistor was the fore-runner, the most revolutionary device may well be the integrated circuit which has brought a new concept into electronic circuit design. The thermionic valve (apart from its more specialised forms such as klystrons and magnetrons) had a commercial life of about 35 years. It may well be that the discrete transistor apart from more specialised forms like photodevices will have a shorter life. ★

550 VOLT MEGOHMMETER MΩ

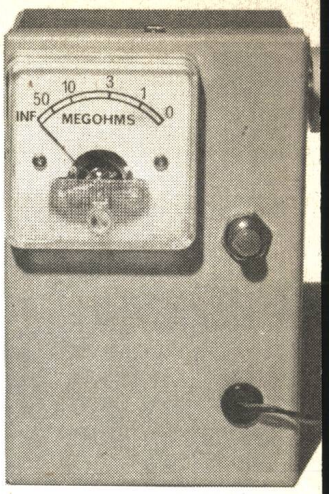

by B. V. Lamb

THE PAST few years have seen more and more householders tackling home wiring installation work. When the work is completed and before the mains can be permanently connected certain safety checks have to be made. This article and project deal with a very useful instrument that will measure the insulation resistance of the wiring.

Poor insulation causes current to flow between the line and earth or neutral. This current in turn will generate heat in the wiring, which if of sufficient temperature could cause fuse blowing or, more seriously, a fire.

Unfortunately, most do-it-yourself wiring enthusiasts do not possess the means for measuring leakage currents at high voltage. Commercially available instruments are expensive and secondhand units are not cheap either. The traditional instrument consists of a hand driven generator that causes a high voltage to appear across a lead terminating in a couple of croc clips, a meter registers the insulation resistance. More recently, electronic testers have tended to replace the hand driven types.

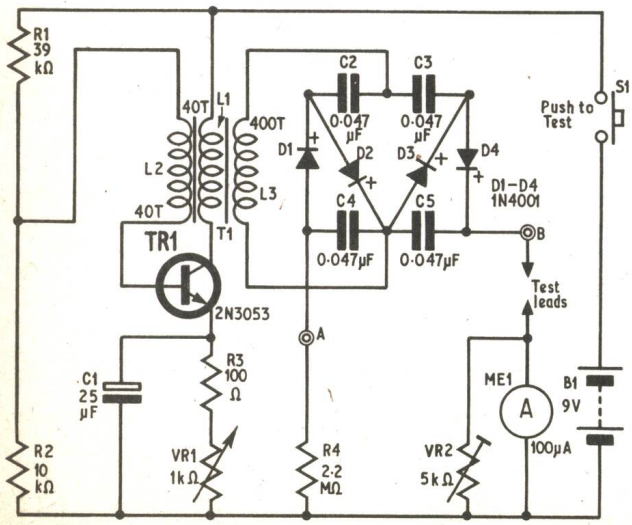

Fig. 1. Circuit diagram of the Megohmmeter

DESIGN CONSIDERATIONS

The a.c. voltage in the United Kingdom is 240 volts r.m.s.. Since we are interested in peak voltage, and $V_{peak} = V_{r.m.s.} \times 1{\cdot}414$ the test voltage generator will need to be at least 340 volts. In practice, however, regulations require that a minimum of 500 volts be used.

The 550 volt megohmmeter here described satisfies the twin requirements of the home electrican; it is easy to build and the price is low compared to commercially available units. Push button operation is employed as this prevents inadvertent battery run down due to a switch being left on. All of the components are readily available.

As to the choice of a suitable transistor high voltage generator; the demands made by the Megohmmeter dictate that a sine wave oscillator type d.c. convertor be used. There are three broad types of d.c. convertor that could be used, namely: ringing choke, multivibrator and sine wave.

Each of these circuits produce an oscillating voltage that is stepped up to a higher voltage by means of a transformer and then rectified to give a d.c. voltage at the required level.

Although the least efficient of the three, the sine wave oscillator is the first choice in favour of the ringing choke method when it comes to ease of starting. In economy of components it beats the multivibrator circuit. Since the Megohmmeter does not need to produce more than about 170 microamps under short circuit conditions, a low efficiency high voltage generator does not matter in the least.

CIRCUIT OPERATION

Transformer T1, TR1 and the associated circuitry form a sine wave oscillator whose period of oscillation is determined by the inductance and self capacitance of T1 (Fig. 1).

The feedback winding of T1 sustains the oscillation and is connected to the junction of R1 and R2 which together with R3 and VR1 set the d.c. bias for TR1. C1 prevents a.c. degeneration. VR1 allows for variation in voltage developed across the collector winding of T1.

The diodes, D1, D2, D3 and D4 plus the capacitors, C2, C3, C4 and C5 comprise a voltage quadrupler circuit. This circuit rectifies the a.c. voltage appearing across L3 and multiplies by four its equivalent d.c. value.

By varying VR1 over its whole range the open circuit output at the test leads can be varied from approximately 300 to 650 volts. In practice however, the voltage will be set at 550 for normal use. The wide range does allow for increased versatility and the constructor will be able to make use of this from time to time.

CONSTRUCTION

Dismantle the Ferroxcube core and carefully mount the bobbin on a suitable arbor — the author used a wheelbrace which had a gear ratio of 3·75 : 1 clamped in a bench vice and a 2BA screw as the arbor.

Strip a 2in length of thin pliable plastic sleeve from some spare wire and thread this onto some 41 s.w.g. enamelled copper wire (L3).

Carefully wind 400 turns and finish off L3 by insulating with one turn of Scotch Tape.

Next wind 40 turns of 41 s.w.g. for L2 and similarly insulate. Finally wind 40 turns of 28 s.w.g. for L1 and complete the transformer with a layer of tape.

The rest of the construction is quite straightforward (Fig. 2). The only caution is that building the circuit on inferior leaky tagboard is bound to cause difficulty in getting an infinity reading since leakage current will cause a standing error. The ideal case is plastic although metal can be used if care is taken with insulation.

SETTING UP

Once the circuit has been built, it is first of all necessary to establish the working of the oscillator.

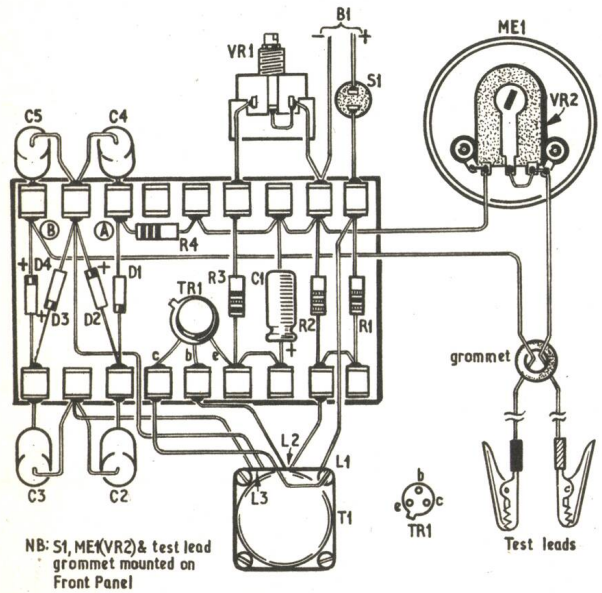

Fig. 2. Layout of the components on the tagboard and interconnections to the transformer, potentiometer, pushbutton and meter.

COMPONENTS . . .

Resistors
R1 39k Ω
R2 10k Ω
R3 100 Ω
R4 2·2M Ω
All ¼W 10% carbon

Potentiometers
VR1 1k Ω
VR2 5k Ω preset

Capacitors
C1 25μF 6·4V electrolytic
C2, 3, 4, 5 0·047μF 400V polyester (4 off)

Semiconductors
TR1 2N3053
D1, 2, 3, 4. 1N4004 *or* any 400 p.i.v. low current diode (4 off)

Miscellaneous
S1 Miniature pushbutton
ME1 100μA f.s.d.
T1 Ferroxcube core type LA1 *or* equivalent
9 way Tagboard
Crocodile Clips (2 off)
9V Battery. PP7 or similar
Metal case 4in × 2½in × 2in
41 and 28 s.w.g. enamelled copper wire

Short the test clips together and the meter should indicate some value. If no movement is seen the oscillator feedback winding (L2) has to be reversed. Once the circuit is working, the output should be set to 550 volts.

Connect a high resistance voltmeter between points A and B then adjust VR1 for 550 volts. During this operation the test clips must of course be open circuited. The meter can now be calibrated in terms of megohms.

Remove the meter from its case and place it on the working surface having previously cleaned up and dusted down. Carefully remove the scaleplate and paint the reverse side matt white with emulsion paint.

When dry place the scaleplate — with its original markings uppermost—on a piece of cardboard. With a compass find the radius of the scale line and the maximum and minimum positions. Transfer these lines to the blank side. Screw the scaleplate back on the meter.

Short out the test clips and mark the scale with a soft pencil at this point. Now connect 1, 3, 10 and 50 megohm resistors and mark these equivalent points in. A professional job can be done by using plastic film ink for the scale lines and Letraset for the letters and numbers.

CONCLUSION

The 550 volt insulation tester that has been described should prove to be a valuable addition to the electricians tool kit. There are of course other uses to which it can be put, insulation tests for the electronic engineer being one example.

By making a simple twin pointed probe, relative dampness in wood and plaster can be measured. ★

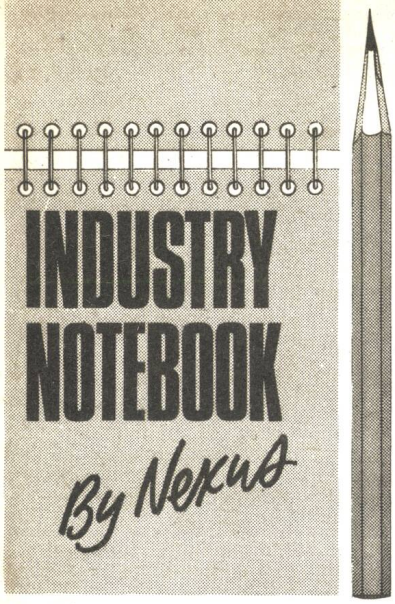

UPTURN

Yesteryear's sobs and groans from industry salesmen were conspicuously absent at the London Electronic Components Show. Nobody seemed to care that the show was smaller than before and, from first reports, less well attended. Those who came were buyers and that was the important thing.

But it wasn't all smiles and sunshine. The spectre of empty order books may have retreated but only to make way for another spectre to give top management some sleepless nights. What is haunting the industry to-day is how to get components made fast enough to meet the demand. Those major companies which had spare capacity have none today. An even worse fear looming up is a shortage of raw materials.

But, on the whole, things look pretty good. Quipped one exhibitor, "If you can't make a few bucks in these conditions you never will."

This year's Chairman of RECMF, Ronald Bulgin, wore one of the biggest smiles at the show. His publicly quoted family business is still a profit leader in the industry and he will preside as the component industry Chairman in a boom period. What could be better?

Wearing his chairman's hat rather than his company's, he put out a public plea for rationalisation of the exhibition calendar. And he was quite right to do so. In the past six months we have had Electronica in Munich, the Paris Salon and the British show at Olympia. What the industry needs is one big international show a year in Europe with London, Paris and Munich in rotation so that each of the three electronics "capitals" puts on a show every three years.

A sensible idea but unlikely to be accepted by exhibition organisers while they still make huge profits from the present spate of shows. The only hope is that the economic forces of the market place will do what exhortation won't. If enough would-be exhibitors opted out, the exhibition organisers would have to adjust their ideas.

ROYAL SPOKESMAN

His Royal Highness The Duke of Kent is tipped to succeed Admiral of the Fleet Earl Mountbatten of Burma as an important independent commentator on electronic industry affairs.

As yet, The Duke admits to being "a complete amateur, hardly knowing the difference between R and C." But having heard him speak on the subject I find him well-informed. Naturally, he is briefed in advance of public utterances but I am reliably told that his interest in electronics borders on the enthusiastic and that he is eager to expand his knowledge of the industry not only in its technology but also in its commercial and social impact.

If knowledge is born of experience he should be learning fast. He is a member of the National Electronics Council and opened the London Electronic Components Show and, more recently, Microwave '73 at Brighton.

THE OLD AND THE NEW

This is a good year for anniversaries. Sperry Gyroscope has just celebrated 60 years in the U.K. with an exhibition opened by Prince Philip, Duke of Edinburgh, at the company's Bracknell HQ. Then there's AVO Ltd., celebrating fifty years in coil winding equipment and instruments (the millionth Avometer left the works as long ago as 1965!).

But what about companies yet unborn? There are plenty on the way to swell the ranks of industry. Expect announcements soon that Jim Griffith, boss of Plastronics, is setting up a manufacturing plant in Germany and that Maurice Hatter, a co-founder of Keyswitch Relays (subsequently sold to Thorn), is moving back into relay manufacture in a plant in Italy. Two new British Euro-babies for the Common Market.

HI-FI

Cosmocord is looking to hi-fi as a logical expansion based on its long history in pick-up cartridges, audio instruments and, more recently, head sets and ear protectors. For a start, the company has won the sole U.K. franchise for quality speakers built by Martin in the USA. There is a complete range from about £30 per pair up to £200 for a single 100W multiple speaker unit.

Cosmocord tell me that there is a possibility of making some of the Martin range in the U.K. but following the recent introduction of the ACOS "Lustre" pick-up arm (reported to be doing well), it is more likely that manufacture will be concentrated on tuners and amplifiers to complete the audio chain. Cosmocord marketing men are scanning the market with a keen eye before committing themselves, but if the Martin speakers are to come as part of a Cosmocord hi-fi package my guess is that they are looking at the top end of the market.

The company has now absorbed the Birch-Stolec thumbwheel switch business — renamed Cosmocord-Stolec—which has a turnover of some £250,000 a year. In all Cosmocord is targeted for £1·85 million turnover in the fiscal year just started.

NOT ALL HONEY

Although the electronics capital goods sector has a more healthy looking order book than last year. things are still sluggish according to the Electronic Engineering Association. Sales at £684·5 million. although marginally higher in total than in the previous year, were in real terms, showing a decline said retiring President Dr B. J. O'Kane in his "state of the industry" address at the EEA annual luncheon. Best areas in the year under review were communications and marine radar, both of which showed gains of better than 20 per cent.

Disturbing and perhaps an uncomfortable experience for Rank-Xerox, brightest and most profitable jewel in the Rank crown, is the impending Monopolies Commission probe. The British inquiry follows the threat to the U.S. parent company of anti-trust action by the U.S. Trade Commission. Curtailing of Rank-Xerox activities could have quite an effect on many of the smaller electronic companies who are engaged in sub-contract work for the company.

Even prosperous Mullard has its black spots. Forecast losses on integrated circuit manufacture this year is £700,000, following losses of nearly £3 million in the past two years. Break-even is forecast by the end of the year and profit by the end of '74, or perhaps a little earlier. Meantime, the really hot lines like colour TV tubes more than make up for the deficiency.

look! electronics really mastered

... practical
... visual
... exciting!

no previous knowledge
no unnecessary theory
no "maths"

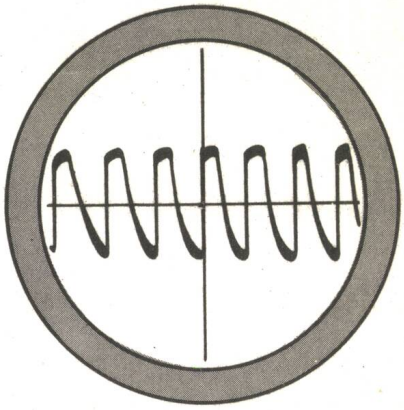

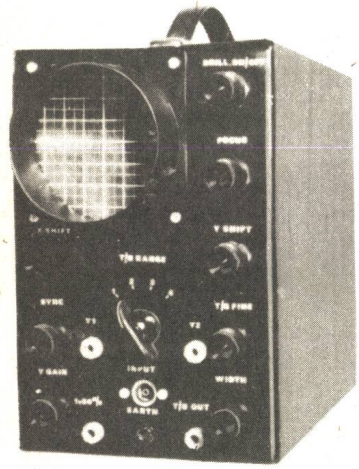

RAPY

BUILD, SEE AND LEARN
step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS

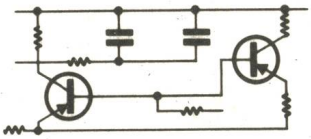

as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW for BROCHURE

or write if you prefer not to cut page

To BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, P.O. BOX 156, JERSEY. Please send your free brochure, without obligation, to: *we do not employ representatives*

NAME BLOCK CAPS

ADDRESS PLEASE EL83

special free gift also to all our students

ELECTRONORAMA

STEPS FORWARD IN TIME . . . .

UNTIL 1970 electronic watches seemed to make very little impact on the market, probably because the manufacturers themselves seemed mostly reluctant to invest in this new technology. However three years ago the major Swiss manufacturers unveiled new electronic models incorporating quartz oscillators and it became clear that the whole industry was actively concerned with "the watch of the future".

THREE TYPES

Since that time electronics have become the major topic of interest and excitement throughout the watch world. Today there are three types of electronic watches driven by batteries. These are tuning fork, quartz and solid state.

Tuning fork watches employ an acoustic resonator (tuning fork) as a timing device and a motor driven by a transistor circuit. Because of this they do not tick but emit a slight hum. The accuracy of these watches is about one minute a month.

Quartz systems with mechanical display use a quartz crystal which oscillates under the effect of an alternating electric field. These oscillations, through a system of circuits and a motor, control the hands of the watch and provide accuracy within 5 seconds a month.

Solid state electronic models show the time in figures with a digital display instead of hands and have no moving parts. They use a quartz crystal oscillator as a timekeeper and activate a liquid crystal or diode display on the face of the watch. Again these have an accuracy of around 5 seconds a month. In addition to these, there are watches which are better described as electric rather than electronic. They employ a conventional hair spring and a balance wheel as the timing mechanism, but are powered by a battery as opposed to a main spring. Their accuracy is no more than that of a comparable conventional watch.

SIMPLE SERVICING

The advent of electronic watches offers considerable benefits as substantial improvements in accuracy and reliability can be achieved. In addition, problems of after-sales service will be reduced at a time when servicing is increasing in cost and there are fewer skilled watchmakers, because the regular cleaning and maintenance necessary for conventional watches is either considerably reduced or eliminated for electronic models.

NEW DESIGN CONCEPTS

Omega, part of SSIH (Société Suisse pour l'Industrie Horlogère SA)—the world's third largest watch manufacturer—have announced new design concepts for electronic watches, which made their international debut last month at the Swiss Industries Fair in Basle.

The three new watches are the Megaquartz 2400, the Time Computer and the Megasonic 720. The Megaquartz is a quartz watch with a mechanical display. It has a precision reaching ± one second a month in normal wear—the world's most accurate watch.

The Time Computer is a solid state electronic watch with no moving parts, which shows the time digitally. This model has an accuracy within five seconds a month.

The third new model, the Megasonic 720, is an original and entirely new development of the basic tuning fork watch, and has an accuracy reaching 10 seconds a month in normal wear.

THE MEGAQUARTZ 2400

The Megaquartz 2400 heralds a new generation of quartz watches. Announced as the world's most accurate watch it only varies within one second a month. This remarkable increase in precision over earlier quartz watches (about 1 minute a year) is achieved with a crystal vibration of 2,359,296 times a second.

The first generation of quartz watches used frequencies of up to 65,536Hz. In order to achieve any further technical progress beyond this point it was necessary to increase frequency up to at least 1,000,000Hz, but microelectronic technology was not available to make this practical.

Now with the Megaquartz 2400 Omega have developed a unique electronic microcircuit. This has been achieved by using an analogue circuit dividing the quartz frequency, and by the most advanced CMOS technology in the area of integrated circuits of micropower.

One characteristic of the watch would be important to the "Jet Set", who travel between time zones. In order to maintain the accuracy of the minute and second hands the watch can be immediately adjusted by moving the hour hand alone.

Megaquartz 2400 is now in production, and it is expected that it will be available in the U.K. in 1974, at prices starting from £425.

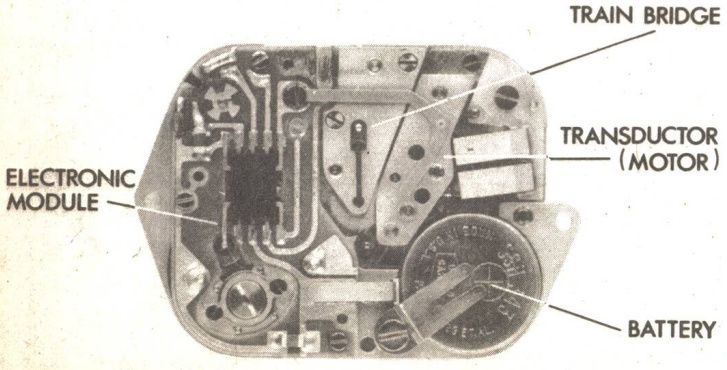

Photograph showing the movement of the Megaquartz 2400, claimed to be the world's most accurate watch

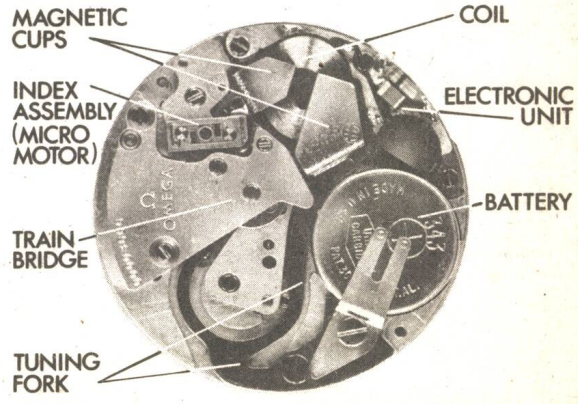

Movement of the Megasonic 720 — the first original development on the basic tuning fork watch

The Time Computer. A solid state digital watch with no moving parts

THE TIME COMPUTER

The Time Computer is a completely solid state digital watch with no moving parts. The display is by red light emitting diodes arranged for four digits.

Time is shown "on demand" by pushing a command button which illuminates the light emitting diodes covered by a synthetic ruby face, chosen for its hardness and filtering qualities. When the command button is pressed the time in hours and minutes is shown for 1·25 seconds and is then replaced by the seconds for as long as the button remains depressed.

Another advance in this timepiece is its unique system for resetting time that allows hours or minutes to be changed independently. This is an obvious advantage for international travellers constantly flying from one time zone to another. Time is changed by inserting a tiny magnetic key into one of the two timeset recesses in the back of the watch, one linked to the minute digits, the other to the hours. To change the hour only, the magnet is placed into the hour recess, when the face lights up to show the hour digits moving forward.

The Time Computer has the equivalent of 1,238 transistors in a surface area of only 3·8 × 3·8mm. Its brain is an electronically operated quartz crystal vibrating 32,768 times a second.

The vibrations are counted and the results are fed to the driver decoder circuit, which activates the time display on demand. The watch is powered by two tiny batteries.

Because the watch has no moving parts there is no need for the oiling and cleaning advised for conventional movements.

The Omega Time Computer will be available in the shops within a few months at around £300.

MEGASONIC 720

Electronic tuning fork (acoustic resonator) watches are well established and proven on the market. Almost all the major manufacturers offer models which are basically derived from the original invention in the 1950's by Max Hetzel.

The Megasonic 720 has distinct advantages over earlier tuning fork watches. It gives a considerable improvement in accuracy to within ±10 seconds a month in normal wear, compared with 60 seconds in similar watches. This is achieved by increasing the frequency at which the resonator vibrates to 720 hertz compared to 300/360.

The acoustic resonator is stimulated by an integrated circuit. The movement is transmitted to the train by an original micromotor. The train is driven by magnetic gear, and conventional display shows seconds, minutes, hours, day and date. A mercury battery powers the movement and guarantees it for one year's running.

Its launch is scheduled for 1974 in a new range of models styled Omega Megasonic 720. Retail prices have not yet been finalised, but are expected to be only slightly above existing models.

TRANSFORMERS

MAINS ISOLATING SERIES
Primary 200-250 Volts Secondary 240 Volts Centre Tapped (120V) and Earth Shielded
ALSO AVAILABLE WITH 115/120V SEC. WINDING

Ref. No.	VA (Watts)	Weight lb	Weight oz	Size cm.	P & P £	P & P p
07	20	1	11	7·0 × 6·0 × 6·5	1·77	30
100	60	3	8	8·9 × 8·0 × 7·7	2·62	36
61	100	5	12	10·2 × 8·9 × 8·3	2·88	52
30	200	9	8	12·0 × 10·3 × 10·0	4·83	52
62	250	12	4	9·5 × 12·7 × 11·4	6·38	67
55	350	15	0	14·0 × 10·8 × 12·4	8·55	82
63	500	27	0	17·1 × 11·4 × 15·9	12·32	*
92	1000	40	0	17·8 × 17·1 × 21·6	22·70	*
128	2000	63	0	24·1 × 21·6 × 15·2	37·50	*

PLEASE NOTE NEW ADDRESS AS BELOW

AUTO SERIES (NOT ISOLATED)

Ref. No.	VA (Watts)	Weight lb	Weight oz	Size cm.	Auto Taps	P & P £	P & P p
113	20		11	7·3 × 4·3 × 4·4	0-115-210-240	0·93	22
64	75	1	14	7·0 × 6·4 × 6·0	0-115-210-240	1·82	30
4	150	3	0	8·9 × 6·4 × 7·6	0-115-200-220-240	2·20	36
66	300	6	0	10·2 × 10·2 × 9·5	,, ,,	4·28	52
67	500	12	8	14·0 × 10·2 × 11·4	,, ,,	6·35	67
84	1000	16	0	11·4 × 14·0 × 14·0	,, ,,	11·54	82
93	1500	28	9	13·5 × 14·9 × 16·5	,, ,,	16·72	*
95	2000	40	0	17·8 × 16·5 × 21·6	,, ,,	21·82	*
73	3000	45	8	17·4 × 18·1 × 21·3	,, ,,	29·70	*

TOTALLY ENCLOSED 115V AUTO TRANSFORMERS
115V 500 Watt totally enclosed auto transformer, complete with mains lead and two 115V outlet sockets, £8·63. P & P 67p.
Also available a 20 Watt version. £1·84. P & P 22p.

LOW VOLTAGE SERIES (ISOLATED)
PRIMARY 200-250 VOLTS 12 AND/OR 24 VOLT RANGE

Ref. No.	Amps. 12V	Amps. 24V	Weight lb	Weight oz	Size cm.	Secondary Windings	P & P £	P & P p
111	0·5	0·25		12	7·6 × 5·7 × 4·4	0-12V at 0·25A × 2	0·93	22
213	1·0	0·5	1	0	8·3 × 5·1 × 5·1	0-12V at 0·5A × 2	1·11	22
71	2	1	1	0	7·0 × 6·4 × 5·7	0-12V at 1A × 2	1·46	22
18	4	2	2	4	8·3 × 7·0 × 7·0	0-12V at 2A × 2	2·04	36
70	6	3	3	12	10·2 × 7·6 × 8·6	0-12V at 3A × 2	2·46	42
108	8	4	5	4	10·0 × 8·3 × 8·2	0-12V at 4A × 2	2·73	52
72	10	5	6	3	7·9 × 10·8 × 10·2	0-12V at 5A × 2	3·23	52
17	16	8	7	8	12·1 × 9·5 × 10·2	0-12V at 8A × 2	4·99	52
115	20	10	11	13	12·1 × 11·4 × 10·2	0-12V at 10A × 2	6·35	67
187	30	15	16	12	13·3 × 12·1 × 12·1	0-12V at 15A × 2	11·73	82
226	60	30	34	0	17·0 × 14·5 × 12·5	0-12V at 30A × 2	21·57	*

30 VOLT RANGE

Ref. No.	Amps.	Weight lb	Weight oz	Size cm.	Secondary Taps	P & P £	P & P p
112	0·5	1	4	8·3 × 3·7 × 4·9	0-12-15-20-24-30V	1·11	22
79	1·0	2	0	7·0 × 6·4 × 6·0	,, ,,	1·48	36
3	2·0	3	2	8·9 × 7·0 × 7·6	,, ,,	2·21	36
20	3·0	4	6	10·2 × 8·9 × 8·6	,, ,,	2·72	42
21	4·0	6	0	10·2 × 10·0 × 8·6	,, ,,	3·23	52
51	5·0	6	8	12·1 × 10·0 × 8·6	,, ,,	4·02	52
117	6·0	7	8	12·1 × 10·0 × 10·2	,, ,,	4·80	52
88	8·0	10	0	14·0 × 11·7 × 10·0	,, ,,	6·20	67
89	10·0	12	2	14·0 × 10·2 × 11·4	,, ,,	7·85	67

50 VOLT RANGE

Ref. No.	Amps.	Weight lb	Weight oz	Size cm.	Secondary Taps	P & P £	P & P p
102	0·5	1	11	7·0 × 7·0 × 5·7	0-19-25-33-40-50V	1·46	30
103	1·0	2	10	8·3 × 7·3 × 7·0	,, ,,	2·13	36
104	2·0	5	0	10·2 × 8·9 × 8·6	,, ,,	2·96	42
105	3·0	6	0	10·2 × 10·2 × 8·3	,, ,,	4·01	52
106	4·0	9	4	12·1 × 11·4 × 10·2	,, ,,	5·31	52
107	6·0	12	4	12·1 × 11·1 × 13·3	,, ,,	7·85	67
118	8·0	18	9	13·3 × 13·3 × 12·1	,, ,,	10·25	97
119	10·0	19	12	16·5 × 11·4 × 15·9	,, ,,	12·85	97

60 VOLT RANGE

Ref. No.	Amps.	Weight lb	Weight oz	Size cm.	Secondary Taps	P & P £	P & P p
124	0·5	2	4	8·3 × 9·5 × 6·7	0-24-30-40-48-60V	1·48	36
126	1·0	3	0	8·9 × 7·6 × 7·6	,, ,,	2·06	36
127	2·0	5	6	10·2 × 8·9 × 8·6	,, ,,	3·23	42
125	3·0	8	8	11·9 × 9·5 × 10·0	,, ,,	4·92	52
123	4·0	10	6	11·4 × 9·5 × 11·4	,, ,,	6·35	67
120	6·0	16	12	13·3 × 12·1 × 12·1	,, ,,	9·20	82
122	10·0	23	2	16·5 × 12·7 × 16·5	,, ,,	15·23	*

LEAD ACID BATTERY CHARGER TYPES

Ref. No.	Amps.	Weight lb	Weight oz	Size cm.		P & P £	P & P p
45	1·5	1	9	7·0 × 6·0 × 6·0	Please note, these units do not include rectifiers	1·47	30
5	4·0	3	11	10·2 × 7·0 × 8·3		2·23	42
86	6·0	5	12	10·2 × 8·9 × 8·3		3·37	52
146	8·0	6	4	8·9 × 10·2 × 10·2		3·84	52
50	12·5	11	14	13·3 × 10·8 × 12·1		5·72	67

All ratings are continuous. Standard construction: open with solder tags and wax impregnation. Enclosed styles to order.

FULL SPEC. TRANSISTORS (E.G.)
BC107/108/109 **10p** each. | 2N 3055 **60p** each + mica and bushes | AD161/162 **60p** pair + mica and bushes

Carriage via B.R.S.

★ **Quantity prices on application**
ELECTROSIL RESISTORS • AVOMETERS
PLEASE ADD 10% FOR V.A.T.
INC. P. & P.

BARRIE electronics
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/8
NEAREST TUBE STATIONS ALDGATE & ALDGATE EAST

SIMPLE FLASHER

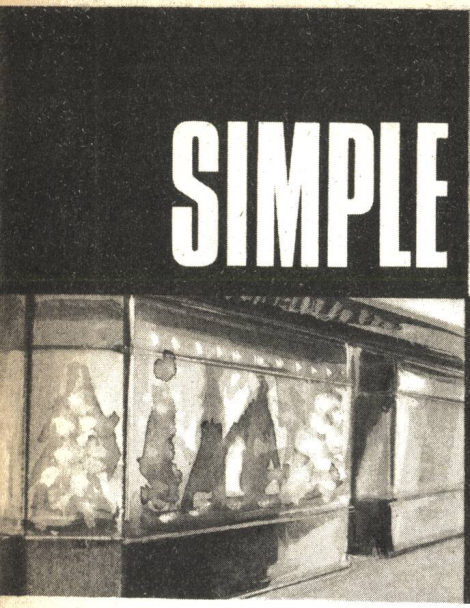

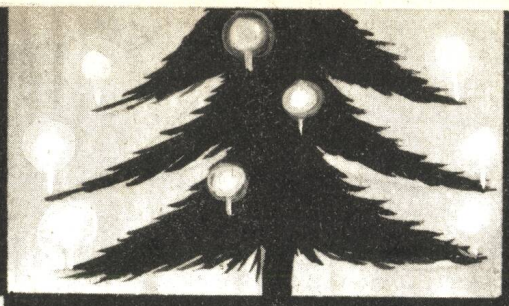

By J. B. DANCE, M.Sc.

IN THE June issue of PRACTICAL ELECTRONICS the introduction of a new integrated circuit, the 555, was discussed in detail from both the theoretical and practical point of view. Only one application as a timer suitable for photography or event control was considered as a constructional project.

Thus we now consider the application of this i.c. to the control of such items as the lights on the Christmas tree or in a window display so as to provide a flashing effect. At the instant the one set of lights is switched off, another set can be switched on if this is desired. The two sets are then illuminated alternately.

THE CIRCUIT

The type NE555V i.c. which has a dual-in-line encapsulation was used by the writer, but the NE555T in the circular TO-99 encapsulation is equally suitable. Both types have eight connecting leads and contain the equivalent of 23 transistors, two diodes and 16 resistors in a small package.

The 555 is used in the astable mode in this application. In the circuit shown in Fig. 1, the capacitor C1 alternately charges and discharges so that the potential across it varies between $V_{cc}/3$ and $2V_{cc}/3$. Each time the voltage across C1 falls to $V_{cc}/3$, the 555 is automatically re-triggered by means of the connection to the trigger pin 2; the capacitor then commences to charge again.

TIMING

The charging current flows through both R1 and R2. It can be shown that the time for charging from $V_{cc}/3$ to $2V_{cc}/3$ is $0{\cdot}693(R_1 + R_2)C_1$ seconds where R_1 and R_2 are expressed in ohms and C_1 is expressed in farads. During discharge the current from C1 flows through R2 only; thus discharging takes the shorter time $0{\cdot}693R_2C_1$. The frequency of oscillation is $1{\cdot}44/(R_1 + 2R_2)C_1$. The charging time cannot be made shorter than the discharging time.

If one uses the values for R1, R2 and C1 shown in the circuit, one can calculate that the charging time is 4·8 seconds and the discharging time 3·3 seconds. This should be suitable for the automatic switching of lights in a shop window or on a Christmas tree.

In practice the times will not be exactly equal to the calculated values since the values of the three components will differ somewhat from their marked values. In particular, electrolytic capacitors have very wide tolerances.

The component values can be altered to obtain the desired switching times. However, for applications of this type one does not need to adjust the values critically. One may require shorter times for use in a flashing toy; for example, C1 may be reduced to 2μF of 1μF. The value of the power supply voltage, V_{cc}, does not affect the switching times appreciably.

THE RELAY

The relay remains open whilst the capacitor is charging, but closes during the discharging time. A diode must be placed in parallel with the relay in order to suppress the transient back e.m.f.; the latter is generated across the inductive relay coil when the current ceases to flow through it. If the transient voltage is not suppressed with a diode, it could damage the integrated circuit.

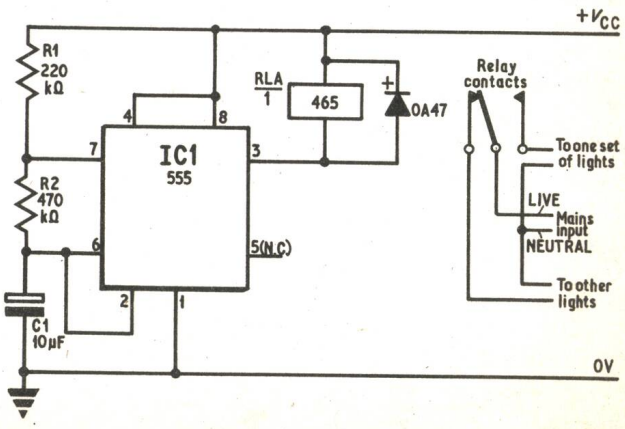

Fig. 1. Circuit diagram for the simple i.c. flasher

The writer used an economical microswitch relay type MS1B designed for printed circuit board mounting. It is readily available (through retailers) from Keyswitch Relays Ltd. The value of the power supply voltage, V_{cc}, used must match the recommended relay operating voltage to within about 20 per cent. If V_{cc} is between five and seven volts, an MS1B with a 6V, 50mA coil rating should be employed. Alternatively V_{cc} may be between 9·5 and 15·5V, in which case the MS1B employed should have a 12V, 26mA coil rating.

The MS1B relay has a single group of change-over contacts which can switch 250V at up to 5A in a.c. circuits. This maximum power of 1·25kW is more than is likely to be required in any shop window of moderate size.

Nevertheless, a larger relay can be used in this circuit if necessary provided that it does not require a current of over 200mA to operate it. Another type of microswitch relay, the Keyswitch Relay type MS2B, has two pairs of change-over contacts each of which can control a current of up to 2A in a 250V a.c. circuit. In d.c. circuits the current ratings of relay contacts are lower (0·2A at 250V and 0·25A at 100V for both the MS1B and MS2B).

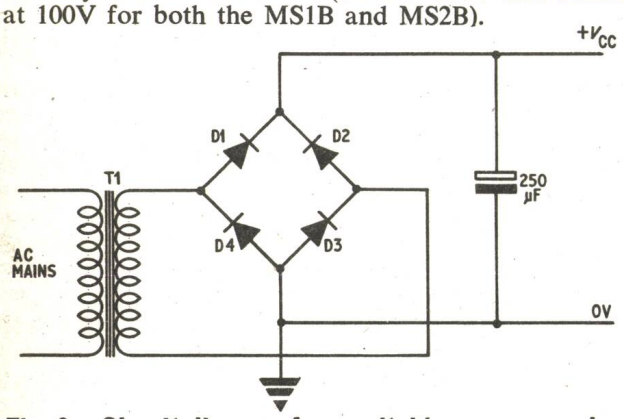

Fig. 2. Circuit diagram for a suitable power supply

POWER SUPPLY

The circuit of Fig. 1 can be operated from a small battery. Indeed, this is the most sensible source of power to use in a toy for children. The integrated circuit itself requires a current of about 3mA (maximum 6mA) when V_{cc} is 5V, but the current rises to about 10mA (maximum 15mA) when V_{cc} is 15V. The relay coil current is additional to these values.

When the circuit is used to switch 250V lamps on and off, it is normally more convenient to employ a small power pack which operates from the mains.

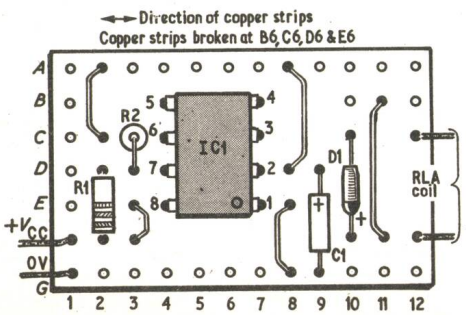

Fig. 3. Board layout for the flasher circuit

Components

Resistors
R1* 220k Ω, 1/10W, 10%
R2* 470k Ω, 1/10W, 10%

Capacitors
C1* 10µF, 15V electrolytic

Miscellaneous
NE555V (or NE555T) Signetics integrated circuit
OA47 gold bonded germanium diode.
MS1B relay, 6V or 12V coil (see text).
Mains three-way input plug if needed.
One or two two-way output connectors (depending on whether one or two sets of lights are to be switched).
Eight pin dual-in-line socket (if NE555V used).
* Values may be altered to obtain desired switching times.

POWER PACK

T1 Small mains transformer with an output of either about 5V or about 10V r.m.s., depending on the relay used (see text).
D1–4 1N4001 or similar or alternatively one bridge rectifier such as REC 41A (RS Components Ltd.).
250µF capacitor, 15V, electrolytic.

The whole system can then be operated from a supply which is switched off at a preset time at night by the normal type of time switch used for controlling the lighting in many shop windows.

A suitable power supply circuit is shown in Fig. 2. The output of the secondary winding of the transformer T1 should be chosen so that it is suitable for the coil operating voltage of the relay used. A 5V r.m.s. transformer winding is suitable for a relay with a 6V coil rating, whilst a 10V r.m.s. winding may be used with a 12V relay. However, these voltages are not very critical.

The output voltage of the transformer may be rectified by four separate diodes (D1 to D4), such as type 1N4001. Alternatively a single bridge rectifier (such as the RS Components type REC 41A) may be used instead of the four diodes.

CONSTRUCTION

The whole unit, including the mains power pack, may be placed in a small die-cast metal box. One suitable box of approximate external dimensions 114 × 89 × 55mm is available from RS Components Ltd., whilst another type of approximate dimensions 119 × 93 × 52mm is available from Eddystone Radio Ltd.

The metal box should be connected to the mains earth when used with mains equipment for safety reasons. The small mains transformer can be mounted directly on the box, but the remaining components are conveniently mounted on a small circuit board. One can solder directly to the contacts of the 555 integrated circuit, but it is generally more convenient to employ an eight-pin dual-in-line socket if the NE555V is used.

In view of the simplicity of the circuitry and mechanics involved it is deemed unnecessary to discuss construction in greater depth on this project. ★

LOGIC TUTOR EXPERIMENTS..

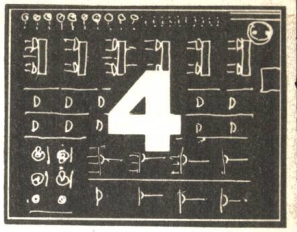

DE MORGAN'S THEOREM

FIRSTLY the answer to last month's question. There are various ways of getting the six input AND but they all use the same principle. There is an Associative rule in Boolean algebra which says that if you have a number of variables coupled by the same logical functions then the variables can be grouped together in sub-groups and combined by their function independently; the independent groups can then be coupled together with like functions to produce the final desired effect.

Thus if we want to AND together inputs A, B, C, D, E and F we can carry out the operation in three stages; firstly we AND A with B and C (as a sub-group) then D with E and F as a separate sub-group. Finally we take the outputs of each of the sub-groups and AND them together in a two input gate to give the total effect.

One form of six input AND gate using NANDS is shown in Fig. 4.1. Notice that it is necessary to use a lot of gates to carry out what is basically a very simple function. It would be much more economical—in space and cost—to use a six input NAND followed by an inverter or alternatively convert a four input NAND into a six input version using an expander before inverting.

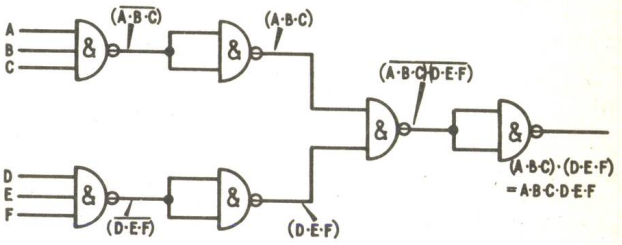

Fig. 4.1. A solution to last month's problem.

DE MORGAN'S THEOREM

Referring to the truth table for the NAND we could say that the output is 1 when A is 0 OR B is 0. Remember we are describing the same function as last month but are using a different point of view. Using the Boolean nomenclature that $\overline{A}$ represents "when A is nought" we can say that the output Q is given by $\overline{A}$ or $\overline{B}$

$$Q = \overline{A} + \overline{B}$$

But from a different view point—last month we saw that

$$Q = \overline{A.B}$$

Therefore by normal algebraic argument we can say that

$$\overline{A} + \overline{B} = \overline{A.B}$$

This proves the first of De Morgan's Theorems which—in very simple terms—says that an inverted AND is identical to a sort of inverted OR.

There is a second theorem which is very similar (it is worth you thinking how to argue it out) which says:—

$$\overline{A.B} = \overline{A} + \overline{B}$$

Again in simple terms an inverted OR is the same as a sort of inverted AND.

Before moving on, take note of a catch that beginners sometimes fall into. $\overline{A.B}$ is *not* the same as saying A.B. This means that when writing Boolean expressions you have to be careful with the length and breaks of the negate bar over the top of the alphabetical characters. Sometimes brackets are used to make the distinction clear in complex expressions.

OR FROM NAND

De Morgan's Theorem is one of the most used in Boolean algebra because it gives a NAND gate a duality of purpose. Depending on how we want to think we can say that the output is either $\overline{A.B}$ or $\overline{A} + \overline{B}$. We have already utilised the former to give us AND from NAND. Now we can use the latter to give us basic OR.

Fig. 4.2 shows the way of producing a fundamental two input OR function. The inputs A with B become A with B at the outputs of their respective inverters. The output of the final NAND can be considered to be an OR function coupling the inverted form of its inputs. Therefore the output in this case is $\overline{A} + \overline{B}$. The double negates over each variable cancel and we are left with A + B.

Use the toggle switches on the Logic Tutor to provide inputs to this circuit and monitor the logic levels at the various nodes on the lamps and check these against the truth table for the circuit shown in Fig. 4.2.

As an exercise try and use the knowledge you now have of the Associative rule and the gates available on Logic Tutor to produce a six input OR. (One answer to be given next month).

by M. Hughes

Next month we shall deal with the EXCLUSIVE OR function.

A	B	$\overline{A \cdot B}$
0	0	1
1	0	1
0	1	1
1	1	0

This column also describes $\overline{A}+\overline{B}$

A	B	$\overline{A}$	$\overline{B}$	A+B
0	0	1	1	0
1	0	0	1	1
0	1	1	0	1
1	1	0	0	1

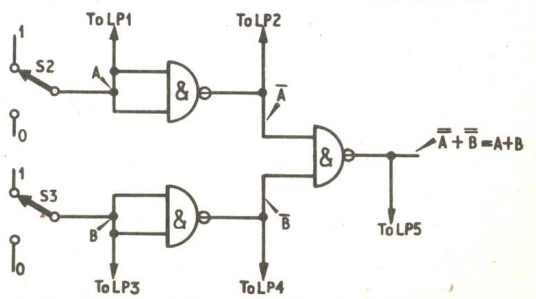

Fig. 4.2. OR from NAND logic.

NEW DEVICES ...APPLICATIONS

I.C. TRIAC CONTROL

In this section we present a selection of both new devices and applications, with news of applications developed for existing devices.

Generally only basic circuit details will be given sufficient for the experimenter to create his own equipment.

THE TRIAC is, without a doubt, one of the most convenient forms of a.c. power control yet devised. Provided one supplies it with correctly timed trigger pulses, it will control large amounts of power reliably without taking up too much space.

A variety of methods of supplying the trigger pulse have been developed but thus far these have involved discrete components. Now a new integrated circuit has been developed by Plessey specifically for triac control circuitry. Of necessity it is internally fairly complex as can be seen from the block schematic of Fig. 1.

It includes an amplifier, capacitor charge and discharge control circuitry, a comparator, a voltage stabilizer, a zero crossing detector and a triac firing circuit.

The basic function performed by this SL440 as the device is identified is in phase control circuits in which the power in the load depends on the phase angle or point on the a.c. cycle, at which the triac is fired. The extra facilities offered by the SL440 enable various circuits to be implemented with the bare minimum of external discrete components.

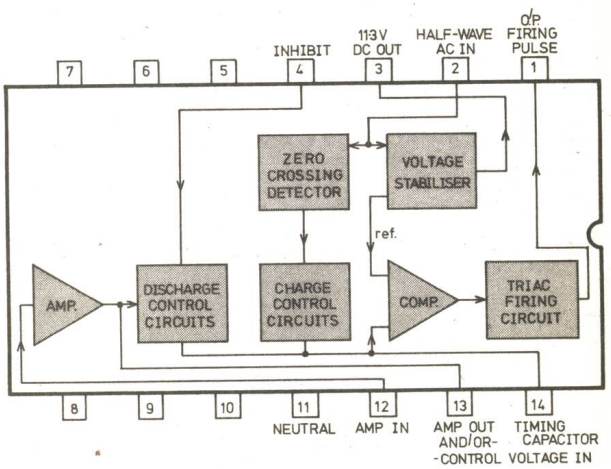

Fig. 1 Block schematic diagram of the SL440

TIMING CIRCUIT

The SL440 contains a timing circuit with a period determined by external control voltages. It is the timing circuit's period which determines exactly when in each half cycle of the mains power supply the triac is fired.

This is illustrated diagrammatically in Fig. 2. Whenever the mains power supply crosses through zero volts,

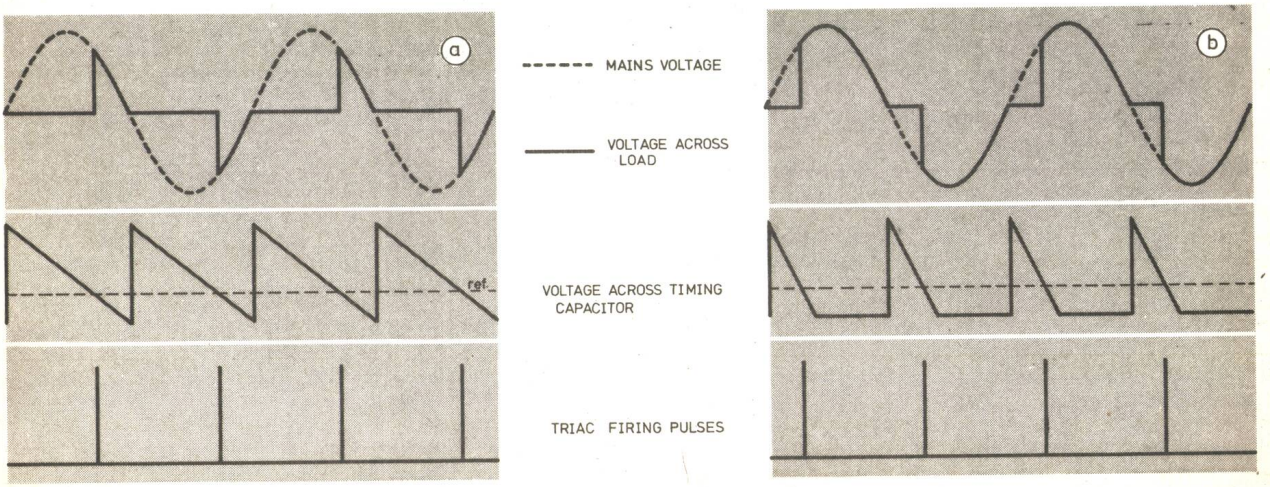

Fig. 2 (a) When the voltage across the timing capacitor falls below the on-chip reference voltage a triac firing pulse is generated. (b) When the capacitor is discharged more quickly, more power is applied to the load

either in the positive or negative direction, a capacitor external to the i.c., but connected to it, is rapidly charged.

During the following half cycle the capacitor discharges at a rate determined by an external control voltage until the voltage across the capacitor falls to a level set within the i.c. When this occurs a pulse is generated which fires the triac.

In Fig. 2a the effect of quite a long timing period is illustrated. As the mains power supply crosses through zero the timing capacitor connected to pin 14 is charged. During each half cycle the capacitor discharges at a constant rate until the voltage across it reaches the same value as the reference when a triac firing pulse is generated.

In the illustration the dotted sinewave represents the mains supply while the solid line indicates the voltage across the load.

integrator in automatic lamp dimmer circuits and the like.

VOLTAGE STABILIZER

The SL440 contains a voltage stabilizer which performs three main functions. Firstly, it provides a stabilized 11·3 V supply for the rest of the chip; it also provides the reference voltage against which the voltage across the timing capacitor is compared and, finally, it provides a stabilized 11·3 V supply for circuitry external to the chip. However, the current available for off-chip circuits is extremely limited and must not be allowed to exceed 3 mA.

MAINS INPUT

The SL440 does not require a d.c. power supply in the conventional sense. Power input is obtained directly from the mains *via* a diode and series dropping resistor. With

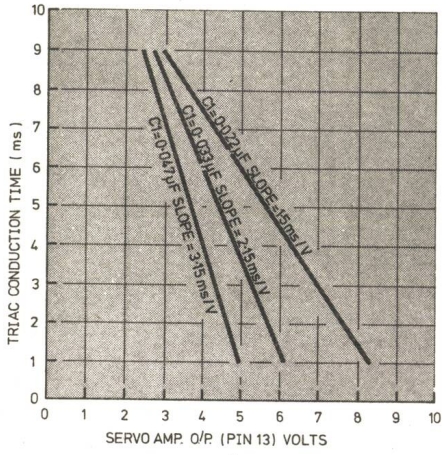

Fig. 3 Showing triac conduction time for different values of timing capacitor and different voltages at pin 13

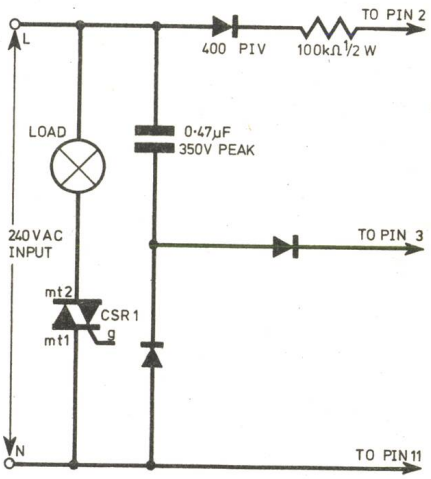

Fig. 4 A circuit to replace the heat dissipating mains dropper resistor

DISCHARGE RATE

The external control voltage setting the discharge rate would normally range from 3 to 8 V, this being sufficient to alter the power in the load from zero to full power. An inverse law applies in that the lower the control voltage the higher the power in the load. The actual power in the load for a given control voltage is also dependent on the value chosen for the timing capacitor.

The larger the capacitor's value the greater the power applied to the load for a given control voltage. These relationships can be seen in Fig. 3, which plots the control voltage against triac conduction time for three different values of timing capacitors.

ON-CHIP AMPLIFIER

The SL440 integrated circuit incorporates an amplifier, called a servo amplifier by Plessey, which can be used to produce the control voltage. It can really be looked at as a grounded emitter amplifier with a beta of about 2,000 and a 2 kΩ resistor in the emitter. It is necessary to connect a suitable external load resistor.

The amplifier is useful in motor speed control as an error voltage amplifier or it can be connected as an

the values recommended by Plessey, the half-wave rectified input has a peak value of about 60 or 70 V. The series resistor (6·8 kΩ, 5 W) can be eliminated with the circuit shown in Fig. 4.

The half-wave rectified input, as well as supplying power, also allows the chip to detect the zero crossings of the mains. Each time a zero crossing is detected the circuitry on the chip charges the external timing capacitor.

OUTPUT AND INHIBIT

When the voltage across the timing capacitor falls below that of the reference voltage supplied to the comparator from the voltage stabilizer, an output triac firing pulse is generated. This pulse is 50 μS wide and must not be allowed to exceed 60 mA. However, this will be more than sufficient for most applications.

An inhibit input is provided which, when connected to the common line (or less than 5 V), prevents any firing pulses from being generated. This input could be used in conjunction with current sensing circuits for protection purposes.

ALL OUR PRICES INCLUDE V.A.T.

BSR LATEST SUPERSLIM STEREO & MONO

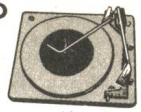

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250V
Size 13½ × 11½in.
Above motor board 3¼in. below motor board 2½in.

with STEREO and MONO XTAL **£8·25** Post 25p.

PORTABLE PLAYER CABINET

Modern design. Black rexine covered. Silver front grille. Chrome fittings.
Motor board cut for BSR deck **£4·50** Post 25p

E.M.I. WOOFER AND TWEETER KIT £5·75

Post 25p.

Available separately
Woofer £4·25 Tweeter £1·90
Comprising a fine example of a Woofer 10¾ × 6¾in. with a massive Ceramic Magnet, 44oz. Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3¼in. square has a special lightweight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.

Impedance Standard	8 ohms
Maximum Power	12 watts
Useful Response	35 to 18,000 c/s
Base Resonance	45 c/s

SUITABLE ENCLOSURE 20 x 13 x 9in.
MODERN GROOVED FRONT DESIGN, TEAK FINISH **£9·90** Post 25p

SPECIAL OFFER!

SMITH'S CLOCKWORK 15 AMP TIME SWITCH
Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Two types available 0 to 60 minutes Type A or 0 to 6 hours Type B. Makers last list price £4·50. Brand new and fully guaranteed. Fully insulated.
OUR PRICE £1·65. P. & P. 15p or £3 pair.
(PLEASE STATE TYPE A OR B WHEN ORDERING)

WEYRAD P50 — TRANSISTOR COILS

RA2W Ferrite Aerial	72p	Spare Cores	3p
Osc. P50/1AC	33p	Driver Trans. LFDT4	58p
I.F. P50/2CC 470 kc/s	36p	Printed Circuit, PCA1	58p
3rd I.F. P50/3CC	36p	J.B. Tuning Gang	65p
P51/1 or P51/2	36p	Weyrad Booklet	10p
P50/3V	36p	OPT1	58p

Mullard Ferrite Rod 8 × ⅜in, 20p. 6 × ½in, 20p.

VOLUME CONTROLS

5 K. ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p.
STEREO L/S 55p. D.P. 75p.
Edge 5K.S.P. Transistor 25p.

80 Ohm Coax 4p yd.

BRITISH AERIALITE
AERAXIAL-AIR SPACED
40 yd, £1·40; 60 yd, £2.
FRINGE LOW LOSS 10p yd
Ideal 625 and colour

8in. or 10in. ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50–16,000 c/s. Bass resonance 55 c/s. 8 ohm impedance, 8in 10 watts, 10in 12 watts music power. **£3·75** Post 25p

E.M.I. 13½ × 8in. SPEAKER SALE!

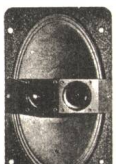

With twin tweeters. And crossover. 10 watt. State 3 or 8 or 15 ohm. As illustrated. **£4·50** Post 25p

With flared tweeter cone and ceramic magnet. 10 watt. Bass res. 45-60 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 25p **£2·75**

Bookshelf Cabinet 16 × 10 × 9in. **£5·50** Post 25p

BRITISH MADE STEREO MULTIPLEX DECODER

£6.95 Post 15p

Brand New. 7 transistors Plus integrated circuit. Fibre-Glass printed circuit board. Size 2½ × 6½ × ¾. Pre-Aligned. Complete with stereo beacon indicator. 12V d.c. operation. 400mV Output for 100mV Input. Full instructions for any FM Tuner. Some technical experience essential.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2½in sides 6 × 4in 45p; 8 × 6in 53p; 10 × 7in 65p; 12 × 8in 85p; 14 × 9in 90p; 16 × 6in 90p; 12 × 3in 50p; 16 × 10in £1.
ALUMINIUM BOX 6 × 4 × 4in 80p.
ALUMINIUM PANELS 18 s.w.g. 6 × 4in 9p; 8 × 6in 15p; 14 × 3in 16p; 10 × 7in 19p; 12 × 5in 20p; 12 × 8in 28p; 16 × 6in 28p; 14 × 9in 34p; 12 × 12in 40p; 16 × 10in 50p.
PAXOLIN PANEL 10 × 8in 15p.

ANOTHER R.C.S. BARGAIN!

4 TRANSISTOR MONO AMPLIFIER

Powerful 3 watt output, 15 ohm. AC mains operated with transformer. 3-Controls, volume, treble, bass and On/Off switch with knobs. Ready made on printed circuit board. Fused inputs and outputs. Famous make, size 8in wide × 4in deep × 3in high. **£5·95** Post 25p
Suitable 7"×4" speaker, £1.

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less
PLEASE STATE VOLTAGE REQUIRED. **£2·20** Post
Details S.A.E. Size 3½ × 1½ × 1¼in. 15p

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or H.T. line 200-300V d.c. operation. Size: 1¾ x 1¼ x ¾ in. Response 25 c/s to 25 kc/s, 26 dB gain. For use with valve or transistor equipment. **99p** Post 10p
Full instructions supplied. Details S.A.E.

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 13¾ × 10 × 3¾in. Player unit clips to loudspeakers making it extremely compact, overall size only 13¾ × 10 × 8¼in. 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls. 240V AC mains. Attractive Brown colour, weight 13 lb. **£25** Plus 85p carriage.

BRITISH FM/VHF TUNING HEART

88 to 108 M/CS British made. 2 Transistors ready aligned requires 10·7 M/CS I.F. Complete with tuning gang. Connections supplied but some technical experience essential. **Our price £3·95** Post 20p

MAINS TRANSFORMERS

	All post 25p each
Eagle MT12 12-0-12V 50mA	90p
250-0-250 80mA 6·3V 3·5A, 6·3V 1A, or 5V 2A	£2·50
350-0-350 80mA, 6·3V 3·5A, 6·3V 1A, or 5V 2A	£3
300-0-300V 120mA, 6·3V 4A C.T.; 6.3V 2A	£3·25
MINIATURE 200V, 20mA, 6·3V 1A, 2½ × 2½ × 2in	75p
MIDGET 220V 45mA, 6·3V 2A, 2½ × 2½ × 2in	90p
HEATER TRANS. 6·3V 3A	60p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2A, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V	£2·25
1A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V	£2·25
2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V	£3·25
5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V	£8·75
3A, 5, 8, 13V £1·00, Ditto 5A	£1·20
3A, 5, 8, 10, 13V, 5-0-5V £1·30, Ditto 5A	£1·50
6–0–6 500 mA	90p
9V 1 amp	95p
12V 300 mA	75p
12V 500 mA	85p
12V 750 mA	95p

AUTO TRANSFORMERS. 115V to 230V or 230V to 115V. 150W £2·25; 500W £6·25; 750W £10; 1000W £15.
CHARGER TRANSFORMERS. Input 200/250V. for 6 or 12V, 1½A, £1·50; 2A, £1·80; 4A, £2·50.
BATTERY CHARGERS. 1½A £2; 3A £3; 4A £4; 5A £4·50.

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 3A. 720W. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. Famous make. (Value £19) OUR PRICE **£10** Carr. 50p
Can be used 800W auto transformers 240-110V.
IDEAL FOR COLOUR T.V.

NEW ELECTROLYTIC CONDENSERS

2/350V	14p	250/25V	14p	50+50/350V	35p
4/350V	14p	500/25V	20p	60+100/350V	58p
8/450V	14p	1000/25V	35p	32+32/250V	18p
16/450V	15p	1000/50V	47p	32+32/450V	33p
32/450V	20p	8+8/450V	18p	350+50/325V	50p
25/25V	10p	8+16/450V	20p	32+32+32/350V	43p
50/50V	10p	16+16/450V	25p	100+50+50/350V	48p
100/25V	10p	32+32/350V	25p		

LOW VOLTAGE ELECTROLYTICS.
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p.
1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p.
2000mF 6V 25p; 25V 42p; 50V 57p.
2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.
5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.

CERAMIC, 1pF to 0·01mF, 4p. Silver Mica 2 to 5000pF, 4p.
PAPER 350V-0·1 4p, 0·5 13p; 1mF 15p; 2mF 150V 15p.
500V-0·001 to 0·05 4p; 0·1 5p; 0·25 8p; 0·47 25p.
SILVER MICA. Close tolerance 1%. 2·2-500pF 8p; 560-2,200pF 10p; 2,700-5,600pF 20p; 6,800pF-0·01, mfd 30p each.
TWIN GANG. "0-0" 208pF+176pF, 65p; 500pF standard 45p.
365pF+365pF with 25pF+25pF, Slow motion drive 50p; SHORT WAVE SINGLE. 10pF, 30p, 25pF, 55p, 50pF, 55p.
NEON PANEL INDICATORS 250V AC/DC. Amber 20p.
RESISTORS. ¼W, ⅓W, 1W, 20% 1p; 2W, 5p. 10Ω to 10M.
HIGH STABILITY. ½W 2% 10 ohms to 6 meg., 10p.
Ditto 5%. Preferred values 10 ohms to 10 meg., 4p.
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 10p each; 0·5 ohm to 8·2 ohms 10p.
TAPE OSCILLATOR COIL Valve type 35p.

ALL MODELS "BAKER SPEAKERS" IN STOCK
Hi Fi Enclosure Manual containing 20 plans, designs, crossover data and cubic tables. 42p Post Free

BAKER MAJOR 12" £9·90

Post 25p

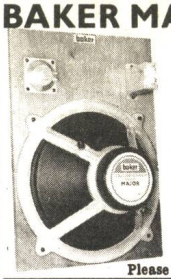

30-14,500 c/s, 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 20W. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£12·50**
Please state 3 or 8 or 15 ohms. Post 25p

BAKER "BIG-SOUND" SPEAKERS Post 25p

'Group 25'	'Group 35'	'Group 50'
12in. 25W **£8·80**	12in. 35W **£9·90**	15in. 50W **£22**
3 or 8 or 15 ohm	3 or 8 or 15 ohm	8 or 15 ohm

TEAK VENEERED HI-FI SPEAKER CABINETS.

For 12in or 10in dia. speaker	20 × 13 × 9in, £9·90. Post 25p.
For 13 × 8in or 8in speaker	16 × 10 × 9in, £5·50. Post 25p.
For 8 × 5in speaker	16× 8 × 6in, £4·40. Post 25p.
For 6in and Tweeter	12× 8 × 6in. £4·00. Post 25p.

LOUDSPEAKER CABINET WADDING 18in wide, 15p ft.

GOODMANS 6½in. HI-FI WOOFER

8 ohm. 10W. Large ceramic magnet.
Special Cambric cone surround.
Frequency response 30-12,000 c/s. Ideal P.A. **£4**
Columns. Hi-Fi Enclosure Systems, etc.
Suitable Cabinet 12 × 8 × 6 £4 Suitable Tweeter £2

ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 3¼ × 3¼ × 2in deep. Rating 10W, 3 ohm or 15 ohm models. **£1·90** Post 10p.
Crossover 95p

SPEAKER COVERING MATERIALS. Samples Large S.A.E.
Horn Tweeters 2-16kc/s, 10W 8 ohm or 15 ohm £1·95.
De Luxe Horn Tweeters 2-18kc/s, 15W, 15 ohm £3.
CROSSOVERS, TWO-WAY 3,000 c/s 3 or 8 or 15 ohm 95p.
LOUDSPEAKERS P.M. 3 OHMS. 7x4in., £1·25; 6¼in., £1·50; 8 × 5in, £1·60; 10in, £2·00; 8in, £1·75; 10 × 6in, £1·90.
SPECIAL OFFER! 80 ohm, 2¼in, 2¼in; 35 ohm, 2in, 3in, 25 ohm, 2½in dia., 3in dia., 5in dia. **£1** EACH TYPE
15 ohm, 3¼in dia, 6 × 4in, 7 × 4in, 8 × 5in.
3 ohm, 2¼in, 2¼in, 3¼in, 5in dia. 6 × 4in 8 ohms £1·50.
RICHARD ALLAN TWIN CONE LOUDSPEAKERS, 8in. diameter 4W; 10in diameter 5W £2·20; 12in diameter, 6W, £2·50; 3 or 8 or 15 ohm models, £2·20 each. Post 15p.
VALVE OUTPUT TRANS. 25p; MIKE TRANS. 50:1 25p.
5 WATT MULTI-RATIO, 3, 8 and 15 ohms 80p.
Mike trans. mu metal 100:1 £1·25.

MAJOR 100 WATT ALL PURPOSE GROUP AMPLIFIER

All purpose transistorised.
Ideal for Groups, Disco and P.A.
4 inputs speech and music. 4 way mixing. Output 8/15 ohm. a.c. Mains. Separate treble and bass controls. Guaranteed. Details SAE. **£49** Carr. £1·00

BARGAIN AM TUNER. Medium Wave. Transistor Superhet, Ferrite aerial. 9 volt. **£4·95**

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9V. **£3·95**

STEREO VERSION OF ABOVE **£5·95**

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control and on/off switch, 18 volt. **£4·50**

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p. OUTLET BOXES. SURFACE OR FLUSH 25p.
BALANCED TWIN RIBBON FEEDER 300 ohms. 5p yd.
JACK SOCKET Std. open-circuit 14p, closed circuit 23p; Chrome Lead-Socket 45p. Phono Plugs 5p. Phono Socket 5p.
JACK PLUGS Std. Chrome 15p; 3·5mm Chrome 12p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10. DIN SOCKETS Lead 3-pin 18p; 5-pin 15p. DIN PLUGS 3-pin 18p; 5-pin 25p.
VALVE HOLDERS, 5p; CERAMICS 8p; CANS 5p.

DELUXE 4 POLE MOTOR

1,400 r.p.m. 42 Watt, spindle 1½" × 7/32", size 3½" × 3". As illustrated. Post 25p. **£1·95**

TWO RPM GEARED MOTORS 95p Post 25p.

240V A.C. mains.
Ideal for displays/disco light wheels.

E.M.I. GRAM. MOTOR. 120V or 240V a.c. **£1**
2,400 r.p.m. 2 pole 70mA. Size 2⅞ × 2½ × 2⅜in.
Post 25p.

RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD, CROYDON

Open 9-6. Wed. 9-1, Sat. 9-5 (Closed for lunch 1.15-2.30)

Illustrated Colour Brochure, Radio Books and Component Lists 10p. (Minimum posting charge 15p.) Buses 50, 68, 159. Rail Selhurst. Tel. 01-684-1665

YATES ELECTRONICS

(FLITWICK) LTD.

ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK
BEDFORD

C.W.O. PLEASE. POST AND PACKING PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the components listed will be sent free on request. 10p stamp appreciated.

OPEN ALL DAY SATURDAYS

ALL PRICES SUBJECT TO V.A.T.

RESISTORS

¼W Iskra high stability carbon film—very low noise—capless construction. ¼W Mullard CR25 carbon film—very small body size 7·5 x 2·5mm. ½W 2% ELECTROSIL TR5

Power watts	Tolerance	Range	Values available	Price 1–99	Price 100+
¼	5%	4·7Ω–2·2MΩ	E24	1p	0·8p
¼	10%	3·3MΩ–10MΩ	E12	1p	0·8p
½	2%	10Ω–1MΩ	E24	3·5p	3p
½	10%	1Ω– 3·9Ω	E12	1p	0·8p
½	5%	4·7Ω–1MΩ	E12	1p	0·8p
4	10%	1Ω–10Ω	E12	6p	5·5p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0·5 watt 5% Iskra resistors 5 off each value 4·7Ω to 1MΩ. E12 pack 325 resistors **£2·40**. E24 pack 650 resistors **£4·70.**

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log ¼W, lin ½W). Single, **12p.** Dual gang (stereo), **40p.** Single D.P. switch **24p.**

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0·1 matrix). Sub-miniature 0·1W, **5p** each. Miniature 0·25W, **6p** each.

TRANSISTORS

AC107	15p	AF125	20p	BD132	75p	OC28	50p	2N3702	13p
AC126	12p	AF126	20p	BD133	75p	OC35	50p	2N3703	12p
AC127	12p	AF127	20p	BFI15	25p	OC42	12p	2N3704	13p
AC128	12p	AF139	32p	BFI73	20p	OC44	12p	2N3705	12p
AC131	12p	AFI78	32p	BFI77	28p	OC45	12p	2N3706	11p
AC132	12p	AFI80	40p	BFI78	32p	OC70	12p	2N3707	12p
AC176	12p	AFI81	40p	BFI79	32p	OC71	12p	2N3708	10p
AC187	22p	BC107	9p	BFI80	32p	OC72	12p	2N3709	11p
AC188	22p	BC108	9p	BFI81	32p	OC81	12p	2N3710	11p
AD140	50p	BC109	9p	BFI94	15p	OC82D	12p	2N3711	11p
AD149	45p	BC147	13p	BFI95	15p	2N2904	20p	2N4062	12p
AD161	33p	BC148	13p	BFI97	15p	2N2926R	9p	40360	35p
AD162	36p	BC149	13p	BF200	32p	2N2926O	9p	40361	35p
AFI14	20p	BC157	14p	BFY50	20p	2N2926Y	9p	40362	40p
AFI15	20p	BC158	14p	BFY51	20p	2N2926G		40408	40p
AFI16	20p	BC159	14p	BFY52	20p		10p	ZTX302	15p
AFI17	20p	BC187	22p	BU105	225p	2N3054	58p	ZTX500	15p
AFI17	38p	BD131	75p	OC26	45p	2N3055	60p	ZTX502	20p

ZENER DIODES

400mW 5% 3·3V to 30V, **12p.**

WIRE WOUND POTS, 3W, 10, 25, 50Ω and decades to 100kΩ, 35p.

DIODES

RECTIFIER				SIGNAL	
BY127	1250V	1A	12p	OA85	7p
BZY10	800V	6A	25p	OA90	5p
BZY13	200V	6A	20p	OA91	5p
IN4001	50V	1A	7p	OA202	7p
IN4004	400V	1A	8p	IN4148	5p
IN4007	1000V	1A	10p	BA114	8p

BRUSHED ALUMINIUM PANELS

12in × 6in=**25p**; 12in × 2½in=**10p**; 9in × 2in=**7p**

SLIDER POTENTIOMETERS

86mm × 9mm × 16mm, length of track 59mm. SINGLE 10K, 25K, 100K log. or lin. **40p.** DUAL GANG, 10K + 10K etc. log. or lin. **60p.** KNOB FOR ABOVE **12p.** FRONT PANEL **65p.** 18 Gauge panel 12in × 4in with slots cut for use with slider pots. Grey or matt black finish complete with fixings for 4 pots.

THERMISTORS

VA1055S	15p
VA1066S	15p
VA1077	13p
R53	£1·35

THYRISTORS

2N5060 50V 0·8A **30p**, 2N5064 200V 0·8A **47p**, CRS1/40 400V 1A **25p**, 106F 50V 4A **40p**, 106D 400V 4A **55p.**

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0·001μF, 0·0015μF, 0·0022μF, 0·0033μF, 0·0047μF, **2½p.** 0·0068μF, 0·01μF, 0·015μF, 0·022μF, 0·033μF, **3p.** 0·047μF, 0·068μF, 0·1μF, **4p.** 0·15μF, **6p.** 0·22μF, **7½p.** 0·33μF, **11p.** 0·47μF, **13p.**
160V: 0·01μF, 0·015μF, 0·022μF, 0·033μF, 0·047μF, 0·068μF, **3p.** 0·1μF **3½p.** 0·15μF **4½p.** 0·22μF, **5p.** 0·33μF, **6p.** 0·47μF, **7½p.** 0·68μF, **11p.** 1·0μF, **13p.**

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0·01μF, 0·015μF, 0·022μF, **3p.** 0·033μF, 0·047μF, 0·068μF, **3½p.** 0·1μF, **4p.** 0·15μF, 0·22μF, **5p.** 0·33μF, **6½p.** 0·47μF, **8½p.** 0·68μF, **11p.** 1·0μF, **13p.** 1·5μF, **20p.** 2·2μF, **24p.**

MYLAR FILM CAPACITORS 100V

0·001μF, 0·002μF, 0·005μF, 0·01μF, 0·02μF, **2½p.** 0·04μF, 0·05μF, 0·068μF, 0·1μF, **3½p.**

CERAMIC DISC CAPACITORS

100pF to 10,000pF, **2p** each.

ELECTROLYTIC CAPACITORS—MULLARD 015/6/7 RANGE REPLACES C426, C457 RANGES.

(μF/v) 1·0/63, 1·5/63, 2·2/63, 3·3/63, 4·7/63, 6·8/40, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33/6·3, 33/40, 47/4, 47/10, 47/25, 47/40, 47/63, 68/6·3, 68/16, 100/4, 100/10, 100/25, 100/40, 150/6·3, 150/16, 150/25, 220/4, 220/10, 220/16, 330/4, 330/10, 470/6·3, **5p** each. 68/63, 150/40, 220/25, 330/16, 470/10, 680/6·3, 1,000/4, **9p.** 100/63, 150/63, 220/40, 470/25, 680/16, 1,000/10, 1,500/6·3, **12p.** 220/63, 470/40, 680/25, 1,000/16, 1,500/10, 2,200/6·3, **15p.** 330/63, 680/40, 1,000/25, 1,500/16, 2,200/10, 3,300/6·3, 4,700/4, **18p.**

SOLID TANTALUM BEAD CAPACITORS 12p

0·1μF	35V	2·2μF	35V	22μF	16V
0·22μF	35V	4·7μF	35V	33μF	10V
0·47μF	35V	6·8μF	25V	47μF	6·3V
1·0μF	35V	10μF	25V	100μF	3V

VEROBOARD

	0·1	0·15
2½ × 3¾	22p	16p
2½ × 5	24p	24p
3¾ × 3¾	24p	24p
3¾ × 5	27p	27p
17 × 2½	75p	57½p
17 × 3¾	100p	78p
17 × 5 (plain)	—	82p
17 × 3¾ (plain)	—	60p
17 × 2½ (plain)	—	42p
2½ × 5 (plain)	—	12p
2½ × 3¾ (plain)	—	11p
Pin insertion tool	52p	52p
Spot face cutter	42p	42p
Pkt. 50 pins	20p	20p

JACK PLUGS AND SOCKETS

Standard screened	18p	2·5mm insulated	8p
Standard insulated	12p	3·5mm insulated	8p
Stereo screened	35p	3·5mm screened	13p
Standard socket	15p	2·5mm socket	8p
Stereo socket	18p	3·5mm socket	8p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin **Plug 12p. Socket 8p.** 4 way screened cable, 15p/metre. 6 way screened cable **22p**/metre.

BATTERY ELIMINATOR £1·50

9V mains power supply. Same size as PP9 battery.

LARGE (CAN) ELECTROLYTICS

1600μF	64V	74p	2500μF	64V	80p	4500μF	16V	50p
2500μF	40V	74p	2800μF	100V	£2·60	4500μF	25V	£1·68
2500μF	50V	58p	3200μF	16V	50p	5000μF	50V	£1·10

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0·01μF	10p	0·047μF	13p	0·22μF	20p
0·022μF	12p	0·1μF	13p	0·47μF	22p

POLYSTYRENE CAPACITORS 160V 2½%

10pF to 1,000pF E12 Series Values **4p each.**

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector.
Detector GDI, **£2.** Kit of parts for detectors including GDI and P.C. board but excluding case. Mains operated detector **£5·20.** 12 or 24V battery operated audible alarm **£7·30.** As above for PP9 battery, **£6·40.**

PRINTED BOARD MARKER 97p

Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to dry, and immerse the board in the etchant. On removal the circuit remains in high relief.

LARGE RANGE ITT/TEXAS IC's NOW IN STOCK

PRICES ARE CALCULATED ON TOTAL NUMBER ORDERED REGARDLESS OF MIX

	1–11 p	12–24 p	25–99 p	100+ p
7400	18	16	14	13
7401	18	16	14	13
7402	18	16	14	13
7403	18	16	14	13
7404	20	18	16	14
7405	20	18	16	14
7406	50	45	40	35
7407	56	50	44	38
7408	36	30	27	23
7409	36	30	27	33
7410	18	16	14	13
7411	23	21	20	18
7412	36	30	27	23
7413	34	28	26	22
7416	45	43	39	34
7420	18	16	14	13
7421	36	30	27	23
7426	32	29	23	20
7430	20	18	16	14
7432	40	36	32	28
7440	20	18	16	14
7441	80	75	70	65
7442	80	75	70	65
7443	125	120	115	115
7447	175	165	150	120
7448	185	175	170	165
7450	18	16	14	13
7451	18	16	14	13
7453	18	16	14	13
7454	18	16	14	13
7460	18	16	14	13
7470	30	28	25	24
7472	30	28	27	23
7473	40	38	36	30
7474	40	36	32	28
7475	55	52	50	49
7476	40	36	32	30
7480	100	95	90	85
7481	125	115	110	105
7482	100	96	90	85
7483	100	97	95	92
7484	120	115	110	105
7485	250	245	240	230
7486	45	42	37	33
7490	75	67	60	52
7491A	100	92	85	79
7492	75	70	65	60
7493	75	68	60	52
7494	95	90	85	80
7495	105	100	95	90
7496	100	95	90	85
74100	250	240	235	230
74118	100	82	73	64
74121	43	40	38	36
74141	100	95	90	85
74145	150	140	135	130
74150	330	280	250	220
74151	110	100	95	89
74153	120	110	105	95
74154	200	180	170	160
74155	150	120	100	86
74156	130	120	100	96
74180	155	136	112	105
74190	195	190	185	180
74191	195	190	185	180
74192	200	190	180	164
74193	200	180	170	150
74196	200	190	180	170
74197	200	195	180	170

LINEAR IC's

709	14 pin DIL	32p
741	8 pin DIL	34p
741	14 pin DIL	28p
723	14 pin DIL	95p
747	14 pin DIL	85p
748	8 pin DIL	35p
DIL socket,	14 pin and 16 pin	16p

Typical APPLICATIONS

LIGHT DIMMER

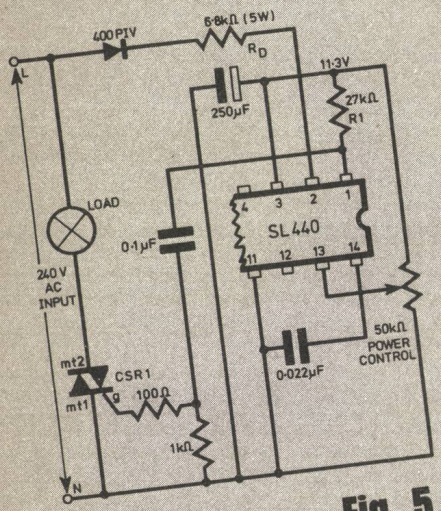

Fig. 5.

AUTO LIGHT

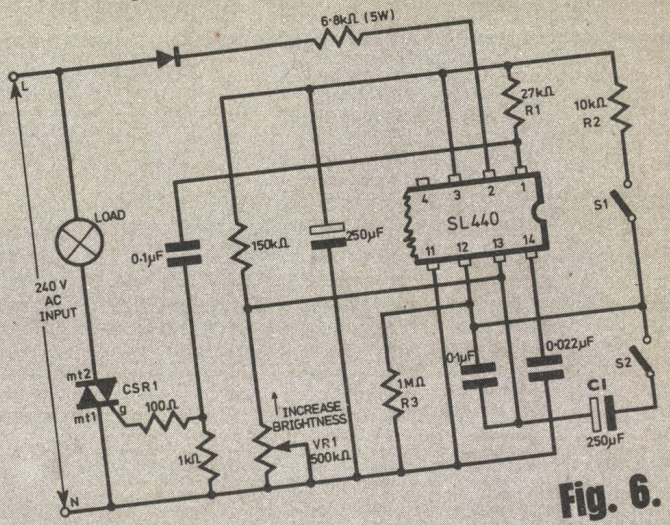

Fig. 6.

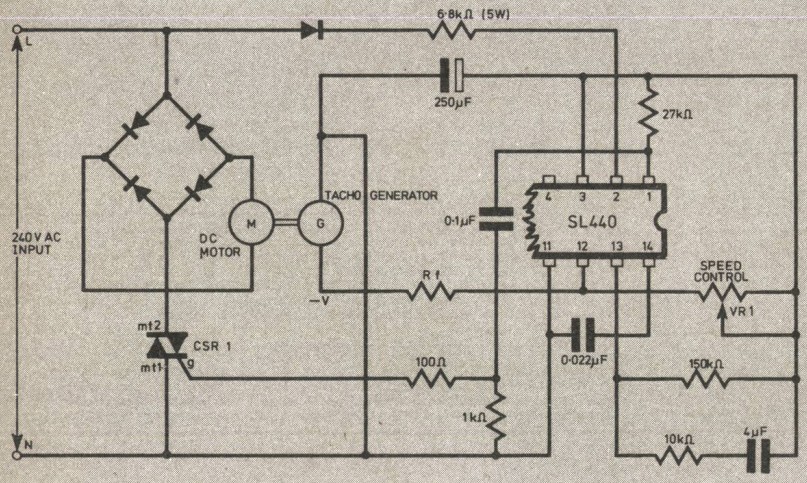

SPEED CONTROL

Fig. 7.

APPLICATIONS

Numerous applications for the device will have probably already suggested themselves to the reader. Plessey have developed several circuits.

Fig. 5 shows the SL440 used in a basic lamp dimmer circuit with the minimum of external components. Resistor R1 provides the triac firing circuit with its load.

The potentiometer forms a potential divider across the 11·3 V supply and varies the light output by varying the voltage at pin 13. The input impedance at this point is very high and current flow can be measured in nA. The internal amplifier is not employed in this circuit.

The automatic lamp fader circuit of Fig. 6 is a variation on the same theme, the main difference being that the internal amplifier can be switched to perform an integration of the control voltage.

When S1 is open, the brilliance of the lamp is set by RV1. When S1 is closed, the positive potential derived from the divider R2, R3 is presented to the input causing the lamp to give full output.

If now S2 is closed and S1 is opened, the lamp will gradually reduce in brightness until it reaches the brightness level corresponding to the setting of RV1. The time taken for the fade to occur will depend on the value of the integration capacitor C1. With the value shown, this will be between 20 and 30 minutes.

A motor speed control circuit is shown in Fig. 7. This is basically similar to the previous circuits except that one leg of the potential divider is formed by a tachometer generator driven by the motor.

The device is available from SDS Components Ltd., Hilsea Trading Estate, Portsmouth, Hants. at £2·08p for one-off, £1·82 for 25 off. ★

D. TROTMAN (SDS COMPONENTS)

Readout—
A SELECTION FROM OUR POSTBAG

Correspondents wishing to have a reply must enclose a stamped addressed envelope. We regret we are unable to guarantee a reply on matters not relating to articles published in the magazine. Technical queries cannot be dealt with on the telephone.

THE TOPICAL SYNTHESISER

Sir—In answer to Mr. Baily's letter (last month)—he admits that the building of a stable, accurate log law circuit is difficult. I would tend to go further and say that for the average amateur constructor the task is almost impossible. This statement is in no way intended as a slight to the amateur but serves to highlight a situation which seems to be occurring all too often these days. Although there are many more avenues for the amateur to explore than there were a few years ago it is frequently found that exploitation of a particular circuit or function requires the possession of a bewildering array of test equipment and the technical expertise to interpret their respective readings.

This situation is very much in evidence in the case of designing and building a log law v.c.o. as Mr. Baily has testified. There is little point in publishing designs for such circuits since the problems arise, not so much in the building, but in the final setting-up and matching. Thus, from this point of view alone, there is considerable justification in the presentation of a linear v.c.o. which can be built with a minimum of test equipment and which behaves, with few limitations, in an exactly determinable manner. I would like to underline the fact that the P.E. Synthesiser is very much an experimental project which has been designed, as far as possible, to allow the widest possible licence to the individual constructor for the incorporation of modifications and/or additions to the system. In the case of the v.c.o. the overall response is determined by the response of the "front-end" as it is in most commercially available units. Thus by changing the response of the front end only the circuit can be made to obey a variety of laws to suit the whim of the constructor and this without disturbing the settings of the oscillator section at all.

With regard to Mr. Baily's specific criticisms of the linear v.c.o. the following observations apply:

1. No chording facility. This is a perfectly valid criticism and without doubt is the major disadvantage of the linear v.c.o. Octave chords can be played however and the keyboard incorporates a harmony switch for this purpose. If the Synthesiser is to be used for *musique concrete* purposes the lack of chording facility is no disadvantage since a full range of four note chords may be set up and recorded as discrete sounds.

2. No variable keyboard pitch. Not strictly true since the keyboard oscillators have their own manual frequency control with which it is possible to vary the "spread" by about an octave either way. Since the keyboard oscillators are tuned an octave apart this effectively gives a register of seven octaves although the upper and lower ends are not tightly in tune due to the "non-logarity" of the oscillators.

3. Difficulties in tuning . . . Again not entirely valid. The variation in programming voltage from end of the keyboard to the other is only about 65 millivolts (see Fig. 3.4.) consequently there are only two values of fixed resistor and one value of preset per key. The values of fixed resistor are chosen such that the majority of presets are operating within the middle 60 per cent of their rotation. There is thus not such a vast range of adjustment as Mr. Baily anticipates. Furthermore, and to the advantage of this particular system, the resistive value set-up during tuning affects only one note whereas in the series chain system used with log v.c.o.s any one resistor going unstable will affect all the others downstream in the chain.

4. Poor frequency stability. Voltage and resistance wander can scarcely be cited as being problematical in this respect since they are relatively easy to correct. The use of a well regulated power supply together with adequate decoupling and the use of high stability resistors in the frequency determining networks will largely dispose of the problem. Mr. Baily correctly pinpoints the problem of thermal drift with the linear v.c.o. circuit as published.

On test at an ambient temperature of 18°C and with the oscillator running at 256Hz rapid cycling between about 0°C (induced with a freezer aerosol) and 25°C (close proximity 100 watt lamp) resulted in a variation in frequency of between 222Hz at 0°C and 312Hz at 25°C. This approximates to −10 per cent, +20 per cent on the basic frequency. On the other hand the oscillator in its case was monitored over a 48 hour period with a digital frequency meter and normal changes in day/night ambient temperatures resulted in frequency changes within ±2 per cent. Extreme changes in ambient temperatures are unlikely under what might be termed normal operating conditions and such light changes as do occur can be adequately compensated for by adjustment of the manual frequency bias on the oscillators.

5. Uneven swing in pitch control. There is no real answer to this one since Mr. Baily is correctly citing the characteristic of the linear circuit, i.e. the requirement for a progressively increasing programming voltage in order to maintain the same rate of change of frequency as frequency increases. I feel bound to say, however, that I have never noticed this as a problem.

Two final points are worth mentioning. Mr. Baily cites the increase in power required from the use of integrated circuits as opposed to discrete components. This is undoubtedly true and while there is probably a hard core of amateur constructors who enjoy the challenge of design there is a far larger group who build for the sake of building and whose principal requirement from their hobby is results. To this latter group the integrated circuit, in its many forms, represents a release from many of the problems associated with design and allows them to enjoy their hobby more fully as a result. The increase in power required is thus surely a small price to pay?

Finally, on the subject of price, I would be very interested to have full details of the range of Dewtron modules offering the same specification as the P.E. Sound Synthesiser at under £200.

D. Shaw.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0–260V
All Types from ¼ to 50 amp from stock.

SHROUDED TYPE

1 amp, £7·70	20 amp, £53·90
2·5 amp, £8·86	25 amp, £63·80
5 amp, £12·98	37·5 amp, £90·20
10 amp, £24·75	50 amp, £107·80
15 amp, £27·50	

2·5 amp OPEN TYPE

(Panel Mounting) ¼ amp, £5·28. 1 amp, £7·70. 2½ amp, £8·80. All carriage paid.

L.T. TRANSFORMERS

All primaries 220–240V

Type No.	Sec. Taps	Price
1	30, 32, 34, 36V at 5A	£5·50
2	30, 40, 50V at 5A	£7·92
3	10, 17, 18V at 10A	£5·83
4	6, 12V at 20A	£7·70
5	17, 18, 20V at 20A	£8·58
6	6, 12, 20V at 20A	£8·14
7	24A at 10A	£6·16
8	4, 6, 24, 32V at 12A	£8·47
9	6 and 12V at 10A	£4·51

PARVALUX TYPE SD19 230/250 VOLT A.C. REVERSIBLE GEARED MOTORS
30 r.p.m. 40 lb. ins. Position of drive spindle adjustable to 3 different angles. Ex-equipment. Tested and in first-class running order. A really powerful motor offered at a fraction of makers' price. **£7·48.**

PARVALUX TYPE SD2. 200/250 VOLT A.C./D.C. HIGH SPEED MOTOR
Speed 9,000 r.p.m. approx. or 3,200 r.p.m. if used with built-in governor, or variable speed over a wide range if used in conjunction with our Dimmer Switch, illustrated below. PRICE **£2·20.**

600 WATT DIMMER SWITCH. Easily fitted. Fully guaranteed by makers. Will control up to 600W of all lights except fluorescent at mains voltage. Complete with simple instructions. **£3·30.**

240V A.C. SOLENOID FLUID VALVE
Will handle liquids or gases up to 7 p.s.i. Forged brass body, stainless steel core and spring. ⅛in b.s.p. inlet/outlet. Precision made, British mfg. PRICE: **£2·09.**
Special quotation for quantity.
(New in makers' carton)

INSULATION TESTERS ***NEW!***
Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L.8in, W.4in, H.6in, weight 6lb. **1,000V,** 1,000 megohms, **£37·40. 500V,** 500 megohms, **£30·80.**

UNISELECTOR SWITCHES
NEW **4 Bank 25 Way,** 24V d.c. operation. **£7·04. 6 Bank 25 Way,** 24V d.c. **£8·14. 8 Bank 25 Way,** 24V d.c. operation. **£9·46.**

24-HOUR TIMER
Can be adjusted to give a switching delay of between 2 hrs. to 24 hrs. Driven by 200/250V A.C. synchronous motor. 15 amp c/o contacts. Mfg. Crater Controls Ltd. Supplied with scale calibrated 0-10 (2 hrs, per division). Brand New. **£2·20.**

HONEYWELL PROGRAMME TIMERS
240V. A.C. 5 r.p.m. motor. Each cam operating a c/o micro switch. Cams are individually variable, allowing inumerable combinations. Ideally suited for machinery control, automation, etc. Also in the field of entertainment, for chaser lights, animated displays, etc.
15 cam model **£6·60.**
10 cam model **£5·50.**

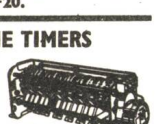

SIMPLE 12 CAM PROGRAMMER 240V A.C. 15 RPM MOTOR with 4 adjustable cams and 8 that may be profiled to individual requirements, **£4·18.**

36V 30 AMP. A.C. or D.C.
VARIABLE L.T. SUPPLY UNIT
INPUT 220/240V a.c.
OUTPUT CONTINUOUSLY VARIABLE 0–36V

Fully isolated. Fitted in robust metal case with Voltmeter. Ammeter Panel Indicator and handles. Input and output fully fused. Ideally suited for Lab. or Industrial use. **£77.**

MOTOROLA MAC 11/6 PLASTIC TRIAC 400 PIV. 10 AMP
Now available **EX STOCK.** Supplied with full data and applications sheet. Price **£1·21.**
Suitable DIAC **22p** each.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT
Speed adjustable 1 to 30 flash per sec. All electronic components including Xenon Tube and instructions **£7·26.**

NEW INDUSTRIAL KIT
Ideally suitable for schools, laboratories, etc. Speed adjustable 1-80 f.p.s.
Approx. ¼ output of Hy-Lyght. Price **£12·10.**

HY-LYGHT STROBE MK III
For use in large rooms, halls and utilises a silica tube, printed circuit. Speed adjustable 0-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. **£13·75.**

THE 'SUPER' HY-LYGHT KIT
Approx. four times the light output of our well proven Hy-Lyght strobe.

- Variable speed from 1-3 flash per sec.
- Reactor control circuit producing an intense white light. ONLY **£22·88.**

ROBUST, FULLY VENTILATED METAL CASE. For Hy-Lyght Kit including reflector **£4·95.** Super Hy-Lyght Kit including reflector **£8·25.**
7-inch POLISHED REFLECTOR
Ideally suited for above Strobe kits. Price **66p.**

RAINBOW STROBE FOUR LIGHT CONTROL MODULE
Will operate four of our Hy-Lyght or Super Hy-Lyght Strobes in either 1, 2, 3, 4 sequence; 2 + 2; or all together. Thoroughly tested and reliable. Complete with full connection instructions. Price: **£20·63.**
Send S.A.E. for details.

COLOUR WHEEL PROJECTOR
Complete with oil-filled colour wheel. 100 watt lamp. 200/240V AC. Features extremely efficient optical system. **£20·74.**

6 INCH COLOUR WHEEL
As used for Disco lighting effects, etc. Price **£5·72.**

BIG BLACK LIGHT
400Watt. Mercury vapour ultra violet lamp. Powerful source of u.v. Innumerable industrial applications also ideal for stage, display, discos, etc. P.F. ballast is essential with these bulbs. Price of matched ballast and bulb **£18·15.**
Spare bulb **£8·03.**

BLACK LIGHT FLUORESCENT U.V. TUBES
4ft. 40 watt. Price **£6·38.** (For use in standard bi-pin fluorescent fittings). MINI 9 in. 6 watt black light U.V. tube. **£1·60.** Complete ballast unit and holders for 9 in. tube. **£2·04.**

ELECTRONIC ORGAN KIT
Easy to build. Solid State. Two full octaves (less sharps and flats). Fitted hardwood case. Powered by two penlite 1½V batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes, Price **£3·50.**

FOOT SWITCH
Suitable for Motors, Drills, Sewing Machines, etc., etc. 5 amp. 250 volt. Price **£1.**

ALL PRICES INCLUDE V.A.T.
POSTAGE AND PACKING
Overseas orders ask for quote

Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.
25 WATT 10/25/50/100/250/500/1k/1·5k ohm **£1·10.**
50 WATT 1/5/10/25/50/100/250/500/1k/1·5k/2·5k/5k ohm **£1·54.**
100 WATT 1/5/10/25/50/100/250/500/1k/1·5k/2·5k/3·5k/5k ohm **£2·20.**
Black Silver Skirted knob calibrated in Nos. 1-9. 1¼in. dia. brass bush. Ideal for above Rheostats, **22p** each.

RELAYS

SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col.(1) Coil ohms	1	2	3	4
Col. (2) Working d.c. volts	52	4-6	6M	66p*
	52	4-6	4 c/o	88p*
	150	6-12	4 c/o	88p*
	185	8-12	6M	66p*
Col. 3 Contracts	410	10-18	4 c/o	77p*
	600	9-18	2 c/o	66p*
	700	16-24	4M 2B	66p*
Col. (4) Price	700	16-24	4 c/o	88p*
	700	15-35	2 c/o HD	77p*
	700	16-24	6M	66p*
HD = Heavy duty	700	6-12	1 c/o HD	55p*
	700	20-30	6 c/o	88p*
	1,250	24-36	4 c/o	66p*
*Incl. Base	2,500	36-45	6M	66p*
	2,400	30-48	4 c/o	55p
All prices incl. P. & P.	9,000	40-70	2 c/o	55p*
	15k	85-110	6M	55p*

12 VOLT D.C. RELAY 140 ohm coil
Type 1: Three sets c/o contacts rated at 5 amps. **88p**
(Similar to illustration below.)
Type 2: 4-8 volt, 3 c/o HD, 67 ohm coil. **88p.**

SPECIAL OFFER
700 ohm 4 c/o. Ex. new equipment. **£55** per 100 incl. bases (minimum 100).

230 VOLT A.C. 'DIAMOND H' RELAYS (Unused)
Three sets c/o contacts rated at 5 amps. PRICE: **66p.** (100 lots) **£44.**
24 volt A.C. 3 c/o **66p.** Incl. P. & P.

MINIATURE LATCHING RELAY
Manufactured by Clare-Elliott Ltd. Type F. 2 c/o permanent latching in either direction. Coil 1150 ohm, 15-30 Volt D.C. Size ⅞" high, ¾" wide, ¾" thick. Complete with 3" leads. New **77p,**

BLOWER UNIT
200-240 Volt A.C. Precision German built. Dynamically balanced, quiet, continuously rated, reversible motor. Consumption 60mA. Size 120 mm. dia. × 60 mm. deep. Price **£3·52.**

230V FAN ASSEMBLY
Continuously rated, special sealed bearing, removable aluminium blades. Price **£1·10.**

4 BANK 3c/o PUSH BUTTON ASSEMBLY
Black rectangular buttons, 5 units (min. order) **£1·10.**

"HONEYWELL" PUSH BUTTON, PANEL MOUNTING MICRO SWITCH ASSEMBLY
Each bank comprises a c/o rated at 10 amps 240V. A.C. Black knob 1 in. Fixing hole ⅛ in. ONE bank **33p;** TWO bank **44p;** THREE bank **61p.** Quot. for quantity.

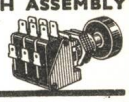

'HONEYWELL' LEVER OPERATED MICRO SWITCH
15 amps 250 volt A.C. c/ contacts. In maker's carton.
PRICE: 10 for **£2·09.**

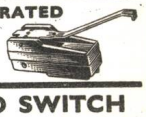

Very special offer **MICRO SWITCH**
5 amp c/o contacts. Fitted with removable metal panel assembly. Ex. P.O. 20 for **£1·10** (Min. order 20.)

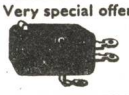

METER BARGAIN
BALANCE/LEVEL METERS
100-0-100 Micro Amp. Size 1½in + 1½in + ⅝in. Price only **83p.**

AMMETERS NEW! 2½in. Flush round. Available in D.C. Amps 1, 5, 15, 20 or A.C. Amps 5, 10, 15, 20, both types ***£1·98.** 0-300V. A.C. **£2·09.**

All Mail Orders—Callers—Ample Parking
Dept. PE6, 57 BRIDGMAN ROAD
CHISWICK, LONDON W4 5BB
Phone 01-995 1560
Showroom open Mon.-Fri.

SERVICE TRADING CO.

Personal callers only. Open Sat.
9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
Phone 01-437 0576

LOUDSPEAKER BARGAINS

Fane Pop 100W, 18", 8/15 ohm	£21·45
Fane Pop 60W, 15", 8/15 ohm	£12·26
Fane Pop 50W, 12", 8/15 ohm	£10·17
Fane Pop 25/2 25W, 8/15 ohm	£5·94
Fane Pop 15 12" 15W, 8/15 ohm	£4·40
Fane 122/10a or 122/12	£9·90
Fane Crescendo 15", 8 or 15 ohm	£27·50
Fane Crescendo 12", 8 or 15 ohm	£24·20
Fane 8" d/cone 808T, 8 or 15 ohm	£2·64
Fane 8" d/cone, roll surr. 807T, 8 or 15 ohm	£3·16
Baker Group 25, 3, 8 or 15 ohm	£6·00
Baker Group 35, 3, 8 or 15 ohm	£7·50
Baker De Luxe 12" d/cone	£9·62
Baker Major	£7·50
EMI 13" × 8", 3, 8 or 15 ohm	£2·25
EMI 13" × 8" type 150 d/cone, 3, 8 or 15 ohm	£2·58
EMI 13" × 8" type t/tw, 3, 8 or 15 ohm	£3·85
EMI 13" × 8" type 350, 8 ohm	£8·25
EMI 6½" 93850, 4 or 8 ohm	£2·80
Elac 9" × 5" 59RMLO9, 15 ohm	£2·53
Elac 9" × 5" 59RMLL4, 8 ohm	£2·53
Elac 6½" d/cone 6RM220, 8 ohm	£2·59
Elac 6½" d/cone, roll surr. 6RM171, 8 ohm	£3·22
Elac 4" tweeter TW4, 8 or 15 ohm	£1·21
Celestion PS8 for Unilex	£2·16
Celestion MFL000 25W horn, 8 or 15 ohm	£10·45
Elac 5" 3 ohm	£1·75
Elac 7" × 4", 3 or 8 ohm	£1·52
Elac 8" × 5", 3, 8 or 15 ohm	£1·93
Wharfedale Bronze 8 RS/DD	£3·11
Wharfedale Super 8 RS/DD	£5·50
Wharfedale Super 10 RS/DD	£9·80
Goodmans 8P, 8 or 15 ohm	£3·80
Goodmans 10P, 8 or 15 ohm	£4·49
Goodmans 12P, 8 or 15 ohm	£11·55
Goodmans 15P, 8 or 15 ohm	£17·05
Goodmans 18P, 8 or 15 ohm	£29·70
Goodmans Twinaxiom 8	£6·79
Goodmans Twinaxiom 10	£7·61
Goodmans Axent 100	£6·60
Eagle DT33 dome tweeter, 8 ohm	£4·95
Eagle HT15 tweeter, 8 ohm	£3·46
Eagle CT5 tweeter, 8 ohm	£1·21
Eagle MT10 tweeter	£3·30
Eagle CT10 tweeter	£1·92
Eagle Xovers CN23, 28, 216	£1·10
Kef T27	£4·67
Kef T15	£5·50
Kef B110	£6·16
Kef B200	£7·42
Kef BL39	£10·72
Kefkit 2	£24·75
Richard Allan 12" d/cone, 3 or 15 ohm	£2·20
Richard Allan 8", 3, 8 or 15 ohm	£2·27
10" × 6", 3, 8 or 15 ohm	£1·92
8" × 5", 3 or 8 ohm	£1·38
7" × 4", 3 or 8 ohm	£1·38
3", 8 ohm or 80 ohm	65p
2½", 64 ohm	65p
Speaker matching transformer, 3/8/15 ohm	£1·10
Adastra Hiten 10", 10W, 8 or 15 ohm	£2·80
Adastra Top 20 12", 25W, 8 or 15 ohm	£6·32

Stephen speaker kits and cabinets—send for illustrated brochure and list of recommended speakers.

Car stereo speakers—ask for leaflet.

PA/Disco amplifiers (carr. and ins. £1):

Baker 100W	£46·00
Linear 30/40	£25·00
Linear 40/60	£30·00
Linear 80/100	£50·00

FREE with speaker orders over £7—"Hi-Fi Loudspeaker Enclosures" book.

All units guaranteed new and perfect.

Prompt despatch.

Carriage and insurance 25p per speaker.

(Tweeters and Crossovers 15p each.)

All prices quoted inclusive of V.A.T.

WILMSLOW AUDIO, Dept. PE

SWAN WORKS, BANK SQUARE, WILMSLOW CHESHIRE SK9 1HF

DECADE T.T.L COUNTER UNIT

COMPLETE OR IN KIT FORM

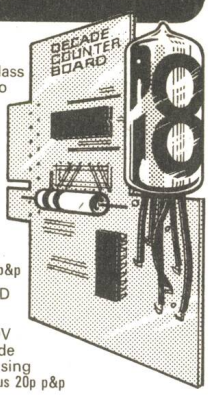

COMPLETE UNIT

Decade TTL Unit on fibreglass PCB using 74 series TTL to count up to 18MHz with Nixie tube display. These units may be coupled to provide a multi-digit readout for Frequency Counters, Timers, DVM's, Batch Counters etc. (Application details not available) Requires 200/250V D.C. & 5V D.C. reg.

KIT PRICE: **£5.06** plus 10p p&p

ASSEMBLED AND TESTED **£5.40** plus 10p p&p

TRANSFORMER, 200/250V to 6V, 1A & 250V for decade power supply, with circuit using 5V Regulator I/C: **£2.20** plus 20p p&p

COMPONENTS

400V, 8A Triac isolated tab type 1L48, 125A surge **85p**

32V Diac Type D30 suitable for triggering 1L48 **23p**

5V Voltage Regulator I/C. T03 case 600 m/A output from 7.5V—15V D.C. input, with instructions **£1.98**

Heat Sink, T03, twisted vane, 8°C/W for 5V Regulator **20p**

BC 107, BC 108 ..... **6p**

(All plus 6p p&p)

Prices include VAT. Please send c.w.o to:

DEXTER & COMPANY
1 ULVER HOUSE 19 KING STREET
CHESTER CH1 2AH
Tel: 0244-25883

P.C.B.: For Mullard Transistor Audio and Radio Circuits Handbook

The following boards are now available: 1st Edition: paper base laminate. 10W H.Q. audio amp, p. 102, **66p.** 25W H.Q. audio amp, p. 106, **70p.** 10/25W H.Q. audio pre-amp, p. 108, **73p.**

2nd Edition: fibreglass laminate. 10W Audio Amp, p. 122, **69p.** 15/20W Audio Amp, p. 126, **73p.** 25W Audio Amp, p. 128, **73p** (incorporates protection circuit, p. 130).

Universal pre-amp, mono, p. 148, **78p.** Universal pre-amp, stereo, p. 148, **£1·48.**

No other circuits are available.

Price includes P. & P. but add VAT.

Remittance (not cash or stamps) with order. Allow 14 days for cheque clearance otherwise prompt despatch subject to stocks.

All boards are roller tinned, drilled and have component ident. printed on reverse.

BRIBOND PRINTED CIRCUITS LIMITED
Regd. in England 593908
Terminus Road, Chichester Sussex

PARTRIDGE MAINS ISOLATION TRANSFORMER, Pri: 105-250V, 5V steps, Sec: 240V, 13 amps. **£15,** carr. pack. £1.

PARMEKO MAINS TRANSFORMER isolated windings. Pri: 200-250V. Sec: 90-120V at 4·5 amp., **£4,** carr. pack. 50p.

GARDNER'S POTTED TRANSFORMER, 0-250V. Pri. 200-250V. Sec. Input: 18V 500m/n, 50V 150m/a, 6V 250m/a output. Size: 3in × 2¼in × 2¼in, **£1,** p.p. 20p. Ex equip. tested.

RIPLEY MAINS TRANSFORMER, Pri: 110V-240V, Sec: 12·5V: 0:12·5V 750m/A 7V:0:7 V1A, **£1,** p.p. 25p.

MAINS TRANSFORMER, Pri: 100-250V, Sec: 22:0:22 200m/A. 22:0:22 100m/A 0:24V 20m/A, **80p,** p.p. 25p.

TRANSISTOR OUTPUT TRANSFORMER, Ratio 8:1, 120mH. Centre tap 2 watts. output, **20p,** p.p. 5p.

SMOOTHING CHOKE, 11MH, 1¼in × 1¼in × 1¼in, **20p,** p.p. 7p.

BELLING LEE INSULATED TERMINALS. Red or Black, 5 amp max. **10p** pair, p.p. 4p.

FINNED ALUMINIUM HEATSINK. 9in × 1¾in. Ready drilled. **20p,** p.p. 7p.

FINNED ALUMINIUM HEATSINK. 9in × 8in × 1¼in. in C.: 4 × 2N3055, **£2,** p.p. 29p.

SUB-MIN. CROC. CLIPS. Red or Black, insulated **4p.** Min. quantity, 6, p.p. 4p.

GARRARD MAG. TAPE DECKS: 1¾i.p.s., 50V, solenoid operated brakes, etc. Mains voltage motors **£7·50** each, p.p. 60p.

MOTEK 3 speed tape deck (1¾in × 3¾in × 7¼in) reel to reel 7in mains operated, **£7·50,** p.p. 60p.

10 REED SWITCHES operated by push buttons and magnets, **50p,** p.p. 25p.

COMPONENT PANEL 6 s'crs (200V 4 amps), 6 condensers, 12 resistors, **30p,** p.p. 8p.

COMPONENT PANEL (9 ICs FJH131) (1-CA300), 1 crystal 7·68kHz + various other components, **£1,** p.p. 8p.

COMPONENT PANEL, 4 × 500 mfd, 50V d.c. cap, 1 × 2N1218, 1 × 2N11468, 2 × 2N598, plus various other components, **10p,** p.p. 9p.

NEON PANEL, 24 neon's, wire ended, 90-240V, **20p** p.p. 4p.

MAINS NEONS
Red or Green. Size: ¼in × ¼in × 1¼in. **15p,** p.p. 4p.

LEVER ACTION P.O. 1000 TYPE SWITCHES
Lock 4-pole changeover, **15p,** p.p. 4p. Ex equip. Lock 2-pole changeover, **10p,** p.p. 4p. Ex equip.

MULLARD & MALLORY SCREW TERMINAL CAPACITORS 4,500μF 64V, 7,100μF 40V, **50p** each. 20,000 30V, 25,000 25V, 35,000 15V, **30p** each, p.p. 10p.

MULLARD FULLWAVE RECTIFIERS
6-48V, 15 amp, **75p,** p.p. 9p.

BELLING LEE 1·5 amp in-line rubber covered interference suppressor, **25p,** p.p. 8p.

RUBBER 3 PIN 5 AMP NON-REVERSIBLE CABLE CONNECTORS, 20p, p.p. 5p.

SOLENOIDS 12 VOLT PULL ACTION
2in × 1in × ¾in, **40p,** p.p. 8p.

SOLENOIDS 12-24V d.c. pull action 1¾in × 1¾in × 1¼in, **40p,** p.p. 5p.

SOLENOIDS 240V a.c. pull action 2¼in × 1¾in × 1¼in, **50p,** p.p. 9p.

SANGAMO WESTON TIME LAPSED METER
Mains operated. 1¼in × 1¼in × 2in, **£1·50** p.p. 7p.

ARROW RELAY, 240V a.c. coil, double pole change over, 1 make contact's 10A, 240V a.c., **25p,** p.p. 8p.

OMRON MK2 MIDGET POWER RELAY, 12V d.c. Double pole changeover. New, **70p,** p.p. 5p.

STC MINIATURE RELAY 280Ω, perspex cover, double pole changeover, 6-15V new, **35p,** p.p. 5p.

STC VARLEY, miniature relays 700Ω, perspex cover, 4 pole changeover, **40p,** p.p. 5p.

POTTER BRUMFIELD 12V d.c. 3 pole changeover with base, contacts rated 7A d.c., **£1,** p.p. 10p.

TELESCOPIC AERIALS
Chromed 7in closed, 28in extended, 6 section ball jointed base, **23p,** p.p. 5p new.

MULLARD 4 DM 160 INDICATORS in plastic holder/cover, ex equip., size approx. 1¾in × 1¼in × ¼in, **36p,** p.p. 5p.

PRINTED CIRCUIT BOARD/19 ACY 19's 10 OA200 Diodes: 1 reed relay: 1 AZ 229 zenner ass. capacitor/resistors. Power supply 22V, 250 m/A d.c. Output 240V a.c., **£1,** p.p. 20p. Ex equip.

WIRING CABLE
Size-1·020. Various colours. 350yds, **60p,** p.p. 23p.

TAPE POSITION INDICATOR
Re-settable 3 digits, **30p,** p.p. 5p.

All orders add 10% V.A.T.

FIELD ELECTRIC LIMITED

3 Shenley Road Borehamwood, Herts.
Tel.: 01-953 6009

BRAND NEW SEMICONDUCTORS AND COMPONENTS GUARANTEED

WE SUPPLY NEARLY ALL THE COMPONENTS FOR PROJECTS ADVERTISED IN THIS MAGAZINE

TRANSISTORS

2G301	0·15	2N3414	0·10	40316	0·50	BC125	0·15	BDY20	1·05	BSY26	0·20
2G302	0·15	2N3415	0·10	40318	0·92	BC126	0·20	BDY38	0·65	BSY27	0·15
2G303	0·25	2N3416	0·15	40360	0·46	BC132	0·30	BDY60	0·90	BSY28	0·15
2G306	0·30	2N3417	0·21	40361	0·48	BC134	0·11	BDY61	1·25	BSY38	0·20
2G309	0·30	2N3570	1·25	40362	0·50	BC135	0·11	BDY62	1·00	BSY39	0·20
2G345B	0·25	2N3571	1·12	40363	0·61	BC136	0·15	BF115	0·23	BSY51	0·25
2G371	0·15	2N3572	0·97	40389	0·46	BC137	0·15	BF117	0·43	BSY52	0·25
2G374	0·15	2N3702	0·11	40394	0·56	BC138	0·24	BF119	0·58	BSY53	0·25
2N174	1·40	2N3703	0·10	40395	0·65	BC140	0·34	BF121	0·25	BSY54	0·30
2N404	0·43	2N3704	0·14	40406	0·44	BC141	0·39	BF123	0·27	BSY56	0·79
2N456	0·75	2N3705	0·10	40407	0·38	BC142	0·24	BF125	0·25	BSY65	0·15
2N456A	0·75	2N3706	0·09	40408	0·50	BC143	0·21	BF152	0·20	BSY78	0·40
2N457A	0·80	2N3707	0·13	40409	0·52	BC144	0·24	BF153	0·29	BSY79	0·40
2N491	3·25	2N3708	0·07	40410	0·53	BC145	0·21	BF154	0·16	BSY95A	0·09
2N696	0·15	2N3709	0·09	40411	2·00	BC147	0·11	BF158	0·23	C111	0·53
2N697	0·15	2N3710	0·12	40414	3·55	BC148	0·10	BF159	0·27	D40N3	0·55
2N698	0·25	2N3711	0·09	40467A	0·69	BC149	0·13	BF160	0·23	GET111	0·45
2N699	0·29	2N3712	0·95	40468A	0·44	BC152	0·18	BF161	0·42	GET114	0·20
2N706	0·10	2N3713	1·08	40600	0·69	BC154	0·18	BF163	0·20	GET415	0·50
2N706A	0·12	2N3714	1·15	40601	0·67	BC157	0·14	BF166	0·35	GET119	0·35
2N708	0·13	2N3715	1·23	40602	0·46	BC158	0·13	BF167	0·21	GET535	0·20
2N709	0·38	2N3716	1·30	40603	0·58	BC159	0·14	BF173	0·24	GET536	0·20
2N711	0·30	2N3773	3·00	40604	0·56	BC160	0·37	BF177	0·29	GET880	0·30
2N718	0·21			40636	1·10	BC167B	0·11	BF178	0·35	GET883	0·20
2N718A	0·30	2N3779	3·15	40673	0·70	BC168B	0·13	BF179	0·43	GET887	0·20
2N720	0·50	2N3790	2·20	AC107	0·35	BC168C	0·11	BF180	0·35	TIP29A	0·49
2N721	0·55	2N3794	2·06	AC113	0·16	BC169B	0·13	BF181	0·32	TIP30A	0·58
2N914	0·22	2N3791	2·06	AC115	0·16	BC169C	0·13	BF182	0·40	TIP31A	0·62
2N916	0·17	2N3792	2·20	AC117	0·20	BC170	0·11	BF183	0·40	TIP32A	0·74
2N918	0·30	2N3794	0·10	AC121	0·13	BC171	0·18	BF184	0·17	TIP33A	1·01
2N929	0·14	2N3819	0·37	AC126	0·25	BC172	0·11	BF185	0·17	TIP34A	1·51
2N930	0·14	2N3820	0·47	AC127	0·25	BC182	0·10	BF194	0·14	TIP35A	2·90
2N1090	0·23	2N3823	0·97	AC128	0·25	BC182L	0·12	BF195	0·17	TIP36A	3·70
2N1091	0·24	2N3824	0·75	AC141K	0·30	BC183	0·09	BF196	0·15	TIP41A	0·79
2N1131	0·20	2N3826	0·23	AC142K	0·25	BC183L	0·09	BF197	0·15	TIP42A	0·90
2N1132	0·20	2N3854	0·16	AC151V	0·14	BC184	0·11	BF198	0·15	TIP2955	0·98
2N1302	0·16	2N3854A	0·16	AC152V	0·17	BC184L	0·11	BF199	0·18	TIP3055	0·60
2N1303	0·16	2N3855	0·16	AC153	0·22	BC186	0·25	BF200	0·40	ME0401	0·18
2N1304	0·20	2N3855A	0·16	AC153K	0·25	BC187	0·25	BF224J	0·14	ME0402	0·20
2N1305	0·20	2N3856	0·16	AC154	0·20	BC207	0·12	BF225J	0·19	ME0404	0·13
2N1306	0·22	2N3856A	0·16	AC176	0·18	BC208	0·11	BF237	0·22	ME0411	0·17
2N1307	0·22	2N3858	0·16	AC187K	0·20	BC212K	0·10	BF238	0·22	ME0412	0·18
2N1308	0·25	2N3858A	0·16	AC188K	0·26	BC212L	0·16	BF244	0·16	ME0413	0·14
2N1309	0·25	2N3859	0·16	AC176	0·18	BC214L	0·23	BF245	0·33	ME1120	0·25
2N1483	0·90	2N3859A	0·16	AC187K	0·20	BC237	0·09	BF246	0·43	ME4001	0·09
2N1507	0·24	2N3860	0·16	AC188K	0·26	BC238	0·09	BF247	0·49	ME4002	0·11
2N1613	0·20	2N3866	0·70	AC117	0·35	BC239	0·09	BF254	0·16	ME4003	0·14
2N1631	0·35	2N3877	0·25	AC118	0·24	BC251	0·20	BF255	0·17	ME4101	0·10
2N1637	0·36	2N3877A	0·26	AC119	0·27	BC253	0·23	BF257	0·47	ME4102	0·11
2N1638	0·32	2N3900	0·20	AC121	0·13	BC257	0·09	BF258	0·53	ME4103	0·10
2N1701	1·10	2N3900A	0·21	AC122	0·16	BC258	0·09	BF259	0·45	ME4104	0·11
2N1702	2·15	2N3901	0·32	AC125	0·15	BC259	0·13	BF270	0·25	ME6101	0·14
2N1711	0·22	2N3903	0·22	AC126	0·25	BC261	0·20	BF272	0·53	ME6102	0·16
2N1893	0·34	2N3904	0·17	AC127	0·25	BC262	0·18	BF273	0·25	ME8002	0·17
2N2102	0·30	2N3905	0·21	AC128	0·25	BC263	0·28	BF274	0·23	ME8003	0·16
2N2147	0·70	2N3906	0·22	AC141K	0·30	BC300	0·42	BF457	0·53	MJ400	0·78
2N2148	0·94	2N4036	0·63	AC142K	0·25	BC301	0·34	BF458	0·65	MJ420	0·86
2N2192	0·40	2N4037	0·42	AC151V	0·14	BC302	0·27	BFS21A	2·30	MJ421	0·88
2N2192A	0·40	2N4058	0·16	AC152V	0·17	BC303	0·54	BFS28	0·92	MJ430	0·75
2N2193	0·40	2N4059	0·09	AC153	0·22	BC307	0·10	BFW10	0·61	MJ440	0·71
2N2193A	0·61	2N4060	0·11	AC153K	0·25	BC307A	0·10	BFW11	0·61	MJ480	0·75
2N2194	0·27	2N4061	0·11	AC154	0·20	BC308	0·09	BFX13	0·23	MJ481	0·85
2N2194A	0·30	2N4062	0·11	AC176	0·18	BC308A	0·09	BFX29	0·30	MJ490	0·94
2N2195	0·37	2N4302	0·25	AC187K	0·20	BC308B	0·09	BFX30	0·25	MJ491	1·10
2N2195A	0·18	2N4303	0·47	AC188K	0·26	BC309	0·10	BFX37	0·30	MJ802	4·12
2N2218A	0·30	2N4916	0·20	AD161 }	PR	BC309A	0·10	BFX44	0·33	MJ901	2·65
2N2219	0·37	2N4917	0·17	AD162 }	1·15	BC309B	0·10	BFX63	2·48	MJ1001	2·34
2N2219A	0·51	2N4918	0·50	AF109R	0·40	BC327	0·24	BFX68	0·68	MJ1800	1·88
2N2220	0·20	2N4919	0·63	AF114	0·25	BC328	0·22	BFX84	0·24	MJ2500	2·92
2N2221	0·20	2N4920	0·71	AF115	0·24	BC337	0·19	BFX85	0·29	MJ2501	3·25
2N2221A	0·33	2N4921	0·50	AF116	0·25	BC338	0·19	BFX86	0·24	MJ2955	1·00
2N2222	0·31	2N4922	0·55	AF117	0·20	BCY30	0·43	BFX87	0·28	MJ3000	2·47
2N2222A	0·41	2N4923	0·60	AF118	0·50	BCY31	0·51	BFX88	0·25	MJ3001	2·79
2N2368	0·11	2N5172	0·12	AF121	0·22	BCY32	1·15	BFX89	0·45	MJ3701	0·93
2N2369	0·15	2N5174	0·22	AF124	0·24	BCY33	0·34	BFY10	0·35	MJ4502	4·44
2N2369A	0·17	2N5175	0·26	AF125	0·20	BCY34	0·35	BFY11	0·45	MJE340	0·47
2N2646	0·50	2N5176	0·32	AF126	0·19	BCY38	0·53	BFY17	0·90	MJE370	0·73
2N2647	1·20	2N5245	0·43	AF127	0·20	BCY39	1·05	BFY18	0·35	MJE371	0·80
2N2711	0·12	2N5190	0·92	AF139	0·38	BCY40	0·81	BFY19	0·35	MJE520	0·59
2N2712	0·12	2N5191	0·96	AF172	0·25	BCY42	0·15	BFY20	0·50	MJE521	0·73
2N2713	0·17	2N5192	1·24	AF178	0·55	BCY43	0·15	BFY29	0·40	MJE1092	1·93
2N2714	0·17	2N5193	1·01	AF179	0·65	BCY58	0·21	BFY37	0·20	MJE1102	1·57
2N2904	0·28	2N5194	1·10	AF180	0·50	BCY59	0·22	BFY41	0·43	MJE2801	1·19
2N2904A	0·25	2N5195	1·46	AF186	0·40	BCY70	0·17	BFY43	0·65	MJE2901	1·56
2N2905	0·33	2N5245	0·43	AF200	0·35	BCY71	0·22	BFY50	0·22	MJE2955	1·65
2N2905A	0·35	2N5457	0·35	AF239	0·41	BCY72	0·13	BFY51	0·18	MJE3055	0·83
2N2906	0·24	2N5458	0·33	AF240	0·72	BCY87	3·47	BFY52	0·20	MM1613	0·43
2N2906A	0·30	2N5459	0·33	AF279	0·54	BCY88	2·40	BFY53	0·15	MM1711	0·49
2N2907	0·32	3N128	0·73	AF280	0·54	BCY89	0·97	BFY56	0·34	MM1712	0·64
2N2907A	0·33	3N138	1·65	AFY42	0·74	BD115	0·75	BFY64	0·41	MM2712	0·64
2N2923	0·12	3N139	1·42	AF211	0·55	BD116	0·75	BFY76	0·22	MPF102	0·25
2N2924	0·12	3N140	0·92	AL102	0·75	BD121	0·75	BFY77	0·24	MP8111	0·32
2N2925	0·15	3N141	0·81	AL103	0·70	BD123	0·82	BFY78	0·36	MP8112	0·40
2N2926		3N142	0·58	ASY26	0·30	BD124	0·67	BFY90	0·60	MP8113	0·47
Green	0·12	3N143	0·75	ASY27	0·36	BD130	0·57	BRY39	0·38	MPSA05	0·25
Yellow	0·10	3N152	0·92	ASY28	0·28	BD131	0·40	BSX19	0·13	MPSA06	0·20
Orange	0·10	3N153	0·81	ASY29	0·30	BD132	0·50	BSX20	0·14	MPSA12	0·40
2N3053	0·31	3N154	0·84	ASY50	0·20	BD136	0·49	BSX21	0·20	MPSA14	0·24
2N3054	0·60	3N159	1·17	ASY55	0·35	BD137	0·55	BSX26	0·49	MPSA55	0·30
2N3055	0·60	3N187	1·55	AU103	1·25	BD138	0·68	BSX27	0·84	MPSA56	0·28
2N3390	0·20	3N200	2·49	BC107	0·14	BD139	0·71	BSX28	0·25	MPSA65	0·25
2N3391	0·20	3N201	1·05	BC108	0·13	BD140	0·83	BSX29	0·47	MPSA66	0·28
2N3391A	0·22			BC109	0·14	BDY10	1·25	BSX61	0·42	MPSU01	0·44
2N3392	0·13			BC113	0·13	BDY11	1·50	BSX76	0·15	MPSU05	0·48
2N3393	0·12			BC114	0·12	BDY17	1·50	BSX77	0·20		
2N3394	0·17	40050	0·78	BC115	0·15	BDY18	1·75	BSX78	0·25		
2N3402	0·12	40251	0·81	BC116	0·15	BDY19	1·97	BSY24	0·20		
2N3403	0·19	40309	0·30	BC116A	0·18			BSW70	0·28		
2N3404	0·24	40310	0·50	BC117	0·21			BSY25	0·15		
2N3405	0·27	40313	0·92	BC118	0·11						
				BC119	0·27						
				BC121	0·23						

RETURN OF POST SERVICE

Post and Packing 13p per order. Europe 25p. Commonwealth (Air) 65p (MIN.). Matching charge (audio transistors only) 15p extra per pair. Prices subject to stock availability.

TTL LOGIC I.C.'s

We stock the full range of the low number SN7400 series—some examples:

SN7400	0·20	SN7401	0·20	SN7402	0·20
SN7403	0·20	SN7404	0·22	SN7420	0·20
SN7447	1·30	SN7472	0·36	SN7493	0·75

We also stock the unusual numbers as follows:

SN74100	2·50	SN74153	1·53	SN74176	1·50
SN74107	0·43	SN74154	2·00	SN74180	1·55
SN74118	1·00	SN74155	1·55	SN74181	7·00
SN74119	1·92	SN74157	1·80	SN74190	1·95
SN74121	0·60	SN74160	2·60	SN74191	1·95
SN74122	1·35	SN74161	2·60	SN74192	1·90
SN74123	1·35	SN74164	2·26	SN74173	1·90
SN74141	0·90	SN74165	4·00	SN74196	1·60
SN74145	1·50	SN74167	6·25	SN74198	4·60
SN74150	3·35	SN74174	2·00	SN74199	4·00
SN74151	1·10	SN74175	1·35		

FM multiplex stereo demodulator MC1304 **£3·60**
Dual monolithic stereo preamplifier MC1303 **£2·70**
Stereo Decoder MC1310 **£2·78**

BRIDGE RECTIFIERS

PIV	50	100	200	400	600
1A	24p	26p	35p	35p	40p
2A	32p	37p	41p	46p	52p
4A	60p	70p	75p	85p	95p
6A	62p	75p	80p	£1·10	£1·25

ZENER DIODES

400MW—BZY88 and IN SERIES. **15p.**
1 watt—IN, IZM and I8 SERIES, **22p.** 1·5 watt—ZL SERIES, **25p.**
10 watt—Z8 SERIES, **40p.** 20 watt—BZ 93 SERIES, **52p.**

NE555 TIMER I.C. **90p.**
NE560 PHASE LOCKED LOOP, **£4·48.**
SCORPIO IGNITION KIT for improved performance **£10** + 50p P. & P.

MONTHLY NEWS FEATURE

1. NEW HEAD OFFICE: 42 CRICKLEWOOD BROADWAY, N.W.2
2. 65 BATH STREET, GLASGOW. Tel. 041-332 4133.
3. NEW OFFICE OPENING BRISTOL. WATCH THIS SPACE.
4. SPECIAL OFFER. 3 IN 1 POWER SUPPLIES FOR EDUCATIONAL ESTABLISHMENTS. WRITE FOR DETAILS.

DIODES AND RECTIFIERS

IN5171 (1·5A 50pv)	8d	IN5402 (3A 200pv)	20p
IN5172 (1·5A 100pv)	9p	IN5404 (3A 400pv)	22p
IN4517 (1·5A 200pv)	10p	CL7005 (3A 600pv)	25p
IN5173 (1·5A 400pv)	11p	CL7006 (3A 800pv)	27p
IN5176 (1·5A 600pv)	12p	CL7007 (3A 1000pv)	30p
IN5177 (1·5A 800pv)	15p	CL1002 (10A 100pv)	35p
PL4007 (1·5A 1000pv)	20p	CL1003 (10A 200pv)	40p
IN5400 (3A 50pv)	15p	CL1004 (10A 400pv)	47p
IN5401 (3A 100pv)	17p	CL1005 (10A 600pv)	56p

ANODE AND CATHODE STUD

IN1183 (35A 50pv)	70p	IN1188 (35A 400pv)	£1
IN1184 (35A 100pv)	80p	IN1190 (35A 600pv)	£1·40
IN1186 (35A 200pv)	90p		

CATHODE STUD ONLY

IN3766 (35A 800pv)	£1·50			IN3768 (35A 1000pv)	£2·50
IN34A	10p	BA141	17p	BYZ37	12½p	OA79	7p
IN914	7p	BA142	17p	BYZ10	35p	OA81	8p
IN916	7p	BA144	12p	BYZ11	32p	OA85	10p
AA119	7p	BA145	17p	BYZ12	30p	OA90	7p
AA129	15p	BA154	12p	OA9	10p	OA91	7p
BA100	15p	BY100	15p	OA10	20p	OA95	7p
BA102	25p	BY126	15p	OA47	7½p	OA200	7p
BA110	25p	BY127	17½p	OA70	7½p	OA202	10p
BA115	7p	BY140	£1	OA73	10p		

OPTOELECTRONICS

MINITRON 3015F 7-SEGMENT INDICATOR (16 PIN DIL) **£2.**
DRIVER SN7447 **£1·30**
SOCKETS **20p**

TIL 209 LIGHT EMITTING DIODE. Made by TEXAS INST. (Red). **35p**

MOTOROLA MC SERIES, RCA CA 3000 SERIES AND COSMOS, PLESSEY SL SERIES. TRY US FIRST FOR LINEAR AND DIGITAL INTEGRATED CIRCUITS.

ENCAPSULATED FULL-WAVE RECTIFIER. 1·8A 100 piv **25p** ea.

WIRE-WOUND RESISTORS

2·5 watt 5% (up to 270 ohms only), **7p.**
5 watt 5% (up to 8·2kΩ only), **9p.**
10 watt 5% (up to 26kΩ only), **10p.**

POTENTIOMETERS

Carbon:
Log. or Lin., less switch, **17½p.**
Log. or Lin., with switch, **29p.**
Wire-wound Pots (3W), **38p.**
Twin Ganged Stereo Pots, Log. or Lin., **47p.**

PRESETS (CARBON)

0·1 Watt	6p	VERTICAL	
0·2 Watt	6p	OR	
0·3 Watt	7½p	HORIZONTAL	

SLIDE POTENTIOMETERS

58mm TRACK
SINGLE GANGED. LOG or LIN 1k to 1M. **40p** each.
TWIN GANGED. LOG or LIN 1k to 500k. **60p** each.
KNOBS. **5p** each.

Small value
SUB-MIN. ELECTROLYTICS
wide range of values only 6p each

ALL PRICES EXCLUSIVE OF 10% VAT

Tel. 01-452 0161/2/3
Telex 21492

A. MARSHALL & SON
42 CRICKLEWOOD BROADWAY, LONDON, N.W.2

VISITORS WELCOME
HRS. 9-5.30 MON.-FRI.
9-5 SAT.

MAPLIN ELECTRONIC SUPPLIES

★RETURN OF POST SERVICE

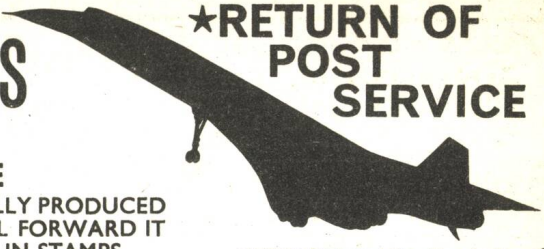

MAPLIN: Projected site of London's third airport.

1973 CATALOGUE

3rd EDITION NOW AVAILABLE

SEND NOW FOR YOUR COPY OF THIS BEAUTIFULLY PRODUCED FULLY ILLUSTRATED CATALOGUE AND WE WILL FORWARD IT TO YOU BY RETURN OF POST. PLEASE SEND 9p IN STAMPS.

EVERYTHING GUARANTEED BRAND NEW MARKED BY THE MANUFACTURER

RESISTORS
Carbon film 5% from 1Ω to 1MΩ, 10% from 1·2MΩ to 10MΩ. E12 series, ¼W 1p; ½W 1·2p.
Metal Oxide 2% 10Ω to 1MΩ. E24 series ¼W 4p.
Also 1W, 2½W, 5W, 10W types stocked.

7 SEGMENT DISPLAY
Minitron 3015F
£1·98 each.

POTENTIOMETERS
Miniature carbon track with ¼in. spindles. 5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2MΩ.
Log or lin (and 1kΩ lin), **12p.**
Log or lin with switch **23p.**
Dual gang less switch **38p.**

P.E. SOUND SYNTHESISER

If this project seems expensive YOU HAVEN'T SEEN OUR PRICES!

We shall be stocking all the parts for this exciting project, from the special I.C.'s right down to the nuts, bolts and spacers for mounting the Veroboards.

Send S.A.E. NOW for our detailed price lists.

YOU SIMPLY **MUST** SEE OUR PRICES!

8 pin DIL OP AMP
741C 36p.
14 pin **741C 45p.**

McMURDO
Socket, RS8, **52p**
Plug, RP8, **36p.**
(As used in P.E. Sound Synthesiser.)

Diodes IN914 **4p.**
OA91 **6p.** BAX 13 **5p.**
IN4001 **6p.** IN4002 **6½p.** IN4003 **7p.** IN4004 **7½p.** IN4005 **8p.** IN4006 **8½p.** IN4007 **9p.**

SEMI-CONDUCTORS
We stock a large range of transistors and I.C.s, for details please see our catalogue. LOOK! These popular devices at amazingly low prices. BC107/8/9 **10p** each. BC169C **12p.** BFY51 **16p.** TIS43 (SS43) **28p.** 2N706 **10p.** 2N2646 **45p.** 2N3055 **49p.** 2N 3819 **24p.**

DIN PLUGS. 3 pin, **9p.** 5 pin A (180°), 5 pin B (240°), **10p** each.

DIN SOCKETS. 3 pin, 5 pin A, 5 pin B, **7p** each.

DIN LOUDSPEAKER. 2 pin plug, **8p.** Socket **6p.**

JACK PLUGS standard ¼in plastic barrel, **13p.** Stereo, **25p.** Bright metal barrel, **17p.** Stereo, **29p.**

JACK SOCKETS standard ¼" open type, **10p.** Moulded 2 break, **13p.** Moulded stereo 3 break, **18p.**

ROTARY SWITCHES
Adjustable stop. 1 pole 2-12 way, 2 pole 2-6 way, 3 pole 2-4 way, 4 pole 2-3 way. Only **24p** each.

SPECIAL IC, for organ builders, 7 stage frequency divider in one 14 pin DIL package, **£2·63** or special price for pack of 12, **£25.**
Why not ask us to slip a data sheet in with your catalogue.

NUDES!

Clothe those naked projects with our superb instrument cases. We are sole distributors of the

Centurion

range, designed for the professional market, now available to you at special low prices. S.A.E. please for free illustrated leaflet.

HARDWARE
Wide range of nuts and bolts, plated brass and nylon types plus solder tags, shakeproof washers, etc.
SOLDER 10 metres of 22 gauge multicore, **20p.**
Insulating sleeving 3 sizes, 6 colours.

MISCELLANEOUS
LT700 Eagle sub-miniature O/P transformer 1200/5Ω 200mW max., **35p.**
Slide switch DPDT, **12p.**
Miniature push to make non-locking switch **12p.**
Silicon grease in special dispenser, 20ml, **38p.**

SEE OUR CATALOGUE
for details of how you can obtain £1 worth of components.
ABSOLUTELY FREE

V.A.T. Please add 10% V.A.T. to final total.
Orders and enquiries for catalogues to
MAPLIN ELECTRONIC SUPPLIES,
P.O. Box 3, Rayleigh, Essex SS6 8LR

Postage and packing FREE in U.K. But we have to ask you to send a 10p handling charge with order under 50p.

become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

RAPY

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
P.O. BOX 156, JERSEY

NAME : _____

ADDRESS : _____ EB83

_____ BLOCK CAPS please

ELECTROKIT

12 Lauderdale Road, London, W.9
Telephone 01-286 0011

LIGHT DIMMER. Kit contains all parts including circuit and construction data, 480 watts, fully suppressed. Price **£2·10**

SCORPIO IGNITION SYSTEMS (P.E. Nov. 1971), **£9·50.** This kit includes all the parts for the assembly of this popular and reliable system. The hardware and the construction data are included.

Send for details of kits available (please enclose S.A.E.).

All kits sent POST FREE within the limits of the U.K.

Please note, prices shown do not allow for V.A.T. Please add 10% to your order.

STEREO IC DECODER

HIGH PERFORMANCE PHASE LOCKED LOOP (as in 'W·W.' July '72)
MOTOROLA MC1310P

EX STOCK DELIVERY

Specn. Separation: 40dB 50Hz—15kHz. Distortion: 0·3%. I/P level: 560mV rms. O/P level: 485mV rms per channel. Input impedance: 50k. Power requirements: 8–12V @ 16mA. Will drive up to 75mA stereo 'on' lamp or LED. Simple to build.

KIT COMPRISES FIBREGLASS PCB
(Printed and tinned), Resistors, I.C., Capacitors, Preset Potm. and Instructions. Only **£3·40** post free + V.A.T.

LIGHT EMITTING DIODE (Red)
Suitable as stereo 'on' indicator. For above with panel mounting clip and instructions. Only **29p** + **p.p.** + V.A.T.

MC1310P only £2·77 + **p.p. 6p** + V.A.T.

14 PIN DIL SOCKETS. 16p each + V.A.T.

NOTE.—As the supplier of the original decoder kit, of which we have sold literally thousands, our customers can benefit from our wide experience.

Fi-Comp Electronics

BURTON ROAD, EGGINTON, DERBY DE6 6GY

PRICES NOW INCLUDE VAT

SUPERSOUND 13 HI-FI MONO AMPLIFIER

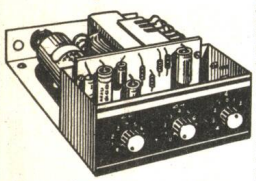

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13W r.m.s. into 8 ohm. Frequency response 12Hz—30KHz ±3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8–15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3in high × 6in wide × 7½in deep. A.C. 200/250V.

PRICE £11·60 P. & P. 25p.

DE LUXE STEREO AMPLIFIER

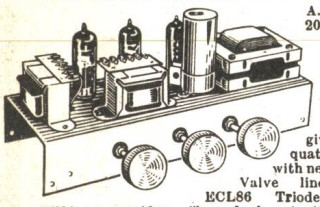

A.c. mains 200–240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up:—2 × ECL86 Triode Pentodes. 1 × EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300m/v for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. w × 4in. x. Overall height including valves 5in. Ready built and tested to a high standard. **Price £9·90.** P. & P. 45p.

NEW! POWER SUPPLY UNIT

200/240V A.C. input. Four switched fully smoothed D.C. outputs giving 6V and 7½V and 9V and 12V at 1 amp continuous (1½ amp intermittent).
Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case, overall size 6″ × 3½″ × 2½″. Suitable for Transistor Radios, Tape Recorders, Amplifiers, etc., etc. Ready built and tested.

PRICE £5 P. & P. 35p.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For TO3, complete with mica's and bushes. Size 2½in × 3in approx. **28p** pair. P. & P: 5p.

HIGH GRADE COPPER LAMINATE BOARDS. 8″ × 6″, 5 for **55p**. P. & P. 13p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-15-20-25-30-35-40-60V half wave at 1 amp or 10-0-10, 20-0-20, 30-0-30V, at 2 amps full wave. Size 3inL × 3½inW × 3inD. Price **£2·10.** P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240V Sec. 9-0-9 at 500mA. **£1** P. & P. 13p.
Pri. 200/240V Sec. 12-0-12 at 1 amp. **£1·10** P. & P. 13p.
Pri. 200/240V Sec. 10-0-10 at 2 amp. **£1·65** P. & P. 30p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER. For P.U. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9–18V. Battery or from H.T. line 200/300V. Frequency response 15Hz–25KHz. Gain 26dB. Solid encapsulation size 1½ × 1½ × ½in. Brand new — complete with instructions. Price **£1.** P. & P. 13p.

3 REFERENCE ENCYCLOPEDIAS FOR ELECTRONIC ENGINEERS AND DESIGNERS, covering between them, transistor characteristics, diode and transistor equivalents. Many thousands of up-to-date European types listed.

Diode Equivalents	**80p**
Transistor Equivalents	**90p**
Transistor Characteristics	**£1·20**
All three together	**£2·60**

POST FREE

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES
A must for servicemen and home constructors. Including many 1000's of British, U.S.A., European and Japanese transistors. ONLY **40p.** Post 5p.

CENTRE ZERO MINIATURE MOVING COIL METER. 100μA for balance or tuning. Approx. size 1in × 1in × ¾in. Limited number **88p.** P. & P. 10p.

RECORD PLAYER BARGAINS
Mains models. All brand new in maker's packing.
LATEST B.S.R. C108/C129 AUTOCHANGER UNITS. With latest stereo/mono compatible cartridge **£7·60** plus 50p P. & P.
Garrard SP25 Mk. III with heavy precision machined die cast turntable. **£10·56.** Carr. 50p.

PRECISION ENGINEERED PLINTHS
Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, SL65B, AT60, etc., or B.S.R. C109, C129, A21, etc. Black leatherette finish. Size 12½in × 14½in × 3½in high (approx. 7½in high, including rigid smoked acrylic cover). P. & P. 35p. **Now only £4·95**

LATEST ACOS GP91/1SC Mono Compatible Cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. **£1·50.** P. & P. 8p.
SONOTONE 9TAHC COMPATIBLE STEREO CARTRIDGE T/O stylus. Diamond Stereo LP and Sapphire 78. ONLY **£2·30.** P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. **£2·80.** P. & P. 10p.
LATEST RONETTE T/O Stereo Compatible Cartridge for EP/LP/Stereo/78. **£1·63.** P. & P. 10p.
LATEST RONETTE T/O Mono Compatible Cartridge for EP/LP/78 mono/stereo records on mono equipment **£1·50.** P. & P 10p.

QUALITY RECORD PLAYER AMPLIFIER MK II
A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. × 3 d. × 6 h. Ready built and tested. PRICE **£4·40.** P. & P. 40p. ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE **£5·85.** P. & P. 50p.

SPECIAL OFFER!!
HI-FI LOUDSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16in high × 10½in wide × 6in deep. Fitted with E.M.I. Ceramic Magnet 13in × 8in bass unit, two H.F. tweeter units and crossover. Max. power handling 10W. Available 3, 8 or 15 ohm impedance.

Our Price £9·25 Carr. 70p.
CABINET AVAILABLE SEPARATELY **£4·95.** Carr. 65p.
Also available in 8 ohm with EMI 13in × 8in. bass speaker with parasitic tweeter. **£7·15.** Carr. 70p.

HARVERSON'S SUPER MONO AMPLIFIER
A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3·5 watts. Volume and tone controls. Chassis size only 7in. wide × 3in. deep × 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer.
OUR ROCK BOTTOM BARGAIN PRICE **£3·30** P. & P. 35p

LOUDSPEAKER BARGAINS
5in 3 ohm **£1·05,** P. & P. 15p. 7 × 4in 3 ohm **£1·15,** P. & P. 20p. 10 × 6in 3 or 15 ohm **£1·90,** P. & P. 30p. E.M.I. 8 × 5in 3 ohm with high flux magnet **£1·62,** P. & P. 20p. E.M.I. 13½ × 8in with high flux ceramic magnet with parasitic tweeter 3, 8, or 15 ohm **£3·50.** P. & P. 30p. E.M.I. 13 × 8in, 3 or 8 or 15 ohm with two inbuilt tweeters and crossover network **£4·65.** P. & P. 30p.
EMI CERAMIC MAGNET HEAVY DUTY TWEETER. pprox. 3½in. Av. 3 or 8 or 15 ohms. **£1·25** plus 15p p. & p.
BRAND NEW. 12in 15w H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with Hiflux ceramic ferrobar magnet assembly **£7·50.** Guitar models: 25w **£7·50.** 35w **£9·35.** P. & P. 40p each.

SPECIAL OFFER!
LIMITED NUMBER OF BRAND NEW ELAC 10″ TWIN CONE LOUDSPEAKERS. With large ceramic magnet and plasticised cone surround. 8 ohm impedance.
£2·70. P. & P. 25p.

12in "RA" TWIN CONE LOUDSPEAKER
10 watts peak handling. 3, 8 or 15 ohm, **£2·45.** P. & P. 30p.
35 ohm SPEAKERS 3″. ONLY **70p.** P. & P. 13p.
"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER
Size 11¾in × 14¾in × 1¾in deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz–20kHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only **£6·55** each. P. & P. 25p.
VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. **Our price 85p yd.** length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

HI-FI STEREO HEADPHONES
Adjustable headband with comfortable flexifoam earmuffs. Wired and fitted with standard stereo ¼in jack plug. Frequency response 30–15,000Hz. Matching impedance 8–16 ohms. Easily converted for mono. PRICE **£3·30.** P. & P. 15p.

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE **£1·15.** P. & P. 10p.

HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT

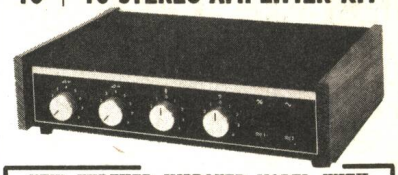

NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED FIBRE GLASS PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. (Very simple to modify to suit magnetic cartridge—instructions included). Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled fibre glass printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 5 ohms. Frequency response ±3dB 12–30,000Hz. Sensitivity better than 80mV into 1MΩ. Full power bandwidth ±3dB 12–15,000Hz. Bass boost approx. to ±12dB. Treble cut approx. to —16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1·0 amp. Overall size—12″ wide × 8″ deep × 2¾″ high.
Fully detailed 7-page construction manual and parts list free with kit or send 18p plus large S.A.E.
PRICES AMPLIFIER KIT, **£11·55** P. & P. 18p.
(Magnetic input components 33p extra)
POWER PACK KIT, **£3.30** P. & P. 33p.
CABINET, **£3·30** P. & P 33p.
(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, **£23·10.** Post Free.
Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.

3-VALVE AUDIO AMPLIFIER HA34 MK II
Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7¼in w. × 4in. d. × 4¾in. h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4½ watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only **£5·50.** P. & P. 35p.

BRITISH MADE SOLID STATE ALL SILICON STEREO AMPLIFIER. 15 watts rms per channel output. Frequency 20Hz to 20KHz. Suitable for magnetic or ceramic pickup tape mic., etc., built-in switchable scratch filter, rumble filter and loudness control. 60 m/m slider controls for bass, treble and volume. 10 way push button function, selector switch. This amplifier has specification and performance usually only found in amplifiers costing twice as much. Each amplifier supplied, tested and fully guaranteed. Finished in the most attractive contemporary style teak cabinet. Size 16½in. × 8½in. × 4½in. Makers' recommended price £46·36. incl. V.A.T. Our price (while stocks last) **£35·75** incl. V.A.T. plus 75p P. & P. Send S.A.E. for full details of specification.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3–15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet **15p** plus S.A.E. (Free with parts). **All parts sold separately. ONLY £8·80.** P. & P. 55p. Also available ready built and tested **£12·10.** P. & P. 60p.

Open 9-5.30 Mon. to Fri. 9-5
Sat. Early closing Wed. 1p.m.

A few minutes from South Wimbledon Tube Station.

HARVERSON SURPLUS CO. LTD.
Dept. PE, 170 High St., Merton, London, S.W.19 Tel. 01-540 3985
SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. All models—Input 230v. 50/60 c/s. Variable output 0-260v.

MODEL S-260 GENERAL PURPOSE BENCH MOUNTING

1 amp.	£7·00
2·5 amp.	£8·05
5 amp.	£11·75
8 amp.	£15·90
10 amp.	£22·50
12 amp.	£23·60
20 amp.	£49·00
25 amp.	£58·00
40 amp.	£82·50

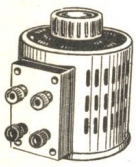

MODEL S-260B

Panel mounting

·1 amp	£7·00
2·5 amp	£8·05

Carriage and Packing Extra

AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.

80W	£2·10	P. & P. 18p
150W	£2·70	P. & P. 18p
300W	£3·60	P. & P. 23p
500W	£5·25	P. & P. 33p
1000W	£7·50	P. & P. 38p
1500W	£10·20	P. & P. 43p
2250W	£17·25	P. & P. 50p
5000W	£35·00	P. & P. £1

MCA.220 AUTOMATIC VOLTAGE STABILISER

Input 88–125V a.c. or 176–250V a.c. Output 120V a.c. or 240V a.c. 200VA rating. **£11·97.** Post 50p.

PS.200 REGULATED P.S.U.

Solid state. Variable output 5–20V d.c. up to 2 amp. Independent meters to monitor voltage and current. Output 220/240V. a.c. Size 7¼in. × 5¼in. × 3¼in. **£19·95.** Post 25p.

PS.1000B REGULATED POWER SUPPLY

Solid state. Output 6, 9 or 12V d.c. up to 3 amps. Meter to monitor current. Input 220/240V a.c. Size 4in. × 3¼in. × 6¼in. **£11·97.** Post 25p.

230V/240V SMITHS SYNCHRONOUS GEARED MOTORS

Built in gearbox. All brand new and boxed. 30 RPH CW; 2 RPH CW; 20 RPH CW; 2 RPH ACW; 30 RRH CW. **50p** each, Post 12p.

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing, ¼in dia. shafts. Bulk quantities available.

25 WATT. 10/25/50/100/250/500/1000 ohms. **95p.** P. & P. 10p.

50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. **£1·35.** P. & P. 10p.

100 WATT. 1·5/10/25/50/100/250/500/1000 or 2500 ohms. **£1·95.** P. & P. 15p.

240° Wide Angle 1mA Meters

MW1-6 60mm square	£3·97
MW1-8 80mm square	£4·97

Post extra

230 VOLT A.C. 50 CYCLES RELAYS

Brand new. 3 sets of changeover contacts at 5 amp. rating. **50p** each. Post 10p (100 lots **£40**) Quantities available.

SEW CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVT. DEPTS., EDUCATIONAL AUTHORITIES, ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

TYPE SW.100 100mm × 80mm Fronts

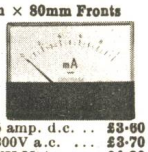

50μA	£4·15	5 amp. d.c. ..	£3·60
50-0-50μA ...	£3·95	300V a.c. ...	£3·70
100μA	£3·95	VU Meter ...	£4·30
100-0-100μA .	£3·90		
500μA	£3·70		
1mA	£3·60		
20V d.c.	£3·60		
50V d.c.	£3·60		
300V d.c. ...	£3·60		
1 amp. d.c. ..	£3·60		

Type SD.830 82·5mm × 110mm Fronts

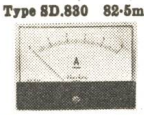

50μA	£3·40	10mA	£3·10
50-0-50μA ...	£3·40	50mA	£3·10
100μA	£3·35	100mA	£3·10
100-0-100μA .	£3·35	500mA	£3·10
200μA	£3·30	1 amp.	£3·10
500μA	£3·15	5 amp.	£3·10
1mA	£3·10	10 amp.	£3·10
5mA	£3·10	5V d.c.	£3·10
		10V d.c.	£3·10
		20V d.c.	£3·10
		50V d.c.	£3·10
		300V d.c. ...	£3·10
		15V a.c.	£3·30
		300V a.c. ...	£3·30
		VU Meter ..	£3·50

Type SD.640 63·5mm × 85mm Fronts

50μA	£3·05	500mA	£2·90
50-0-50μA ...	£3·05	1 amp.	£2·90
100μA	£3·00	5 amp.	£2·90
100-0-100μA .	£3·00	10 amp.	£2·90
200μA	£3·00	5V d.c.	£2·90
500μA	£2·95	20V d.c.	£2·90
1mA	£2·90	50V d.c.	£2·90
5mA	£2·90	300V d.c. ...	£2·90
10mA	£2·90	15V a.c.	£3·00
50mA	£2·90	300V a.c. ...	£3·00
100mA	£2·90	VU Meter ..	£3·15

Type SD.460 46mm × 59·5mm Fronts

50μA	£2·80	1 amp.	£2·60
50-0-50μA ...	£2·80	5 amp.	£2·60
100μA	£2·75	10 amp.	£2·60
100-0-100μA .	£2·75	5V d.c.	£2·60
200μA	£2·70	10V d.c.	£2·60
500μA	£2·55	20V d.c.	£2·60
1mA	£2·60	50V d.c.	£2·60
5mA	£2·60	300V d.c. ...	£2·60
10mA	£2·60	15V a.c.	£2·70
50mA	£2·60	300V a.c. ...	£2·70
100mA	£2·60	VU Meter ...	£2·90
500mA	£2·60		

"SEW" EDGEWISE METERS

Type PE.70. 3 17/32in. × 1 15/32in. × 2¼in. deep.

50μA	£3·75	500μA	£3·20
50-0-50μA ...	£3·60	1mA	£3·20
100μA	£3·60	300V a.c. ...	£3·25
100-0-100μA .	£3·50	VU Meter ...	£3·85
200μA	£3·40		

***MOVING IRON— ALL OTHERS MOVING COIL**

Please add postage

Type MR.85P. 4¼in. × 4¼in. Fronts

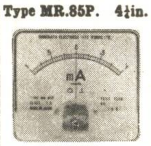

50μA	£4·40	50mA	£3·90
50-0-50μA ...	£4·25	100mA	£3·90
100μA	£4·25	500mA	£3·90
100-0-100μA .	£4·05	1 amp.	£3·90
200μA	£4·05	5 amp.	£3·90
500μA	£3·90	15 amp.	£3·90
5000-500μA .	£3·90	30 amp.	£3·95
1mA	£3·90	20V d.c.	£3·90
1-0-1mA	£3·90	50V d.c.	£3·90
5mA	£3·90	150V d.c. ...	£3·90
10mA	£3·90	300V d.c. ...	£3·90
		15V a.c.	£3·95
		300V a.c. ...	£3·95
		S Meter 1mA.	£3·90
		VU Meter ...	£4·55
		1 amp. a.c.* .	£3·90
		5 amp. a.c.* .	£3·90
		10 amp. a.c.*	£3·90
		20 amp. a.c.*	£3·90
		30 amp. a.c.*	£3·90

Type MR.52P. 2¼in. square Fronts.

50μA	£3·50	10V d.c.	£2·50
50-0-50μA ...	£3·05	20V d.c.	£2·50
100μA	£3·00	50V d.c.	£2·50
100-0-100μA .	£2·95	300V d.c. ...	£2·50
500μA	£2·65	15V a.c.	£2·60
1mA	£2·50	300V a.c. ...	£2·60
5mA	£2·50	S Meter 1mA.	£2·60
10mA	£2·50	VU Meter ...	£3·60
50mA	£2·50	1 amp. a.c.* .	£2·50
100mA	£2·50	5 amp. a.c.* .	£2·50
500mA	£2·50	10 amp. a.c.*	£2·50
1 amp.	£2·50	20 amp. a.c.*	£2·50
5 amp.	£2·50	30 amp. a.c.*	£2·50

Type MR.65P. 3¼in. × 3¼in. Fronts

50μA	£3·70	10V d.c.	£2·60
50-0-50μA ...	£3·15	20V d.c.	£2·60
100μA	£3·15	50V d.c.	£2·60
100-0-100μA .	£3·10	150V d.c. ...	£2·60
200μA	£3·05	300V d.c. ...	£2·60
500μA	£2·75	15V a.c.	£2·80
500-0500μA .	£2·60	50V a.c.	£2·80
1mA	£2·60	150V a.c. ...	£2·80
5mA	£2·60	300V a.c. ...	£2·80
10mA	£2·60	500V a.c. ...	£2·80
50mA	£2·60	S Meter 1mA.	£2·85
100mA	£2·60	VU Meter ...	£3·70
500mA	£2·60	50mA a.c.* ..	£2·60
1 amp.	£2·60	100mA a.c.* .	£2·60
5 amp.	£2·60	200mA a.c.* .	£2·60
10 amp.	£2·60	500mA a.c.* .	£2·60
15 amp.	£2·60	1 amp. a.c.* .	£2·60
20 amp.	£2·60	5 amp. a.c.* .	£2·60
30 amp.	£2·80	10 amp. a.c.*	£2·60
50 amp.	£2·90	20 amp. a.c.*	£2·60
5V d.c.	£2·60	30 amp. a.c.*	£2·60

"SEW" EDUCATIONAL METERS

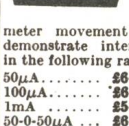

Type ED.107. Size overall 100mm × 90mm × 108mm.

A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3in. mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50μA	£6·90	10V d.c.	£5·95
100μA	£6·40	20V d.c.	£5·95
1mA	£5·95	50V d.c.	£5·95
50-0-50μA ...	£6·40	300V d.c. ...	£5·95
10-0-1mA ...	£5·95	Dual range	
1A d.c.	£5·95	500mA/5A d.c.	£7·00
5A d.c.	£5·95	5V/50V d.c. .	£7·00

Type MR.38P. 1 21/32in. square Fronts.

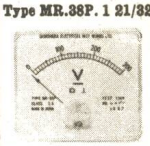

50μA	£2·55	200mA	£2·25
50-0-50μA ...	£2·50	300mA	£2·25
100μA	£2·45	500mA	£2·25
100-0-100μA .	£2·40	750mA	£2·25
200μA	£2·25	1 amp.	£2·25
500μA	£2·25	2 amp.	£2·25
500-0-500μA .	£2·25	5 amp.	£2·25
1mA	£2·25	10 amp.	£2·25
1-0-1mA	£2·25	3V d.c.	£2·25
2mA	£2·25	10V d.c.	£2·25
5mA	£2·25	15V d.c.	£2·25
10mA	£2·25	20V d.c.	£2·25
20mA	£2·25	50V d.c.	£2·25
50mA	£2·25	100V d.c. ...	£2·25
100mA	£2·25	150V d.c. ...	£2·25
150mA	£2·25	300V d.c. ...	£2·25
		500V d.c. ...	£2·25
		750V d.c. ...	£2·25
		15V a.c.	£2·35
		50V d.c.	£2·30
		150V a.c. ...	£2·30
		300V a.c. ...	£2·30
		500V a.c. ...	£2·30
		S Meter 1mA.	£2·30
		VU Meter ...	£2·65

Type MR.45P. 2in. square Fronts.

50μA	£2·70	5 amp.	£2·40
50-0-50μA ...	£2·65	10V d.c.	£2·40
100μA	£2·60	20V d.c.	£2·40
100-0-100μA .	£2·50	50V d.c.	£2·40
200μA	£2·50	300V d.c. ...	£2·40
500μA	£2·45	15V d.c.	£2·40
500-0-500μA .	£2·40	300V d.c. ...	£2·40
1mA	£2·40	S Meter 1mA.	£2·50
5mA	£2·40	VU Meter ...	£2·70
10mA	£2·40	1 amp. a.c.* .	£2·40
50mA	£2·40	5 amp. a.c.* .	£2·40
100mA	£2·40	10 amp. a.c.*	£2·40
500mA	£2·40	20 amp. a.c.*	£2·40
1 amp.	£2·40	30 amp. a.c.*	£2·40

"SEW" BAKELITE PANEL METERS

Type MR.65. 3¼in. square Fronts.

25μA	£4·60	1 amp.	£2·60
50μA	£3·55	5 amp.	£2·60
50-0-50μA ...	£3·05	15 amp.	£2·60
100μA	£3·00	30 amp.	£2·60
100-0-100μA .	£3·00	50 amp.	£2·60
500μA	£2·70	5V d.c.	£2·60
500-0-500μA .	£2·70	10V d.c.	£2·60
1mA	£2·60	20V d.c.	£2·60
5mA	£2·60	50V d.c.	£2·60
10mA	£2·60	150V d.c. ...	£2·60
50mA	£2·60	300V d.c. ...	£2·60
100mA	£2·60	300V a.c.* ..	£2·65
500mA	£2·60	50V a.c.* ..	£2·65
100mV d.c. ..	£2·90	150V a.c.* ..	£2·65
		300V a.c.* ..	£2·65
		500mA a.c.* .	£2·60
		1 amp. a.c.* .	£2·60
		5 amp. a.c.* .	£2·60
		10 amp. a.c.*	£2·60
		20 amp. a.c.*	£2·60
		30 amp. a.c.*	£2·60
		50 amp. a.c.*	£2·60
		VU Meter ...	£3·65
		50mV d.c. ...	£2·90
		100mV d.c. ..	£2·90

Type S-80 80mm square Fronts

50μA	£3·50	1mA	£3·00
50-0-50μA ...	£3·40	20V d.c.	£3·00
100μA	£3·40	50V d.c.	£3·00
100-0-100μA .	£3·30	300V d.c. ..	£3·00
500μA	£3·05	1 amp. d.c. ..	£3·00
		5 amp. d.c. ..	£3·00
		300V a.c. ...	£3·00
		VU Meter ..	£3·70

JOSTY KIT

Post and Packing 15p per Kit. Complete with comprehensive, easy to follow instructions and covered by full guarantee.

AF20—Mono Amplifier, **£4·80.**
AF30—Mono Pre-Amplifier, **£2·61.**
AF310—Mono Amplifier **£5·91.**
AT5—Automatic Light Control, **£2·58.**
AT30—Photo Cell Switching Unit, **£5·70.**
AT50—400W Triac Light Dimmer Speed Control, **£4·80.**
AT55—1,30 0W Triac Light Dimmer Speed Control, **£5·70.**
AT56—2,200W Triac Light Dimmer Speed Control, **£6·90.**
AT60—Psychedelic Light Control, Single Channel, **£7·80.**
AT65—Psychedelic Light Control, 3 Channel, **£14·55.**
HF61—Radio, **£3·33.**
HF65—F.M. Transmitter **£2·70.**
HF75—F.M. Receiver, **£2·88.**
HF310—F.M. Tuner Unit, **£15·81.**
HF325—De-Luxe F.M. Tuner Unit, **£24·12.**
HF330—Stereo Decoder for use with HF310 or HF325, **£9·96.**
HF395—Aerial Amplifier for A.M./F.M. bands I, II and III, **£1·77.**
GP310—Stereo Pre-Amp to use with 2, AF310, **£21·27.**
GU330—Tremolo Unit for guitars, etc., **£7·50.**
NT10—Power Supply 100mA 9V Stab., 12V Unstab., **£6·15.**
NT300—Professional Stab. Power Supply 2 × 30V, 2·2A, **£12·51.**
NT305—Transistor Converter 12/15V a.c./d.c. to 6V, 7·5V or 9V d.c., **£4·50.**
NT310—Power Supply 240V a.c. to 2 × 18V d.c. at 2A, **£4·80.**
NT315—Power Supply 240V a.c. to 4·5–15V d.c., 500mA, **£9·57.**

Send S.A.E. for new 8-page list of Semiconductors and Valves

ALL PRICES ARE EXCLUSIVE OF 10% V.A.T.

GWS

ALSO SEE FOLLOWING PAGES

GWS G.W.SMITH & CO (RADIO) LTD

60 POCKET ULTIMETER
igh-precision at low-cost. anges: D.c. 15V, 150V, 000V (10,000 O.P.V.). A.c. V, 150V, 100V (1,000 P.V.). c. Current 150mA. Resis- nce 100k ohms. **·85.** Post 15p.

UDIOTRONIC MODEL ATM.1
op value 1,000 o.p.v. ocket multimeter. anges : 0/10/50/250/ 000V. A.C. and D.C. .C. Current 0–1mA/ 00mA. esistance: 0/150 K ohms. ecibels: −10 to +22dB. ize: 90 × 60 × 28mm. omplete with test leads. **2·50.** Post 15p.

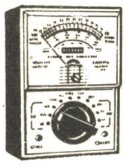

T 601 MULTI-METER
ew style 20,000 .P.V. pocket ultimeter. 5/25/ 0/250/500/2,500V .c. 10/50/100/500/ ,000V a.c. 50μA/ 50A. 6K/6 meg ohms. −20 to +22dB. **3·75.** Post 20p.

MODEL TH-12
20,000 O.P.V. Overload pro- ection. Slide switch selector. 0/0·25/2·5/10/50/250/1,000V a.c. 0/50μA/25/250mA d.c. 0/3K/ 30K/300K/3 meg. −20 to +50dB. **£4·97.** Post 15p.

RUSSIAN 22 RANGE MULTIMETER
Model U437 10,000 O.P.V. A first class versatile in- strument manufactured in U.S.S.R. to the highest standards. Ranges: 2·5/10/ 50/250/500/1,000V d.c. 2·5/ 10/50/250/500/1,000V a.c. D.c. current 100wA/1/10/ 100mA/1A. Resistance 300 ohms/3/30/300K/3mΩ. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE **£5·97.** Post 25p.

HIOKI MODEL 730X
30,000 O.P.V. Overload pro- tection. 6/30/60/300/600/ 1,200V d.c. 12/60/120/600/ 1,200V a.c. 60μA/30mA/ 300 mA. 2K/200K/2 meg. ohm. −10 to +63dB. **£7·50.** Post 15p.

MODEL PL436
20kΩ/V d.c. 8kΩ/V a.c. Mirror scale. 0·6/3/12/30/120/600V d.c. 3/30/120/600V a.c. 50/600μA/60/ 600mA. 10/100K/ 1 Meg/10 MegΩ. −20 to +46dB. **£6·97.** Post 12p.

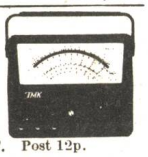

MODEL 500 30,000 O.P.V. with overload protection mirror scale 0/0·5/2·5/20/25/ 100/250/500/1,000V d.c. 0/2·5/10/25/100/250/500/ 1,000V a.c. 0/50μA/5/50/ 500mA. 12 amp. d.c. 0/60/K/6 Meg./60 MegΩ. **£9·95.** Post paid. Leather case **£1·75.**

U4312 MULTIMETER
Extremely sturdy instrument for general electrical use, 667 O.P.V. 0/0·3/1·5/7·5/30/60/150/300/ 600/900V d.c. and 75mV. 0/0·3/1·5/7·5/30/60/150/300/ 600/900V a.c. 0/300μA/1·5/6/15/60/150 600MA/1·5/6 amp. d.c. 0/1·5/15/60/150/600MA/ 1·5/6 amp. a.c. 0/200Ω/3k/30kΩ. Accuracy. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. **£9·50.** Post 25p.

HIOKI MODEL 700X
100,000 O.P.V. Overload protection. Mirror scale. 0·3/0·6/1·2/1·5/8/6/12/30/60/ 120/300/600/1,200V d.c. 1·5/3/6/12/30/60/150/300/ 600/1,200V a.c. 15/30μA/3/6/30/60/150/300mA 6/12 amp. d.c. 2K/200K/ 2 Meg/20 Meg ohm −20 to +63dB. **£13·50.** Post 20p.

MODEL C-7080 EN
Giant 6in mirror scale. 20,000 O.P.V. 0/0·25/1·2·5/10/50/250/ 1,000/5,000V d.c. 0/2·5/10 /50/250/1,000/5,000V a.c. 0/50μA/1/10/100/500mA/ 10 amp. d.c. 0/2K/200K/ 20 meg. −20 to +50dB. **£13·95.** Post 35p.

370 WTR MULTIMETER
Features a.c. current ranges. 20,000 O.P.V. 0/0·5/2·5/10 / 50 / 250 / 500 / 1,000V d.c. 0/2·5/10/50/250/500/ 1,000V a.c. 0/50μA/1/10 / 100mA / 1 / 10 amp. d.c. 0/100mA/1/10 amp. a.c. 0 / 5K / 50K / 500K / 5MEG / 50MEG. −20 +62dB. **£15.** Post 25p.

KAMODEN 72.200 MULTITESTER
High sensitivity tester. 200,000 o.p.v. Overload protection. Mirror scale. Ranges: 0/0·06/0·3/3/30/ 120/600/1,200V d.c., 0/3/ 12/60/300/11,200V a.c. 0/6μA/1·2mA/120mA/ 600mA/12A d.c. 0/12A a.c. −20 to +63dB. 0/ 2kΩ/200kΩ/2MΩ/200 MΩ. **£16·95.** Post 30p.

TMK LAB TESTER
100,000 O.P.V. 6½in scale buzzer short circuit check. Sensitivity: 100,000 OPV d.c. 5/Volt a.c. D.c. volts: 0·5, 2·5, 10, 50, 250, 1,000V. A.c. volts: 3, 10. 50, 250, 500, 1,000V. D.c. current: 10, 100μA, 10, 100, 500mA, 2·5, 10A. Resistance: 1K, 10K, 100K, 10 meg. 100 meg. Decibels: −10 to +49dB. Plastic case with carrying handle, size 7¼in × 6¾in × 3¼in. **£18·95.** P. & P. 25p.

Model S-100TR MULTIMETER/TRANSISTOR TESTER. 100,000 O.P.V. mirror scale/overload protec- tion. 0/0·12/0·6/3/12/30/120/ 600V d.c. 0/6/30/120/600V a.c. 0/12/600μA/12/300mA/12 amp. d.c. 0/10 K/1 MEG/100 MEG. −20 to +50dB. 0·01–2 MFD. Transistor tester measures Alpha, beta and Ico. Complete with batteries instructions and leads. **£13·50.** Post 25p.

LB4 TRANSISTOR TESTER
Tests PNP or NPN transistors, Audio indication. Operates on two 1·5V batteries. Complete with all instructions, etc. **£4·50.** Post 20p.

KAMODEN HM-350 TRANSISTOR TESTER
High quality instrument to test Reverse Leak current and D.C. current. Amplification factor of NPN, PNP, transistors, diodes, SCR's, etc. 4" × 4¾" clear scale meter. Operates from internal batteries. Complete with instructions, leads and carrying handle. **£12·50.** Post 30p.

LB3 TRANSISTOR TESTER
Tests ICO and B. *Pnp/npn*. Operates from 9V battery. Complete with all instructions, etc. **£3·95.** Post 20p.

MODEL 449A IN CIRCUIT TRANSISTOR TESTER
Checks true a.c beta in/out. Checks Icbo. Checks diodes in/out. Checks SCR, etc. Beta HI 10—500 LO 2—50 Ibco 0·5000μA. 220/240V a.c. operation. **£17·50.** Post 25p.

MODEL U4311 SUB-STANDARD MULTI-RANGE VOLT AMMETER
Sensitivity 330 ohms/ Volt a.c. and d.c. Accuracy 0·5% d.c. 1% a.c. Scale length 165mm. 0/300/750μA/1·5/3/7·5/ 15/30/75/150/300/ 750mA/1·5/3/7·5 amp. d.c. 0/3/7·5/15/30/75/150/ 300/750mA/1·5/3/7·5 amp. a.c. 0/75/150/300/ 750mV/1·5/3/7·5·15·30/ 75/150/300/750V d.c. 0/ 750mV/1·5/3/7·5/15/30/ 75/150/300/750V a.c. Automatic cut out. Supplied complete with test leads, manual and test certificates. **£49.** Post 50p.

TE-65 VALVE VOLTMETER
28 ranges. D.c. volts 1·5–1,500V a.c. volts 1·5–1,500V. Resistance up to 1,000 megohms. 200/240V r a.c. operation. Complete with probe and instructions. **£17·50.** Post 30p. Additional probes available: R.F. **£2·12**; H.V. **£2·50.**

KAMODEN HM720B F.E.T. V.O.M.
Input impedance 10MΩ. Ranges: 0/0·25/1/2·5/10/50/ 250/1,000V d.c. 0/2·5/10/50/ 250/1,000V a.c. 0/25μA/2·5/ 25/250MA d.c. −20 to +62dB. 0/5k/50k/500k/ 5MΩ/500MΩ. **£14·95.** Post 30p.

TE-40 HIGH SENSITIVITY A.C. VOLTMETER
10 meg. input 10 ranges: 01/·003/·1/·3/1/3/10/30/100/ 300V. R.M.S. 4cps.-1·2 Mc/s. Decibels −40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V. a.c. **£17·50.** Carr. 25p.

TMK MODEL 117 F.E.T. ELECTRONIC VOLTMETER
Battery-operated, 11 meg input. 26 ranges. Large 4½in mirror scale. Size 5¾in × 4¾in × 2¾in. D.c. volts 0·3–1,200V. A.c. volts 3–300V R.M.S. 8·0·800V P-P. D.c. Current 0·12·12MA. Resistance up to 2,000M ohm. Decibels −20 to +51dB. Complete with leads/instructions. **£17·50.** P. & P. 20p.

MODEL L-55 FET V.O.M.
Input impedance 10 meg ohms. 0/0·3/1·2/6/ 30/120/600V d.c. 0/3/12/ 60/120/600V a.c. 0/120μA /120mA d.c. 0/1K/100K/ 10 meg/100 meg ohms. **£15·97.** Post 25p.

KAMODEN HMG-500 INSULATION RESISTANCE TESTER
Range 0–1,000 Megohms, 500 Volt. Battery operated. Wide range clear meter 4¾" × 4". Complete with deluxe carrying case, batteries, instructions. **£19·95.** Post 30p.

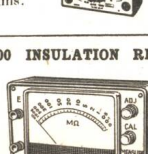

BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR
Sine 18-200,000 Hz: Square 18-50,000 Hz. Output max. +10dB (10 K ohms) Operation internal batteries. Attractive 2-tone case 7⅞in × 5in × 2in. Price **£17·50.** Carr. 17p.

CI-5 PULSE OSCILLOSCOPE
For display of pulsed and periodic waveforms in electronic circuits VERT. AMP. Bandwidth 10MHz. Sensitivity at 100kHz V RMS/mm. 0·1-25; HOR. AMP. Bandwidth 500kHz. Sensitivity at 100kHz, V RMS/mm. 0·3-25; Pre-set triggered sweep 1-3,000μsec.; free running 20-200,000Hz in nine ranges. Calibrator pips. 220mm × 360mm × 430mm, 115-230V a.c. operation. **£39.** Carr. paid.

TO-3 PORTABLE OSCILLOSCOPE
8in tube, Y amp. Sensitivity 0·1V p-p/CM. Bandwidth 1·5cps-1·5MHz. Input imp. 2 meg Ω 25pF X amp sensitivity 0·9V. p-p/CM. Bandwidth 1·5cps-800kHz, Input imp. 2 meg Ω 20pF Time base. 5 ranges 10cps-300kHz. Synchronisation. Internal/external. Illuminated scale 140mm × 215mm × 330mm. Weight 15½lb. 220/240V a.c. Supplied brand new with handbook. **£47·50.** Carr. 50p.

RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE
5MHz Pass Band. Separate Y1 and Y2 amplifiers. Rectangular 5in × 4in C.R.T. Calibrated triggered sweep from 0·2μ/sec to 100 milli-sec per cm. Free running time base 50 Hz-1MHz. Built-in time base calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual. **£87.** Carr. paid.

MODEL AT201 DECADE ATTENUATOR
Frequency range 0-200kHz. Attenuator 0-111dB, 0·1dB step. Impedance 600 ohms. Max. Input power 30dBm. Size 180mm × 90mm × 55mm. **£12·50.** Post 37p.

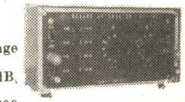

ARF-300 AF/RF SIGNAL GENERATOR
All transistorised, compact, fully portable. AF sine wave 18 Hz to 220 KHz. AF square wave 18 Hz to 100 KHz. Output sine/square 10v. P-P. RF 100 KHz to 200 MHz. Output 1v. maximum. Operation 220/240v. AC. Complete with instructions and leads. **£29·95.** Post 50p.

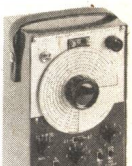

TE-20D RF SIGNAL GENERATOR
Accurate wide range signal generator covering 120 kHz-500 MHz on 6 bands. Directly calibrated. Variable R.F. attenuator audio output, Xtal socket for calibration. 220/240V a.c. Brand new with instructions. **£17·50.** Carr. 37p. Size 140mm × 215mm × 170mm.

TE22 SINE SQUARE WAVE AUDIO GENERATORS
Sine: 20c/s to 200 kc/s on 4 bands. Square: 20c/s to 30 kc/s. Output impedance 5,000 ohms. 200/250V a.c. Supplied brand new and guaranteed with instruction manual and leads. **£17·50.** Carr. 37½p.

GWS G.W.SMITH & CO (RADIO) LTD

UNR 30 RECEIVER

4 Bands covering 550kHz-30MHz. BFO Built-in Speaker 220/240V a.c. Brand new with instructions.

OUR PRICE **£15·75** Carr. 37p

UR-1A RECEIVER

4 Bands covering 550kHz-30MHz. FET, S Meter. Variable BFO for SSB. Built-in Speaker. Bandspread. Sensitivity Control. 220/240V a.c. or 12V d.c. 12¾ × 4¾in × 7in. Brand new with instructions.

OUR PRICE **£25·00** Carr. 37p

SKYWOOD CX203 RECEIVER

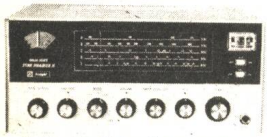

Solid state. 5 bands covering 200-420kHz and 0·55 to 30MHz. Illuminated slide rule dial. Bandspread. Aerial tuning. BFO, AVC, ANL, "S" meter. AM/CW/SS B. Integrated speaker and phone socket, 220/240V a.c. or 12V d.c. Size 325 × 266 × 150mm. Complete with instructions and circuit.

OUR PRICE **£32·50** Carr. 50p

LAFAYETTE HA-600 RECEIVER

General coverage 150-400kHz, 550kHz-30MHz. FET front end, 2 mech. filters, product detector, variable BFO, noise limiter, S Meter Bandspread. RF Gain. 15in × 9¾in × 8¼in. 18 lb. 220/240V a.c. or 12V d.c. Brand new with instructions.

OUR PRICE **£50·00** Carr. 50p

TRIO 9R59DS RECEIVER

4 bands covering 550kHz-30MHz continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. SSB-CW. ANL. Variable BFO. 8 meter. 8ep. bandspread dial. IF frequency 445kHz audio output 1·5W. Variable RF and AF gain controls 115/250V a.c. Size: 7in × 13in × 10in with instruction manual.

OUR PRICE **£49·50** Carr. Paid

FULL RANGE OF TRIO STOCKED

GWS

ALSO SEE PREVIOUS PAGES

EMI LOUDSPEAKERS

Model 350. 13in × 8in with single tweeter /crossover. 20-20,000 Hz. 15W RMS. Available 8 or 15 ohms. **£7·25** each. P. & P. 37p.

Model 450. 13in × 8in with twin tweeters/ crossover. 55-13,000 Hz. 8W RMS.

Available 8 or 15 ohms. **£3·62** each. P. & P. 25p.

SPECIAL OFFER!

STEREO SPEAKERS

Matched pair of bookshelf speakers. De luxe teak veneered finish. Size 14½ in × 9in × 7½ in. 8 ohms. 8W RMS 16W peak. Complete with DIN lead.

OUR PRICE **£12·95** Carr. 50p

HA-10 STEREO HEADPHONE AMPLIFIER

All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. Inputs 5MU/100MU. Output 50MW.

OUR PRICE **£5·97** P. & P. 20p

MP7 MIXER PREAMPLIFIER

5 microphone inputs each with individualgain controls enabling complete mixing facilities. Battery operated. 9¼in × 5in × 3in. Inputs Mics: 3 × 3mV 50K; 2 × 3mV 600 ohm. Phono meg. 4mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K.

OUR PRICE **£8·97** P. & P. 20p

1021 STEREO LISTENING STATION

For balancing and gain selection of loudspks. with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets 6in × 4in × 2¼in.

OUR PRICE **£2·25** P. & P. 20p

HAND HELD 2-WAY WALKIE TALKIES

2 channel 300mW

£52·50 Pair. Post 50p.

3 channel 1W.

£71·25 Pair. Post 50p.

Battery operation. Volume and squelch controls. Call button and press to talk button. Telescopic aerial. Complete carrying cases. 100mW **£24·95** pair. Post 50p.

(Note: Licence required for operation in U.K.)

AUDIOTRONIC

RANGE OF HIGH QUALITY EQUIPMENT

ACR14 BATTERY MAINS CASSETTE RECORDER

Portable twin track mono recorder with automatic recording level control. Built in speaker. Earpiece socket. Input for radio or record player. Fast forward and rewind. Output 500mW; 220/240V a.c. or 6V d.c. operation. Complete with remote control microphone, mains lead, earpiece and batteries.

GWS PRICE **£10·50** P. & P. 50p

Sportsman AM/FM Portable Radio AR1000

5 wavebands covering A.M.: 535 – 1065kHz; F.M. 88–108MHz; A.I.R : 108 – 135MHz; P.B. 147–174MHz; W.B.: 162·5MHz Large horizontal slide dial with logging scale. Slider volume and squelch controls. 7 section telescopic aerial for F.M. and built in ferrite bar for A.M. A.F.C. 3in speaker. Earpiece socket. Green leatherette covered cabinet with metal side panels. Size 152 × 79 × 219mm. Battery/mains operation.

OUR PRICE **£11·50** P.&P. 35p

AMR-9000 GLOBAL AM/FM PORTABLE

10 wavebands covering A.M.: 535–1605kHz; L.W.: 150–380kHz; M.B. 1·6–4·0MHz; S.W.1: 4·0–8·0MHz; S.W.2: 8·0–1·6MHz; S.W.3: 16–24MHz; P.S.B.1: 30–50MHz; P.S.B.2: 148–174MHz; F.M. 88–108MHz; A.I.R.: 108–136MHz. Features time zone map and timing dial. Large clear scale. Telescopic aerial and built in aerial. A.F.C. on F.M. 6in × 4in speaker and personal earpiece. Battery/mains operation. Size: 345 × 133 × 305mm.

OUR PRICE **£36·00** P.&P. 50p

STEREO HEADPHONES

LSH20. Individual volume controls. Stereo mono switch. 8 ohms. 40–19,000Hz.

£3·50 P. & P. 30p

LSH30. Open back type. Individual tone and volume controls. 8 ohms. 30–20,000Hz.

£5·50 P. & P. 30p

LSH40. Two way speaker system. Individual volume controls. 8 ohms. 20–20,000Hz.

£6·95 P. & P. 30p

LSH60. 3in speaker units. 8 ohms. 20–20,000Hz. Complete with zipped carrying case.

£8·50 P. & P. 30p

LQH400. 4-channel dynamic headphones. Each earpiece has 4 drive units. Two stereo jack plugs fitted to leads. 4-32 ohms. 20–20,000Hz.

£9·95 P. & P. 30p

ACD660 STEREO CASSETTE DECK

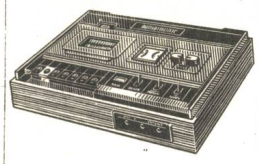

A beautifully styled 4 track stereo deck with an outstanding specification offered at a remarkably low price. Incorporates a host of features including switchable noise filter, normal/chrome tape selector, twin VU meter, slider record/playback level controls, front panel headphone socket, recording indicator lamp, phono/Din. line input sockets, 3·5mm mike input sockets, etc., etc. Frequency response 100-8kHz (100–12kHz CrO2). S/N —45dB. Crosstalk —45dB. Separation —35dB. Noise limiter —6dB at 10kHz. Complete with phone connecting leads.

GWS Price **£39·50** Carr. & Ins. 50p

AHP8D 8 TRACK STEREO TAPE DECK

Can be used with most hi-fi amplifiers. Push button track selector andilluminated track indicators. Attractiv cabinet with black and silver trim Output level 750mV. 220/240V a.c

GWS Price **£11·95** P. & P. 50p, plus V.A.T.

AHP8A 8 TRACK STEREO TAPE PLAYER

Incorporates built in amplifier giving 4½ + 4½W r.m.s. output Pushbutton track selector illuminated track indicators, slide controls for volume, balance and tone. Attractive cabinet with black and silver trim. Output impedance 8 ohms. 220/240V a.c.

GWS Price **£17·25** P. & P. 50p, plus V.A.T.

AUDIOTRONIC DOLBY 'B' NOISE REDUCTION UNITS

Reduce tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Size 16¾in × 8in × 3¼in. a.c. 00/250V2.

PROCESS TWO

For use with cassette and tape recorders. Freq. res. 30Hz—20kHz—2dB. Off tape monitoring. Switchable multiplex filter. Two Dolby calibration meters. S/N better than 70dB. Supplied with test cassette or tape as required.

OUR PRICE **£34·50** P.&P. 50p

PROCESS FOUR

For use with semi professional tape recorders. Freq. res. 30Hz—20kHz ±2dB. S/N better than 70dB. Full source tape monitoring. Record/Replay metering. Switchable multiplex filter. Supplied with test tape.

OUR PRICE **£50·00** P.&P. 50p

LOW NOISE TAPE CASSETTES

Top Hi-Fi quality in library cases

TYPE	5	10	25
C60	£1·29	£2·53	£5·99
C90	£1·85	£3·62	£8·59
C120	£2·29	£4·48	£10·63

P. & P. 15p Post Free

CASSETTE TAPE HEAD CLEANER 30p each. P. & P 5p

ACP-8 8 TRACK CAR PLAYER

Attractive black and silver finish. 12V neg. earth. Slider controls for Volume, Tone and Balance. Channel selector button with red pilot lamp. Complete with speakers, mounting brackets and instructions.

ONLY **£12·50** P. & P. 40p

ACR1 PUSH BUTTON CAR RADIO

Push button tuning of one LW and five MW stations of your choice. 12V pos. or neg. earth. Complete with speaker, mounting brackets and instructions.

OUR PRICE **£8·95** P. & P. 50p

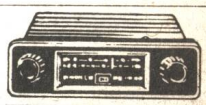

ACR 3500 CAR RADIO

Manual tuning of Medium and Long waves. 12V pos. or neg. earth. Complete with speaker, mounting brackets and instructions.

OUR PRICE **£6·50** P. & P. 50p

ACA 5SE ELECTRIC CAR AERIAL

5 section. Fully automatic. 12V d.c. Extends to approx. 40in. Complete with switch, all leads and instructions.

OUR PRICE **£5·95**

P. & P. 50p

SAVE UP TO 33⅓% OR MORE! GWS

RECORD DECK PACKAGES

Carriage and Packing 75p

Complete units with Stereo cartridge ready wired in plinth and cover.

GARRARD

2025 TC/9TAHCD	£10·65
SP25 111/G800	£15·00
SP25 111/M44E	£16·45
SP25 111/M44-7	£16·10
SP25 111/M55E	£16·90
SP25 111 Module/M75-6	£18·99
AP76/G800	£23·50
AP76/G800E	£25·95
AP76/M44E	£24·95
AP76/M55E	£25·65
AP76/M75ED	£31·70
AP76/M75EJ	£27·85
AP76 Module M75–6	£26·95
AP96 Module M75–6	£30·40
ZERO 100S Module/M93E	£41·85

B.S.R. McDONALD

210/SC7M	£6·85
MP60/G800	£15·00
MP60/TPD1/G800	£15·20
MP60/M44-7	£16·60
HT70/TPD1/G800	£18·60

GOLDRING

GL72/G800	£30·90
GL75/G800	£33·60
GL75/G800E	£36·75

GOODMANS

TD100/G800 Teak	£46·85
TD100/G800 White	£48·60

LEAK

Delta/M75-6	£43·95

PHILIPS

GA105/GP200	£13·80
GA160/GP200 Teak	£19·50
GA212/GP400	£45·25
GA308 (less cartridge)	£23·95
GA308 P.U.	£32·75

PIONEER

PL12D (Less cartridge)	£31·75
PL15C (Less cartridge)	£44·25
PL41D (Less cartridge)	£104·75
PL50 (Less cartridge)	£98·90
PL61 (Less cartridge)	£110·30
PLA35 (Less cartridge)	£61·55

THORENS

TD160C/Ortofon M15E Super	£66·95
TD125 AB/11/Ortofon M15ES	£104·25
TD165/Ortofon M15E Super	£59·60

WHARFEDALE

Linton/M44-7 Teak	£23·70
Linton/M44-7 White	£23·90

SINCLAIR PROJECT 60 PACKAGE DEALS

2 × Z30/Stereo 60/PZ5 **£15·95.** P. & P. 37p.

2 × Z30/Stereo 69/PZ6 **£18·00.** P. & P. 37p.

2 × Z50/Stereo 60/PZ8 **£20·25.** P. & P. 37p.

Transformer for PZ8 **£3** extra.

Active Filter Unit **£4·45.**

Project 60 FM Tuner **£14·95.**

Pair of Q16 Speakers **£10·70.**

Sinclair Project 605 **£20·97.** P. & P. 37p.

All Sinclair Products in stock: 2000 Stereo Amplifier, **£22·95**; 3000 Stereo Amplifier, **£28·95**; 2000/3000 Stereo Tuner, **£26·30.**

Q830 Speakers, **£23·95** pair, P. & P. 50p extra on above items.

RECORD DECKS

Carriage & Packing 50p

B.S.R. McDONALD

C114 Mini	£3·95
C129 Mono	£5·50
C137	£7·00
510/TPD1	£13·95
610	£9·90
610/TPD1	£14·85
710	£19·20
810	£24·50
MP60	£7·65
MP60/G800	£10·25
MP60/TPD1	£12·60
MP60/TPD2	£11·25
HT70	£10·97
HT70/G800	£13·60
HT70/TPD1	£15·95

CONNOISSEUR

BD1 Kit	£9·10
BD1 Chassis	£11·35
BD1/SAU2/Plinth/Cover	£27·60
BD2/SAU2/Chassis	£22·70
BD2/SAU2/Plinth/Cover	£28·20

GARRARD

2025 T/C Stereo	£6·40
SP25 III	£8·50
SP25 III/Acos GP104	£8·50
SP25111/G800	£10·95
SP25/M75–6	£13·90
AP76	£15·55
SL65B	£11·15
SL72B	£17·75
SL95B	£25·25
401	£23·50
ZERO 100A	£30·30
ZERO 100S	£27·95

GOLDRING

G99	£16·85
G101P/C	£16·85
GL69/2	£15·75
GL72	£17·85
GL72/P	£23·20
GL75	£23·75
GL75P	£29·30
GL78 P/C	£46·55
GL85/P/C	£49·50

SPECIAL GARRARD OFFERS!

STEREO 1025T

4 speed autochanger unit fitted with stereo ceramic cartridge.

OUR PRICE **£4·95** Carr. & Ins. 50p

SP25 III WITH ACOS GP 104

4 speed single record player fitted with Acos GP104 stereo ceramic cartridge.

OUR PRICE **£8·50** Carr. & Ins. 50p

AUDIOTRONIC AMB500 MULTI BAND RADIO

5 wavebands covering MW 535 – 1605KHz and F.M. 88–175MHz. All transistor. Battery or mains operation. Built in aerial and 8 section telescopic aerial. Complete with batteries, shoulder strap and earpiece.

ONLY **£6·95** P. & P. 35p

FANTASTIC OFFER!

CASSETTE RECORDER

with a pair of CS88 speakers. List £96·10.

OUR PRICE **£56·50** P. & P. 50p

CASSETTE, P. & P. 50p.

CS35D Deck	£44·45
CS35/CS88 Speakers	£67·95
GXC40D Deck	£57·20
GXC40 Recorder	£67·20
GXC40T Deck/Receiver	£99·05
GXC45 Deck	£78·25
GXC46D Dolby Deck	£83·55
GXC46 Recorder	£89·95
GXC60D Deck	£87·65
GXC65D Dolby Deck	£92·65

CARTRIDGE (P. & P. 50p)

CR81 Deck with amps.	£65·40
CR81D Deck	£53·60
CR81T Recorder/Receiver	£92·75
CR80S88 4 channel Recorder	£114·25
CR80D88 4 chan. Recorder	£93·65

TAPE (P. & P. 75p)

4000DS Deck	£59·95
4000DS Dust Cover	£3·95
1721L Recorder	£60·35
X5000 Recorder	£82·50
X201D Deck	£108·20
GX220D Deck	£123·95
GX221D	£138·40
GX280D Deck	£196·50
GX370 Deck	£211·50

TAPE CASSETTE (P. & P. 75p)

GX1900D Deck	£144·50

MICROPHONES (P. & P. 50p)

ADM.11 Dynamic (pair)	£7·50

STEREO RECEIVERS (P. & P. 75p)

AA6300 20+20 watt	£61·95
AA8030 25+25 watt	£92·50
AA8080 40+40 watt	£117·50
AA8100S 2×36 or 4×18 watt	£175·00
AA8500 65+65 watt	£150·50

STEREO AMPLIFIERS (P. & P. 50p)

AA5200 20+20 watt	£61·75
AA5500 30+30 watt	£78·50
AA5800 45+45 watt	£117·50

STEREO TUNERS (P. & P. 50p)

AT550 AM/FM	£60·50
AT580 AM/FM	£94·50

4-CHANNEL UNIT (P. & P. 50p)

SS1 Synthesiser	£39·95

SPEAKERS

SW155 (each)	£51·00

STEREO HEADPHONES

ASE11	£4·75
ASE20	£7·30
ASE22	£8·25

HOMER INTERCOMS

Ideal for home, office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.

2 Station **£12·97.** P. & P. 15p.
3 Station **£5·25.** P. & P. 15p.
4 Station **£6·62.** P. & P. 17p.

SH628 STEREO HEADPHONES

Outstanding value. Soft earpads, adjustable headband. 8-16 ohms. 20-20,000 Hz. Complete with lead and stereo plug.

OUR PRICE **£1·87** P. & P. 30p

TE1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET

Sensitive magnetic headset with soft earpads. Impedance 2,600 ohms (d.c. 600 ohms). Frequency response 200-4,000 Hz.

OUR PRICE **£2·25** P. & P. 30p

LH02S STEREO HEADPHONES

Lightweight headphones with padded earpieces. 4-16 ohms. 20-20,000 Hz. Complete with 6 ft cord and plug.

OUR PRICE **£1·95** P. & P. 30p

BH001 HEADSET AND BOOM MICROPHONE

Moving coil. Headphone imp. 16 ohms. Mike imp. 200 ohms. Ideal for language teaching, communications etc. Complete with leads and plugs.

OUR PRICE **£4·95** P. & P. 30p

FM TUNER CHASSIS

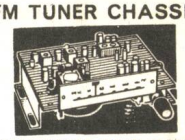

6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6in × 4in × 2½in 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108MHz. Ready built ready for use.

OUR PRICE **£5·95** P. & P. 20p

Stereo Multiplex Adaptor **£4·97.**

SPECIAL PURCHASE!

FERGUSON EXPORT MODELS

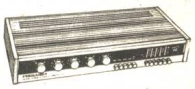

3408 STEREO TUNER AMP. Covers FM 88-108 MHz. Five push button tuning scales. 8+8 watts rms. Inputs for stereo ceramic cartridge and tape, etc. Separate bass, treble, balance and volume controls.

OUR PRICE **£31·50** Carr. 50p

3416 STEREO TAPE DECK

4 track. 7½, 3¾, 1⅞ i.p.s. Stereo/mono record/play. 7in reels. Inputs for dynamic mikes, radio, gram. Complete with cover.

OUR PRICE **£41·95** Carr. 75p

VAT

All prices are subject to **10% VAT** (10p in the £)

Order with confidence by post – but remember to add 10% VAT (10p in the £) to total value of goods including carriage/packing and send cash with order. PLEASE PRINT NAME & ADDRESS CLEARLY.

SEND LARGE S.A.E. FOR FULL HI-FI DISCOUNT LIST

G.W.SMITH & CO (RADIO) LTD

ALL MAIL ORDERS TO
UNIT 4, THE HYDE INDUSTRIAL ESTATE, THE HYDE, LONDON NW9 6JJ
TELEPHONE 01-205 3735

PERSONAL CALLERS WELCOME AT ANY OF OUR RETAIL BRANCHES

CENTRAL LONDON		311, Edgware Road, W.2.	Tel: 01-262 0387
257/8, Tottenham Court Rd, W.1.	Tel: 01-580 0670	382, Edgware Road, W.2.	Tel: 01-723 4194
10, Tottenham Court Rd, W.1.	Tel: 01-637 2232	152/3, Fleet Street, E.C.4.	Tel: 01-353 2833
27, Tottenham Court Rd, W.1.	Tel: 01-636 3715	378, Harrow Road, W.9.	Tel: 01-286 9530
87, Tottenham Court Rd, W.1.	Tel: 01-580 3739	**ESSEX**	
21, Old Compton Street, W.1.	Tel: 01-437 9369	86, South Street, Romford.	Tel: Romford 20218
3, Lisle Street, W.C.2.	Tel: 01-437 8204	**SURREY**	
34, Lisle Street, W.C.2.	Tel: 01-437 9155	1046, Whitgift Centre, Croydon.	Tel: 01-681 3027
118, Edgware Road, W.2.	Tel: 01-723 9789	27 & 21, Eden Street, Kingston.	Tel: 01-546 7845
193, Edgware Road, W.2.	Tel: 01-723 6211	32, Hill Street, Richmond.	Tel: 01-948 1441

ALL BRANCHES OPEN 9 a.m.-6 p.m. MONDAY TO SATURDAY

Access — Buy it with Access
BARCLAYCARD welcome here

CREDIT TERMS FOR CALLERS (£50 and over)

ALL EQUIPMENT IS BRAND NEW, FULLY GUARANTEED AND OFFERED WITH FULL AFTER SALES SERVICE

All items and prices are correct at **21·6·73** but subject to change without notice. E. & O. E.

PART OF THE AUDIOTRONIC GROUP OF COMPANIES

TERMS Retail mail order subject to £1·00 minimum order. Cash with order only.
Trade and educational establishments M/AC on application (minimum £5·00).
Postage 10p inland, 25p, Europe.
GUARANTEE: All goods carry full manufacturer's warranty. Get in touch today for a complete run-down of devices available from SCS (include SAE).

S.C.S. Components Ltd., P.O. Box No. 26, Wembley, Middlesex HA0 1YY
Registered in London No. 888454

Device of the Month NE540L

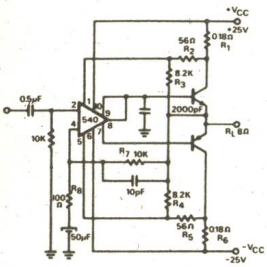

35 Watt Amplifier

The Signetics 540 is a monolithic, class AB power audio amplifier designed specifically to drive a pair of complementary output transistors.

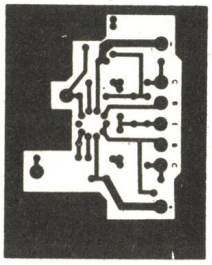

This device features: internal current limiting; low standby current; high output current capability; wide power bandwidth; low distortion – features which make this device ideal for use as an audio power amplifier.

Signetics power driver NE540L
Yours for just

£1·20 + VAT

including application notes.

Compatible device MC1339P

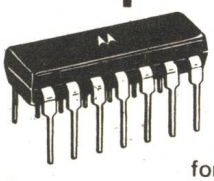

From Motorola, a monolithic dual stereo preamplifier for low noise preamplification of stereo audio signals. Just look at some of these features:

* Low audio noise
* High channel separation
* Single power supply
* High input impedance
* Built-in power supply filter
* Emitter follower output

Motorola monolithic duel stereo preamplifier

only £1·20 + VAT

including applications notes.

PHONOSONICS P. C. BOARDS

All PCBs Fibreglass, Drilled, Roller-Tinned. Layout and Circuit Diagrams Free with each PCB. Unless stated "as published", PCBs are designed by Phonosonics. Pots are rotary unless stated as slider.

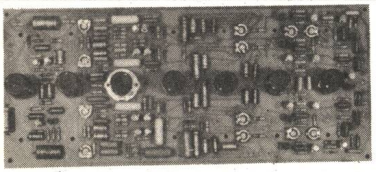

AURORA
Multichannel Sound Controlled Light (PE Apr./Aug. 71). S/c's (excl. SCRs), Rs, Cs, Pots, Cores—8 ch. **£17·75**; 4 ch. **£10·15**. Reg. PSU **£3·65**. PCB—4 ch. control (4¼in × 10¾in) Mk. 2—also holds rotary or slider pots **£2·35**. PCB (4¾in × 5in) Mk. 2—for PSU, Sync Gen. 8 cores, 8 SCRs, **£1·35**. SCRs—1A, **50p**, 3A, **55p**.

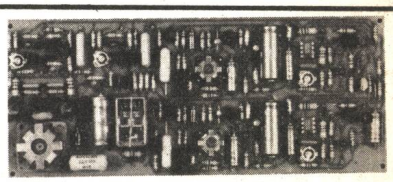

HI-FI TAPE LINK
(PE Mar./Apr. 73). S/c's, i.c.'s, Rs, Cs, Relay and pc-base, Pot Cores and pc-bases, Sw's, Pots, Panel Lamp—Mono, **£11·80**; Stereo, **£18·70**. PSU, **£2·50**. PCB—Main Assy. (3¾in × 9in) (Stereo) also holds relay and cores, **£1·85**. PCB—Sub-Assy. (2¼in × 6¼in) (Stereo) holds Sw-assoc. Rs, Cs, Presets and mounts on Sw's, **80p**.

A.F. SIGNAL GENERATOR
(PE Nov. 72). S/c's, Rs, Cs, Pots, Sw's, PCB (2¼in × 4in) also holds Sw's, **£3·15**.

AUDIO MIXER
(PE Jan. 72). Rs, Cs, Pots, PCB (1¼in × 2in) (i.c. excl.), **£1·55**.

DOOR BELL YODELLER
(PE Apr. 71). S/c's, Rs, Cs, Pots, PCB (3in × 3¼in), **£5·10**. T/fmr **£1·30**. L/spkr **£1·30**.

BIOLOGICAL AMPLIFIER
(PE Jan./Feb. 73). P/A Set—S/c's, i.c.'s, Rs, Cs, Pots, PCB (1¼in × 3¼in), **£3·70**. O/P Stages (S/c's, Rs, Cs, Pots and Sw's as reqd.). Alphaphone **60p**, Cardiophone **75p**, Freq. Meter **£1·90**, Vis-Feedback **60p**. Audio Amp PC7 avail. to order **£4·75**.

ELECTRONIC PIANO
(PE Sep. 72/Jan. 73)—Details in lists

GEMINI STEREO AMPLIFIER
(PE Nov. 70/Mar. 71) Stereo Sets and PCBs. Pre-amp—S/c's **£1·85**. Rs, Cs, Pots, Maka-Sw's—with ¼W MO Rs, **£11·60**—with ¼W CF Rs, **£9·35**—with ½W CF Rs, **£8·90**. PCB (3¼in × 10¾in) for sets with MO and ¼W Rs, also holds rotary or slider pots and Maka-Sw's, **£2·10**. Main Amp—Rs, Cs, Pots, **£5·40**. PCB (3¼in × 5in), **£1·40**. PSU—Rs, Cs, Pot, **£3·70**. PCB (2in × 4in), **75p**.

LOGICAL RADIO CONTROL
(PE Apr./Jun. 72)—Details in lists

MODEL SERVO CONTROL
(PE Feb./Mar. 72)—Details in lists

GEMINI STEREO TUNER
(PE Apr./Jun. 72). Rs, Cs, Pot, **£3·80**. PCB as publ., **£1·50**.

8 WATT AMPLIFIER
(PW Nov./Dec. 72). Pre-amp—S/c's, Rs, Cs, Pots, Sw—Mono, **£2·50**; Stereo, **£5·20**. PCB (3¼in × 7¼in) (Stereo) also holds rotary or slider pots and Sw, **£1·50**. Main Amp—S/c's, Rs, Cs, Pot—Mono, **£3·90**; Stereo, **£7·70**. PCB (2¼in × 3in) Mono), **60p**.

MICROPHONE MIXER
(PE Apr. 69). S/c's, Rs, Cs, Pots, **£2·90**. PCB (3¾in × 4¼in) also holds 6 rotary or 4 slider pots, **£1·20**.

POST AND PACKING
U.K. 10p per order. EXPORT at cost—please allow for this when ordering and also state whether air or surface postage required.

REVERBERATION UNIT
(PW Nov./Dec. 72). S/c's, Rs, Cs, Slider Pots, T/fmr, **£6·80**. PCB (2in × 11¼in) also holds sliders, **£1·20**. 9in Spring Unit avail. to order, **£3·75**.

VIBRASONIC GUITAR PRE-AMP
(PW Sept. 70). Incl. Mic P/A, 2-Guitar P/A, Trem and Tone Controls, Master Volume. S/c's, Rs, Cs, LDR, Rotary Pots, Lamp, Coupling T/fmr, **£7·75**. PSU, **£2·80**. PCB (3½in × 10¾in) Mk. 2, also holds 7 rotary or slider pots, **£2·30**.

ULTRASONIC TRANSMITTER-RECEIVER
(PE May 72). S/c's, Rs, Cs, Pot, Relay, Dual PCB (2in × 5½in), **£3·90**. T/ducers avail. to order, **£7·30** per pair.

ALSO
PCBs as published (while stocks last) for:
DIGICAL PSU (PE Aug. 72), **60p**
OSCILLOSCOPE P/A (PE Aug. 72), **40p**
SCORPIO (PE Nov./Dec. 71), **70p**
TRIFFID (PE Feb. 73), **60p**

AND
DIGITRONIC (PW Mar. 73). Read-out PCB (1¼in × 3¼in), **60p**.

V.A.T.
U.K. Orders only—add 10% to total cost of order.

TAPE NOISE LIMITER
(PE Feb. 72). S/c's, Rs, Cs, Pot, PCB (1¼in × 3in), **£2·20**. Reg. PSU and PCB (1¼in × 2¼in), **£3·20**.

VERSATILE LIGHT EFFECTS UNIT
Single Channel Sound Controlled Light with built-in variable strobe. (PE June 72). S/c's, Rs, Cs, Pots, T/fmrs, Keyswitch, **£8·85**. PCB (3¼in × 7¼in) Mk. 2, also holds pots, Sw, T/T7 T/fmr, **£1·50**. SCRs—1A, **50p**, 3A, **55p**.

PHOTOPRINT PROCESS CONTROL
(PE Jan./Feb. 72). Finds exposures, controls timing, stabs. mains voltage. S/c's, SCR, LDR, Rs, Cs, Pots, Relay, Keyswitch, T/fmr, **£7·60**. PCB (3¼in × 5¼in) also holds pots, Sw, relay, **£1·20**.

SOUND SYNTHESISER (PE Current Series)
Details of PCBs and Components in list. Free mailing list service available for further information about PCBs and Sets for this project.

LIST
S.A.E. for free list and with all enquiries please.

PHONOSONICS, DEPT. PE7, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW **MAIL ORDER ONLY**

TRANNIES

1 DOCKYARD, STATION ROAD, OLD HARLOW, ESSEX
Phone Harlow 37739

P/P 10p. Price list S.A.E. (Saturday callers welcome)

ALL PRICES INCLUDE VAT

£19.50 ELECTRONIC DIGITAL CLOCK

(For complete kit of parts including case.)

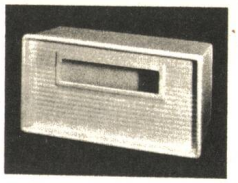

This 4 digit 24 hour clock is available to readers at this special price for 1 month only. Parts would normally cost over £25. Kit of parts includes twelve IC's, indicators, and a smart white plastic case.

74 Series TTL

	1	25		1	25		1	25		1	25
SN7400	16p	15p	SN7423	55p	50p	SN7450	16p	15p	SN7489	6·05p	5·85p
SN7401	16p	15p	SN7425	55p	50p	SN7451	16p	15p	SN7490	74p	72p
SN7402	16p	15p	SN7427	49p	46p	SN7453	16p	15p	SN7491	1·10p	1·04p
SN7403	16p	15p	SN7428	77p	72p	SN7454	16p	15p	SN7492	74p	72p
SN7404	16p	15p	SN7430	16p	15p	SN7460	16p	15p	SN7493	74p	72p
SN7405	16p	15p	SN7432	49p	46p	SN7470	33p	29p	SN7494	85p	72p
SN7406	38p	35p	SN7433	94p	82p	SN7472	33p	29p	SN7495	85p	72p
SN7407	38p	35p	SN7437	72p	69p	SN7473	41p	39p	SN7496	95p	92p
SN7408	20p	18p	SN7438	72p	69p	SN7474	41p	38p	SN74100	1·80p	1·75p
SN7409	20p	18p	SN7440	16p	15p	SN7475	50p	47p	SN74104	1·09p	1·06p
SN7410	17p	15p	SN7441	74p	70p	SN7476	44p	43p	SN74105	1·09p	1·06p
SN7411	27p	25p	SN7442	74p	70p	SN7480	73p	70p	SN74107	44p	42p
SN7412	38p	35p	SN7443	1·43p	1·37p	SN7481	1·32p	1·26p	SN74110	61p	59p
SN7413	32p	29p	SN7444	1·43p	1·37p	SN7482	97p	95p	SN74111	1·37p	1·27p
SN7416	47p	43p	SN7445	2·00p	1·92p	SN7403	1·20p	1·15p	SN74118	1·10p	1·05p
SN7417	47p	43p	SN7446	1·07p	1·02p	SN7484	1·10p	1·05p	SN74119	1·47p	1·37p
SN7420	16p	15p	SN7447	1·10p	1·03p	SN7485	3·96p	3·85p	SN74121	44p	41p
SN7422	55p	50p	SN7448	1·10p	1·03p	SN7486	36p	35p	SN74122	1·54p	1·43p

* Devices may be mixed to qualify for Price Breaks
* 100 Plus less 10% off 25 plus break

Linear Integrated Circuits

301	DIL	50p	723c	DIL	99p
301	TO99	55p	723c	TO99	95p
301	8 PIN DIL	46p	741c	8 PIN DIL	38p
301A	DIL	69p	741c	14 PIN DIL	39p
301A	TO99	69p	741c	TO99	41p
301A	8 PIN DIL	66p	747c	DIL	46p
307	DIL	69p	748c	DIL	39p
307	TO99	69p	748c	TO99	41p
307	8 PIN DIL	66p	1437	DIL	1·27p
308	TO99	6·45p	1458	TO99	1·27p
308A	TO99	6·40p	3046	DIL	84p
709c	DIL	35p	7503	DIL	1·27p
709c	TO99	81p			

Electrolytic Capacitors

4 VOLT		16 VOLT		40 VOLT	
47μF	6½p	15μF	6½p	47μF	6½p
100μF	6½p	33μF	6½p	100μF	9p
220μF	6½p	68μF	6½p	150μF	10p
330μF	6½p	150μF	8p	220μF	11p
1000μF	13p	220μF	9p	470μF	19p
4700μF	29p	680μF	17p	680μF	25p
		1000μF	17p	1000μF	25p
		1500μF	25p	2200μF	44p
		2000μF	43p		
6·3 VOLT					
33μF	6½p				
68μF	6½p				
150μF	6½p	**25 VOLT**			
470μF	11p	10μF	6½p		
680μF	13p	22μF	6½p		
1500μF	18p	47μF	6½p		
2200μF	18p	100μF	8p		
3300μF	26p	150μF	8p	**63 VOLT**	
		220μF	10p	1μF	6½p
		470μF	13p	2·2μF	6½p
10 VOLT		680μF	20p	4·7μF	6½p
22μF	6½p	1000μF	22p	6·8μF	6½p
47μF	6½p	2200μF	39p	10μF	6½p
100μF	6½p	5000μF	68p	22μF	6½p
220μF	8p			68μF	10p
330μF	10p			100μF	11p
470μF	10p	**40 VOLT**		150μF	13p
1000μF	11p	6·8μF	6½p	220μF	19p
1500μF	20p	15μF	6½p	330μF	22p
2200μF	24p	33μF	6½p	470μF	26p
				1000μF	44p

BARGAIN PACKS

Unmarked Packs

Pack of 25 IN4148 **55p**

Pack of 10
BC108 **55p**
BC107 **55p**
(Plastic can)

Pack of 10 Plastic BC109 **55p**

Pack of 10
BC169 **55p**
(unmarked) but tested

2N2646 (unmarked) **33p each**

Pack of 10
2N2926G **55p**
unbranded but tested

Unmarked but fully tested 2N3055
1–9 **33p**
10 plus **27p**

FULLY MARKED TYPES

AD161, AD162 M/P
1–9 **59p**
10 plus **53p**

BC107–BC108 BC109
1–9 **9p**
10–99 **8p**
100 plus **6½p**

BC 182L:-3-4-212-4
1–9 **9p**
10 plus **8p**

AC127 or AC128
1–9 **13p**
10 plus **12p**
100 plus **11p**

ZENER DIODES

400 M/W 5% Miniature **BZY 88** Range
All voltages 3·3–33 Volt **9p each**

1 watt 5%
All voltages 6·8–200 Volts **14p each**

10 watt 5%
All Voltages 7·5–100 Volts **51p each**

Transistors

AC107	16p	BC138	36p	BF260	29p	OC44	14p	**Diodes & Rectifiers**	
AC126	14p	BC142	33p	BF329	18p	OC45	14p		
AC127	13p	BC143	33p	BF330	18p	OC70	23p	1N914	8p
AC128	13p	BC144	30p	BF390	37p	OC71	14p	1N916	8p
AC142K	22p	BC145	26p	BFX84	28p	OC72	14p	1N4148	8p
AC141K	20p	BC147	9p	BFX85	35p	OC81	14p	1S44	10p
AC176	15p	BC148	9p	BFX86	22p	OC83	22p	1N4007	22p
AC187	13p	BC149	9p	BFX87	28p	OC84	28p	18113	17p
AC187K	20p	BC153	16p	BFX88	26p	TIP29A	53p	18120	17p
AC188	13p	BC154	17p	BFY50	21p	TIP30A	64p	18121	15p
AC188K	20p	BC157	13p	BFY51	17p	TIP31A	64p	18130	9p
ACY17	24p	BC158	12p	BFY52	17p	TIP32A	73p	18131	11p
ACY18	21p	BC159	14p	BFY64	39p	TIP33	£1·05	18132	13p
ACY19	25p	BC167	13p	BFY90	72p	TIP34A		18920	8p
ACY20	22p	BC168	11p	BSX20	19p		£1·54	18922	9p
ACY21	23p	BC169	11p	C407	22p	TIP35A		18923	13p
ACY22	18p	BC177	15p	C426	33p		£2·53	18940	6p
ACY39	68p	BC179	15p	C428	31p	TIP36A		AA119	11p
AD140	40p	BC182L	9p	C450	17p		£3·19	AA129	11p
AD142	44p	BC183L	9p	MP8111	35p	TIP41A	79p	AAZ13	11p
AD143	39p	BC184L	9p	MP8112	42p	TIP42A	91p	AAZ15	14p
AD149	38p	BC186	33p	MP8113	35p	2N706	13p	AAZ17	14p
AD150	60p	BC212L	11p	MP8121	33p	2N930	23p	BA100	16p
AD161	29p	BC213L	11p	MP8122	44p	2N1131	22p	BA102	25p
AD162	29p	BC214L	11p	MP8123	50p	2N1132	28p	BA115	8p
AD M/P	50p	BC258	9p	NKT211	28p	2N1613	22p	BA144	14p
AF114	14p	BC259	9p	NKT212	28p	2N1711	26p	BA145	22p
AF115	14p	BC267	14p	NKT214	25p	2N2904	40p	BA154	14p
AF116	14p	BC268	15p	NKT217	55p	2N2904A		BAX13	14p
AF117	14p	BC300	40p	NKT261	23p		44p	BAX16	14p
AF118	92p	BC301	32p	NKT271	20p	2N2905	46p	BAY18	19p
AF124	27p	BC302	30p	NKT274	20p	2N2924	18p	BAY31	9p
AF139	39p	BC303	50p	NKT275	25p	2N2926	10p	BY100	19p
AF239	41p	BC304	40p	NKT403	71p	2N3053	26p	BY126	16p
AL100	77p	BCY70	17p	NKT405	83p	2N3054	55p	BY127	19p
AL102	66p	BCY71	37p	NKY603F		2N3055	52p	BYX10	24p
AL103	55p	BCY72	17p		66p	2N3405	44p	OA5	19p
ASY26	31p	BD123	66p	NKT613G		2N3663	57p	OA9	11p
ASY27	40p	BD130	50p		33p	2N3702	9p	OA10	24p
AU103	99p	BD131	68p	NKT674	26p	2N3703	9p	OA47	9p
AU110	£1·10	BD132	90p	NKT677G		2N3704	9p	OA70	8p
AU111	77p	BD135	42p		24p	2N3705	9p	OA73	11p
BC107	9p	BD136	50p	NKT713	32p	2N3706	9p	OA79	8p
BC108	9p	BD141	£1·87	NKT773	27p	2N3707	9p	OA81	9p
BC109	9p	BD142	50p	OC19	55p	2N3708	9p	OA85	11p
BC113	15½p	BF159	33p	OC20	55p	2N3709	9p	OA90	8p
BC116	16p	BF173	29p	OC23	33p	2N3710	9p	OA91	8p
BC125	16p	BF177	28p	OC25	28p	2N3711	9p	OA95	8p
BC126	25p	BF178	29p	OC28	33p	2N3794	17p	OA200	11p
BC132	16p	BF179	35p	OC29	33p	2N3819	28p		
BC134	16p	BF194	15p	OC35	38p	40361	50p		
BC135	16p	BF195	17p	OC36	38p	40362	50p		
BC137	16p	BF244	27p	OC41	14p	40636	50p		

MULLARD POLYESTER'S

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. mounting: 0·01μF, 0·015μF, 0·22μF, 3½p, 0·33μF, 0·047μF, 0·068μF, 4p, 0·1μF, 4½p 0·15μF, 0·22μF, 5½p, 0·33μF, 7p, 0·47μF, 9½p, 0·68μF, 12p, 1·0μF, 14p, 1·5μF, 22p, 2·2μF, 27p

MULLARD POLYESTER CAPACITORS C296 SERIES
400V: 0·001μF, 0·0015μF, 0·0022μF, 0·0033μF, 0·0047μF, 2½p, 0·0068μF, 0·01μF, 0·015μF 0·022μF, 0·033μF, 3½p, 0·047μF, 0·068μF, 0·1μF, 4½p, 0·15μF, 6½p, 0·22μF, 8½p, 0·33μF, 12p, 0·47μF, 14p.
160V: 0·01μF, 0·015μF, 0·22μF, 0·033μF, 0·047μF, 0·068μF, 8p, 0·1μF 3½p, 0·15μF, 4½p. 0·22μF, 5½p, 0·33μF, 6½p, 0·47μF, 8½p, 0·68μF, 12p, 1·0μF, 14½p.

VOLUME CONTROLS

Potentiometers
Carbon track 500 Ω to 2·2M Ω
Log or Linear
Single **13p**. Dual gang (stereo) **44p**
Single type with D.P. switch **13p** extra.

SLIDE POTENTIOMETERS

58mm, TRACK
SINGLE GANGED, LOG or LIN 1k to 1M. **45p each**
TWIN GANGED, LOG or LIN 1k to 500k. **66p** each.

CARBON SKELETON PRESETS

Small high quality type (linear only).
All valves 100-5 meg ohms.
–1 watt 5½p each
–2·5 watt 6½p each

VEROBOARD

	0·15 Matrix	0·1 Matrix
2½in × 3½in	19p	26p
2½in × 5in	28p	28p
3½in × 3½in	28p	28p
3½in × 5in	33p	32p
5in × 17in (plain)	94p	—

Vero Pins (bag of 36), **22p**
Vero cutter, **50p**; Pin insertion Tools (0·1 and 0·15 matrix) at **61p**.

SLIDE SWITCH

SPST 11p each. D.P.D.T. 13p each.

MINIATURE NEON LAMPS

240V or 110V 1–4 5p, 5 plus 4½p each.

MINITRON DIGITAL INDICATOR TYPE 3015F

Reads 0–9 and decimals
(Data Sheet on request)
ONLY £1·50
16 DIL Socket **33p**
Driven by 7447 **£1·05**

RECTIFIERS

P.I.V.	1 AMP	1·5 AMP
50	IN4001 4½p	PL4001 8p
100	IN4002 4½p	PL4002 9p
200	IN4003 5½p	PL4003 10p
400	IN4004 6½p	PL4004 10p
600	IN4005 8p	PL4005 13p
800	IN4006 9p	PL4006 15p
1000	IN4007 10p	PL4007 20p

BRIDGE RECTIFIERS

P.I.V.	1 AMP	2 AMP	5 AMP	10 AMP
50	33p	53p	£1·76p	£2·20p
100	35p	57p	—	—
200	37p	60p	£1·98p	£2·31p
400	40p	64p	£2·15p	£2·42p
600	44p	66p	£2·42p	£2·75p
800	49p	—	—	—

THYRISTORS

PIV	50	100	200	300	400
1 Amp	28	25	41	44	53
3 Amps	44	50	60	—	66
7 Amps	—	96	1·01	—	1·24

RESISTORS

¼ watt 5% carbon 1p each
¼ watt 10% carbon 1p each
1 watt 10% carbon 2½p each
Range 10 ohms to 4·7 meg.
½ watt m/o 2% 3p each
Range 10–1 meg ohms

RST

VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS

SPECIAL EXPRESS MAIL ORDER SERVICE

Express postage 1p per transistor, over ten post free
INTEGRATED CIRCUITS 5p + 1p each added

	£p		£p		£p		£p		£p
1N21	0·17	AFZ12	1·00	BYZ10	0·35	OAZ211	0·32	ZS170	0·10
1N23	0·20	ASY26	0·25	BYZ11	0·32	OAZ222	0·45	ZS271	0·18
1N85	0·88	ASY27	0·32	BYZ12	0·30	OAZ223	0·45	ZT21	0·25
1N253	0·50	ASY28	0·25	BYZ13	0·25	OAZ224	0·45	ZT43	0·25
1N256	0·50	ASY29	0·30	BYZ15	1·00	OAZ241	0·22	ZTX107	0·15
1N645	0·25	ASY36	0·25	BYZ16	0·62	OAZ242	0·23	ZTX108	0·12
1N725A	0·20	ASY50	0·17	BYZ88C3V3	0·15	OAZ244	0·22	ZTX300	0·12
1N914	0·07	ASY51	0·40	C111	0·65	OAZ246	0·23	ZTX304	0·25
1N4007	0·20	ASY53	0·20	CR81/05	0·25	OAZ290	0·38	ZTX500	0·16
18113	0·15	ASY55	0·20	CR81/40	0·45	OC16	0·50	ZTX503	0·17
18130	0·13	ASY62	0·25	C84B	2·50	OC16T	0·38	ZTX531	0·25
18131	0·13	ASY86	0·33	C810B	3·13	OC19	0·37		
18202	0·23	ASZ21	0·42	DD000	0·15	OC20	0·85	**INTEGRATED CIRCUITS**	
2G371	0·22	ASZ23	0·75	DD003	0·15	OC22	0·50		
2G381	0·25	AUY10	0·98	DD006	0·18	OC23	0·60	7400	0·20
2G414	0·30	AU101	1·50	DD007	0·40	OC24	0·60	7401	0·20
2G417	0·22	BC107	0·10	DD008	0·88	OC25	0·37	7402	0·20
2N404	0·20	BC108	0·10	GD3	0·33	OC26	0·25	7403	0·20
2N697	0·15	BC109	0·10	GD4	0·05	OC28	0·60	7404	0·20
2N698	0·40	BC113	0·15	GD5	0·33	OC29	0·60	7405	0·20
2N706	0·10	BC115	0·20	GD8	0·25	OC30	0·40	7406	0·30
2N706A	0·12	BC116	0·25	GD12	0·05	OC35	0·50	7407	0·30
2N708	0·15	BC116A	0·30	GET102	0·80	OC36	0·60	7408	0·20
2N709	0·63	BC118	0·25	GET103	0·22	OC41	0·25	7409	0·45
2N1091	0·33	BC121	0·20	GET113	0·20	OC42	0·30	7410	0·20
2N1131	0·25	BC122	0·20	GET114	0·15	OC43	0·40	7411	0·23
2N1132	0·25	BC125	0·68	GET115	0·45	OC44	0·17	7412	0·42
2N1302	0·18	BC126	0·65	GET116	0·50	OC44M	0·17	7413	0·30
2N1303	0·18	BC140	0·55	GET120	0·25	OC45	0·12	7416	0·30
2N1304	0·22	BC147	0·15	GET872	0·30	OC45M	0·18	7417	0·30
2N1305	0·22	BC148	0·13	GET875	0·25	OC46	0·27	7420	0·20
2N1306	0·25	BC149	0·15	GET880	0·37	OC57	0·60	7422	0·48
2N1307	0·25	BC157	0·15	GET881	0·25	OC58	0·60	7423	0·48
2N1308	0·25	BC158	0·12	GET882	0·25	OC59	0·65	7425	0·48
2N2147	0·75	BC160	0·63	GET885	0·25	OC66	0·50	7427	0·42
2N2148	0·60	BC169	0·13	GEX44	0·08	OC70	0·12	7428	0·50
2N2160	0·60	BCY31	0·35	GEX45/1	0·10	OC71	0·12	7430	0·20
2N2218	0·20	BCY32	0·55	GEX941	0·15	OC72	0·20	7432	0·42
2N2219	0·20	BCY33	0·25	GJ3M	0·25	OC73	0·30	7433	0·70
2N2369A	0·15	BCY34	0·30	GJ4M	0·38	OC74	0·30	7437	0·65
2N2444	1·99	BCY38	0·40	GJ5M	0·25	OC75	0·25	7438	0·65
2N2613	0·28	BCY39	1·00	GJ7M	0·37	OC76	0·25	7440	0·20
2N2646	0·45	BCY40	0·50	HG1005	0·50	OC77	0·40	7441AN	0·75
2N2904	0·20	BCY42	0·25	HS100A	0·20	OC78	0·20	7442	0·75
2N2904A	0·25	BCY70	0·15	MAT100	0·25	OC79	0·22	7450	0·20
2N2906	0·20	BCY71	0·20	MAT101	0·30	OC81	0·20	7451	0·20
2N2907	0·23	BCZ10	0·35	MAT120	0·25	OC81D	0·20	7453	0·20
2N2924	0·23	BCZ11	0·50	MAT121	0·30	OC81M	0·20	7454	0·20
2N2925	0·15	BD121	0·65	MJE520	0·87	OC81DM	0·18	7460	0·20
2N2926	0·10	BD123	0·80	MJE2955	1·37	OC81Z	0·40	7470	0·30
2N3054	0·50	BD124	0·75	MJE3055	0·87	OC82	0·25	7472	0·30
2N3055	0·75	BDY11	1·62	NKT128	0·35	OC82D	0·20	7473	0·40
2N3702	0·10	BF115	0·25	NKT129	0·30	OC83	0·25	7474	0·40
2N3705	0·10	BF117	0·50	NKT211	0·25	OC84	0·25	7475	0·55
2N3706	0·23	BF167	0·25	NKT213	0·25	OC114	0·38	7476	0·45
2N3707	0·12	BF173	0·25	NKT214	0·15	OC122	0·60	7480	0·80
2N3709	0·10	BF181	0·35	NKT216	0·37	OC123	0·65	7482	0·87
2N3710	0·10	BF184	0·20	NKT217	0·35	OC139	0·25	7483	1·00
2N3711	0·10	BF185	0·20	NKT218	1·13	OC140	0·35	7484	0·90
2N3819	0·35	BF194	0·17	NKT219	0·33	OC141	0·60	7486	0·45
2N5027	0·53	BF195	0·15	NKT222	0·20	OC169	0·20	7490	0·75
2N5088	0·33	BF196	0·15	NKT224	0·22	OC170	0·25	7491AN	1·00
28301	0·50	BF197	0·15	NKT251	0·24	OC171	0·30	7492	0·75
28304	0·75	BF861	0·28	NKT271	0·25	OC200	0·40	7493	0·75
28501	0·37	BF898	0·28	NKT272	0·25	OC201	0·70	7494	0·80
28703	0·62	BFX12	0·20	NKT273	0·15	OC202	0·80	7495	0·80
AA129	0·20	BFX13	0·25	NKT274	0·20	OC203	0·40	7496	1·00
AAZ12	0·30	BFX29	0·25	NKT275	0·25	OC204	0·40	7497	6·25
AAZ13	0·12	BFX30	0·25	NKT277	0·20	OC205	0·75	74100	2·50
AC107	0·37	BFX35	0·98	NKT278	0·25	OC206	0·90	74107	0·50
AC126	0·20	BFX63	0·50	NKT301	0·40	OC207	0·90	74110	0·80
AC127	0·25	BFX84	0·25	NKT304	0·75	OC460	0·20	74111	1·45
AC128	0·20	BFX85	0·30	NKT403	0·75	OC470	0·30	74118	1·00
AC187	0·25	BFX86	0·25	NKT404	0·55	OCP71	0·97	74119	1·90
AC188	0·25	BFX87	0·25	NKT678	0·30	ORP12	0·50	74121	0·60
ACY17	0·30	BFX88	0·20	NKT713	0·25	ORP60	0·40	74122	1·35
ACY18	0·25	BFY10	1·00	NKT773	0·25	ORP61	0·42	74123	2·70
ACY19	0·25	BFY11	1·25	NKT777	0·38	S19T	0·30	74141	1·00
ACY20	0·20	BFY17	0·25	O78B	0·38	SAC40	0·25	74145	1·50
ACY21	0·20	BFY18	0·25			SFT308	0·38	74150	3·35
ACY22	0·10	BFY19	0·25	OA6	0·12	ST722	0·38	74151	1·10
ACY27	0·25	BFY24	0·45	OA47	0·10	ST7231	0·63	74154	2·00
ACY28	0·17	BFY44	1·00	OA70	0·10	SX68	0·20	74155	1·55
ACY39	0·50	BFY50	0·22	OA71	0·10	SX631	0·30	74156	1·55
ACY40	0·15	BFY51	0·20	OA73	0·10	SX635	0·40	74157	1·80
ACY41	0·15	BFY52	0·22	OA74	0·10	SX640	0·50	74170	4·10
ACY44	0·25	BFY53	0·17	OA79	0·10	SX641	0·55	74174	2·00
AD140	0·50	BFY64	0·42	OA81	0·08	SX642	0·60	74175	1·35
AD149	0·50	BFY90	0·65	OA85	0·12	SX644	0·75	74176	1·60
AD161	0·37	BSX27	0·50	OA86	0·15	SX645	0·75	74190	1·95
AD162	0·37	BSX60	0·93	OA90	0·08	V15/30P	0·50	74191	1·95
AF106	0·30	BSX76	0·15	OA91	0·07	V30/201P	0·75	74192	2·00
AF114	0·25	BSY26	0·18	OA95	0·07	V60/201	0·50	74193	2·00
AF115	0·25	BSY27	0·17	OA200	0·07	V60/201P	0·75	74194	2·50
AF116	0·25	BSY51	0·50	OA202	0·10	XA101	0·10	74195	1·85
AF117	0·25	BSY95A	0·12	OA210	0·25	XA102	0·18	74196	1·50
AF118	0·62	BSY95	0·12	OA211	0·30	XA151	0·15	74197	1·50
AF119	0·20	BT102/500R	0·75	OAZ200	0·55	XA152	0·15	74198	4·60
AF124	0·25	BTY42	0·92	OAZ201	0·50	XA161	0·25	74199	4·60
AF125	0·20	BTY79/100R	0·75	OAZ202	0·42	XA162	0·25		
AF126	0·17	BTY79/400R	1·25	OAZ203	0·42	XB101	0·43	Plug in sockets --low profile	
AF127	0·17	BY100	0·15	OAZ204	0·30	XB102	0·10	14 pin DIL	0·15
AF139	0·30	BY126	0·15	OAZ205	0·42	XB103	0·25	16 pin DIL	0·17
AF178	0·55	BY127	0·17	OAZ206	0·42	XB113	0·12		
AF179	0·65	BY182	0·85	OAZ207	0·47	XB121	0·43		
AF180	0·52	BY213	0·25	OAZ208	0·32	ZR24	0·63		
AF181	0·42			OAZ209	0·32				
AF186	0·40			OAZ210	0·32				
AFY19	1·13								
AFZ11	0·60								

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.
Valves, Tubes and Transistors • Closed Sat. 1 p.m.-3 p.m.
Terms C.W.O. only Tel. 01-677 2424-7
All orders subject to V.A.T. at 10% rate. This must be added to the total order including postage.

VARICAP STEREO TUNER F.M.

(ACTUAL BEECHING UNITS)

MODULES LP1185/86	£9 pair
REGULATOR MFC4060	£0·78 each
DECODER MC1310P	£3·15 each
(100's in stock)	
PRINTED CIRCUIT BOARD—GLASS FIBRE	£1·87 each
READY BUILT AND TESTED BOARDS	£23 each
COMPLETED TUNERS IN TEAK CABINETS	£34 each

(BRUSH ALU. FRONT PANEL with 6 BUTTONS, MAINS + 5 STATIONS)

(ADD 25p POSTAGE TO ABOVE)

SUPER SPECIAL OFFER WHILE STOCKS LAST

25 W. R.M.S. DISCO AMPLIFIERS ONLY £10 each ! !

WHAT A LINE UP:

0·2% DISTORTION, 25W RMS INTO 8Ω, FLAT RESPONSE, S/C PROTECTION! AND USING 40361/40362/MJ481/MJ491 TRANSISTORS.

WE ARE MAD! EACH ONE TESTED AND WORKING AND YET ONLY £10 Ready to use.

The catch is you need a 100K log VOLUME CONTROL ONLY!

B & B ELECTRONICS

64 MANNERS ROAD, BALDERTON, NEWARK NOTTS. Telephone: NEWARK 6895

ALL PRICES *INCLUDE* V.A.T.

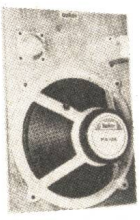

BAKER 12" MAJOR £9·90

30-14,500 cps. Double cone woofer and tweeter combination. Baker ceramic magnet assembly, flux density 145,000 gauss. BASS RESONANCE 40 cps 20 watt RMS.

MAJOR MODULE KIT £12·50

30-17,000 cps. response. Tweeter, crossover and baffle as illustrated.

BAKER LOUDSPEAKERS

Regent 12 in. 15W	£8·80	Superb 12 in. 20W	£16·50
Major 12 in. 20W	£9·90	Group 25 12 in. 25W	£8·80
Deluxe 12 in. 15W	£11·00	Group 35 12 in. 35W	£9.90

ALL PRICES INCLUDE V.A.T.

BAKER LOUDSPEAKER CO., BENSHAM MANOR PASSAGE THORNTON HEATH, SURREY Tel. 01-684 1665
LOUDSPEAKERS CATALOGUE AND ENCLOSURE PLAN 5p

NSS

DO-IT-YOURSELF ELECTRICAL EQUIPMENT

TRANSFORMERS • RECTIFIERS
INDICATOR LAMPS • RELAYS
CONTACTS • KEY SWITCHES
BURGLAR ALARM EQUIPMENT
SOLDERING IRONS • COMPONENT CASES
HOLE CUTTERS • TERMINAL BOXES
plus numerous other electrical components.

Send 10p for full price list and illustrated catalogue to:

NORTHERN SECURITY SUPPLIES (DEPT. PE)
104 KENT CRESCENT, KENT ROAD, PUDSEY, YORKSHIRE

MULLARD AMP

Sensational 'Once in a Life-time Offer' Unrepeatable once stocks are cleared. The amplifier is made by Mullard. Carries maker's Guarantee. In neat case. May be used for Mono or Stereo. Music or speech. Works off dry tery, car batt. or mains power pack. FREE—all o purchase we send copy of Mullard booklet DIY reo. **£1·60**

DRILL CONTROLLER
NEW IKW MODEL

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. **£1·65.** Made up model also available. **£2·48.**

MIGHTY MIDGET

obably the tiniest possible radio, as described in actical Wireless, 4 January 73. All electronic rts **£2·20** post paid.

TIME SWITCH

Smith's mains driven clock with 15 amp switch, also notes showing how you can wake up with music playing kettle boiling or come home to a warm house, warn off burglars, keep pets warm, halve your heating bill, etc. **£1·95.**

CHIP RADIO

rranti's latest device ZN414—gives results better an superhet. Supplied complete with technical otes and circuits. **£1·38** each. 10 for **£11·11.**

HI-Q TUNER COMPONENTS

or experimenting with the ZN414.
IT NO. 1. Plessey Miniature Tuning Condenser ith built in LW switch and 3" ferrit slab and litz ound MW coil, **72p.**
IT NO. 2. Air spaced tuning condenser 6" ferrite od litz wound MW and LW coils, **94p**
IT NO. 3. Air spaced TC with slow motion drive 8" ferrite rod, with litz wound LW and MW coils. **£1·10.**
IT NO. 4. Permeability tuner with fast and slow notion drive and LW loading coils, **45p.**

12 VOLT 1½ AMP POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mF smoothing. Price **£2·20,** plus 20p post and packing.

Heavy Duty Mains Power Pack. Output voltage adjustable from 15-40V in steps—maximum load 250W—that is from 6 amp at 40V to 15amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push on leads. Silicon rectifiers and smoothing by 3,000mF. Price **£6·33** plus 65p post.

MICRO SWITCH

5 amp changeover contacts, **11p** each. 10 for **99p.** 15 amp Model **15p** Changeover **15p** each.

MAINS RELAY BARGAIN

Special this month are some single, double and treble pole changeover relays. Contacts rated at 15 amps. Operating coil wound for 240V A.C. Good British Make. Unused. Size approx. 1½" × 1". Open construction.
Single pole **28p** each 10 for **£2·48.**
Treble pole **39p** each 10 for **£3·57.**

MAINS OPERATED SOLENOIDS

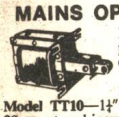

Model 772—small but powerful 1" pull—approx. size 1½ × 1½ × 1½". **66p.**
Model 400/1—½" pull. Size 2½" × 2 × 1½". **83p.**
Model TT10—1½" pull. Size 3 × 2½ × 2". **£1·98** plus 20p post and insurance.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6V, 9V, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor condensers and instructions. Real snip at only **£1·10** plus 20p postage.

DESK TELEPHONES

Ex G.P.O. Black standard model with dialing dial but no internal bell. Supplied with connection diagram **94p** each—post etc. **40p** for single then **65p** per pair. Ditto, with bell but without dialing dial **98p** each plus 40p post for single then **65p** per pair.

PAPST MOTORS

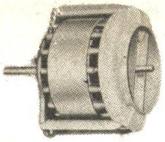

Est. 1/40th h.p. Made for 110–120V working, but two of these work ideally together off our standard 240V mains. A really beautiful motor, extremely quiet running and reversible. **£1·65** each. Postage one 23p, two 33p. 230V model **£3·30.**

10 AMP DIMMER CONTROL

For the control of lighting on stage or in a studio or for control of portable equipment in workshops, etc. This has two 13 amp socket outlets each is controlled by a 5 amp solid state regulator. The overall length is 17in., width 3½in. and depth 1½in. In the end is fitted a master On/Off switch indicator, lamp and fuse. Price **£8·25.**

STANDARD WAFER SWITCHES

Standard size 1½" wafer—silver-plated 5-amp contact, standard ¼" spindle 2" long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way
1 pole	44p	44p	44p	44p	44p	44p	44p	44p	44p
2 poles	44p	44p	44p	44p	44p	44p	44p	77p	77p
3 poles	44p	44p	44p	44p	77p	77p	77p	£1·04	£1·04
4 poles	44p	44p	44p	77p	77p	77p	77p	£1·32	£1·32
5 poles	44p	44p	77p	77p	£1·04	£1·04	£1·04	£1·60	£1·60
6 poles	44p	77p	77p	77p	£1·04	£1·04	£1·04	£1·87	£1·87
7 poles	77p	77p	77p	£1·04	£1·32	£1·32	£1·32	£2·15	£2·15
8 poles	77p	77p	77p	£1·04	£1·32	£1·32	£1·32	£2·42	£2·42
9 poles	77p	77p	£1·04	£1·04	£1·60	£1·60	£1·60	£2·70	£2·70
10 poles	77p	77p	£1·04	£1·32	£1·60	£1·60	£1·70	£3·00	£3·00
11 poles	77p	£1·04	£1·04	£1·32	£1·87	£1·87	£1·87	£3·25	£3·25
12 poles	77p	£1·04	£1·04	£1·32	£1·87	£1·87	£1·87	£3·52	£3·52

CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient and reliable was first described in the *Wireless World* about a year ago. We can supply kit of parts for an improved and even more efficient version (*Practical Wireless*, June). Price **£6·55** plus 20p post. When ordering please state whether for positive or negative systems. De-luxe model including printed circuit board, etc. **£7·95.**

MULLARD UNILEX

This D.I.Y. Stereo Amplifier is still available complete at **£7·00** for the four Mullard Modules, or Modules can be bought separately as follows:—4 watt amplifier module (2 required) Mullard Ref. No. E.P. 9000—**£1·60.**
Pre-amp module Mullard Ref. No. E.P. 9001—**£1·98** each.
Power Module—Mullard Ref. No. E.P. 9002—**£2·53** each.
In addition and made to Mullard specification we offer:—
Standard Control Unit with escutcheon and knobs—**£3·30.**
Knobs—Set of 4—**50p.**
Special offer the complete Unilex with control panel at Pre VAT price—**£10·00** post paid.

ZPM MODULATION MOTOR

Could also be used to open ventilators, doors, valve, damper, etc. particularly suitable for remote control. Made by Satchwell. Essentially a reversible geared motor fitted with internal limit switches to stop it at the end of its travel. Size approx. 6in. × 6in. × 5½in. and weighing approx. 10 lb. This is extremely powerful and would lift a heavy door or open a long line of ventilators. To operate this motor you put the 50 cycle supply through a changeover switch. For instance a thermostat with changeover contacts could automatically regulate the temperature in a growing house, chicken hatchery, etc. An indicator on the motor graduated 0–10 shows the state of open or close. Also internally fitted is a variable resistor, wires from this to a volt meter would give a remote indication of the open or close position. A very expensive motor if both direct from Satchwell, our price complete with step down Transformer is **£16·50.**

CENTRIFUGAL FAN

Mains operated, turbo blower type. Pressed steel housing contains motor and impeller. Motor is 1/10th h.p. giving considerable air flow but virtually no noise. Approx. dimensions 10½in. wide × 12in. dia. outlet into trunking 10½ × 4½in. **£6·55** plus £1 post and insurance.

THIS MONTH'S SNIP

TAPE PLAYBACK UNITS

Mains operated. Made by Reditune the famous "music in background people". These are complete units ready to work and we understand that they are in good going order. We have not tested them but would exchange any that do not work properly. These have a superior motor driven fly wheel to control the tape through the capstan and also an even equally useful valve amplifier with EL84 output. In a steel case with carrying handle. Two models offered, good as new **£6·50** and somewhat used at **£3·50.** 75p carriage up to 200 miles then 50p per 100 miles extra.
3-hour cassettes, already recorded light music **£1·10** *each extra*

24-HOUR TIME SWITCH

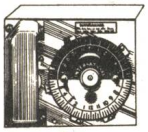

Made by Smiths, these are A.C. mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours, 5A changeover contacts will switch circuit on or off during these periods. **£2·75** post and ins. 25p. Additional time contacts **55p** pair.

MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied.
Model 1153 500mW power output **72p.**
Model 1172 750mW power output **94p.**
Model EP9000 4 watt power output **£1·60.**
EP9001 twin channel or stereo pre amp. **£1·99.**
10% discount if 10 or more ordered.

NEW ITEMS THIS MONTH

MINI SEALED RELAY

American made. Our Ref: REL A1. Measures only 3" wide × ¼" thick and ¾" high and it's a double changeover, we don't know the contact rating but estimate this at 3/5 amps. The coil resistance is 600 ohms and 9–12 volt will close it. Ideal for models and miniaturised equipment. It's a plug in relay but we supply complete with base. Price **28p** including base.

SUB-MINIATURE MICROSWITCH

Made by Burgess, their Ref V476—our Ref MS.A1. These measure only ¾" × ⅜" × ¼" thick—have changeover contacts and tag connection. Price **16p** each or 10 for **£1·44.**

3-CORE MAINS FLEX

Metric size. 5mm which is approx. equivalent to the old 14/36 rating. Suitable therefore for mower or similar portable tools. Cores are colour coded to the new European standard. Brown—live . . . Blue—neutral . . . Yellow/Green—earth. Grey P.V.C. covered overall. 100mm coils **£5,** 50m coils **£3** and 25m coils **£1·75.** Post 40p on 100m. **25p** for 50m coils and **20p** for 25m coils.

PANIC SWITCHES

Tough enough to be foot switches and elegant enough to be panel switches. Bakelite construction with white push rod. Price **40p** less quantity discounts. Switch is rated 250V—2 amp.

20 WATT CAMPING LIGHT

Also makes good car emergency light. This uses a standard 2 foot 20 watt tube and operates from a 12V car battery drawing approx. 1A. This gives illumination per amp/hour of battery life far in excess to filament lamps and in fact to the miniature 8–13 watt camping lights often offered. Complete unit ready to operate, in strong white enamelled metal frame. These would normally sell at £6 are unused but slightly soiled and we offer these at **£3·50** plus 40p post and packing.

6 MAINS TRANSFORMERS

Our Ref: MTM1 27 volt at 8 amp. Upright mounting fully shrouded—flying leads—fully tapped primary. Price **£3·30.**
Our Ref: MTM2 12V at 1 amp. Upright mounting with fixing lugs, tag connection. 240V primary—12V 1 amp secondary. Price **82p.**
Our Ref: MTM3 6·3V 2 amp upright mounting with fixing lugs, tag connections. 240V primary 6·3V 2 amp secondary. Price **77p.**
Our Ref: MTM4 18V—½ amp with thermal cut-out, upright mounting with fixing lugs—tag connections. Primary 240V—secondary 18V at ½ amp. Price **88p.**
Mains Isolation MTM5 350 watts earth shielded—flex leads—upright mounting lugs for fixing. Price **£4·40** each.

6 VOLT RELAYS

Our Ref: REL M1. Removable clear plastic enclosed two screw fixing. Have a 6 volt D.C. operated coil but two changeover contacts, each rated to make and break 240V A.C. at 15 amps. Price **66p** each.

P.O. TYPE 3000 RELAY

Our Ref: REL M2—100 ohms coil and 2 pair normally open heavy duty contacts. Price **75p** each.

PHOTO-MULTIPLIER TUBE

American R.C.A. type No. 4555. These tubes have a gain of a million or more. Regular Price—over £15. We have a limited quantity and offer these at **£4·50.**

TANGENTIAL AIR MOVING UNITS

Work as extractors or blowers especially quiet running, perfectly balanced, plastic impeller—self oiling bearings induction motor—outlet size 12" × 2" approx. Ideal to fit in cooker hood. **£2·20** plus 30p post and ins.

6 DIGIT COUNTER

Resettable. 440 ohm coil up to 25 impulses per second. Ex-equipment but guaranteed perfect. **£2·20** each.

COMBINATION SWITCH

This comprises of 12 miniature changeover micro switches. Joined in banks of 3 and mounted on frame with four digital numbered thumb wheels and a removable lever for locking the thumb wheel—the thumb wheel operates 3 banks. Over 4,000 combinations are possible but by re-wiring the switch connections underneath then thousands more variations are possible. If you are making equipment which you don't want switched on accidentally or without authority then this is a switch to consider—this can also be used as a coding switch for many other operations. Very neat and compact and measuring approx. 4" × 1½" × 1½" deep. Priced at **£3·03.**

PUSH BUTTON SWITCH

Type 14 D.M.G. A very fine switch made by Honeywell. The switch is intended for mounting on panel through oblong hole. No screws required for fixing it's sprung clips secure it quite firmly. The operating button is approx. 1" dia. round and dished for ease of operation. Has 2 sets of 10 amp changeover contacts. Spring loaded, returns to normal when pressure is released. Ideal for instrument or quality gear. Price **50p** each. 10 for **£4·50.** 100 for **£40.**

TERMS:—10% discount if ten of an item ordered, send postage where quoted—other terms, post free if order for these over £6·00 otherwise add 20p.

J. BULL (ELECTRICAL) LTD.

(Dept. P.E.), 7 Park Street, Croydon CRO 1YD

Callers to: 102/3 Tamworth Road, CROYDON.

Practical Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p extra. Semi-Display £7 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House Farringdon Street, London EC4H 4AD

SITUATIONS VACANT

Brunel Technical College Bristol

Ashley Down, Bristol BS7 9BU

Department of Marine and Aero-Electronics

Marine Radio and Electronic Officers

The Department offers the following Courses:
(a) For prospective Radio Officers in the Merchant Navy a Course of 2½ years leading to the MPT General Certificate in Radiocommunications and the DoTI Radar Maintenance Certificate. Commences September and January.
(b) A 3-year Course for prospective Radio Officers leading to the Marine Radio and Radar Technicians Certificate (CGLI 292) and incorporating the MPT and DoTI Certificates.
(c) For qualified Marine Radio or Electronic Officers the MNTB Additional Certificate in Marine Electronics, in two modules of 3 months each.
(d) Short advanced technique Courses for serving Radio Officers.
(e) MPT R/T Licences.

Licensed Aircraft Radio Engineers

The Department provides a 2-year Full-time Course leading to a career in Civil Aviation. The Course is fully approved by the CAA so that successful students may obtain a full Category R Licence at the end of the Course if over 21 years of age.
The Department's aircraft, workshops and laboratories cover:
12.1 Airborne Communication Systems.
12.2 Airborne Navigation Systems.
12.3 Airborne Pulse and FM Systems.
Courses commence each September.
Courses are also provided for Aeronautical Engineering Certificates (AEC 7-12), Aeronautical Engineering Technicians Certificate (CGLI 258), Aeronautical R/T Licences, and Category X Compass Licences.

For further information apply to the Head of Department of Marine and Aero-Electronics, Brunel Technical College, Ashley Down, Bristol BS7 9BU. Telephone (0272) 41241.

MEN! £50 p.w. can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £2500+p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you **FREE** to world-wide opportunities. Write or 'phone **TODAY**, without obligation.

London Computer Operators Training Centre
M88, Oxford House
9-15 Oxford Street, W.1
Telephone 01-734 2874

127 The Piazza, Dept. M88
Piccadilly Plaza, Manchester 1
Telephone 061-236 2935

Electro-Medical Service Department requires

ENGINEERS

for testing and servicing electronic apparatus. Applicants should be aged 20-30, and should be of O.N.C. standard.

Apply in first instance in writing to:

SIEREX LIMITED
Electro-Medical Department
Heron House, Wembley Hill Road
Wembley, Middlesex HA9 8BZ

LADDERS

LADDERS, 24½ft **£9·80,** carr. 80p. Please add 10% V.A.T. to total order. Leaflet. HOME SALES LADDER CENTRE (PEE2), Haldane, Halesfield (1) North, Telford, Salop. Tel. 0952-586644.

BOOKS AND PUBLICATIONS

THOSE 1,000 BANBURY UFO'S! Details our prediction. List **10p** and S.A.E. Prediction Chart **50p.** Flight Pattern **42p.** R & E, Highlands, Needham, Suffolk.

DIGITAL COMPUTER Logic and Electronics. A four volume Self-instructional course, **£2·99** post free. Money back assurance. CAMBRIDGE LEARNING, 8a Rose Crescent, Cambridge.

WANTED

TOP PRICES PAID AND TRANSISTORS
Popular T.V. and Radio types
KENSINGTON SUPPLIES (B)
367 Kensington Street
Bradford 8, Yorks.

SERVICE SHEETS

SERVICE SHEETS, Radio, TV, etc. 8,000 models. Catalogue **15p.** S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from **5p** with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue **15p.** HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

MUSICAL INSTRUMENTS

HALO—the new gear as supplied to Hawkwind, Solid Gold Cadillac. Tone generators **£12·11,** ring modulators **£12·77,** fuzz box **£11·34,** Wah-wah **£11·81,** treble boost **£8·81.** Contact: HALO, Estuary House, Exmouth, Devon.

EDUCATIONAL

ENGINEERS. Get a technical certificate. Postal courses in Engineering, Electronics, Radio, TV, Computers, Draughtsmanship, Buildings, etc., FREE book from: BIET (Dept. ZC BPE 29), Aldermaston Court, Reading, RG7 4PF. Accredited by CACC.

A SUCCESSFUL CAREER IN RADIO

Get the success you deserve—take an ICS home study course. Pass C&G, M.P.T. exams FIRST TIME! Free books. Low cost. Personal tuition. Send TODAY for FREE Guide on Radio, TV, Electronics, Electrical Engineering.

Name _____

Address _____

_____

ICS Dept. 730S Stewarts Road, London SW8 4UJ

FOR SALE

SEEN MY CAT? 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

TV LINE OUT-PUT TRANSFORMERS
Tidman Mail Order Ltd., 236 Sandycombe Road, Richmond, Surrey TW9 2EQ
01-948 3702

CATALOGUE NO. 18, Electronic and Mechanical Components and manufacturers' surplus. Credit vouchers value 50p. Price **23p,** including post. ARTHUR SALLIS RADIO CONTROL LTD., 28 Gardner Street, Brighton, Sussex.

FIBRE OPTICS

Flexible Light Pipe for conveying light to inaccessible positions. Fibroflex Type I. Glass 1·14mm effective dia. PVC sheathed. **44p** per metre. (VAT inc.), P. & P. 10p. Any quantity.

Polariser Sheet up to 1 sq. ft. max. size. **16½p** per sq. in. (VAT inc.), P. & P. up to 6 in. square **10p**; over 6 in. square **30p**

★ Cut down glare
★ See those nixie tubes
★ Cross them for light control
★ Make your own strain gauge for plastics and glass

Circuit Board Etching Kits. Full instructions. **£1·37½** (VAT inc.), P. & P. **14p**

Photographic CDS Light Cells—used (with part of original circuit free), **33p** (VAT inc.), Post free.

All items are strictly C.W.O.

From: ARVIN SERVICE COMPANY
12 CAMBRIDGE ROAD
ST. ALBANS

MORSE MADE EASY!!

FACT NOT FICTION. If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code **RHYTHM** without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

Beginner's Section only **£3·30**, complete course **£4·50** (Overseas £1 extra) details only, 4p stamp. **01-660 2896**

G3HSC (Box 19), 45 GREEN LANE, PURLEY, SURREY

METER REPAIRS. Ammeters. Voltmeters, Multi-Range meters, etc., also Linear scale Transistorised Ohmmeters for sale. METER REPAIRS, 39 Chesholm Rd., London N16 0DS.

U.K. DISTRIBUTOR "W2AU" baluns, antenna hardware, toroid cores also electro-voice microphones plus more. Large S.A.E. T.M.P. (ELECTRONIC SUPPLIES), (Dept. PE), 3 Bryn Clyd, Leeswood, Mold, Flintshire, CH7 4RU.

LARGE QUANTITY test equipment, receivers, transceivers, meters, variacs, P.S.U.S. Over 1,000 items for immediate disposal. S.A.E. plus **25p.** Refund on purchase over **£2.** F.J.C., Colne Mill, Alvington, Lydney, Gloucester.

FOR SALE SPRAGUE HYPASS CAPACITORS. Axle fitting. Complete with bracket. 1,400 0·5mF 600V d.c. 20 amps, 1,100 0·1mF 250V a.c. 40 amps. SPERRY UNIVAC, Grange Road, Houstoun Industrial Estate, Livingston, West Lothian.

FOR SALE TECH. TE200 R.F. Signal generator **£8.** Tech. to 0·3 oscilloscope **£30.** Radio/TV servicing volumes 1969-1971 **£20.** All in new condition. Phone: Pagham 2187.

PRACTICAL ELECTRONICS. Volumes 1-5. Offers. CHASE, 20 Greenside Road, West Croydon, Surrey.

RECEIVERS AND COMPONENTS

5—N-Channel FETs 3819E—£1

Full specification devices complete with circuit details for building voltmeter, timer, ohmmeter, etc.

Send 10p for full list of field effect transistors and other top quality transistors available at bargain prices.

REDHAWK SALES LTD.
45 Station Road, Gerrards Cross, Bucks.
MAIL ORDER ONLY

COMPONENTS GALORE. Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, capacitors, transistors, diodes, I.C., gang, pots, etc. Tremendous value. Send £1 plus 10p P. & P. C.W.O. to CALEDONIAN COMPONENTS, Fosterton Firs, Strathore Road, Thornton, Fife.

PRECISION
POLYCARBONATE CAPACITORS

Close tolerance. High stability. All 63V d.c.

0·47μF:	±5% 30p;	±2% 40p;	±1% 50p
1·0μF:	±5% 40p;	±2% 50p;	±1% 60p
2·2μF:	±5% 50p;	±2% 60p;	±1% 75p
4·7μF:	±5% 70p;	±2% 90p;	±1% £1·15
6·8μF:	±5% 95p;	±2% £1·15;	±1% £1·50
10μF:	±5% £1·10;	±2% £1·40;	±1% £1·80
15μF:	±5% £1·60;	±2% £2·10;	±1% £2·70

TANTALUM BEAD CAPACITORS. Values available 0·1, 0·22, 0·47, 1·0, 2·2, 4·7, 6·8μF at 35V, 10μF 25V, 15μF 20V, 22μF 15V, 33μF 10V, 47μF 6V, 100μF 3V—all at **9p** each; 6 for **50p**; 14 for **£1.** Special pack 6 off each value (78 capacitors) **£5.**

NEW!—TRANSISTORS. BC107, BC108, BC109. All at **9p** each; 6 for **50p**; 14 for **£1.** All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices. **AF178** at **35p** each or 3 for **95p.**

POPULAR DIODES. IN914, 7p each; 8 for **50p**; 18 for **£1. IN916, 9p** each; 6 for **50p**; 14 for **£1. 1S44, 5p** each; 11 for **50p**; 24 for **£1.** All brand new and marked.

NEW LOW PRICE—400 mW Zeners. Values available 4·7, 5·6, 6·8, 7·5, 8·2, 9·1, 10, 11, 12, 13·5, 15V. Tol. ±5% at 5mA. All new and marked. Price **9p** each; 6 for **50p**; 14 for **£1.** Special offer 6 off each voltage (66 zeners) **£4·25.**

RESISTORS. Carbon film 5%, ¼W at 40°C, ⅓W at 70°C. Range from 2·2Ω to 2·2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at **1p** each; **8p** for 10 of any one value; **70p** for 100 of any one value. Special pack—10 off each value 2·2Ω to 2·2MΩ (730 resistors) **£5.**

440V A.C. CAPACITORS. 0·1μF, size 1½in × ½in, **25p**; 0·25μF, size 1⅝in × ⅝in, **30p**; 0·47 and 0·5μF, size 1⅝in × ⅝in, **35p**; 1·0μF, size 2in × ⅝in, **45p**; 2·0μF, size 2in × 1in **75p.**

SILICON PLASTIC RECTIFIERS 1·5A—Brand new wire-ended DO27. **100PIV** at **8p** each or 4 for **30p**; **400PIV** at **9p** each or 4 for **34p**; **800PIV** at **14p** each or 4 for **50p.**

5p post and packing on all orders below £5.
Please add 10% VAT to all orders

MARCO TRADING
Dept. E8, The Maltings, Station Road
Wem, Shropshire

DRY REED INSERTS

Overall length 1·85" (Body length 1·1"). Diameter 0·14" to switch up to 500 mA at up to 250v D.C. Gold clad contacts. **69p** per doz.; **£4·12** per 100; **£30·25** per 1,000; **£275** per 10,000. All carriage paid.

G.W.M. RADIO LTD.
40/42 Portland Road, Worthing, Sussex 0903 34897

COMPUTER PANELS, 9in × 7½in long lead trans. and comps., E4, 8 trans., **27p** (10p); E45, 16 trans., **44p** (10p); E47, 10 trans., **33p** (10p).
PANELS with epoxy and TO18 silicon trans. 4 for **66p** (12p).
MC METERS, 2in or 3in, three assorted **£1·15** (25p).
MAINS STEPPING SWITCH, 22 way with reset **88p** (15p).
RESETTABLE COUNTER, 5 figure, 18/22V, works on 12V, **£2·20** (15p).
SILICON DIODES, 650V 1½A, 10 on tag board, **35p** (5p). New 800V ¾A, 6 for **25p** (5p).
UNIT WITH 4 × BFY51, 4 silicon diodes, 4 zeners, caps and resistors, **45p** (8p).
COPPER CLAD PAX. PANELS, 5½in × 5½in, 6 for **33p** (10p).
MIXED POLYSTYRENE/S. MICA CAPS., 100 for **50p.**
7lb ASSORTED COMPONENTS, £1·60.
2lb ASSORTED COMPUTER PANELS, £1·60.
S.A.E. (9in × 4in) for list of computer panels, etc.

J.W.B. RADIO
75 Hayfield Road, Salford 6, Lancs.
Postage in brackets Mail order only

BRAND NEW COMPONENTS by return. Electrolytics 16V, 25V, 50V—0·47, 1, 2·2, 4·7, 10 mF, **4p**; 22, 47, **4½p** (50V, **5p**); 100, **5½p** (50V, **7p**); 220, **6p** (50V, **9p**). Subminiature bead-type tantalums 0·1/35V, 0·22/35V, 0·47/35V, 1/35V, 2·2/35V, 4·7/35V, 10/16V, **8p.** Mylar Film 100V—0·001, 0·002, 0·005, 0·01, 0·02; **2p**; 0·04, 0·05, **3p**; 0·068, 0·1, **3½p.** Polystyrene 63V E12 series 10–1,000pF, **2p**; 1,200–10,000pF, **3p.** Miniature highstab resistors, 5%, E12 series—Carbon Film ⅓W, 1Ω–10MΩ (10% over 1 MΩ). Metal Film ¼W, 10Ω–2·2MΩ and 1W, 27Ω–10MΩ all **3½p** each. Postage 8p. The C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8 0RN.

Trampus electronics

Add 10% VAT (⅛) to all prices. All brand new, no rejects. **Money Back Warranty.**
5V DIGITAL INDICATOR: 0–9DP socket and filter **£1·45.**
LED TYPE ½" 0–9DP DIL **£2·25** each; 6× **£2·19** each. 4 digit type **£11.**
LIGHT EMITTING DIODES. All with data and panel clip. TIL 209 ¼" dia. **26p.** Red ½" dia. type **33p.** Green **75p.** INFRA RED beam LED **£1·10.**
GAS detector **£1·69.** Ultrasonic transducer **£2.**
DALO PCB resist marking pen 69p. Copper board 12" × 6" SRBP **40p.** FeC etch PAK **19p.**
INTEGRATED CIRCUITS: with data if required.
IC LITE SWITCH: Photo amp/trigger 40mA/11–20V relay or TTL **87p.** Dil relay **£1·10.**

IC digital clock

MOS/LSI type. 28 pin, 4 or 6 digit, 12/24hr. Chip with socket **£13**; PCB **£1·69**; KIT **£21·49.** DVM voltmeter **£12.** Data **39p.** 3W AF amp **£1·24.**
741 Dil 8 pin **28p**; 709 **19p.** Dil **29p**; 748 **29p**; mono 710 **33p.** **555 TIMER**/mono/astable osc. clock **93p.** REGULATORS: 1½A 5 to 20V **£1·49**; 723 **57p.**
RECEIVER ZN414 **£1·19.** Mini Rx Kit **£1·99.** 1310 stereo decoder for tuner **£2·69**, KIT **£3·45.**

74N TTL NEW LOW PRICES

GATES 7400/1/2/3/4/5/10/20/30/40/50, etc., **14p** each. 7413 **27p**; 7441 **73p**; 7447 **£1·09**; 7470, 7472 **28p**; 7473, 7474 **36p**; 7475 **60p**; 7476 **32p**; 7490 **59p**; 7492 **67p**; 7480 **69p**; 7483 **£1·10**; 7486 **37p**; 7493 **73p**; 7494 **83p**; 7495 **83p**; 7496 **89p**; 74121 **45p**; 74141 **99p**; 74190/91/92/93/96 **£2·39.** DIL Plugs/IC case 10mm high 16 pin **35p.**
DIL SOCKETS: low or high profile 8/14/16 pin **13p.**
SEMICONDUCTORS:
2N3055 **40p**; BC107 **8p**; BC108 **8p**; BC109 **8p**; BC147/8/9 **10p**; BC167/8/9 **13p**; BC177/8/9 **15p**; BC182/3/4 **10p**; BC212/3/4 **11p**; BCY70/72 **13p**; BD131/2 **55p**; BFY50/51/52 **13p**; TIS43 UJT **24p**; 2N706 **11p**; 2N2369 **12p**; 2N2926Oy **8p**; 2N2646 **49p**; 2N3053 **17p**; 2N3055 **40p**; 2N3614 **55p**; 2N3702/3/4/5/6/7/8/9/10/11 All **9p** each.
FETS: 2N3819 **27p**; 2N3823 **29p**; SCR 400V; 1A **23p**; 4A **55p.** TRANSFORMER: ½A 6 and 12V **£1.**
CAPACITORS: Disc 22pF to 0·1μF **4p.** 25V electrolytic 10, 50, 100μF **5p**; 1,000μF **15p.** **PRESETS 5p** each. RESISTORS ¼W 5% **1½p** each. **CARBON POTS 12p** each. Dual **40p.** Switch +**12p.** All Din Plugs **13p**; sockets **9p**; Vero RRP.

FLUORESCENT LIGHTS 12VOLT **£2·79**

13" 8 watt fully built with diffuser.
TRIO and **CODAR** communications and Hi-Fi retailer. ELECTRONIC ORGANS from **£67,**
PW ELECTRONIC CAR IGNITION KIT £6·67.
VAT: YOU MUST ADD 10% (⅛) to all prices.
FREE CAT. S.A.E. Data sheets 8p each. P. & P. 8p. C.W.O. P.O. BOX 29, BRACKNELL, BERKS.

R.T. SERVICES
(MAIL ORDER ONLY)
77 Hayfield Rd., Salford 6, Lancs.

Veroboard 6×5 0·1 Matrix, 2 for **£1.** 4×4½ 0·1 Matrix, 4 for **£1.** 12×3¾ 0·15 Matrix, **75p** each.
Mullard A.M. Module. I.F. Strip, LP1166, **£1·10** inc. P.P.
FM Tuner with R.F. Stage and A.G.C., 3 transistors, neg. earth, 2½×2×1½ in with circuit, **£1·37½** inc. P.P.
Crouzet Geared Motors, 10-30-60 r.p.m. New, **£1·54** inc. P.P.
UHF TV Tuners. Transistorised, **£1·65** inc. P.P.
3BPI with Base and Screen, **£2·75** inc. P.P.
VCR138 CRT. New, boxed, **£3·30** inc. P.P.
Brand New Panel VU Meters, 4½×3¼ in calibrated, **£3·30** inc. P.P.
Transformers. 7·5V + 7·5V ½A, **66p** inc. P.P. 18-0-18V, 200mA + 24V, **77p** inc. P.P. 9-0-9V, 100mA, **69p** inc. P.P. 12-0-12V, 100mA **69p** P.P. 20V, 1A **88p** inc. P.P.
Transformers. 52-0-52V, 1A + 22-0-22V, 200mA, **£2·20** inc. P.P.
P.C. Board. S/S, 5½ × 5½in, 10 for **70p** inc. P.P.
Panel with 5-200 PIV 1A SCRs + 14 OA200 diodes plus components **70p** inc. P.P.
2,500 mfd 100VW capacitor 4½"×1¾". New, **85p** inc. P.P.
Panel Meter 50μA. Brand new, 4½"×3½". **£3·30.**

SPECIAL RESISTOR KIT. ¼W 5% Carbon Film. 10 each E12 value. 22Ω to 2·2M. Total 610 for **£3.** P. & P. 8p. NEK ELECTRONICS. 28 Carnegie Road, St. Albans, Herts.

SPECIAL INTRODUCTORY OFFER OF BRAND NEW & MARKED COMPONENTS ALL PRICES INCLUDE V.A.T.

TRANSISTORS: BC107B, BC108A/B/C, BC109B/C all at 8½p; BFY50/51 14p; 2N3055 38p. **DIODES:** 1N4148 4½p; IN914 4½p. **CARBON FILM RESISTORS:** ¼W 5%, ½p each, 30p/50 any mix (22Ω-2·2M) E12.

UNMARKED BARGAIN PAKS: These transistors have been properly tested and are guaranteed to have the specified hfe spreads. Pak of 5, Plastic BC108A hfe 125–240, 25p; Pak of 5, Plastic BC109B hfe 240–500, 25p; Pak of 5, Plastic BC179A hfe 125–240, 25p; Pak of 4, BFY51 20p; Pak of 4, 2N697 20p. **DIODES:** Pak of 5 OA200 20p; Pak of 12 1N4148 20p.

C.W.O. P. & P. 10p. on orders below £4. Overseas at cost. S.A.E. for lists. Mail Order only. **Money back if not satisfied.**

ADFONIC (Dept. PE), 18 YEW LANE ASHLEY, NEW MILTON, HANTS BH25 5BA

BRAND NEW FULL SPEC. DEVICES SATISFACTION OR YOUR MONEY BACK

U.K. ORDERS—Add 10% VAT to Total

MICROCIRCUITS: 709 24p; 710 36p; 723 51p; 741 27p; 748 37p; FET Op. Amp. £1·62. **SOLDERCON** IC Pin Sockets: 0·5p per pin. **SOCKETS:** 14 pin DIL HI or LO 12p each. **RECTIFIERS.** 1A 50V 3½p; 100V 4p; 200V 4½p; 400V 5p; 800V 6p; 1,000V 7p. **ZENERS** (BZY88): 2·7V to 33V 8p each. **DIODES:** IN916 4p; OA90 6p; IN4148 4p. **LED PANEL LAMP** with Bush and Data 28p. **DALO PC RESIST PEN** 68p. **SUB-MIN. VERTICAL PRESET POTS** (50mW) 100ohms to 220K Ω 4p each. **TRANSISTORS:** 2N2926 Brown 6p; 2N3053 15p; 2N3055 35p; 2N3702 10p; 2N3704 10p; 2N3819 26p; BC107A 8p; BC108B 8p; BC109B 8p; BC109C 8p; BCY70 15p; BFY50/51/52 15p; AC126/7/8 12p; OC44/45/71/72 12p.

Above prices on 30th May. Check our list.

JEF ELECTRONICS (P.E.8)

York House, 12 York Drive, Grappenhall, Warrington WA4 2EJ. Mail Order Only. C.W.O. P. & P. at cost. 10p min. List free.

TOROIDAL MAINS TRANSFORMERS

Slimline and compact, with very low stray hum field, suitable for audio amplifiers up to 60 Watts/channel, etc.

Type TI—primary 0-110-120-220-230-240V, 40/60Hz. Secondary 0-45V at 150VA max. Electrostatic screen. Size—only 1¼" high × 4½" diameter. Weight 3½lb. Mail order only

Price—only **£5·70,** post free in U.K.

Other types available—send S.A.E.

Amplification and Recording
36 Bermuda Terrace, Cambridge

RADIO & TELEVISION AERIAL BOOSTERS £2.95, five television valves **45p. 50p** bargain transistor packs, bargain **£1** resistor and capacitor packs. UHF-VHF televisions **£7·50.** Carr. £1·50. S.A.E. for 3 leaflets. VELCO ELECTRONICS, Bridge St., Ramsbottom, Bury, Lancs.

TUNBRIDGE WELLS. Components from TELESERVICE, 108 Camden Road, Tunbridge Wells, Kent. Telephone 31803.

---

555 TIMER I.C. only **90p** each inc. VAT. P. & P. 5p. 2 or more post free. C.W.O. to: CHARNWOOD (D.P.E. 3), Castle Hill, Holmesfield, Sheffield, S18 5WQ. Mail order only.

BEDFORD ELECTRONICS

2 Grove Place · Bedford

Bedford 51961

YOUR LOCAL COMPONENTS SUPPLIER

FREE CATALOGUE ON REQUEST

MISCELLANEOUS

CLEARING LABORATORY, scopes, V.T.V.M's, V.O.M's, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, M C relays, components, etc. Lower Beeding 236.

AT LAST YOU CAN TRANSMIT AND FORGET ABOUT LICENCE EXAMINATIONS

because this Ministry approved transmitter/receiver kit does not use R.F.

Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND **£5·80** (inc. VAT) NOW
S.A.E. for details) MAIL ORDER ONLY

TO: 'BOFFIN PROJECTS'
DEPT. KE2010
4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY

A Perfect toast every time. Automatic pop-up toaster has adjustable time control to vary the colour and crispness just the way you like it. Chromium plated with black plastic sides. 220/240V, 800. Comes with 6ft of flex and 3 months' guarantee. Size 8in × 4¾in × 7in high.

E341 **£7·20** *Toaster*

11 Compact go-anywhere cassette tape recorder can be operated by battery or a.c. mains, 220/240V. Automatic recording level. Piano-type keys control play, rewind, wind, stop and record. Sockets for remote control and microphone. Complete with four U2 batteries. Wood grain finish. Size 9in × 5in × 2¼in. Weight approx. 6lb.

E365 **£15·30** *Tape recorder*

ACME ELECTRIC CO. (FINSBURY) LTD.
74 Gt. Eastern Street
London E.C.2
Tel. 01-739 6486-8

HARDWARE—Screws, nuts, washers and other useful items in small quantities. Sheet aluminium to individual requirements, punched/drilled. Send 6p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwickshire.

NEW FROM ELBON

L.E.D.'s (Red Emitting) Ideally suited for panel indicators
Price only: **33p** each or **£2·50** for 10

Light SENSITIVE SWITCHES

Two types available giving wide operating voltages:

LITE-IC2 11V-20V working – **£1** each – **£8·50** for 10

LITE-IC3 20V-30V working – **£1** each – **£8·50** for 10

Applications include: Relay, Triac or Logic Drive, automatic light switching and door control, beam/break detection – burglar alarm, batch counting and code reading.

BARGAIN PACK!

2 LITE-IC2, 2 LITE-IC3 and 5 LED's all for **£5·00**

ALL PRICES INCLUDE VAT, PACKING AND CARRIAGE

Please send C.W.O. to:
LITE-IC, ELBON, SUMMERFIELD, THE CRESCENT, WEST WITTERING, SUSSEX

Build the Mullard C.C.T.V. Camera

Kits are now available with comprehensive construction manual (also available separately at 76½p)

SEND 5" 7" S.A.E. FOR DETAILS TO:

CROFTON ELECTRONICS
15/17 Cambridge Road, Kingston-on-Thames, Surrey KT1 3NG

CONSTRUCTION AIDS. Screws, nuts, spacers, etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and boards, one-off or small numbers Send 6p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwks.

THERMOCOUPLES

Acramet and Acraspeed thermocouples, from IC are:-

Extremely accurate for fluid, gas or metal temperature measurement.

Individually calibrated and carry a certificate plus a one year guarantee.

Available with immersion or contact, non-earthed, multiples, boss or plug.

Details available on request.

International Combustion Limited, Sinfin Lane, Derby DE2 9GJ

ENAMELLED COPPER WIRE

S.W.G.	1lb Reel	¼lb Reel
10–14	£1·15	65p
15–19	£1·15	65p
20–24	£1·18	68p
25–29	£1·25	75p
30–34	£1·30	80p
35–40	£1·40	85p

Please add 10% to all above prices to cover VAT

The above prices cover P. & P. in U.K. Supplied by

INDUSTRIAL SUPPLIES

102 Parrswood Rd., Withington, Manchester 20
Telephone No. 061-224 3553

---

standard german plugs & sockets

With EARTHING CONTACTS

Plug 131 34p incVAT With cable side entry

Socket 200 £1·10 inc VAT Twin socket outlet to fit wall box

Socket 210 61p incVAT For bench mounting

Socket 230 55p incVAT For chassis mounting

Postage & packing–1 item 3p each additional item 2p over 10 post free

TRADE ENQUIRIES WELCOME

michael wheeler ltd 01-388 0575
18–19 WARREN STREET LONDON W1P 5DB

P.E. SYNTHESISER KNOB KIT

Complete kit as Feb. issue 43 knobs, 7 calibrated discs. **£3·91** post free

DE LUXE KIT as above but calibrated for programming. **£5·89** post free

Inclusive postage and V.A.T.

RE-AN PRODUCTS LTD.
Burnham Road, Dartford, Kent
Tel.: Dartford 20785

PSYCHEDELIC MINI-STROBE

A very POWERFUL, POCKET-SIZED STROBE-LIGHT that is SELF-CONTAINED and you can take anywhere. Go to parties and really BRAIN-FREEZE them with DAZZLING PSYCHEDELIC EFFECTS and STOP-MOTION FLASHES. Boffin's new MINI-STROBE kit constitutes a fully solid-state electronic device which is COMPLETE with FUTURISTIC case/reflector unit, printed-circuit board, electronics, and source-lamp—the only extra is a battery which you can buy locally. The whole thing can be easily built in a few hours.

A veritable FLICKERING FASCINATOR! Adjustable flash-rate.

GET ONE (or two) NOW and BEGIN STEALING THE THUNDER at DISCOS and PARTIES with your own POCKET-LIGHTNING!

SEND **£2·10** (inc. VAT) for *YOUR* MINI-STROBE. MAIL ORDER ONLY

To: Boffin Projects
4 Cunliffe Rd., Stoneleigh, Ewell, Surrey

ELECTRONICS FANATICS

whether beginner or advanced — we offer a range of over 35 SUPER projects.

Have you ever wanted to build A MACHINE THAT LEARNS? Or perhaps make a TEACHING DEVICE? Maybe you fancy the idea of an ELECTRONIC FANTASY MACHINE? How about a "Thing" capable of REPRODUCING ITSELF? Whatever your electronic turn-of-mind, there's just GOT TO BE LOADS TO INTEREST YOU in the science-fiction-world of BOFFIN.

GET YOUR CATALOGUE — SEND JUST 15p NOW!

MAIL ORDER ONLY

TO: BOFFIN PROJECTS
4 CUNLIFFE ROAD
STONELEIGH, EWELL
SURREY

Designs by GERRY BROWN and JOHN SALMON and presented on TV.

ASS FIBRE P.C. BOARD—large supplies ilable. $\frac{1}{16}$in single sided one ounce copper, per 3 sq in (under 1ft); **75p** per sq ft (over). $\frac{1}{16}$in double sided one ounce copper, **1p** per in (under 1ft); **£1** per sq ft (over 1ft). ase add 10p per sq ft postage and packing. can cut to your size at 1p per cut. SOLID ATE LIGHTING, The Firs, Smallworth ne, Garboldisham, Diss, Norfolk.

UMINIUM SHEET to individual sizes or in ndard packs, **3p** stamp for details. RAMAR NSTRUCTOR SERVICES, 29 Shelbourne ad, Stratford-on-Avon, Warwks.

URGLAR AND FIRE ALARMS. Complete aster Control Module now available from our n panels. Ideal for all Alarm/switching cuits with data sheet, etc. **£6·85.** Complete arm kits **£49·50.** Magnetic Switches, Sensors, nels, available. CASTLE ALARMS, P.O. ox WO6, Windsor, Berks.

ZIGGY'S 2001
ELECTRONICS Co. Ltd.

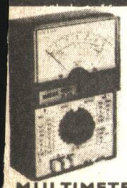

SPECS. MULTIMETER U4324. Sensitivity 20,000 OPV DC. Usually high current ranges. 3 amps a.c./d.c. Voltages AC3 to 900V d.c. 0·6 to 1200V. Resistance 500 ohms–20-200-2,000kΩ. Transmission level —10 to +12dB. This high quality instrument has diode protection. Complete with test leads, batteries, etc. PRICE **£8** plus 25p post, etc.

MULTIMETER 4313. Similar to above but special features include 3 amp current range and instrument is housed in metal case with carrying handle. (Illustrated leaflet sent on request.) ONLY **£9·50** plus 25p P. & P.

SANWA JP-5D. Diode protected. D.C. and A.C. volts 0–500V. D.C. current 0–500 mA. Res. 0–1MΩ. **£5·95.** P. & P. 20p.

EAGLE LT700 TRANS., LT44 TRANS. Our price **32p** each, postage 6p.

P.U. HEAD SHELLS AND SLIDES.

GARRARD C2 (SP25 Mk III, etc.) **45p.** M7 (SP25 Mk II and earlier models) **£1.**

BSR McDonald (310, 510, 610, MP60) **45p.** Postage 6p per shell.

ARE YOU HUMBLE ABOUT YOUR RUMBLE? SP25 drive wheels, **65p** plus 5p P. & P. MP60 drive wheels, **65p** plus 5p P. & P.

SUBMINIATURE TOGGLE SWITCHES—very useful, very small. S/P, **25p,** DP/ST, **33p.** Postage 5p each, over 10, post free.

SUBMINIATURE MAINS TRANSFORMERS. Eagle MT6, 6–0–6, 100 M/A, **80p,** postage 10p. MT12, 12–0–12, 50 M/A **80p,** postage 10p.

MINIATURE TYPE MAINS TRANSFORMERS. Eagle Type MT280, 6–0–6 280 M/A, **£1·20;** MT150, 12–0–12, 150M/A, **£1·20,** MT100, 24–0–24, 100 M/A, **£1·20.** R/S types, 13V, 0·5 amp, C. Tapped, **£1·06,** 16·3V, 0·3 amp, C.T., **£1·06. Post 15p on min. size.**

DIAMOND STYLI FOR SONOTONE 9TAHC, LP/78, **65p** plus 5p P. & P. LP/LP, **95p** plus 5p P. & P.

FOR SPEEDY DELIVERY OF THESE MINT CONDITION COMPONENTS PLEASE SEND C.W.O. to ZIGGY'S 2001 ELECTRONICS CO. LTD., DEPT. P.E.3, 34 MABLEY STREET, LONDON, E.9.

N.B.—Please add 10% for VAT—Sorry.

LOW COST LEDs

MLED 500 in standard TO92 package for P.C. mounting. MV54 is T$\frac{3}{4}$ size, 2 mm, miniature. Both provide visible red light from 1·65V, 20mA. 150Ω resistors available for 5V d.c. (TTL) operation.

	5	10	25	50	100
MLED 500	£1·10	£2·20	£3·74	£6·60	£2·65
MV54	£1·10	£2·09	£3·52	£6·05	£2·10
150Ω	—	—	11p	22p	44p

MARE'S TAILS: Spray of several thousand glass fibres, ready to use as part of decorative displays. **£11** each including P. & P. and VAT.

POLARISERS for light control, glare reduction, modulators, stress analysis, S/N enhancement for displays.

HN32 Linear Polariser, for Kerr cells, etc.

HRCP7 Red Circular Polariser, for LED displays.

HNCP37 Neutral Circular Polariser, for c.r.t.s, meters, etc.

Send 9 × 6in S.A.E. for full details of the above plus our full range of Fibre Optics.

FIBRE OPTIC SUPPLIERS

P.O. Box 702 **LONDON W10 6SL**

SINGLE CHANNEL SOUND-TO-LIGHT CONVERTER

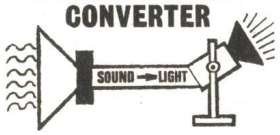

WITH LIGHT DIMMER
Max. Load 2kW at 250V a.c.

Price includes ready built and tested module, edge connector/mounting bracket, dimmer potentiometer, audio sensitivity potentiometer, full connecting data. **Price £7·90** inc. VAT + 25p P. & P.

EXTRA FACILITIES. Push-button for Manual Pulsing, **25p** extra. Photocell for turning on the lights as the ambient light decreases, **75p** extra.

THREE CHANNEL FILTER UNIT

When used with three single channel modules this unit filters the sound into bass, middle and top frequencies enabling three coloured light displays to be shown. Independent sensitivity controls on each channel. Ready built and tested.

Price £3·40 inc. VAT + 15p P. & P.

OIL WHEEL PROJECTOR

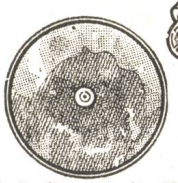

Build your own using our **MULTI-COLOURED OIL WHEEL AND MOTOR KIT** Suitable for mounting on virtually all Slide Projectors.

Kit contains:

★ 6in dia. or 4in dia. OIL WHEEL (please state size required when ordering).
★ Suitable Miniature mains motor.
★ Full instructions.

For Professional Discotheque use or home enjoyment. **Price £7·15** inc. VAT & P. & P.

ELECTRONIC COMPONENTS BARGAIN COMPONENT PACKS

Pack No.
1 500 Carbon resistors, $\frac{1}{4}$, $\frac{1}{2}$, 1, 2W.
2 100 Electrolytic Condensers.
3 250 Ceramic, Polystyrene, Silver Mica, etc. Condensers.
4 250 Polyester, Polycarbonate, Paper, etc. Condensers.
5 25 Potentiometers, assorted.
6 250 High-stab. 1%, 2%, 5% resistors.
7 50 Assorted Tagstrips.
8 1lb wt. Assorted Nuts, bolts, washers, spacers, etc.
9 25 Assorted switches, rotary, lever, micro, toggle, etc.
10 50 Preset Potentiometers.

ALL COMPONENTS NEW AND UNUSED
£1 + 25p P. & P. per pack £5 for 5 packs post free.

C.T. ELECTRONICS
267 Acton Lane, London W4 5DG
01-994 6275

4-STATION INTERCOM

£7·99

Solve your communication problems with this **4-Station Transistor Intercom** system (**1 master** and **3 Subs**), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from **Master** to **Subs** and **Subs** to **Master.** Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft and other accessories. P. & P. 44p.

MAINS INTERCOM (new model)

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price **£16·40.** P. & P. 60p extra.

INTERCOM/BABY ALARM

£3·99

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft connecting wire. Complete with battery. P. & P. 30p.

£3·46

Why not boost business efficiency with this incredible De-Luxe **Telephone Amplifier.** Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Complete with battery. P. & P. 24p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/7)
169 KENSINGTON HIGH STREET, LONDON, W.8

NEW EDITION

TV ENGINEERS' POCKET BOOK

P. J. McGoldrick Price **£2·65**

THE RADIO AMATEUR'S HANDBOOK 1973 by A.R.R.L. Price **£2·95.**

1-2-3-4 SERVICING CASSETTES by F. H. Belt. Price **£2·30.**

110 THYRISTOR PROJECTS USING SCRs AND TRIACS by R. M. Marston. Price **£1·50.**

VIDEO TAPE PRODUCTION AND COMMUNICATION TECHNIQUES by J. L. Efrein. Price **£1·40.**

INTEGRATED CIRCUIT POCKET BOOK by R. G. Hibberd. Price **£2·60.**

AUDIO SYSTEMS HANDBOOK by N. H. Crowhurst. Price **£1·35.**

BEGINNER'S GUIDE TO PRACTICAL ELECTRONICS by R. H. Warring. Price **£1·40.**

SIMPLE TRANSISTOR PROJECTS FOR HOBBYISTS AND STUDENTS by L. Steckler. Price **£1·35.**

PRINCIPLES OF TRANSISTOR CIRCUITS by S. W. Amos. Price **£1·65.**

NEW IC FET PRINCIPLES AND PROJECTS by K. W. Sessions. Price **£1·20.**

GE TRANSISTOR MANUAL. Price **£1·20.**

ALL PRICES INCLUDE POSTAGE

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET
LONDON W2 1NP

Phone 01-723 4185
Closed Saturday 1 p.m.

BUILD A CHORDING PROFESSIONAL SYNTHESISER

The Synthesiser shown above is the **Dewtron** "Apollo" A.1. which we sell ready-built to professionals. Believe it or not, it uses the SAME precision modules as we sell to you, the Constructor, to build any kind you like. The revolutionary Modumatrix system of routing makes old-fashioned patching a thing of the past. VCO-2 voltage-controlled oscillator module has accurate built-in log-law for chording and other professional effects. 3 and 4 octave keyboards and contacts.

VCO-2 STABLE, PRECISION V/C OSCILLATOR gives SINE, TRIANGULAR AND SQUAREWAVE outputs, 1 volt/octave voltage control. **£22** each or **£25** each 2 or more matched. **SHE-1 SAMPLE, HOLD AND ENVELOPE MODULE** gives variable attack, sustain, touch sensitive playing when used with VCO-2 signals. **£15.** OFT-1 chording module **£7·50.** Modules (except VCO-1) guaranteed two years.

using **Dewtron** (Regd. Trademark)

PROFESSIONAL MODULES
CASH SAVINGS
by buying modules and parts in bulk!
All modules are available separately:
Ring Modulator RM2, **£8.** Voltage-controlled Oscillator VC01, **£10·50,** giving sawtooth and square-wave outputs. Envelope shapers, ES1, self-triggered or ES2 keyboard-triggered, either type **£13.** White noise type WN1, **£7.** Voltage-controlled amplifier VCA1, **£10.** Voltage-controlled selective amplifier (filter for waa-waa, etc.) SA1, **£12.** Voltage-controlled Phase PH1, **£17.** Automatic Announcement Fader module for fading of music by microphone announcement, AF1, **£9.** etc., etc. ALL MODULES ARE BUILT, TESTED AND SEALED FOR LONG LIFE. Simply connect coloured wire connections as per easy instructions, build cabinet and wire in controls and patchboard connections! Joystick controls **£4·50.** REVERB Module and spring unit **£15.** V.A.T. 10% extra. V.A.T. paid orders over **£75.**

With over 7 years' unblemished reputation in these pages, ***Dewtron*** *continues to lead in new technical developments in electronic sound effects! Ask any of our customers. See our products in the music stores, too. Suppliers of special equipment to leading group. Our modules are used in professional equipment by other manufacturers and in our own built synthesisers, e.g. "Gipsy" G.I.* ***Approved by the Association of Musical Instrument Industries.*** *Send 15p for full catalogue of our famous musical effects.*

D.E.W. LTD.

254 Ringwood Road, FERNDOWN, Dorset BH22 9AR

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND

C.W.O. Please. P. & P. please add 10p to orders under £2
MAIL ORDER. CALLERS SATURDAYS ONLY

SEMICONDUCTORS

TRANSISTORS

AC125	12p	BC147	12p	OC70	10p
AC126	12p	BC148	12p	OC71	10p
AC127	12p	BC149	12p	OC72	10p
AC128	12p	BD131	49p	2N2218A	13p
AC187	12p	BD132	49p	2N2220	10p
AC188	12p	BF194	15p	2N2221	10p
AD161	30p	BF195	15p	2N2483	10p
AD162	30p	BFY50	22p	2N2484	10p
AF114	12p	BFY51	22p	2N2926R	9p
AF115	12p	OC26	40p	2N2926O	9p
AF116	12p	OC28	40p	2N2926V	9p
AF117	12p	OC35	40p	2N2926G	10p
BC107	9p	OC42	10p	2N3014	10p
BC108	9p	OC44	10p	2N3055	55p
BC109	9p	OC45	10p		

DIODES

OA85	7p
OA90	5p
OA91	5p
OA200	8p
OA202	8p
IN914	5p
IN4001	6p
IN4004	7p
IN4007	8p
IN4148	5p
BYZ10	20p
BYZ13	16p
WO1 BRIDGE RECTIFIER 1A. Price 30p	

LINEAR IC's

709C 8 pin	32p
709C 14 pin	32p
741C 8 pin	36p
741C 14 pin	36p
723C 14 pin	80p

DIL SOCKETS

8 pin	23p
14 & 16 pin	15p

ZENER DIODES
BYZ 88 series 400mW 3·3V–30V. Price 12p each

THYRISTOR
200V 4A 60p

VEROBOARD

	0·1	0·15
2½ × 3¾in	20p	18p
2½ × 5in	24p	22p
3¾ × 3¾in	24p	22p
3¾ × 5in	27p	30p
2½ × 17in	75p	60p
3¾ × 17in	97p	84p
5 × 17in	128p	—
2½ × 17in (plain)	40p	
3¾ × 17in (plain)	60p	
5 × 17in (plain)	80p	
Pkt. 50 pins	20p	
Spot face cutter	42p	
Pin insertion tool	52p	

JACK PLUGS AND SOCKETS
Standard Screened, 12p
Stereo Screened, 30p
Standard Socket, 12p
Stereo Screened, 15p
2·5mm Screened, 8p
3·5mm Screened, 10p
2·5mm Socket, 7p
3·5mm Socket, 7p

DIN PLUGS & SOCKETS
Pin: 2, 3, 4, 5 (180° or 240°) Plugs, 12p. Socket 8p.

COMPACT CASSETTES
C60 40p; C90 55p; C120 75p.

PHONO PLUGS AND SOCKETS: PLUGS assorted colours 5p.
Socket: Single 5p, Double 7p, Triple 10p

SWITCHES

TOGGLE SPST	18p
DPDT	22p
SLIDE DP 1A	10p
ROTARY Wafer 12 Way	25p

D.C. POWER SUPPLY
Current: 500mA.
O/P Voltage: 3, 4·5, 6, 7·5, 9, 12.
PRICE: £3·40 P. & P. 15p.

STEREO HEADPHONES. HOSIDEN DH-02V-S.
8 ohm: Individual vol. control. Soft ear padding. Light wt. PRICE: £2·85. P & P. 15p.

RESISTORS
High stability low noise carbon film. Miniature wire wound.

Power Watts	Tol.	Range	Values Available	1–9	PRICE 10–99	100+
¼	5%	2·2–2·2M	E12	1p	0·8p	0·7p
½	5%	2·2–4·7M	E12	1p	0·8p	0·7p
1	5%	2·2–10M	E12	2p	1·6p	1·4p
4	10%	1–10 ohm	E12	6p	5p	—

Do not mix ohmic values to obtain quantity prices. Ignore fraction

POLYESTER CAPACITORS. Axial lead type:
400V: 0·001μF, 0·0015μF, 0·0022μF, 0·0033μF, 0·0047μF, 0·0068μF, 2½p; 0·01μF, 0·015μF, 0·022μF, 0·047μF, 3p; 0·068μF, 0·1μF, 0·15μF, 4p; 0·22μF, 7p; 0·33μF, 10p; 0·47μF, 13p.
160V: 0·1μF, 0·15μF, 4p; 0·22μF, 5p; 0·33, 6p; 0·47μF, 7p; 0·68μF, 10p; 1μF, 13p.
Radial lead P.C. type:
250V: 0·01μF, 0·015μF, 0·022μF, 3p; 0·033μF, 0·047μF, 0·068μF, 3½p; 0·1μF, 4p; 0·15μF, 4p; 0·22μF, 0·33μF, 5p; 0·47μF, 7p; 0·68μF, 10p; 1·0μF, 11p.

ELECTROLYTIC CAPACITORS. Miniature axial lead type.
63V: 1μF, 1·5μF, 2·2μF, 3·3μF, 4·7μF, 6·8μF, 10μF, 15μF, 22μF, 47μF, 68μF, 6p each.
40V: 100μF, 6p; 150μF 25V, 6p; 25V: 220μF, 11p; 470μF, 13p; 680μF, 20p; 1,000μF, 25p.

CERAMIC CAPACITORS: 50V d.c. Plaquette body 25mm leads.
Range: 22pF–10,000pF. Price 2p each.

POTENTIOMETERS: Carbon Track 0·25W, Log and linear values

5k Ω – 2M Ω Single Gang	12p
5k Ω – 2M Ω s/gang W/switch	24p
5k Ω – 2M Ω Dual gang	37p
1K linear single gang	12p
Knobs Pointer type	8p
Small Aluminium	10p
Black chrome rim	15p

SLIDER POTENTIOMETERS

0·25W log and linear values	
10k Ω – 100k Ω Single gang	35p
10k Ω – 100k Ω Dual gang	50p
Knobs	10p

PRESET POTENTIOMETERS

0·25W 1k Ω – 1M, Hor. and Vert.	5p
0·1W Vert. only	3p

WATFORD ELECTRONICS
35 CARDIFF RD., WATFORD, HERTS, ENGLAND.
Enclose 10p stamps for our comprehensive catalogue.

Name.....

Address.....

.....

FREE!

Over 150 ways to engineer a better future

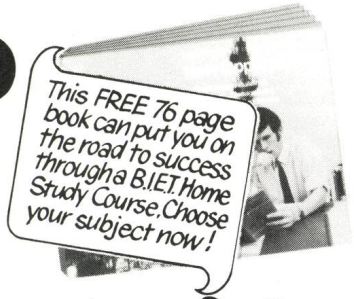

HIGHER PAY

A BETTER JOB

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, *you* could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained – a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters – and there are many more on file at Aldermaston Court – speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help *you*. **Write to B.I.E.T. Dept.** BPE07 **Aldermaston Court, Reading RG7 4PF.**

Practical Radio & Electronics Certificate course includes a learn while you build ***3 transistor radio kit.*** Everything you need to know about ***Radio & Electronics*** maintenance and repairs for a ***spare time income*** and a ***career*** for a better future.

CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

MECHANICAL
- A.M.S.E. (Mech.) ☐
- Boiler Inspect. & Operation ☐
- C & G Eng. Crafts ☐
- C & G Fabricat. ☐
- Diesel Eng. ☐
- Eng. Inspection ☐
- Eng. Metallurgy ☐
- Inst. Eng. & Tech. ☐
- Inst. Motor Ind. ☐
- Mainten. Eng. ☐
- Mechanical Eng. ☐
- Sheet Metal Work ☐
- Welding ☐

ELECTRICAL & ELECTRONIC
- A.M.S.E. (Elec.) ☐
- C & G Elec. Eng. ☐
- C & G Elec. Inst. ☐
- C & G Elec. Tech. ☐
- Computer Elect. ☐
- Elec. Maths ☐
- Elec. Science ☐
- Electronic Eng. ☐
- Electrical Eng. ☐
- Install. & Wiring ☐
- Meters & Measuring Instruments ☐

MANAGEMENT & PRODUCTION
- Auto. Control ☐
- Computer Prog. ☐
- Electronic Data Processing ☐
- Estimating ☐
- Foremanship ☐
- Inst. Cost & Man Accountants ☐
- Inst. Marketing ☐
- Management ☐
- Metrication ☐
- Motor Trade Man. ☐
- Network Plan. ☐
- Numerical Cont. ☐
- Operational Research ☐
- Personnel Man. ☐
- Planning Eng. ☐
- Production Eng. ☐

Man. Prod.—cont.
- Quality Control ☐
- Salesmanship ☐
- Storekeeping ☐
- Work Study ☐
- Works Management ☐

DRAUGHTSMANSHIP
- A.M.I.E.D. ☐
- Design of Elec. Machines ☐
- Die & Press Tool Design ☐
- Electrical Draughtsmanship ☐
- Gen. Draughtsmanship ☐
- Jig & Tool Des. ☐
- Tech. Drawing ☐

RADIO & TELE-COMMUNICATIONS
- Colour TV ☐
- C & G Radio/TV/Electronics ☐
- C & G Telecomm. Tech. ☐
- Prac. Rad. Elec. (with kit) ☐
- Radio Amateurs Exam. ☐
- Radio Servicing & Repairs ☐
- Radio & TV Eng. ☐
- Trans. Course ☐
- TV Main. & Serv. ☐

AUTO & AERO
- Aero Eng. ☐
- A.M.I.M.I. ☐
- A.E.C. Cert. ☐
- Auto Engineer. ☐
- Auto Repair ☐
- C & G Auto. Eng. ☐
- Garage Management ☐
- MAA/IMI Dipl. ☐
- Motor Vehicle Mechanics ☐

CONSTRUCTIONAL
- A.M.S.E. (Civil) ☐
- Architecture ☐

Constructional-cont.
- Building ☐
- Building Drawing ☐
- Build. Foreman ☐
- Carpentry & Join. ☐
- Civil & Municipal Engineering ☐
- Constructional Engineering ☐
- Construction ☐
- Surveyors ☐
- Institute Clerk of Works ☐
- Council Eng. ☐
- Geology ☐
- Health Eng. ☐
- Hydraulics ☐
- Inst. of Builders ☐
- Inst. Works & Highway Sup. ☐
- Painting & Dec. ☐
- Public Hygiene ☐
- Road Engineer. ☐
- Structural Eng. ☐
- Surveying ☐

GENERAL
- Agricultural Eng. ☐
- Council of Eng. Inst. ☐
- Farm Science ☐
- General Educat. ☐
- Gen. Plastics ☐
- Pract. Maths ☐
- Pract. Slide Rule ☐
- Pure & Applied Maths ☐
- Refrigeration ☐
- Rubber Tech. ☐
- Sales Engineers ☐
- Tech. Report Writing ☐
- Timber Trade ☐
- University Ent. ☐

Coaching for many major exams. including C & G and assistance in ONC/HNC.

G.C.E.
58 'O' & 'A' LEVELS SUBJECTS
Over 10,000 group passes

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPE07
Aldermaston Court, Reading RG7 4PF

QN BPE07

NAME.....
Block Capitals Please
ADDRESS.....

.....

.....

OTHER SUBJECTS..... AGE.....

Accredited by C.A.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/sia) Ltd.: South Africa—Central News Agency Ltd.: Rhodesia and Zambia—Kingstons Ltd.: East Africa—Stationery and Office Supplies Ltd. Subscription Rate (including postage): For one year to any part of the world £2·65 (£2.13.0).

Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

Henry's

YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards – call and see for yourself.

BUILD THE TEXAN

★ **FREE TEAK CASE** with complete kits!

FEATURES: New slim design with 6 ICs, IC sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. Special Gardners low field slim line transformer. Fibre glass PC panel. Complete chassis work.

HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES —DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.

FACILITIES: On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, Input selector: Mag. P.U., Radio Tuner, Aux. Can be altered for Mic, Tape, Tape head etc. (Parts list Ref. 20 on request). Constructional Details Ref. No. 21. 30p.

SPECIAL KIT PRICE **£28·50** P. & P. 45p

COMPLETE WITH FREE TEAK CABINET

20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

(As featured in "Practical Wireless" May to August 1972)

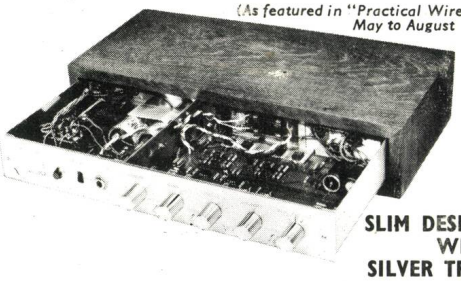

SLIM DESIGN WITH SILVER TRIM

Overall chassis size 14½ in. x 6 in. x 2 in. high

Designer approved kits distributed by Henry's!

LOW COST HI-FI SPEAKERS

E.M.I. Size 13½in x 8½in and Ceramic Magnet

TYPE 150 6 watt, 3, 8 or 15 ohms **£2·20.** Post 22p.
TYPE 150TC Twin cone version **£2·75.** Post 22p.
TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. **£3·50.** Post 25p.
TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. **£7·50.** Post 28p.

POLISHED CABINETS 150, 150TC, 450 **£4·60.** Post 30p.
ASSEMBLED IN POLISHED CABINETS (8 OHM)
SERIES 6 (Assembled 150TC) per pair **£16·50.** Post 70p.
SERIES 8 (Assembled 450) per pair **£18·95.** Post 70p.

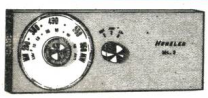

ML3 MW/LW TUNER TO BUILD

Uses Mullard Module. Slow motion tuning. Built-in battery. Ferrite aerial. Overall size 7in x 2¾in x 3¼in. TOTAL COST TO BUILD **£4·85.** Post 15p. All parts sold separately—Leaflet No. 6.

"BANDSPREAD" PORTABLE TO BUILD

Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. 600mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. TOTAL COST TO BUILD **£7·98,** p.p. 32p (Batt. 22p).

CATALOGUE

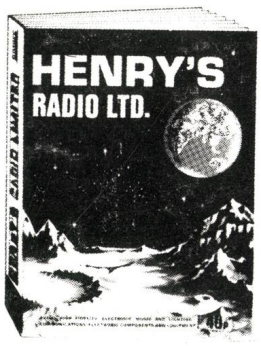

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information. 10,000 Stock lines at Special Low Prices and Fully Guaranteed.

PRICE 55p Post paid **(40p FOR CALLERS)**

PLUS! FIVE 10p VOUCHERS

Send to this address—Henry's Radio Ltd. (Dept. PE), 3 Albemarle Way, London, E.C.1—for catalogue by post only. All other mail and callers to "303", see above.

TEST EQUIPMENT Just a selection

SE250B Pocket Pencil Signal Injector, **£1·90**
SE500 Pocket Pencil Signal Tracer, **£1·50**
THL33D Robust 2 K/Volt, **£4·55;** with case **£4·95**
TE15 Grid Dip Meter 440 KHz—280 MHz, **£13·45**
500 30 K/Volt Multimeter, **£9·25;** with leather case, **£10·50**
200H 20 K/Volt Multimeter, **£4·20;** with case **£4·95**
AF105 50K/V Multimeter, **£8·50;** with case, **£9·50**
U4341 AC/DC Multimeter with transistor tester with steel case, **£10·50**
TE20D RF Generator 120KHz—500MHz, **£16·50.** Carr. 35p
TE22D Audio Generator 20Hz—200KHz, **£17·50.** Carr. 35p
CI-5 3in Pulse Scope 10Hz—10MHz, **£39·00.** Carr. 50p
TE65 Valve Voltmeter 28 ranges, **£17·50.** Carr. 40p

ALL NOMBREX MODELS IN STOCK

BUILD THIS VHF FM TUNER

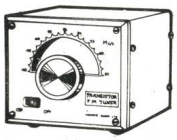

5 TRANSISTORS 300kc/s BANDWIDTH PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately.
Free Leaflet No. 3 & 7. **TOTAL £6·97,** p.p. 20p.
Mk1 Decoder Kit **£5·97.** Built IC Decoder **£6·50.** Tuning meter unit **£1·75.**
Mains unit (optional) Model PS900 **£2·47.** Post 20p.
Mains unit for Tuner and/or Decoder PS6/12 **£3·25.** Post 20p.

PA—DISCO—LIGHTING

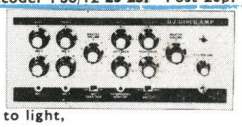

UK's Largest Range—Write phone or call in. Details and demonstrations on request.
DJ30L 3 Channel sound to light unit, 3kW. **£29·50**
DJ40L 3 Channel Mic (Built-in) to light, 3kW. **£38·75**
DJ70S 70 watt Disco amp/mixer, **£49·75**
DISCOAMP 100 watt Disco amp/mixer, **£65·85**
DJ105S 30 watt Disco amp/mixer, **£32·25**
Anti-Feedback Quality Mic., **£11·50**
DJ500 50 watt PA amplifier, **£43·95**
DJ700 70 watt **£52.75**
DJ1000 100 watt **£63·00**
Group 300 150 watt rms Group Valve amplifier, **£86·00**
● **Portable discos—details on request**
● **Credit terms for callers**

FIBRE OPTICS · LIGHTING · MICS · EFFECTS · PROJECTORS · SPOTS · DIMMERS · STANDS · MIXERS · SPEAKERS
Everything for PA — Disco — Lighting.
FREE Stock List Ref. No. 18.

SINCLAIR PROJECT 60 MODULES —SAVE POUNDS

Z30 **£3·57** Z50 **£4·37**
STEREO 60 **£7·97** PZ5 **£3·97**
PZ6 **£6·37** PZ8 **£4·77.**
Transformer for PZ8 **£2·95.**
Active Filter Unit **£4·45.**
Stereo FM Tuner **£16·95.**
IC12 **£1·80** Q16's **£15** pair.
Post, etc. 20p per item.

PACKAGE DEALS Post 25p
2 x Z30, Stereo 60, PZ5 **£15·95**
2 x Z30, Stereo 60, PZ6 **£18·00**
2 x Z50, Stereo 60, PZ8 **£20·25**
Transformer for PZ8 **£2·95**
PROJECT 605 KIT **£19·95**

ELECTRONIC KITS

Henry's introduce new hug range of audio and electron kits now in stock, everythin supplied, tremendous valu Detailed list Ref. No. 14 o request.

IC RECEIVER

ZN414 Radio integrated circui as featured in Practical Wire less, January, 1973. Articl reprint Ref. No. 19. **10p.**

BATTERY TAPE DECK

Garrard 9V tape deck wit heads, etc. As previousl advertised. Limited quantity **£9·50.** Post 30p.

LEARN A LANGUAGE

Recorded Cassettes with ste by step phrase books. French German, Spanish, Italian. **£1·3** per course. **£5·00** per set o four.

DISCO SPOTBANK

As illustrated on the front cover of Practical Wireless, April, 1973. **£12·75.** P. & P. 35p.

HI-FI EQUIPMENT

Warehouse prices with BIG DISCOUNTS plus demonstrations (for callers) and GUARANTEES.

FREE 24-page detailed brochure (Ref. No. 17).

★ **You can see the savings** ★

HIGH QUALITY CASSETTES

The best U.K. low noise tapes but at a special price. "Living Sound" cassettes meet the highest international standard (IEC94A). Fantastic price savings.

	C60	C90	C120
3 for	**£1·00**	**£1·33**	**£1·62**
6 for	**£1·80**	**£2·57**	**£3·15**
10 for	**£2·80**	**£4·20**	**£5·00**

Full guarantee. Post paid.
Made by EMI especially for Henry's.

ULTRASONIC TRANSDUCERS

Operate at 40kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and new I.C. circuits.
PRICE PER PAIR **£5·90.** Post 10p.

MARRIOT TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO

"17" High Impedance	**£2·00**
"18" Med. Impedance	**£2·00**
"36" Med.-Low Imp.	**£3·50**
Erase Heads for above	**75p**
"63" 2 track mono — High Impedance	**£1·75**
"43" Erase Head for above	**75p**

7 SEG & NIXIE TUBES

(Post 15p per 1 to 6)

XN3, XN13, GN6 0–9 side view with data, **85p.**
GNP-7, GNP-8 0–9 side view with decimal points and data, **95p.**
3015F 7 seg. **£2** each, **£7** per 4 with data.
12 and 24 hour clock circuits. Ref. No. 31 **15p.**

MINIATURE AMPLIFIER

5 transistor. 300mW o/p. Fitted volume and sensitivity control 9 volt operated. **£1·75** each, p.p. 15p.

QUALITY SLIDER CONTROLS

60mm stroke singles and ganged. Complete with knobs. 5kΩ, 10kΩ, 25kΩ, 100kΩ, 250kΩ, 500kΩ. 1 meg. Log and Lin. **40p** each, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, Log and Lin. ganged. **60p** each.

VAT All prices are exclusive of 10% VAT which must be added to all orders inc. carr./packing. (Note: Catalogue is not subject to VAT).

See earlier page of this magazine for transistors, I.C.'s and Semiconductor prices. Latest List Ref. No. 36 on request

E & OE

Henry's RADIO LIMITED

EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Open:- 9 am-6 pm 6 days a week (309 closed Thursday) All stores open all day Saturday